

# Ch.2 | Boolean Algebra and logic gates

By: Rawan Alfares



# Boolean Algebra

- \* A Set of two values  $B = \{0, 1\}$
- \* Three basic operation  $\&$  AND, OR, NOT.  
\* denoted by:  $(\cdot)$   $(+)$   $(\bar{\phantom{x}})$ ,  $(\downarrow)$

AND		OR		Complement	
x	y	x	y	x	x'
0	0	0	0	0	1
0	1	0	1	1	0
1	0	1	0		
1	1	1	1		

two inputs  $\swarrow$   $\searrow$  one input.

## Postulates Of Boolean Algebra

1. Closure :- the result of any Boolean operation is 0 or 1.
2. 0 is The Identity element for  $(+)$  :-  
 $0 + x = x + 0 = x$   
1 is The Identity element for  $(\cdot)$  :-  
 $1 \cdot x = x \cdot 1 = x$
3. Commutative law  $x + y = y + x$   
 $x \cdot y = y \cdot x$
4. Distributive law :-  $x \cdot (y + z) = xy + xz$   
 $x + yz = (x + y)(x + z)$
5. Complement law :- "for any  $x, \exists x'$ "  
 $x + \bar{x} = 1$   
 $x \cdot \bar{x} = 0$

## Boolean Functions

Consists of :-

1. variables  $x, y, \dots$
2. Boolean Constants  $0$ 's and  $1$ 's
3. Boolean Operators  $\&$  AND, OR, NOT
4. parentheses

operator precedence :-

1. parentheses  $( )$
2. NOT  $(\bar{\phantom{x}})$
3. AND  $(\cdot)$
4. OR  $(+)$



\* number of rows  $2^n$  → number of variables

ex. The truth table for  $f = xy' + x'z$

x	y	z	y'	xy'	x'	xz	xy'+x'z
0	0	0	1	0	1	0	0
0	0	1	1	0	1	1	1
0	1	0	0	0	1	0	0
0	1	1	0	0	1	1	1
1	0	0	1	1	0	0	1
1	0	1	1	1	0	0	1
1	1	0	0	0	0	0	0
1	1	1	0	0	0	0	0

NOTEg-

- $1+y = 1$
- $x+\bar{x} = 1$
- $x.\bar{x} = 0$
- $x+x = x$

ex.  $(x+y)' = x'y'$   
 $(xy)' = x'+y'$

demorgan law

- (x') Convert to (x)
- (x) Convert to (x')
- (+) Convert to (.)
- (.) Convert to (+)

x	y	x'	y'	x+y	(x+y)'	x'y'
0	0	1	1	0	1	1
0	1	1	0	1	0	0
1	0	0	1	1	0	0
1	1	0	0	1	0	0

Identical.

what's the Complement of  $f = x'yz' + xy'z$

$$f' = (x+y'+z).(x'+y+z')$$

ex. what's the complement of  $g = (a'+bc)d'+e$

$$g' = (a.(b+c') + d).e'$$

Dual Pairs :- we only change,  $\left[ \begin{matrix} 0's \leftrightarrow 1's \\ + \leftrightarrow \cdot \end{matrix} \right]$   
 and keep variables as they are.



## Proving Some Expressions

ex. prove  $x + xy = x$

absorption theorem

$$\begin{aligned}x + xy &= x \cdot 1 + xy \\ &= x \cdot (1 + y) \\ &= x \cdot 1 \\ &= x \quad \# \end{aligned}$$

ex. prove  $x + x'y = x + y$

$$\begin{aligned}x + x'y &= (x + \bar{x}) \cdot (x + y) \\ &= 1 \cdot (x + y) \\ &= x + y\end{aligned}$$

ex. prove that  $xy + x'z + yz = xy + x'z$

$$\begin{aligned}&= xy + x'z + yz \cdot 1 \\ &= xy + x'z + yz \cdot (x + \bar{x}) \\ &= xy + x'z + yzx + yz\bar{x} \\ &= xy + xy z + x'z + \bar{x}zy \\ &= xy(1 + z) + x'z(1 + y) \\ &= xy \cdot 1 + \bar{x}z \cdot 1 \\ &= xy + \bar{x}z \quad \# \end{aligned}$$

ex. Simplify the following Boolean function to a minimum number of literals

$$F(A, C) = (A + C)' + (A + C)(A' + C') \quad 6 \text{ literal}$$

$$\begin{aligned}&= x' + xy \\ &= x' + y\end{aligned}$$

$$\begin{aligned}x &= (A + C) \\ y &= (\bar{A} + \bar{C})\end{aligned}$$

$$= (A + C)' + (A' + C')$$

$$= A' \cdot C' + A' + C'$$

4 literal.

$$= A' + C'$$

2 literal.



ex.  $A'B' + B'C + AB'C' + AB$

$= B'(A' + C + AC') + AB$

$= B'((A' + A) + C) + AB$

$= B'(1 + C) + AB$

$= B' \cdot 1 + AB$

$= B' + AB$

$= A + B'$

distributive law 9 literals  
7 literals

simplification law 6 literals

Complement law 4 literals

null law 3 literals

Identity law 3 literals

2 literals

ex.  $ab + a'cd + a'bd + a'cd' + abcd$

$= ab + abcd + a'cd + a'bd + a'cd'$  15 literals

$= ab(1 + cd) + a'c(d + d') + a'bd$

$= ab + a'c + a'bd$

$= b(a + a'd) + a'c$

$= b(a + d) + a'c$

ex.  $(A' + B' + C')(A + C')(B + C')(B' + C)$

Product of Sum

$= (A'B'C') + (AC') + (BC') + (B'C)$

$= C'(A'B' + A + B) + B'C$

$= C'(A + B' + B) + B'C$

$= C'(A + 1) + B'C$

$= C' + B'C$

$= C' + B'$

$= C' \cdot B'$  by dual

by duality:-  
they are not equivalent, so at the end we have to reuse duality.

### NOTE 8

the complement of a function is by taking the dual then complementing each literal

ex. Complement  $f = x'y'z' + xyz'$

1. dual  $(x + y + z') \cdot (x' + y' + z)$

2. Complement  $(x + y' + z) \cdot (x' + y + z')$

Uploaded By: Rawan Fares




ex.  $g = (\bar{a} + bc)d' + e$

1.  $((\bar{a} \cdot (b + c)) + d')$  .  $e$


2.  $g' = ((a \cdot (b' + c')) + d) \cdot e'$

\* 0 → low voltage


\* 1 → high voltage

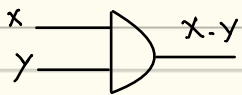

AND gate

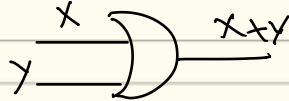

OR gate

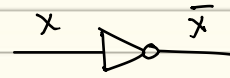

NOT gate (inverter).



# Canonical and Standard Form

نبي استخرج لغة أرقامنا والبياني \*

Canonical

minterms ← → max terms

they are complement to each other.

• must have the all variables in same order for all terms.

\* إحدى سالياتنا، إننا نتحوي على أعداد كبيرة من variables

ex.	variables			always 1 min terms		always 0 max terms	
	x	y	z	term	design	term	design
	0	0	0	$x'y'z'$	$m_0$	$x+y+z$	$M_0$
	0	0	1	$x'y'z$	$m_1$	$x+y+z'$	$M_1$
	0	1	0	$x'y z'$	$m_2$	$x+y+z$	$M_2$
	0	1	1	$x'y z$	$m_3$	$x+y+z'$	$M_3$
	1	0	0	$x y'z'$	$m_4$	$x+z+y$	$M_4$
	1	0	1	$x y'z$	$m_5$	$x+z+y'$	$M_5$
	1	1	0	$x y z'$	$m_6$	$x+z+y+z$	$M_6$
	1	1	1	$x y z$	$m_7$	$x+z+y+z'$	$M_7$

inside: product | in : sum  
outside: sum | out : product

ex.  $f(x,y,z) = x'y'z' + x'y'z + xyz$  [Sum of product.]  
 $= 0' \cdot 0' \cdot 0' + 0' \cdot 0' \cdot 1 + 1 \cdot 1 \cdot 1$   
 $= m_0 + m_1 + m_7$   
 $= \sum 0, 1, 7$

ex.  $F(A,B,C) = \sum 0, 2, 4, 6$   
 $= m_0 + m_2 + m_4 + m_6$   
 $= 000 + 010 + 100 + 110$   
 $= A'B'C' + A'BC' + AB'C' + ABC'$

ex.  $F(A,B,C,D) = \sum 0, 2, 10, 15$   
 $= m_0 + m_2 + m_{10} + m_{15}$   
 $= 0000 + 0010 + 1010 + 1111$   
 $= A'B'C'D' + A'B'CD' + A'B'CD + ABCD$

ex.  $F(x,y,z) = (x+y+z) \cdot (x+\bar{y}+z) \cdot (\bar{x}+\bar{y}+\bar{z})$   
 $(0+0+0) \cdot (0+1+0) \cdot (1+1+1)$   
 $= M_0 \cdot M_2 \cdot M_7$   
 $= \prod (0, 2, 7)$



$$\begin{aligned} \text{ex. } F(A, B, C) &= \prod(0, 2, 5) \\ &= M_0 \cdot M_2 \cdot M_5 \\ &= (0+0+0) \cdot (0+1+0) \cdot (1+0+1) \\ &= (A+B+C) \cdot (A+B+C) \cdot (A+B+C) \end{aligned}$$

$$\begin{aligned} \text{ex. } F(A, B, C, D) &= (A+B+C+D) \cdot (\bar{A}+\bar{B}+C+D) \cdot (\bar{A}+B+\bar{C}+D) \\ &= (0+0+0+0) \cdot (1+1+0+0) \cdot (1+0+1+0) \\ &= M_0 \cdot M_{12} \cdot M_{10} \\ &= \prod(0, 10, 12) \end{aligned}$$

$$\begin{aligned} \text{ex. } F(A, B, C) &= \Sigma(0, 7) \\ &= m_0 + m_7 \\ &= \bar{A}\bar{B}\bar{C} + ABC \end{aligned}$$

$$\begin{aligned} \text{ex. } F(A, B, C) &= (A+B+C) \cdot (\bar{A}+\bar{B}+\bar{C}) \\ &= M_0 \cdot M_7 \\ &= \prod(0, 7) \end{aligned}$$

$$\text{ex. write } F(A, B, C) = \Sigma(0, 2, 4)$$

- 1) mathematical expression.
- 2) truth table.
- 3) product of Max term.

$$\begin{aligned} \text{1)} &= m_0 + m_2 + m_4 \\ &= m_{000} + m_{010} + m_{100} \\ &= (\bar{A}\bar{B}\bar{C}) + (\bar{A}B\bar{C}) + (A\bar{B}\bar{C}) \end{aligned}$$

2)	A	B	C	min term	max term
$m_0$	0	0	0	1	1
$m_1$	0	0	1	0	0
$m_2$	0	1	0	1	1
$m_3$	0	1	1	0	0
$m_4$	1	0	0	1	1
$m_5$	1	0	1	0	0
$m_6$	1	1	0	0	0
$m_7$	1	1	1	0	0

$$\text{3)} F(A, B, C) = \prod(1, 3, 5, 6, 7)$$

$$F \text{ for product} = \prod(1, 3, 5, 6, 7)$$

complement

$$\rightarrow F(A, B, C) = \Sigma(0, 2, 4) = \prod(1, 3, 5, 6, 7)$$

$$\rightarrow F'(A, B, C) = \prod(0, 2, 4) = \Sigma(1, 3, 5, 6, 7)$$

$$F \cdot F' = 0$$



من الفقه

الأنف



ex. express the Boolean function  $F(A,B,C) = A + B'C$  as

A Sum of minterms.  
 missing two variables

$$A = A(B + B') = AB + AB'$$

$$AB(C + C') = ABC + ABC'$$

$$AB'(C + C') = AB'C + AB'C'$$

Second term is missing one variable  
 $B'C(A + A') = AB'C + A'B'C$

$$F(A,B,C) = ABC + ABC' + AB'C + AB'C' + A'B'C$$

$$= m_7 + m_6 + m_5 + m_4 + m_1$$

$$= \Sigma(1, 4, 5, 6, 7) = \Pi(0, 2, 3)$$

Complement  $F(A,B,C) = \Pi(1, 4, 5, 6, 7) = \Sigma(0, 2, 3)$ .

Express the following in the Sum of min terms 8-

1)  $f(a,b,c,d) = \Sigma(2, 3, 6, 10, 11)$

0010 0011 0110 1010 1011

$$= m_2 + m_3 + m_6 + m_{10} + m_{11}$$

$$= a'b'cd' + a'b'cd + a'bcd' + ab'cd' + ab'cd$$

2)  $g(a,b,c,d) = \Sigma(0, 1, 12, 15)$

0000 0001 1100 1111

$$= m_0 + m_1 + m_{12} + m_{15}$$

$$= a'b'c'd' + a'b'cd + abc'd' + abcd$$

\*Express the following function as a Product of max terms 8-

$f(x,y,z) = xy + x'z$  → مشتق كل المتغيرات مع مجموعة قدينا  
 نحطهم بكل ترتيب

① Convert function into OR terms by using the distributive law.

$$f = (xy + x') \cdot (xy + z)$$

$$= (x + \bar{x}) \cdot (y + \bar{y}) \cdot (x + z) \cdot (y + z)$$

$$= (y + \bar{y}) \cdot (x + z) \cdot (y + z)$$



② each term missing one variable;

$$= (y + \bar{x} + z \cdot \bar{z}) \cdot (x + z + y \bar{y}) \cdot (y + z + x \bar{x})$$

$$= (y + \bar{x} + \bar{z}) \cdot (y + \bar{x} + z) \cdot (x + z + y) \cdot (x + z + \bar{y}) \cdot (y + z + \bar{x})$$

$$= (\bar{x} + y + z) \cdot (\bar{x} + y + \bar{z}) \cdot (x + y + z) \cdot (x + \bar{y} + z)$$

$$= M_4 \cdot M_5 \cdot M_0 \cdot M_2$$

$$= \Pi(0, 2, 4, 5)$$

\* express  $f(a, b, c, d) = \Pi(1, 3, 11)$  in the product of max terms form

$$= M_1 \cdot M_3 \cdot M_{11}$$

$$= (0+0+0+1) \cdot (0+0+1+1) \cdot (1+0+1+1)$$

$$= (a+b+c+d') \cdot (a+b+c'+d') \cdot (a'+b+c'+d')$$

\*  $g(a, b, c, d) = \Pi(0, 5, 13)$

$$= M_0 \cdot M_5 \cdot M_{13}$$

$$= (0+0+0+0) \cdot (0+1+0+1) \cdot (1+1+0+1)$$

$$= (a+b+c+d) \cdot (a+b'+c+d') \cdot (a'+b'+c+d')$$

1100

To convert from one canonical to another, interchange the symbols  $\Sigma$  and  $\Pi$  and list those number missing from the original form.

The complement of a function expressed by a sum of minterms is the product of max terms  
↳ interchange  $\Sigma$  and  $\Pi$ , and keep the same list of indices.

ex. write the complement of the following function using sum of minterms.

$$f(x, y, z) = \Sigma(0, 2, 3, 4, 6)$$

$$f'(x, y, z) = \Pi(0, 2, 3, 4, 6) = \Sigma(1, 5, 7)$$

$$f'(x, y, z) = \bar{x}\bar{y}\bar{z} + x\bar{y}z + x\bar{y}z$$

Uploaded By: Rawan Fares



من الفقه

الأندلس

ex.  $f(x, y, z, w) = \sigma(0, 1, 2, 4, 5, 7)$

Since the system has 4 input variables, then the number of minterm and maxterms =  $2^4 = 16$ , 0 → 15

$$f(x, y, z, w) = \Sigma(0, 1, 2, 4, 5, 7) \\ = \Pi(3, 6, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$f'(x, y, z, w) = \Pi(0, 1, 2, 4, 5, 7) \\ = \Sigma(3, 6, 8, 9, 10, 11, 12, 13, 14, 15).$$

\* the number of Minterms and Maxterms =  $2^n$  → number of variables

\* Minterms → always 1 entries

\* Max terms → always 0 entries

\* the complement of a sum of minterms is product of Maxterms to the same indices and vice versa.

\* for Boolean function, given the list Minterms indices one can determine the list of Maxterms indices and vice versa.

\* باختصار، إذا أعطاك معلومة واحدة بتقديم تطلع منها باقي المعلومات،

Complement\* ← بتحويل  $\Sigma \rightarrow \Pi$  ونحوها  
 [ الأرقام الأرقام  
 نفسها

\* لكي إن أمكن نكتب  $\Sigma$  بطريقة  $\Pi$  (بغير جواب مكافئ)  
 بناءً الأرقام التي ضايلت، والعكس كذلك...



## Operation on Functions

And = intersection

التقاطع

OR = union

اتحاد

ex.  $F(A,B,C) = \sum m(1,3,6,7)$  ,  $F'(A,B,C) = \sum (0,2,4,5)$

$G(A,B,C) = \sum m(0,1,2,4,6,7)$  ,  $G'(A,B,C) = \sum (3,5)$

Find  $F \cdot G = \sum m(1,6,7)$

$F+G = \sum m(0,1,2,3,4,6,7)$

$F' \cdot G = \sum m(0,2,4)$

## Equality functions

1. Same sum of minterms
2. Same product of Max terms

ex.  $F_1 = a'b' + ac + bc'$   
 $F_2 = a'b' + ab + b'c$

$F_1$	a	b	c	
	0	0	0/1	0, 1
	1	0/1	1	5, 7
	1/0	1	0	2, 6

$\Rightarrow F_1 = \sum (0,1,2,5,6,7)$   
 $= \prod (3,4)$

$F_2$	a	b	c	
	0	1/0	0	0, 2
	1	1	0/1	6, 7
	0/1	0	1	1, 5

$\rightarrow F_2 = \sum (0,2,6,7,1,5)$   
 $= \prod (3,4)$

yes, they are equivalent.

ex.  $F_1(x,y,z) = \sum m(1,2,4,5,6,7) = \text{Combinations} = 2^3 = 8$

$F_2(a,b) = \prod (0,3) \rightarrow \text{Combinations} = 2^2 = 4$

$F_2(a,b) = \sum (1,2)$

$F_1(x,y,z) = \prod (0,3)$

thus, they are not equal.



## Standard form

another way to express Boolean functions

Sum of product SOP

Product of sum POS

### 1) SOP

Boolean expression is the ORing (sum) of AND terms (product).

$$\text{ex. } f_1 = xy' + xz$$
$$f_2 = y + xy'z$$

↳ similar to min term

### 2) POS


Boolean expression is the ANDing (product) of OR terms (sums).

$$\text{ex. } f_3 = (x+z)(x'+y')$$
$$f_4 = x(x+y+z)$$


↳ similar to max term.

## Two level Gate Implementation

$$f_1 = xy' + xz$$

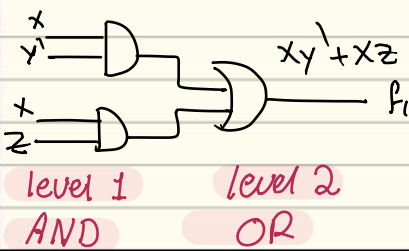


$$f_2 = y + xy'z$$

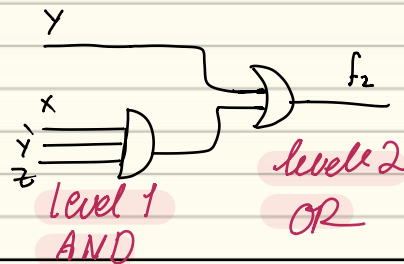


AND-OR  
implementation  
SOP

$$f_3 = (x+z)(x'+y')$$

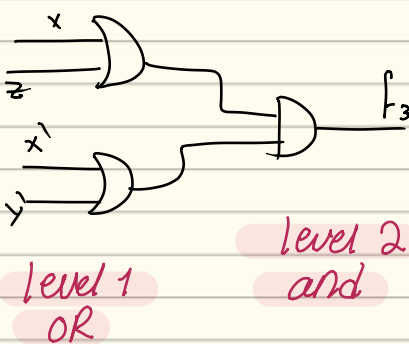

$$f_4 = x(x'+y'+z)$$

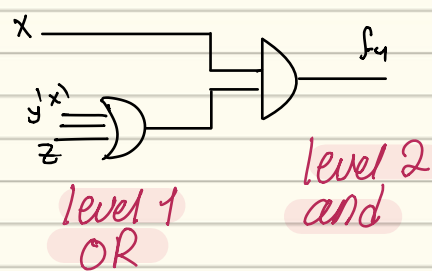


OR-AND  
implementation  
POS




ex.  $h = ab + cd + ce$  (6 literal)  $\rightarrow$  standard form SOP

$h = ab + c(d+e)$  (5 literal)  $\rightarrow$  non-standard form

(a) standard form

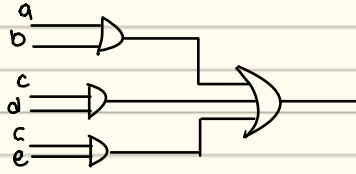


(b) non-standard form

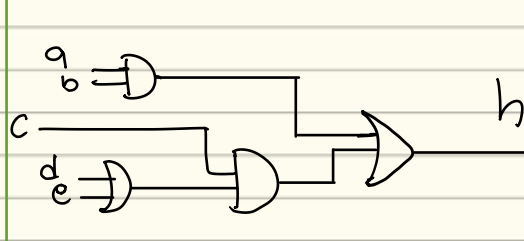

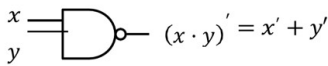
## Additional Logic Gates

low cost implementation  
useful in implementing Boolean function.

**NAND Gate**  $\rightarrow$  NOT AND  
opposite of AND



NAND gate

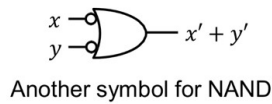


x	y	NAND
0	0	1
0	1	1
1	0	1
1	1	0


universal gate :-  $\begin{cases} \text{NAND} \\ \text{NOR} \end{cases}$

يعني بقدر نبني أكثر من  
gate  
سواء كان  
Inverter  
AND  
OR

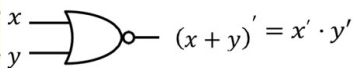**NOR Gate**  $\rightarrow$  NOT OR  
opposite of OR



NOR gate

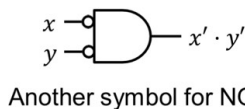

x	y	NOR
0	0	1
0	1	0
1	0	0
1	1	0


\* NAND/NOR

Not associative.


\*  $(x \text{ NAND } y) \text{ NAND } z \neq x \text{ NAND } (y \text{ NAND } z)$

\*  $(x \text{ NOR } y) \text{ NOR } z \neq x \text{ NOR } (y \text{ NOR } z)$

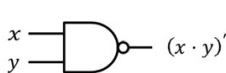
NAND/NOR gates can have multiple inputs, similar to AND/OR gates




2-input NAND gate

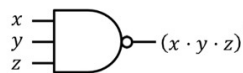


3-input NAND gate

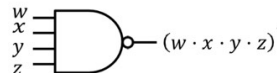


4-input NAND gate

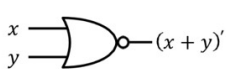

2-input NOR gate

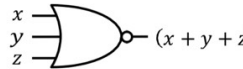

3-input NOR gate

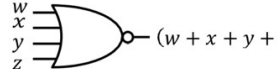

4-input NOR gate




# NAND

using NAND gate to build inverter } gates  
AND  
OR


❖ A single-input NAND gate is an inverter
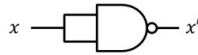
$$x \text{ NAND } x = (x \cdot x)' = x'$$




❖ AND is equivalent to NAND with **inverted output**
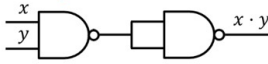
$$(x \text{ NAND } y)' = ((x \cdot y)')' = x \cdot y \text{ (AND)}$$



❖ OR is equivalent to NAND with **inverted inputs**
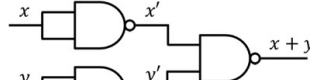
$$(x' \text{ NAND } y') = (x' \cdot y')' = x + y \text{ (OR)}$$



Uploaded by Mahamoud Abu Hijleh to BZU-Lib.com

# NOR

using NOR gate to build inverter } gate  
AND  
OR


❖ A single-input NOR gate is an inverter

$$x \text{ NOR } x = (x + x)' = x'$$




❖ OR is equivalent to NOR with **inverted output**
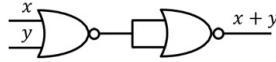
$$(x \text{ NOR } y)' = ((x + y)')' = x + y \text{ (OR)}$$



❖ AND is equivalent to NOR with **inverted inputs**

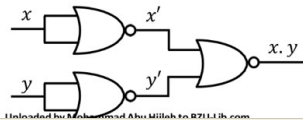
$$(x' \text{ NOR } y') = (x' + y')' = x \cdot y \text{ (AND)}$$




Uploaded by Mahamoud Abu Hijleh to BZU-Lib.com

\* the multiple Input NAND/NOR Gates are a single gate, NOT a combination of 2-input gates.


ex.  $f = bd + d'cd'$

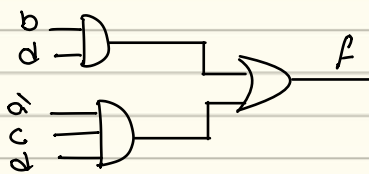

AND-OR Implementation

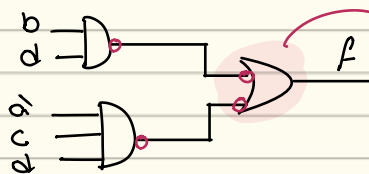


NAND-NOR Implementation

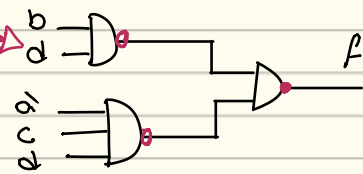


NAND-NAND Implementation

\* two successive bubbles on same line cancel each other

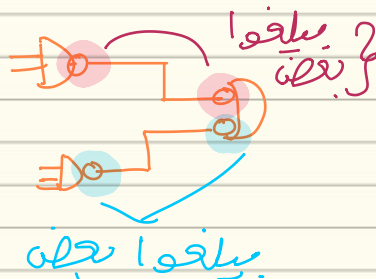إذ كان فيه أكثر من (NOT) على نفس السلك يلغوا بعضهما





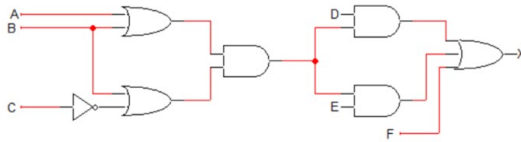❖ Example: Implement the given circuit using only NAND gates




Start from output toward inputs converting gate by gate

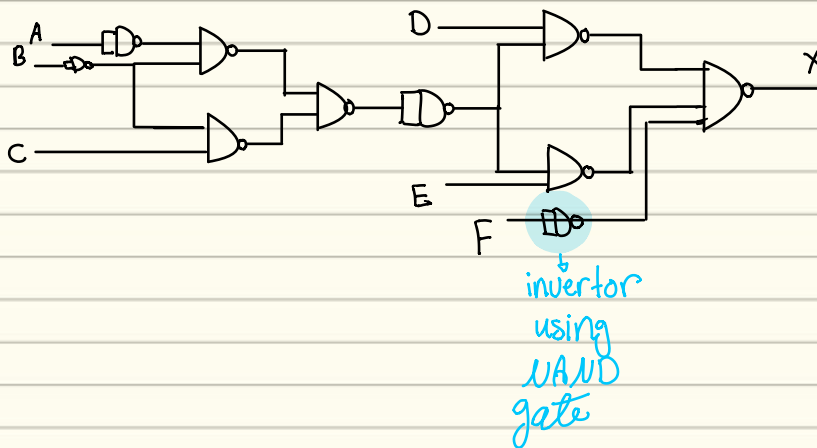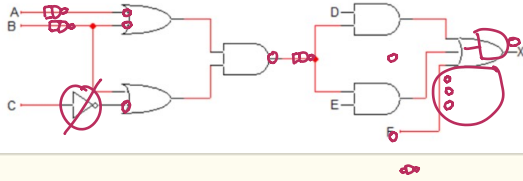❖ Example: Implement the given circuit using only NAND gates




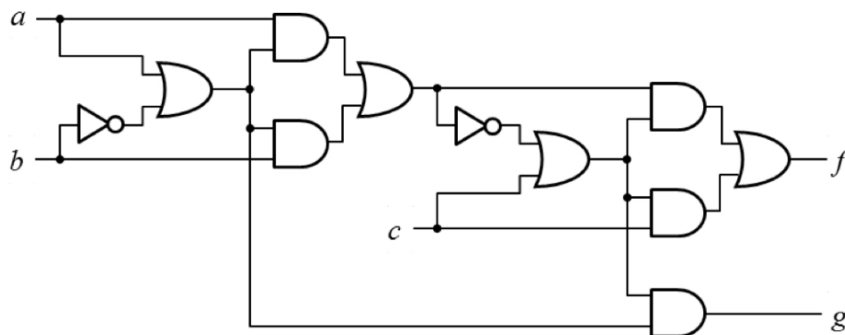❖ Example: Implement the given circuit using only NOR gates




Start from output toward inputs converting gate by gate

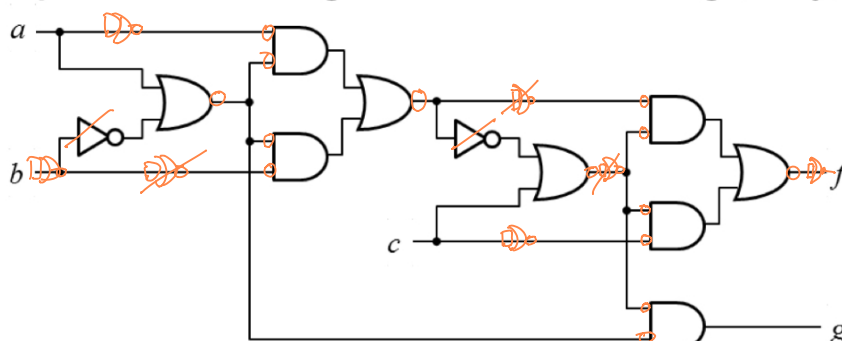❖ Example: Implement the given circuit using only NOR gates





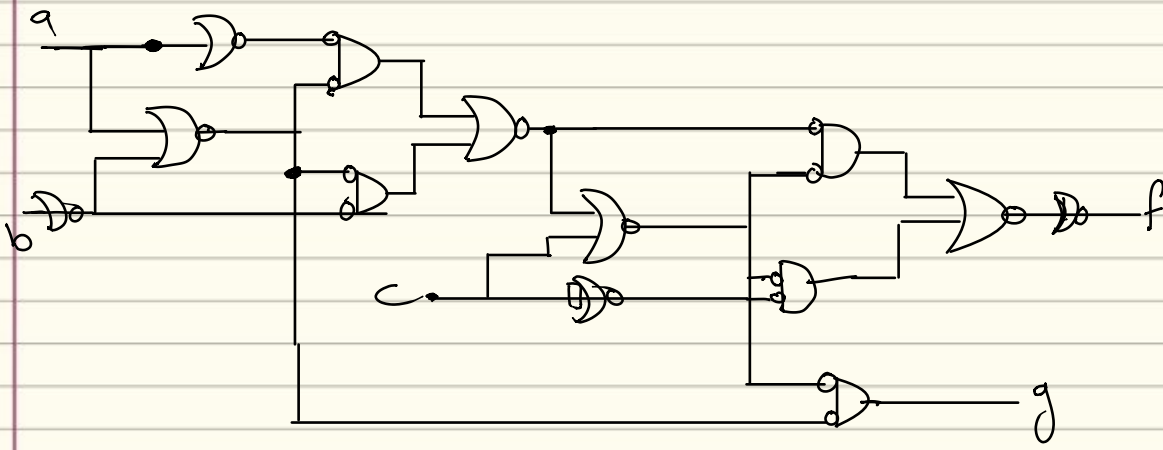


NAND  $\rightarrow$  NOR  $\leftarrow$  *شيفرة*  
 NOR  $\rightarrow$  NAND  $\leftarrow$  *input*

❖ Example: Find the complement of the following expression and implement it using (1) NAND gates, and (2) NOR gates:

$$G(A, B, C) = (A + B' + C)(A'B' + C)(A + B'C')$$


$$G'(A, B, C) = (A + B' + C)' + (A'B' + C)' + (A + B'C)'$$

$$= A'BC' + (A+B).C' + (A'.(B+C))$$

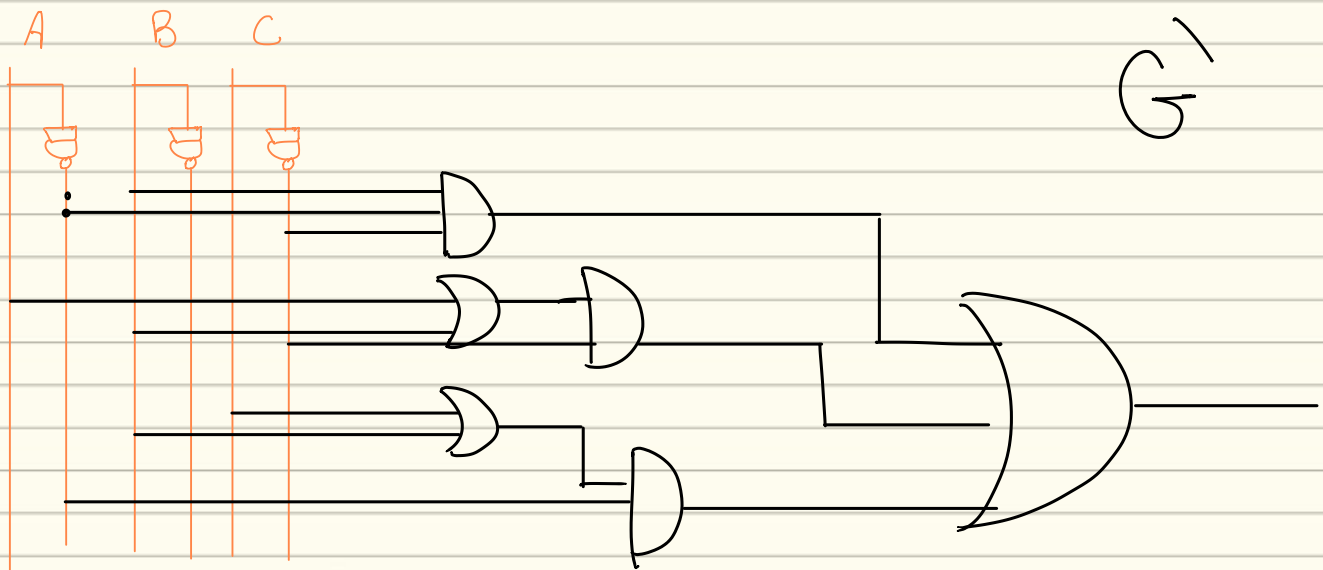


$G'$



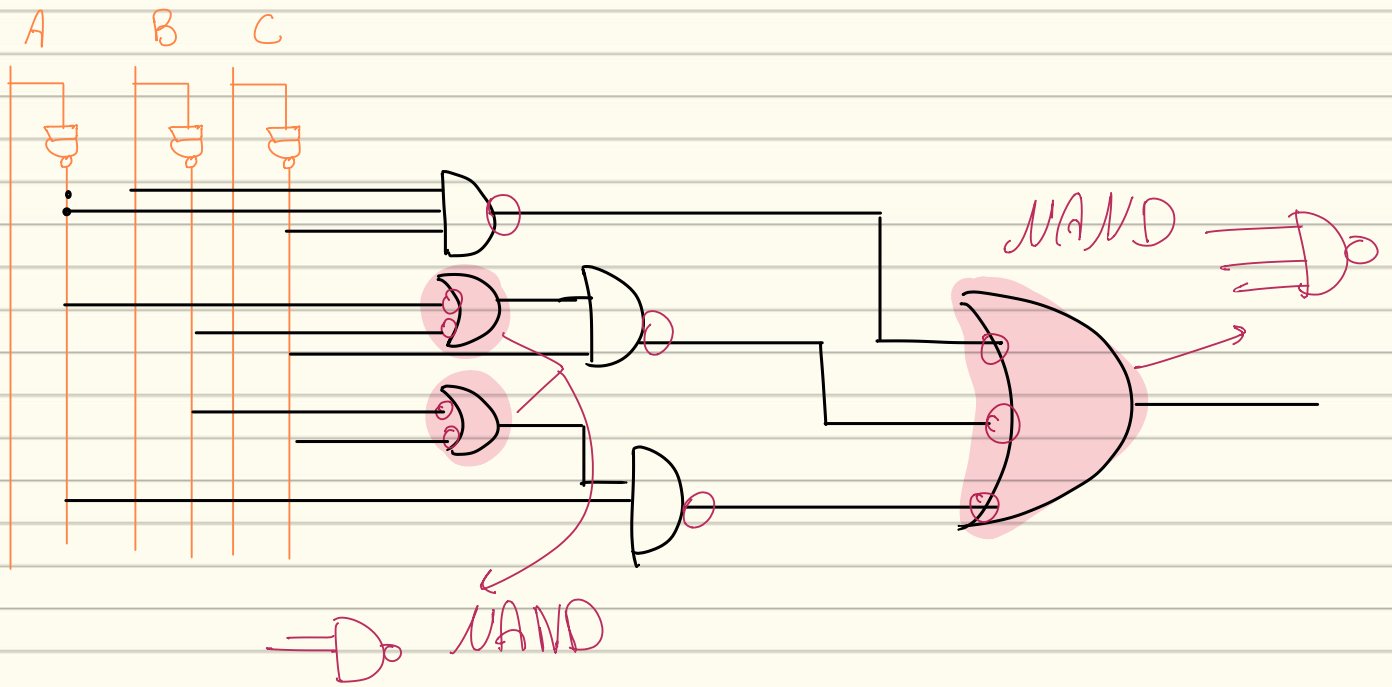

Something to NOR

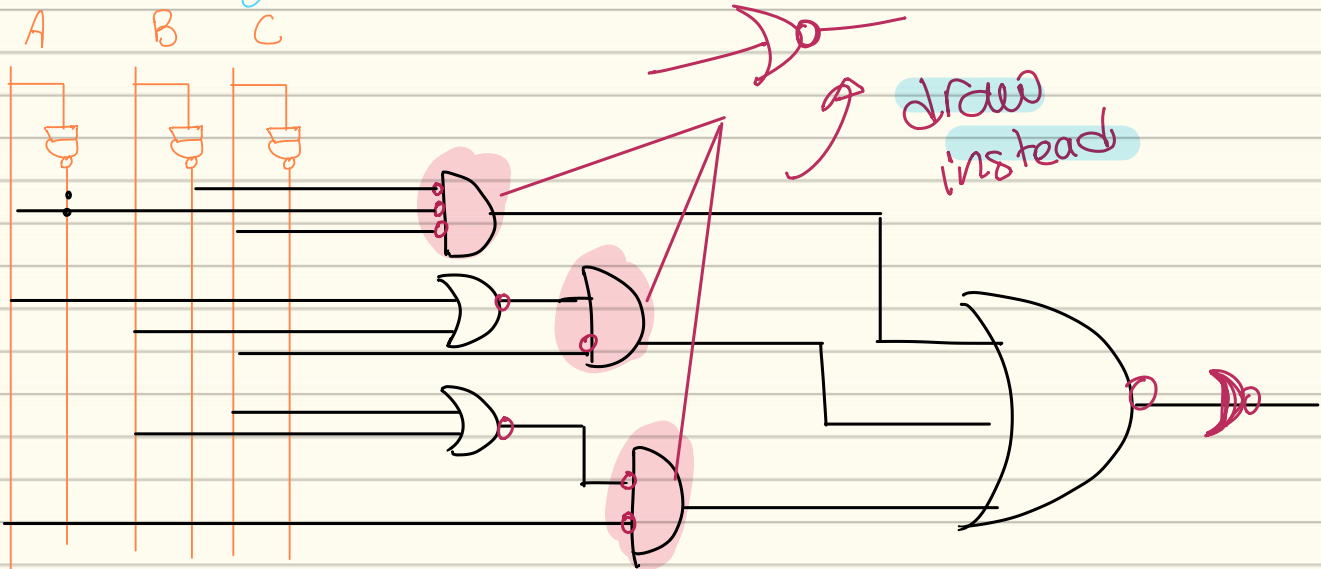

# XOR / XNOR


Complement for each other.

❖ Exclusive NOR (XNOR) is the complement of XOR

x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0

x	y	XNOR
0	0	1
0	1	0
1	0	0
1	1	1

XNOR is also known as **equivalence**

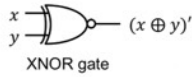

**XOR** : Odd function  
↳ equals 1, when has odd # of ones

**XNOR** : equals 0, when has odd # of zeros.

\* they don't exist for more than two inputs.

✦ **XOR function** :  $x \oplus y = xy' + x'y$

✦ **XNOR function** :  $(x \oplus y)' = xy + x'y'$

❖  $x \oplus 0 = x$

❖  $x \oplus 1 = x'$

❖  $x \oplus x = 0$

❖  $x \oplus x' = 1$

❖  $x \oplus y = y \oplus x$

❖  $x' \oplus y' = x \oplus y$

❖  $(x \oplus y)' = x' \oplus y = x \oplus y'$

XOR and XNOR are **associative** operations

❖  $(x \oplus y) \oplus z = x \oplus (y \oplus z) = x \oplus y \oplus z$

❖  $((x \oplus y)' \oplus z)' = (x \oplus (y \oplus z)')' = x \oplus y \oplus z$




# Positive and negative logic


\* Choosing (1) to High level  $\rightarrow$  positive logic system.

\* choosing (1) to low level  $\rightarrow$  negative logic system.

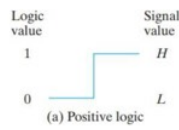❖ Choosing the high-level H to represent logic 1 defines a **positive logic system**



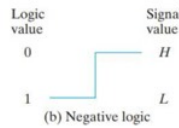❖ Choosing the low-level L to represent logic 1 defines a **negative logic system**



❖ It is up to the user to decide on a positive or negative logic polarity

\* the conversion from positive to negative logic it as using dual.


\* changing 0s to 1s and vice versa.

\* changing (+) to (-) and vice versa.

❖ The conversion from positive logic to negative logic and vice versa is essentially an operation that changes 1's to 0's and 0's to 1's in both the inputs and the output of a gate

x	y	z
L	L	L
L	H	L
H	L	L
H	H	H


(a) Truth table with H and L

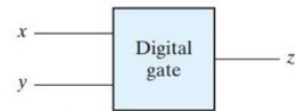

(b) Gate block diagram

x	y	z
0	0	0
0	1	0
1	0	0
1	1	1

(c) Truth table for positive logic

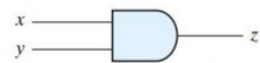


(d) Positive logic AND gate

❖ Since this operation produces the *dual* of a function, the change of all terminals from one polarity to the other results in taking the dual of the function

x	y	z
1	1	1
1	0	1
0	1	1
0	0	0

(e) Truth table for negative logic

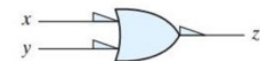

(f) Negative logic OR gate

ربنا تقبل منا إنك أنت السميع العليم

روان فارس

