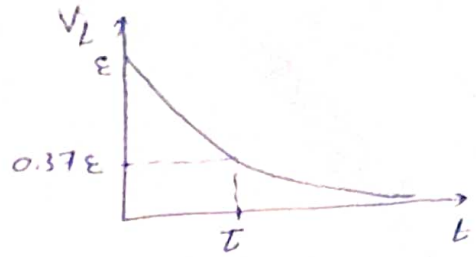


→ at  $t = \frac{L}{R} \rightarrow V_L = \epsilon e^{-1} = 0.37\epsilon$



$\tau = \frac{L}{R}$  : time const. for RL-circuit


\* Voltage across Resistor :

$$V_R = IR = \epsilon(1 - e^{-\frac{Rt}{L}})$$

\* at  $t=0 \rightarrow V_R = 0$

\* at  $t=\infty \rightarrow V_R = \epsilon$

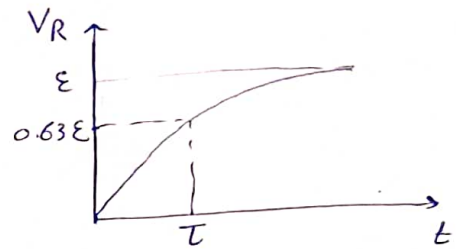→ at  $t = \frac{L}{R} \Rightarrow V_R = \epsilon(1 - e^{-1}) = 0.63\epsilon$



$\tau = \frac{L}{R}$

