

# Digital Systems

## Section 2

### Chapter (4)


☉ In Digital Systems, Logic circuits can be categorized as **combinational** or **sequential**

☉ **Combinational** Circuit

- ☐ Circuit made of **logic gates only** and perform an operation that can be specified logically by a set of Boolean functions.
- ☐ Circuit output at any time are determined **only by the current combination** (**current state/value**) of inputs.

☉ **Sequential** Circuit

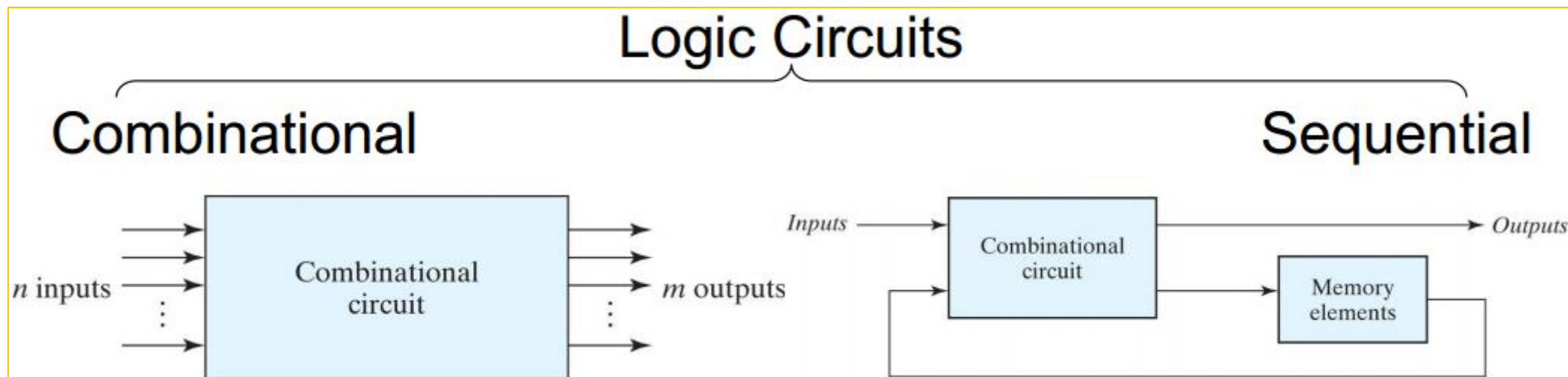- ☐ Circuit is made of **storage/memory** elements and **logic gates**.
- ☐ Circuit output depend on the current combination of inputs and **previously stored values**.



- ⊗ A logic circuit is combinational if its outputs at any time are a function of **only** the **present** inputs
- ⊗ A combinational circuit is an interconnection of **logic gates only**
- ⊗ A combinational circuit does **NOT** have **memory elements or feedback loops**

ⓓ A combinational circuit is a **block** of logic gates having:


- 1)  $n$  inputs:  $x_1, x_2 \dots, x_n$
- 2)  $m$  outputs:  $f_1, f_2 \dots, f_m$
- 3) Logic Gates and wires

ⓓ For  $n$ -input variables, there are  $2^n$  possible **input combinations**.

ⓓ There are  $m$ -outputs, and  $m$  can be **greater** than  $n$ .

ⓓ Each output variable can be described with a Boolean function expressed in terms of  $n$  or **less** input variables

 **Block** diagram of a combinational circuit





- 🌀 For any logic circuit, there are two main activities: **analysis and design**.
- 🌀 **Analysis:** Examine how the circuit **behaves** by **determining the outputs** based on given inputs and logic gates.
  - 📌 Circuit/Logic Gate → Boolean Expression/Truth Table
- 🌀 **Design:** **Construct** circuits that **deliver the desired outputs** by using logic gates and Boolean expressions.
  - 📌 Desired Outputs/Truth Table → Boolean Expression → Circuit/Logic Gates



**Analysis** determines the **logic function** that a circuit implements

- 🌀 Given: a logic circuit
  
- 🌀 Desired: A **description** of the circuit either in the form of:
  - 📌 Boolean functions
  - 📌 Truth tables
  - 📌 Simply an explanation of the circuit

## I. Obtain Boolean expression/function from logic diagram

- 1) Make sure that the given circuit is **combinational** and **NOT** sequential. The diagram of a combinational circuit has logic gates with **NO feedback** paths **or memory** elements.
- 2) **Label** all gate outputs that are a function of input variables.
  - Ⓜ Obtain Boolean function for **each gate**.
- 3) **Label** all gate outputs that are a function of input variables and **previously labeled** gates.
  - Ⓜ Obtain Boolean function for each of these gates.
- 4) **Repeat** step (3) until the outputs of the circuit are obtained.
- 5) **Substitute** of previously defined variables to obtain the output Boolean functions in terms of **input variables only**
- 6) **Convert** and/or **simplify** the resultant Output functions to the **required final form** (SOP, POS, SOM,POM) using previously explained methods (Algebraic Manipulation, Expansion, K-Map)

**Example:**


- 1) **Combinational** ✓
- 2) **Label** all gate outputs that are a function of input variables. ( **$T_1, T_2, F_2$** )
- 3) Label all gate outputs that are a function of input variables and **previously labeled** gates. ( **$T_3$** )
- 4) Repeat step (3) until the outputs of the circuit are obtained. ( **$F_1$** )
- 5) **Substitute**  $\rightarrow$   **$F_1 (A, B, C)$**

Two outputs of this combinational circuit  $F_1, F_2$

**First** find  **$T_1, T_2, F_2$**

**Next** find  **$T_3$**

**Finally**, find  **$F_1$**

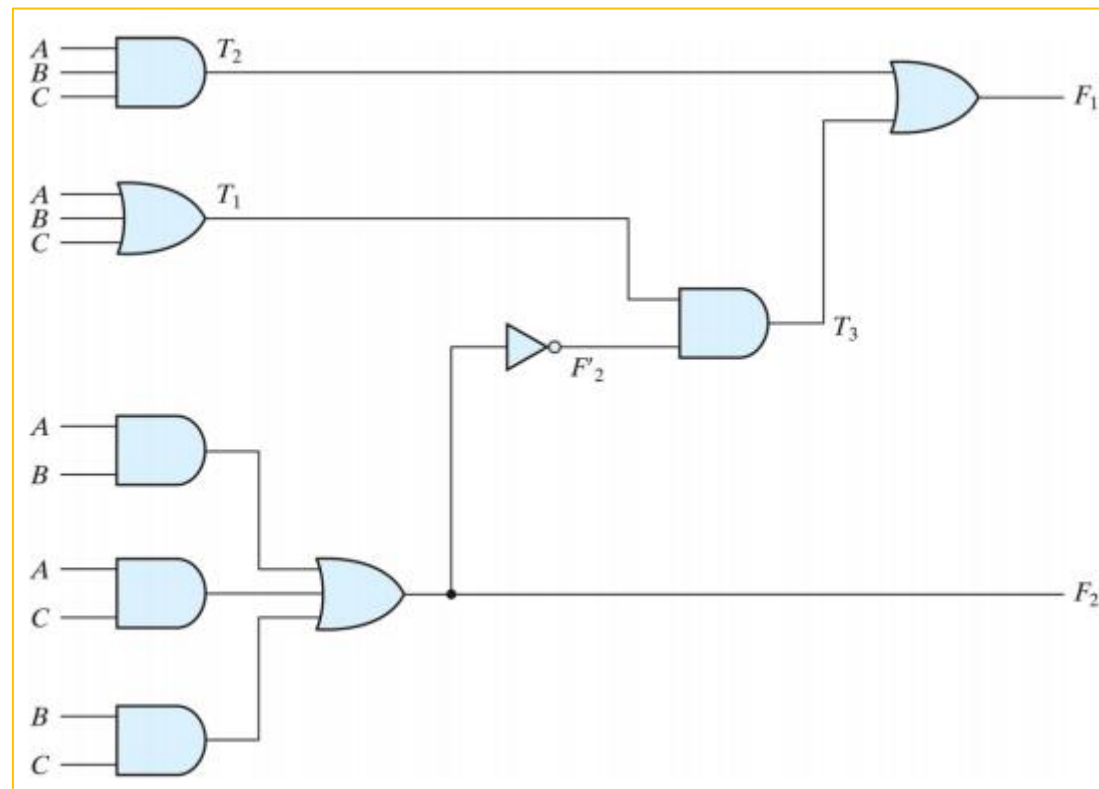


**Example Cont.:**

$$F_2 = AB + AC + BC \quad \checkmark$$

$$T_1 = A + B + C, \quad T_2 = ABC$$

$$T_3 = F_2' T_1$$

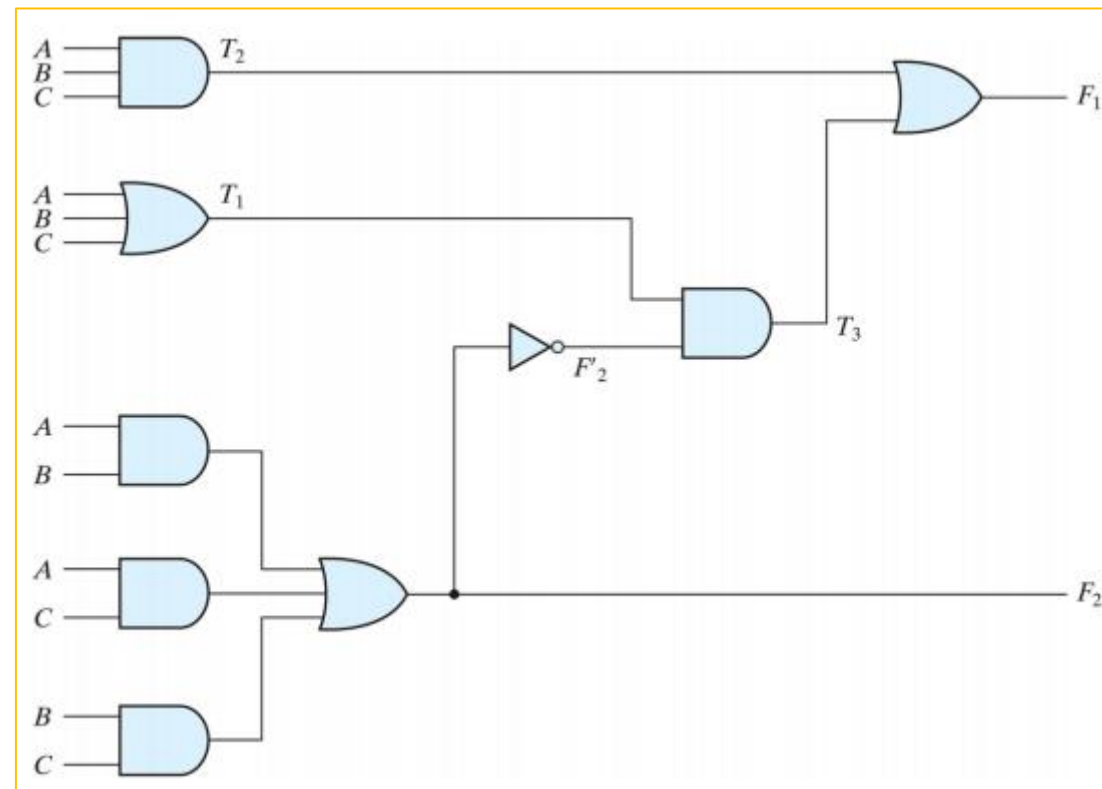No need to find T1 as a function of input variables only, because it is an **intermediate** gate output



$$F_1 = T_3 + T_2$$

$$= F_2' T_1 + ABC = (AB + AC + BC)'(A + B + C) + ABC$$

$$= (A' + B')(A' + C')(B' + C')(A + B + C) + ABC$$

$$= A'BC' + A'B'C + AB'C' + ABC \quad \checkmark$$



**Extra Example:**

$$T_1 = BC$$

$$T_2 = (A'D)' = A + D'$$

$$T_3 = (A'T_2)' = A + T_2' = A + A'D = A + D$$


$$T_4 = A' + T_1 = A' + BC$$

$$F = T_3 T_4 = (A + D)(A' + BC) = AA' + ABC + A'D + BCD$$

$$= ABC + A'D + BCD = ABC + A'D \quad \checkmark$$

$$G = T_2 T_4 = (A + D')(A' + BC) = AA' + ABC + A'D' + BCD'$$
 
$$= ABC + A'D' + BCD' = ABC + A'D' \quad \checkmark$$






## II. Obtain the Truth Table from the Logic Diagram

- 1) Prepare the **truth table** for **n** input variables and **2<sup>n</sup>** input **combinations**
- 2) **Label** all gate outputs that are a function of **input variables**
  - ⌚ **Fill** in the truth table for these outputs
- 3) **Label** all gate outputs that are functions of input variables and **previously labeled gates**
  - ⌚ **Fill** in the truth table columns for these outputs
- 4) **Repeat** step (3) until the columns for **all** the outputs are obtained
- 5) **Simplify** the obtained Output Function using K-Map (**if required**)

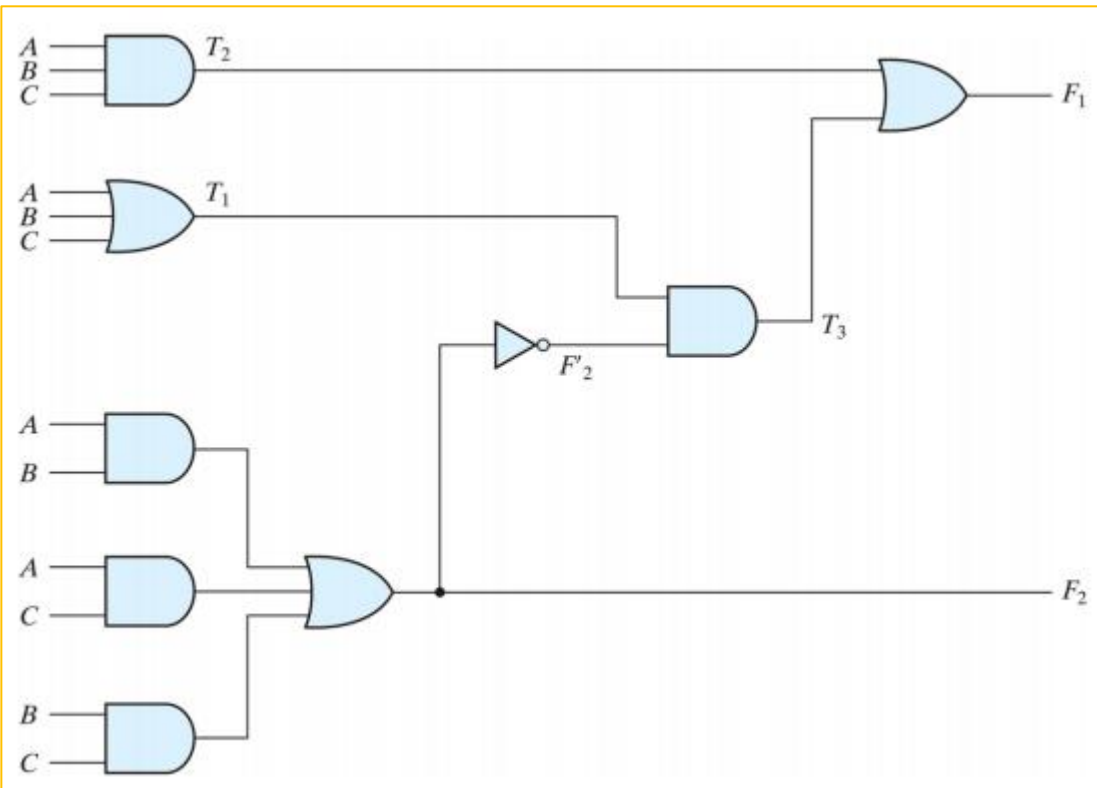**Example:**


Analyze the below logic circuit by establishing the **truth table** for  $F_1$  and  $F_2$ .



<b>A</b>	<b>B</b>	<b>C</b>	<b><math>F_2</math></b>	<b><math>F_2'</math></b>	<b><math>T_1</math></b>	<b><math>T_2</math></b>	<b><math>T_3</math></b>	<b><math>F_1</math></b>
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

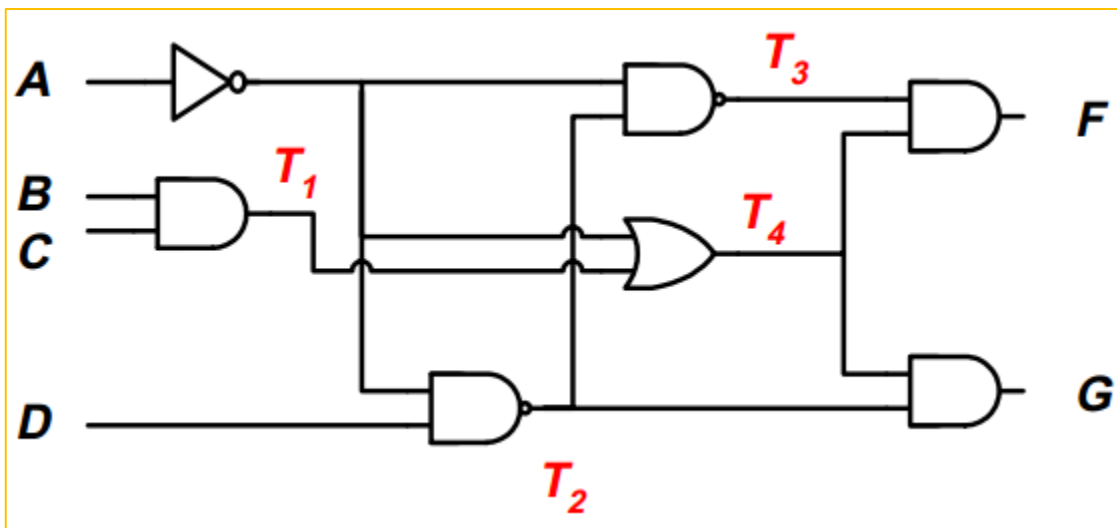**Extra Example:**

Analyze the below logic circuit by establishing the **truth table** for **F** and **G**.



Inputs								Outputs	
A	B	C	D	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>	T <sub>4</sub>	F	G
0	0	0	0	0	1	0	1	0	1
0	0	0	1	0	0	1	1	1	0
0	0	1	0	0	1	0	1	0	1
0	0	1	1	0	0	1	1	1	0
0	1	0	0	0	1	0	1	0	1
0	1	0	1	0	0	1	1	1	0
0	1	1	0	1	1	0	1	0	1
0	1	1	1	1	0	1	1	1	0
1	0	0	0	0	1	1	0	0	0
1	0	0	1	0	1	1	0	0	0
1	0	1	0	0	1	1	0	0	0
1	0	1	1	0	1	1	0	0	0
1	1	0	0	0	1	1	0	0	0
1	1	0	1	0	1	1	0	0	0
1	1	1	0	1	1	1	1	1	1
1	1	1	1	1	1	1	1	1	1

**Design** involves the specifications of **design objectives** and the creation of the **logic circuit diagram** according to these specifications

### 1) Specification

- Describe the problem
- Specify the **number** of inputs and outputs
- Assign a **letter symbol** to each input/output

### 2) Formulation

- Convert the specification into **truth tables** for outputs

### 3) Logic Minimization

- Derive a Boolean function for each output as a function of inputs and **minimize** these functions using **K-map** or **Boolean algebra**

### 4) Technology Mapping

- Draw a **logic diagram** using logic gates/functional blocks

### 5) Verification

- Verify the **correctness** of the design, either **manually** or using **simulation**

**Example:** Design a circuit that takes **BCD** and convert it to **excess-3**


### 1) Specification

- ⌚ **Describe:** Convert BCD code to Excess-3 code.
- ⌚ **Specify:** Input: 4-bit BCD code , Output: 4-bit Excess-3 code
- ⌚ **Assign:** BCD input: **A, B, C, D** , Excess-3 output: **w, x, y, z**


### 2) Formulation

- ⌚ Done easily with a **truth table**
- ⌚ **Note:** Output is **don't care** for 1010 to 1111


Inputs (BCD Code)				Outputs(Excess-3)			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

 **Example Cont.:**Design a circuit that takes **BCD** and convert it to **excess-3****3) Logic Minimization using K-maps**4 outputs  $\rightarrow$  4 K-Maps


$$w = A + BC + BD$$

 

$$x = B'C + B'D + BC'D'$$

 

$$y = CD + C'D'$$

 

$$z = D'$$

**Example Cont.:**

		K-map for w				K-map for x				K-map for y				K-map for z			
		cd				cd				cd				cd			
		00	01	11	10	00	01	11	10	00	01	11	10	00	01	11	10
ab	00						1	1	1	1		1		1			1
	01		1	1	1	1				1		1		1			1
	11	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
	10	1	1	X	X		1	X	X	1		X	X	1		X	X

Minimal Sum-of-Product expressions:

$$w = a + bc + bd, \quad x = b'c + b'd + bc'd', \quad y = cd + c'd', \quad z = d'$$

Additional 3-Level Optimizations: extract common term  $(c + d)$

$$w = a + b(c + d), \quad x = b'(c + d) + b(c + d)', \quad y = cd + (c + d)'$$


Double  
DeMorgan's Law  
(in x, y)



**Example Cont.:** Design a circuit that takes **BCD** and convert it to **excess-3**

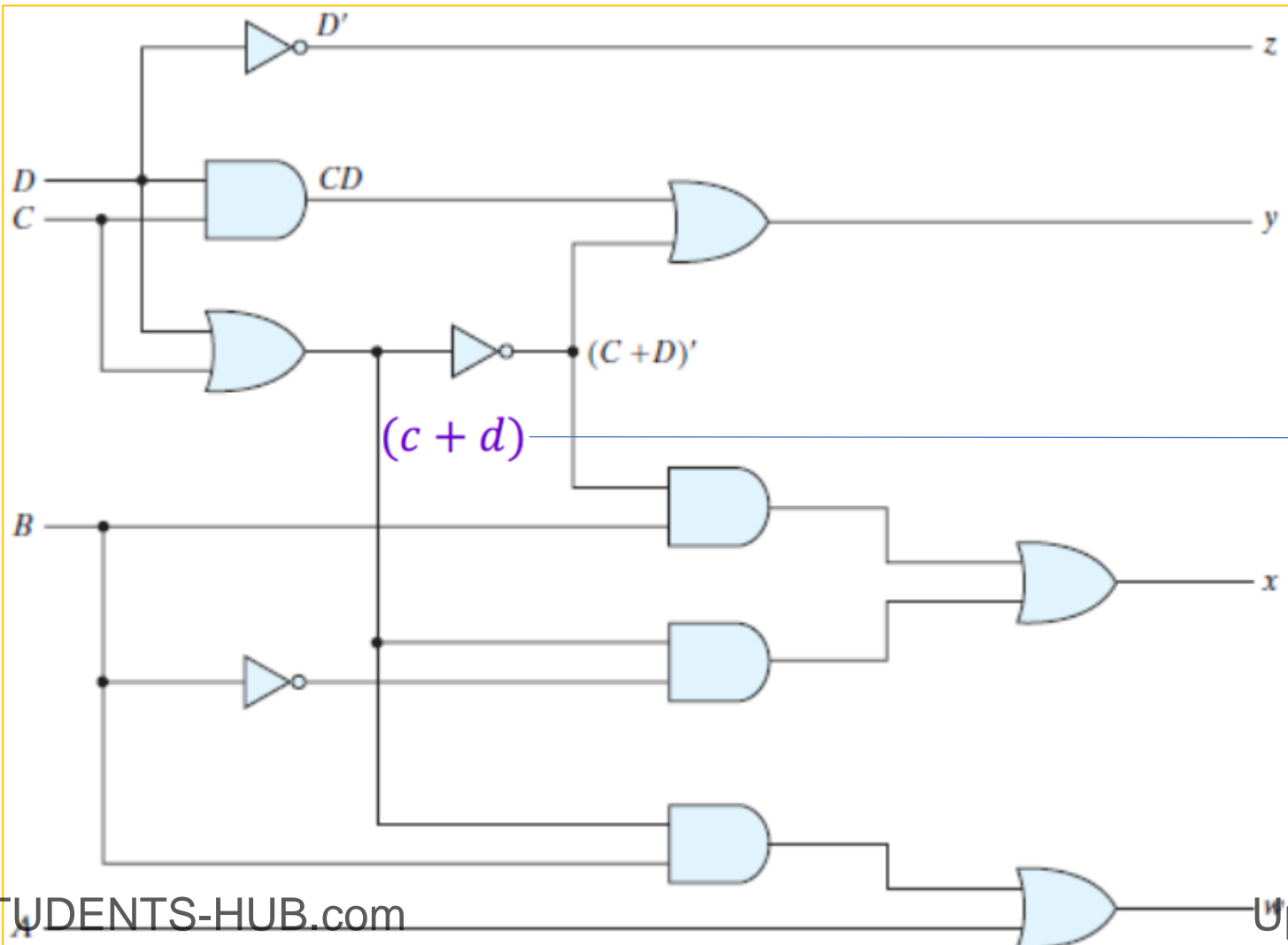**4) Technology Mapping** (Draw a **logic diagram** using ANDs, ORs, and inverters)

$$w = a + b(c + d), x = b'(c + d) + b(c + d)', y = cd + (c + d)', z = d'$$



When **multiple** outputs exist, it is common practice to optimize their functions to create **common** gates across them, even if this leads to **nonstandard** forms.

**Example Cont.:**Design a circuit that takes **BCD** and convert it to **excess-3****5) Verification**

- ⊗ Can be done **manually**
  - Ⓜ **Extract** output functions from circuit diagram
  - Ⓜ Find the **truth table** of the circuit diagram
  - Ⓜ **Match** it against the **specification truth table**
- ⊗ Verification process can be **automated**
  - Ⓜ Using a **simulator** for complex designs



- ☉ There are several **combinational** circuits that are **employed extensively** in the design of digital systems.
- ☉ These circuits are available in integrated circuits and are classified as **standard components**. They perform **specific** digital functions commonly needed in the **design** of digital systems.
- ☉ Most **important** standard combinational circuits
  - ☐ Adders and Subtractors
  - ☐ Comparators
  - ☐ Decoders
  - ☐ Encoders
  - ☐ Multiplexers

A combinational circuit that performs the **addition** of **two bits** is called a **Half Adder**

### Recall that

- 0+0 = 0 and **carry** of 0
- 0+1 = **1** and **carry** of 0
- 1+0 = **1** and **carry** of 0
- 1+1 = 0 and **carry** of **1**

Inputs: **2** bits (x, y)


Outputs: **2** bits (**Sum**, **Carry**)

<b>x</b>	<b>y</b>	<b>C</b>	<b>S</b>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Obtain the simplified Boolean functions.


$$S = xy' + x'y = x \oplus y$$

$$C = xy$$

 

$$S = xy' + x'y$$

$$C = xy$$

 

$$S = x \oplus y$$

$$C = xy$$


🌀 A **full adder** is a combinational circuit that forms the arithmetic **sum of three bits**

- 🌀 **Inputs: 3 bits**
- 📌 Two bits → significant **input** bits to be added
  - 📌 Third bit → **carry** from the **previous** stage

- 🌀 **Outputs: 2 bits**
- 📌 Sum (S)
  - 📌 Carry (C)


1

3

 

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

2

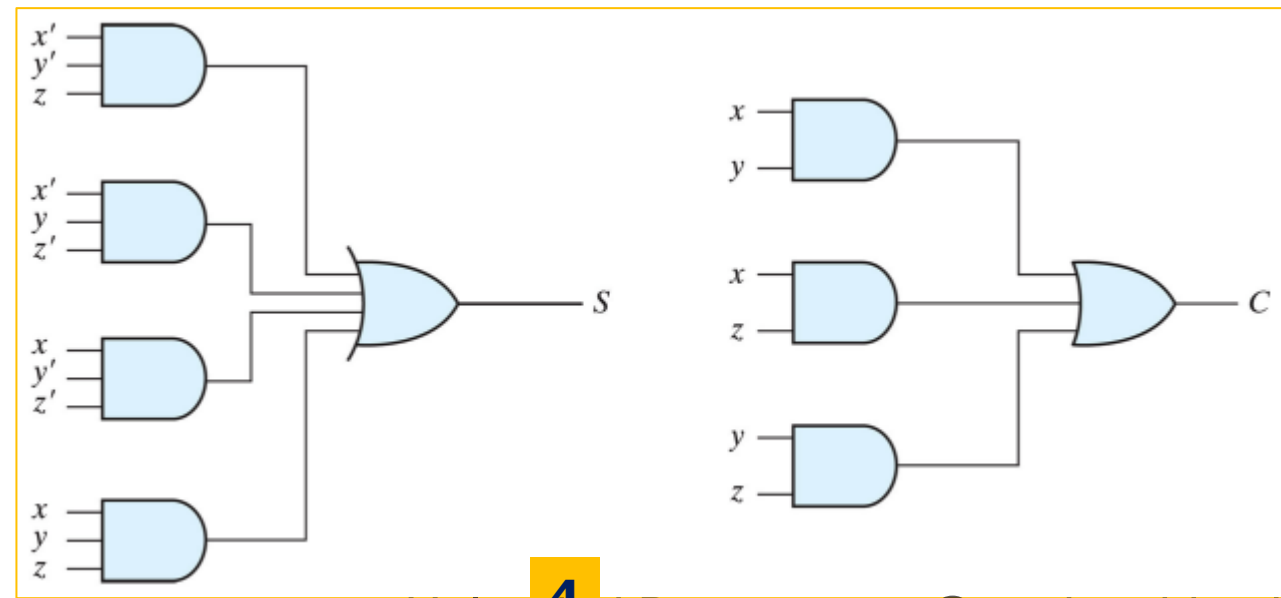

4

🌀 **Manipulate** the expressions of **S,C** to get more **familiar** forms

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = \sum(1,2,4,7)$$

$$= x' y' z + x' y z' + x y' z' + x y z$$

$$= (x' y' + x y) z + (x' y + x y') z'$$

$$= (x \oplus y)' z + (x \oplus y) z'$$

$$= (x \oplus y) \oplus z$$


$$C = \sum(3,5,6,7)$$

$$= x y + x z + y z$$


$$= x' y z + x y' z + x y$$

$$= (x' y + x y') z + x y$$

$$= (x \oplus y) z + x y$$

 

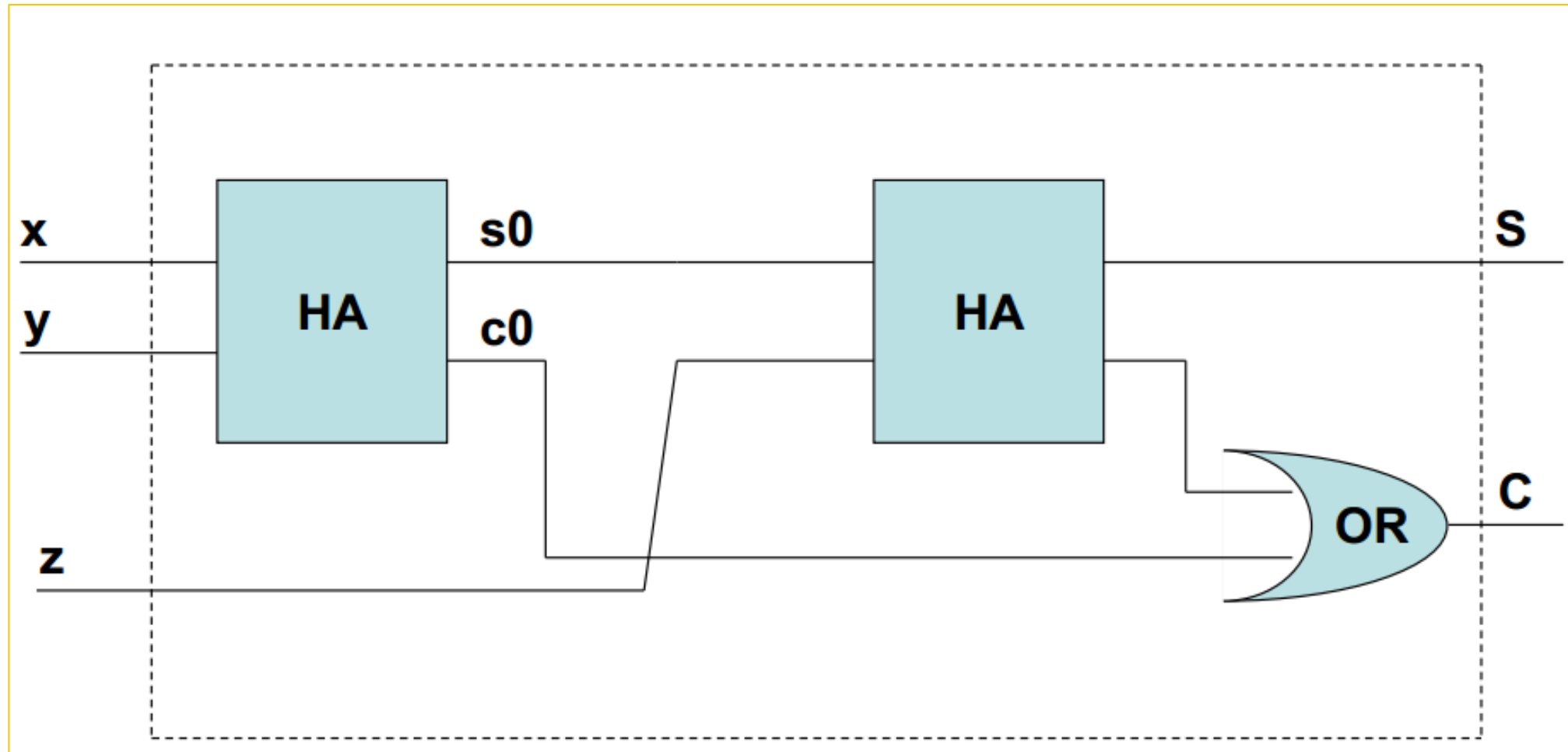Utilize the Standard HA circuit to build FA



## 🌀 Practical **Arithmetic/Logical** Functions

- 📌 **Bitwise Operations:** Perform operations on binary bit **vectors** (e.g., adding, subtracting, multiplying). Each bit position can utilize the same basic **sub-function**, allowing for consistency across operations.
- 📌 **Modular Design Approach:** To simplify the complexity of handling large inputs and outputs, design a **reusable sub-function block** (cell) for each bit. This block can be **replicated** (iterative array) to create larger functional blocks for overall operations, facilitating more manageable and efficient circuit design across various arithmetic and logical functions.




- ⌘ The process of addition proceeds on a **bit-by-bit** basis, **right to left**, beginning with the **least significant bit (LSB)**
- ⌘ Include the **carry** in the addition

carry		1	1	1	1				
	0	0	1	1	0	1	1	0	(54)
+	0	0	0	1	1	1	0	1	(29)
<hr/>									
	0	1	0	1	0	0	1	1	(83)
bit position:	7	6	5	4	3	2	1	0	

- ⊗ A **Parallel Binary Adder** is a digital circuit that produces the arithmetic **sum** of **two** binary numbers
- ⊗ We can construct it by **cascading FAs**. We need **n-FA** for an **n-bit** number
  - Ⓜ Each **FA** adds **3** bits:  $A_i, B_i, C_i \rightarrow$  producing:  $S_i$  and  $C_{i+1}$ 
    - ★ ( $C_i$  : Carry in,  $C_{i+1}$  : Carry out)

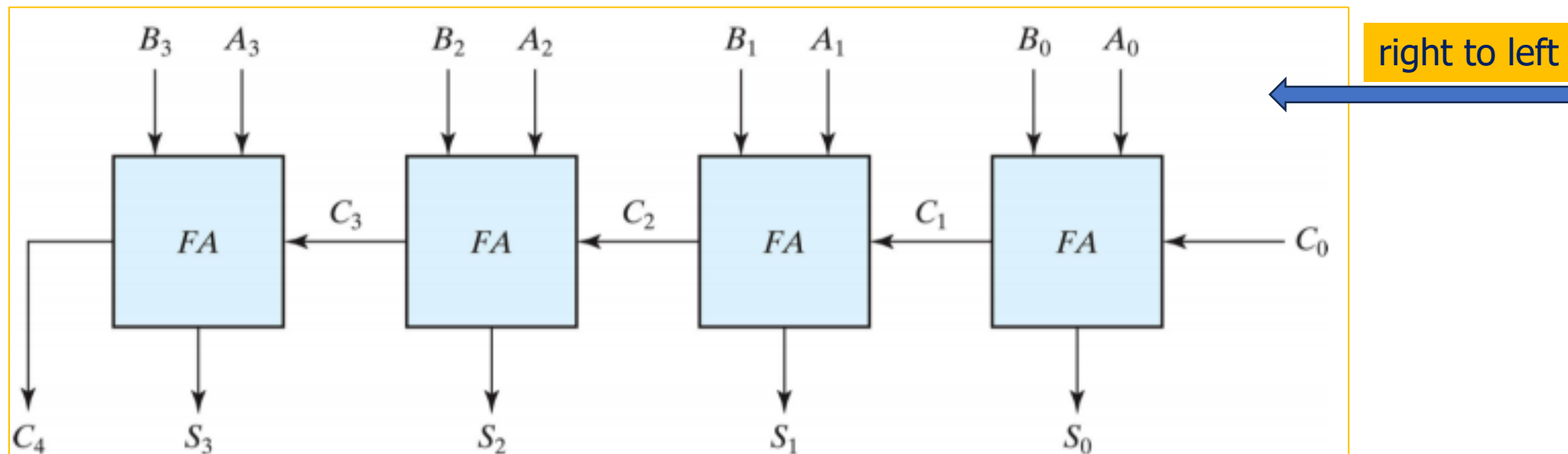For 4-bit numbers  $A + B \equiv A_3A_2A_1A_0 + B_3B_2B_1B_0$




**Example:**

A = 1011

B = 0011

Subscript $i$ :	3	2	1	0	
Input carry	0	1	1	0	$C_i$
Augend	1	0	1	1	$A_i$
Addend	0	0	1	1	$B_i$
Sum	1	1	1	0	$S_i$
Output carry	0	0	1	1	$C_{i+1}$


right to left

 




- 🌀 The **four-bit** Parallel Adder is a typical example of a **standard component**. It can be used in many applications involving arithmetic operations
- 🌀 Observe that the design of this circuit by the **classical** method would require a truth table with  $2^9 = 512$  entries (  $n=9 : A_0A_1A_2A_3 B_0B_1B_2B_3 C_0$  )
- 🌀 It becomes possible to obtain a simple and straightforward implementation by using the previously mentioned **Modular Design Approach** to construct iteratively the **4-bit Parallel Binary Adder** using **sub-function blocks/cells** of the **Full Adder (FA)**
- 🌀 This Parallel Binary Adder is commonly known as **Ripple-Carry Binary Adder**

- ☉ The **sum bits** are readily available
- ☉ We need to **wait** for the **last carry bit** ( $C_4$ ) to be calculated (**Propagated**)
- ☉ Each gate needs **some time** to produce output
- ☉ **Two** gates (one AND & one OR) are used to generate each carry bit
  - 📌 For a **four-bits** Adder,  $C_4$  is generated using ( $2 \times 4$ ) gates
- ☉ This **Carry waiting time** is called **Carry propagation** and it limits the **speed** of overall computations

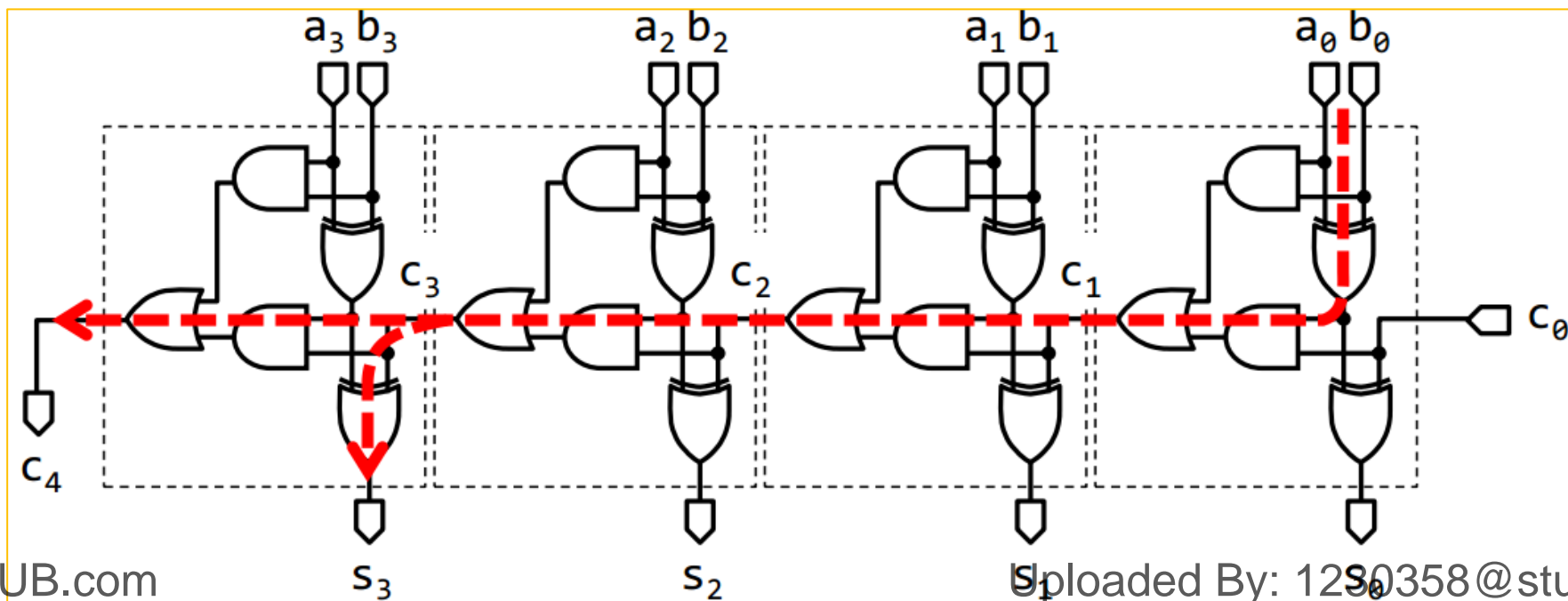

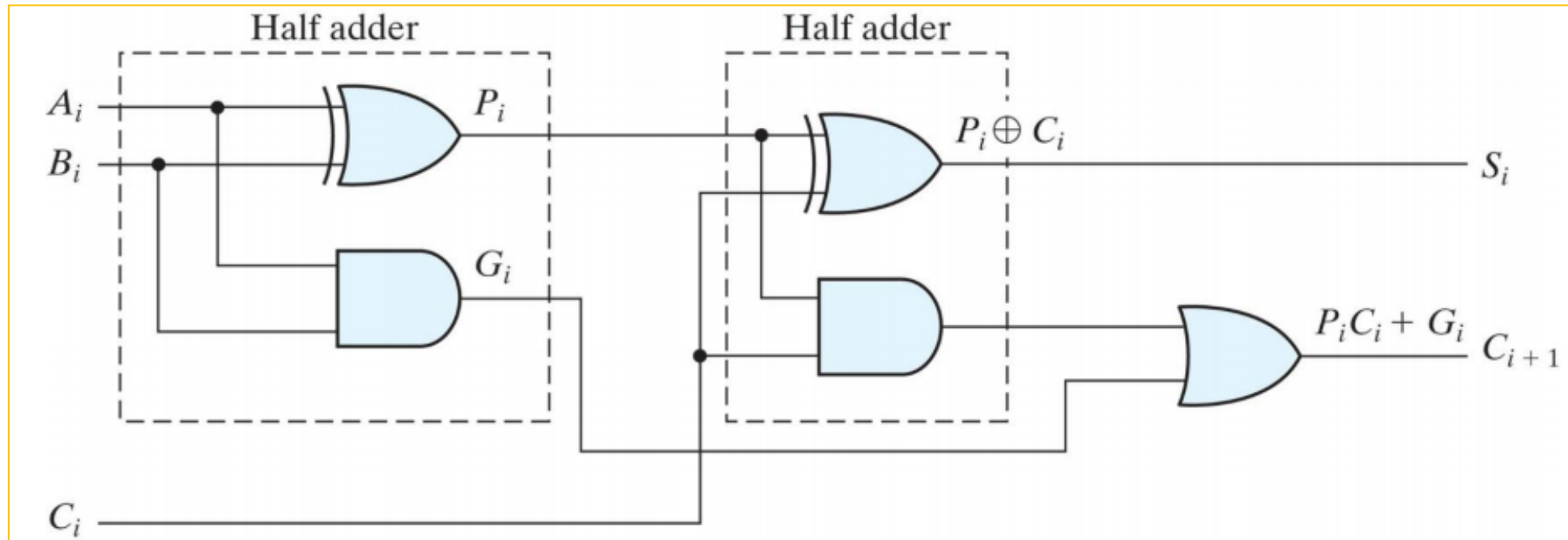- 🌀 The most widely used method to reducing the carry propagation in a parallel binary adder is called the **Carry Lookahead Logic**.



$$P_i = A_i \oplus B_i$$

$$G_i = A_i \cdot B_i$$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

Carry Propagate

Carry Generate ( $C_{i+1} = 1$  if  $G_i = 1$ )

Output Sum

Output Carry

Write the Boolean functions for the **Carry outputs** of each stage

$$C_{i+1} = G_i + P_i C_i$$

$C_0 =$  input carry

$$C_1 = G_0 + P_0 C_0$$


$$C_2 = G_1 + P_1 C_1$$

$$= G_1 + P_1 (G_0 + P_0 C_0)$$


$$= G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

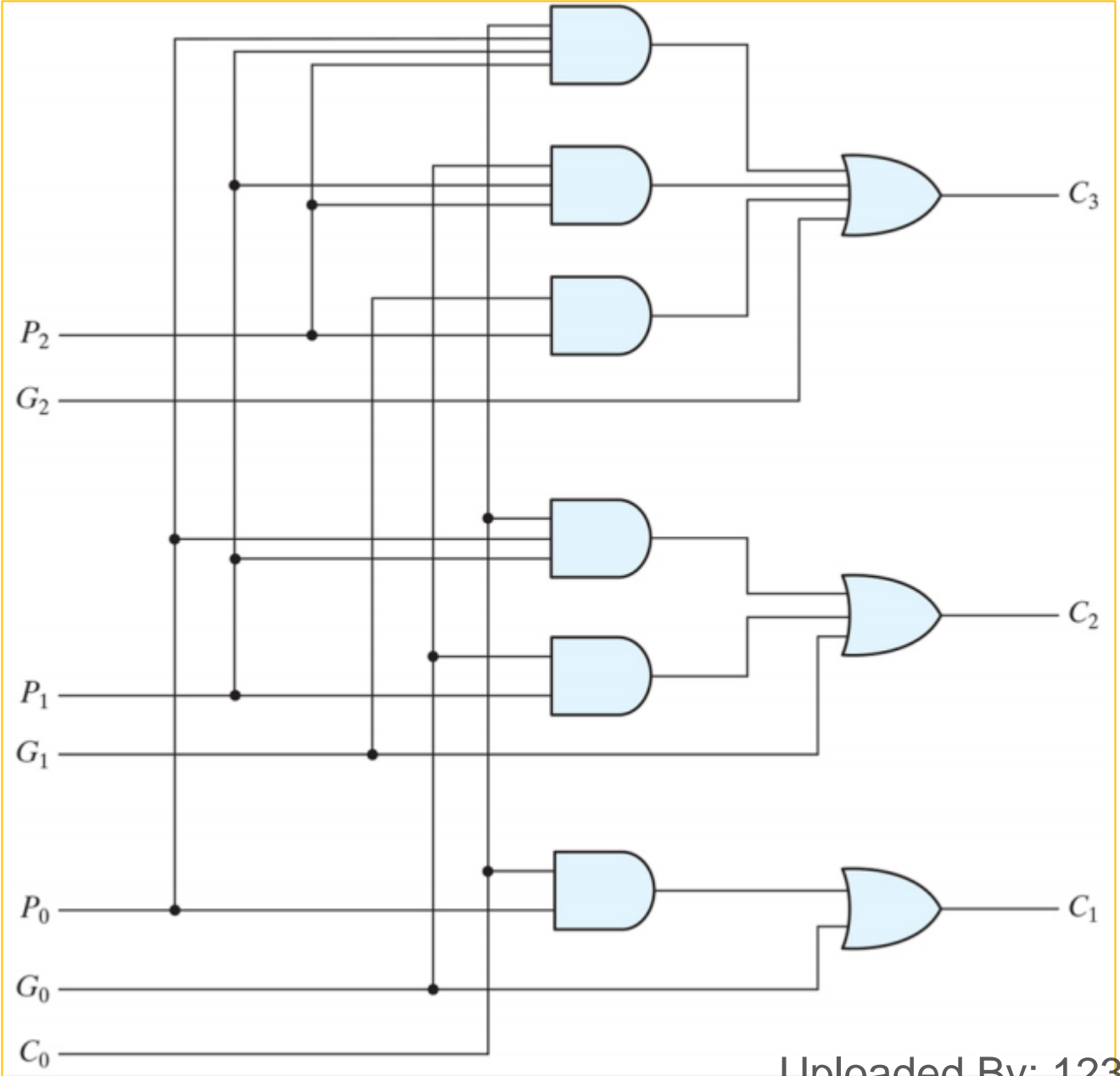- Note that **P's and G's** are functions of **only** A's and B's (**inputs**)
- ALL** carries are **dependent** on the **inputs only** ( $C_3$  does not have to wait for  $C_2$  and  $C_1$  to become available;  $C_3$  is propagated at the **SAME TIME** as  $C_2$  and  $C_1$ ).
- This **SPEED GAIN** is traded off with increase in **COMPLEXITY (No. of Gates)**





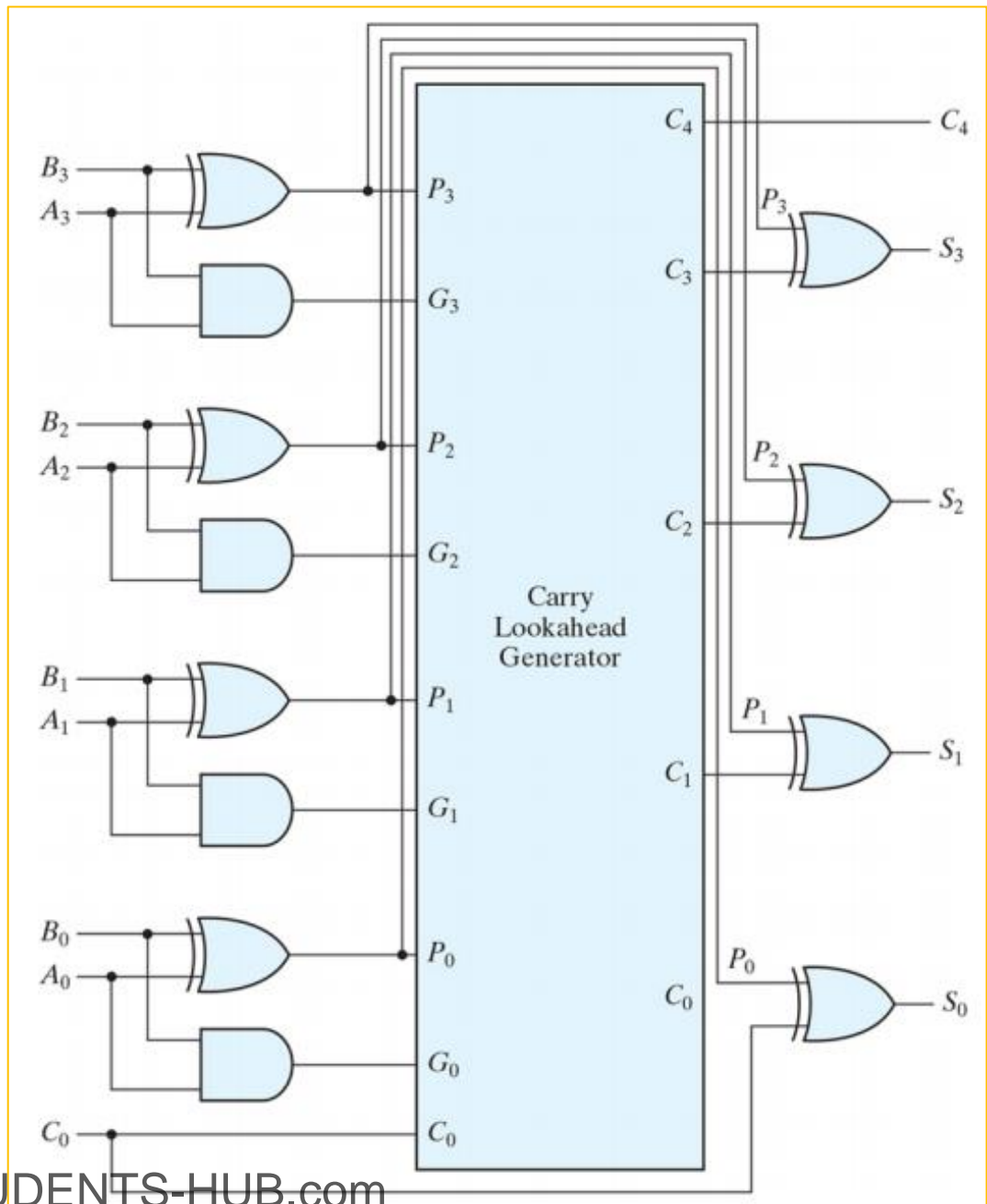

- Each **sum** output requires **two** XOR gates.
- All output **carries** are generated after exactly a **delay** through **two levels** of gates.
- The **delay** of the carry lookahead adder is **constant**.


☞ **Recall:**  $A - B = A + 2's(B)$

☞ 2's complement of B is taken by first finding the 1's complement (**inverting each bit of B**), then a **1** is added.

☞ This implies that, **Subtraction** can be performed using an **adder by:**

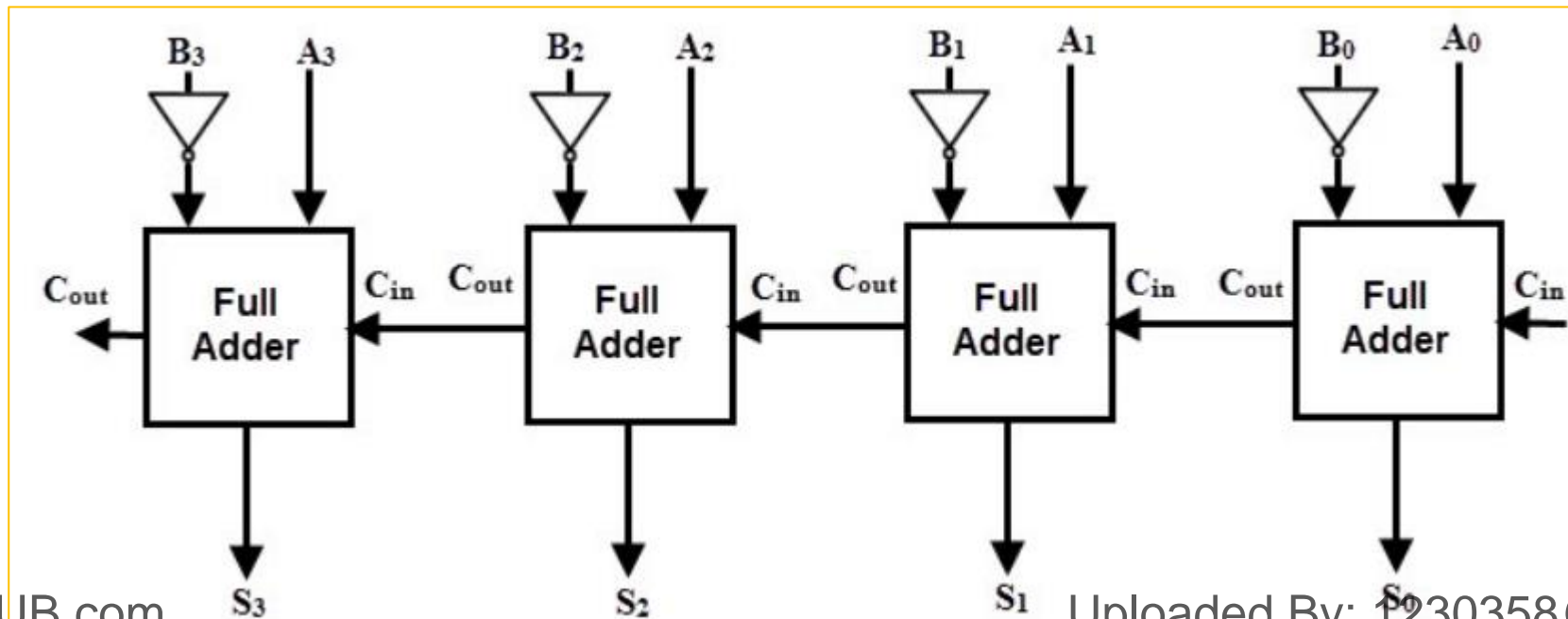
- 1) **Invert** the bits of input B ( $\rightarrow$  1's complement of B)
  - 2) Change  $C_0$  to **1** ( $\rightarrow +1$ )
  - 3) Add A & **2's (B)** ( $\rightarrow A-B$ )
- } 2's complement of B

☞ Binary **subtractor** can be used to perform subtraction for both **signed and unsigned** number systems



☉ A four-bit adder can be used to design a circuit that can perform **both** the **addition** and **subtraction** operations by Introducing a **Mode Bit (M)** and **4 XOR Gates**

 ☉ **Recall:**  $B \oplus 1 = B'$  ( $\rightarrow$  B can be inverted if **Xored** with 1)



- 1)  $M = 1 \rightarrow (A + 1's \text{ complement } B + 1)$ 
  - I) Unsigned numbers Case:
    - if  $A \geq B \rightarrow A - B$
    - if  $A < B \rightarrow 2's \text{ complement of } (B - A).$
  - II) Signed numbers Case:
    - $\rightarrow A - B$  if there is no overflow (V)
- 2)  $M = 0 \rightarrow \text{Adder} \rightarrow (A + B)$

The mode bit:  $M = 0$  for **adder**

The mode bit:  $M = 1$  for **subtractor**

## 4-bit adder-subtractor

example:

				C0	M	S3	S2	S1	S0
A = 6	0	1	1	0	0	A + B			
	0	1	0	0		1	0	1	0
A = 5	0	1	0	1	1	A - B			
	0	1	0	0		0	0	0	1
A = -4	1	1	0	0	1	A - B (signed)			
	1	0	0	1		0	0	1	1

☯ Overflow occurred when two numbers with **n digits** each are added/subtracted and the **result** is a number with **n+1 digits**

1) For **Unsigned numbers** an **overflow** is detected from the **end carry** out of the **most significant position**.

☯ In a 4-bit adder, **A=1111, B=0001** →  $A+B=1\ 0000$  [S = 0000 , C = 1 → **Overflow**]

2) For Signed Numbers:

☯ The **leftmost** bit represents the **sign**

☯ When two signed numbers are added, the sign bit is treated as part of the number and the **end carry does NOT** indicate an **overflow**.

☯ An overflow may occur if the two numbers added are **both** positive or **both** negative.

☯ An overflow condition can be detected by observing the carry into the sign bit position and the carry out of the sign bit position

☯ If these **two carries** are **NOT** equal, an **overflow** has occurred → **XOR gate** function

carries:

0 1

+70

0 1000110

+80

0 1010000

+150

1 0010110

carries:

1 0

-70


1 0111010

-80

1 0110000

-150

0 1101010

 

- 1)  $M = 1 \rightarrow (A + 1\text{'s complement } B + 1)$ 
  - I) **Unsigned** numbers Case:
    - if  $A \geq B \rightarrow A - B$
    - if  $A < B \rightarrow 2\text{'s compl. of } (B - A)$
  - II) **Signed** numbers Case:
    - $\rightarrow A - B$  if there is **NO** overflow (V)
- 2)  $M = 0 \rightarrow \text{Adder} \rightarrow (A + B)$


**I. Unsigned** numbers Case: **C** bit detects a carry after addition or a borrow after subtraction

**II. Signed** numbers Case: **V** bit detects an **overflow**

1)  $V = 0$  means **NO** overflow occurred and the n-bit result is correct

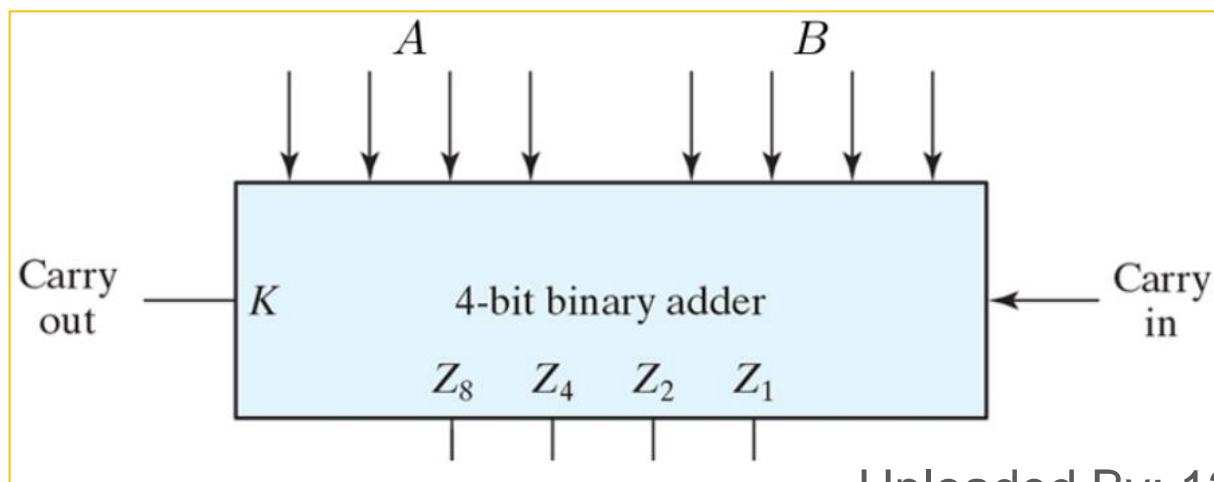2)  $V = 1$  means **overflow has occurred** and the result needs **n + 1** bits to fit  $\rightarrow$  The n-bit result is **incorrect**

- Used to add two decimal digits in BCD
- This adder is present in systems used to perform **decimal addition directly** (e.g. calculators, etc.)
- This adder accepts **two** decimal numbers (**A and B**) in coded form (**BCD**) and **one** carry digit from the previous stage
- The carry digit from the previous stage could be either 0 or 1. → need just **one-bit** for the carry digit
- The **minimum** possible sum at any stage could be  $0 + 0 + 0 = 0$
- The **maximum** possible sum at any stage could be  $9 + 9 + 1 = \mathbf{19}$
- Requires a minimum of **9 inputs** and **5 outputs**
  - Input (A: 4 Bits , B: 4 Bits, Carry in: 1 Bit)                      Output (Result: 4 Bits, Carry out: 1 Bit)





Binary Sum					BCD Sum					Decimal
K	Z <sub>8</sub>	Z <sub>4</sub>	Z <sub>2</sub>	Z <sub>1</sub>	C	S <sub>8</sub>	S <sub>4</sub>	S <sub>2</sub>	S <sub>1</sub>	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19


**Recall:** a **correction** in the sum is needed when the sum is **greater** than 9. The correction is **adding 6** to the sum.

→ The BCD adder will then consist of the 4-bit binary adder. **A second 4-bit** binary adder is needed to add **6** to the sum when it is greater than 9.


When C = 0,  
**Do Nothing!**

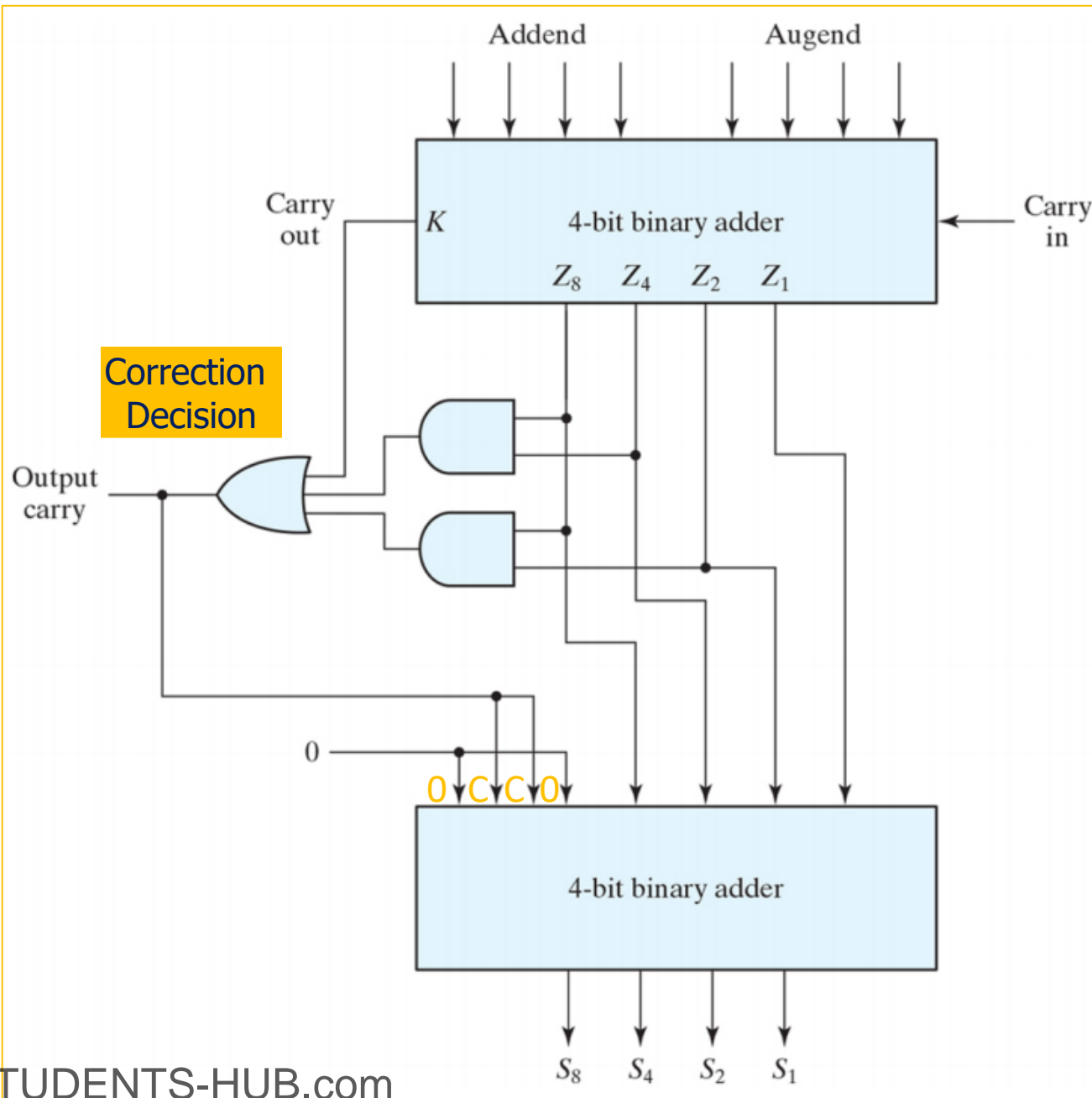When C = 1, **Add 0110** to the binary sum and provide an output carry for the next stage.






$$C = K + Z_8Z_4 + Z_8Z_2$$

 


- 🌀 **Recall:** Binary multiplication is done in the same way as decimal multiplication
- 🌀 When multiplying two binary numbers, A and B, the **multiplicand** is multiplied by **each** bit of the **multiplier** starting from the **least significant** bit.
- 🌀 Each such multiplication forms a **partial product**.
- 🌀 **Successive partial** products are **shifted one** position to the **left**.
- 🌀 The **final** product is obtained from the **sum** of the **partial** products.

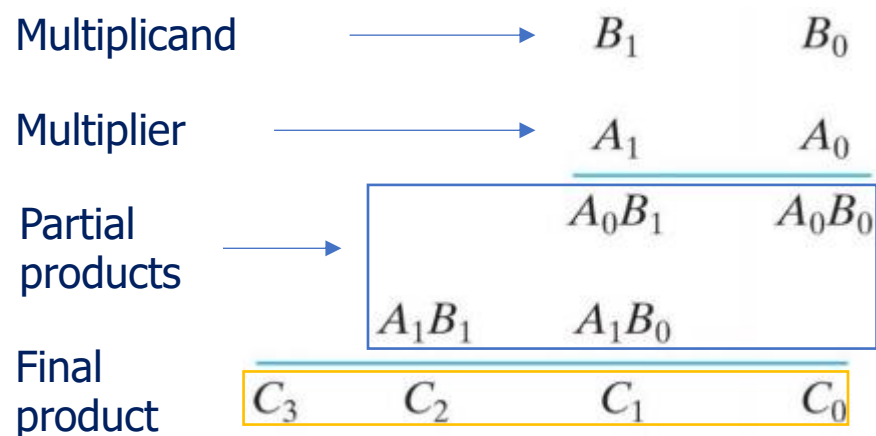

**Observe:** The **multiplication** of two bits such as  $A_0$  and  $B_0$  produces a **1** if **both** bits are 1; otherwise, it produces a **0**. This is **identical** to an **AND** operation.

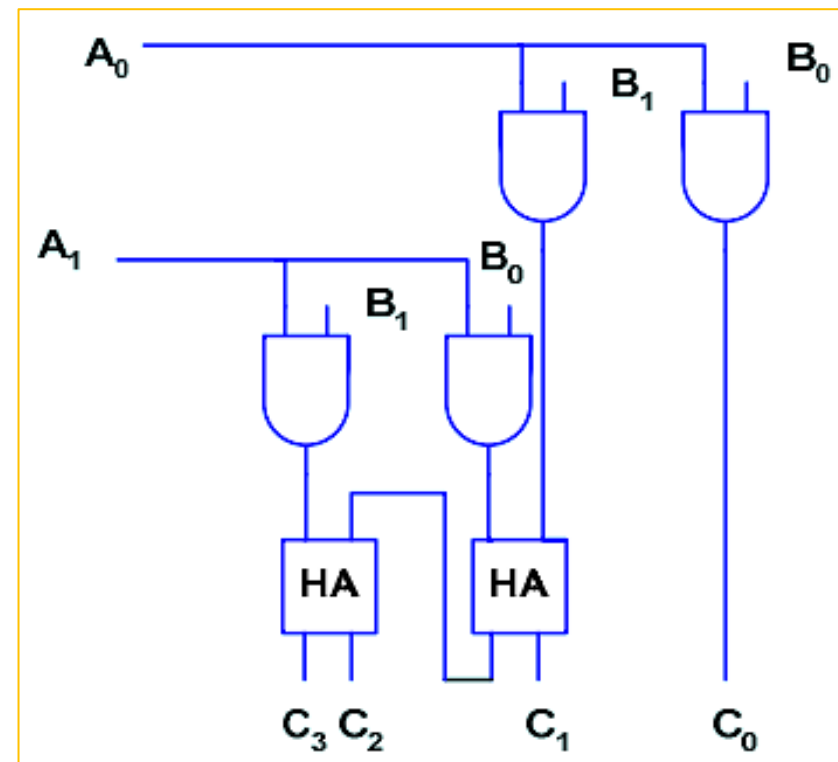Implementation could be done using **Half** adders & **AND** gates



For **J-bits Multiplier** and **K-bits multiplicand** we need:

- Ⓛ **J x K AND** gates, and
- Ⓛ **(J - 1) K-bit** adders
- Ⓛ The result will be a **product** of **(J + K)** bits.

### Example:

<b>K=4</b>	$B_3$	$B_2$	$B_1$	$B_0$		
<b>J=3</b>		$A_2$	$A_1$	$A_0$		
	$A_0B_3$	$A_0B_2$	$A_0B_1$	$A_0B_0$		
	$A_1B_3$	$A_1B_2$	$A_1B_1$	$A_1B_0$	+	
	$A_2B_3$	$A_2B_2$	$A_2B_1$	$A_2B_0$	+	
$C_6$	$C_5$	$C_4$	$C_3$	$C_2$	$C_1$	$C_0$


$J \times K = 3 \times 4 = \mathbf{12}$  AND Gates

$J - 1 = 3 - 1 = \mathbf{2}$  (4-bit) Adders


$J + K = 3 + 4 = \mathbf{7}$  bits Result

**Example:**

🌀 Design a 4-bit by 3-bit Binary Multiplier

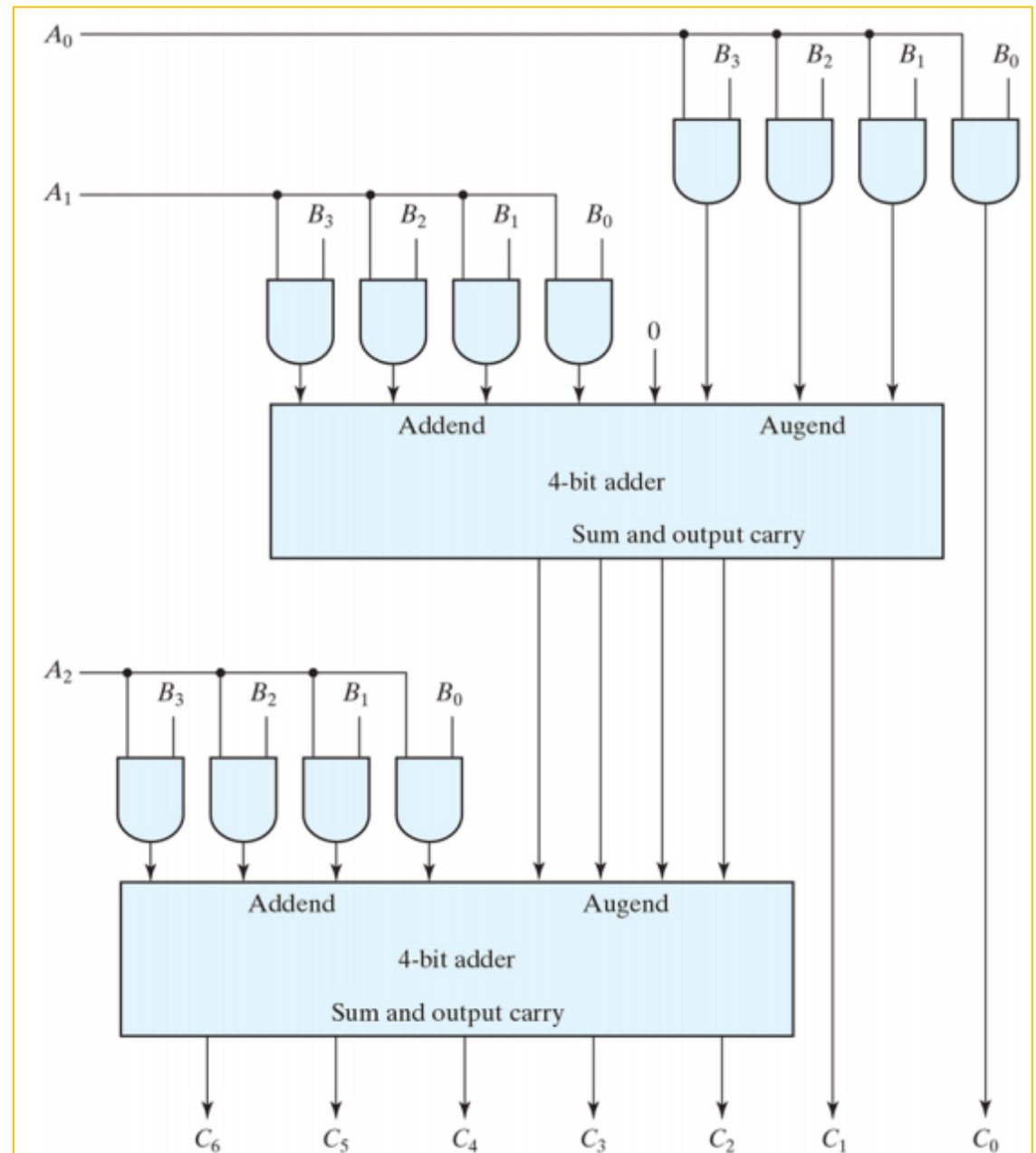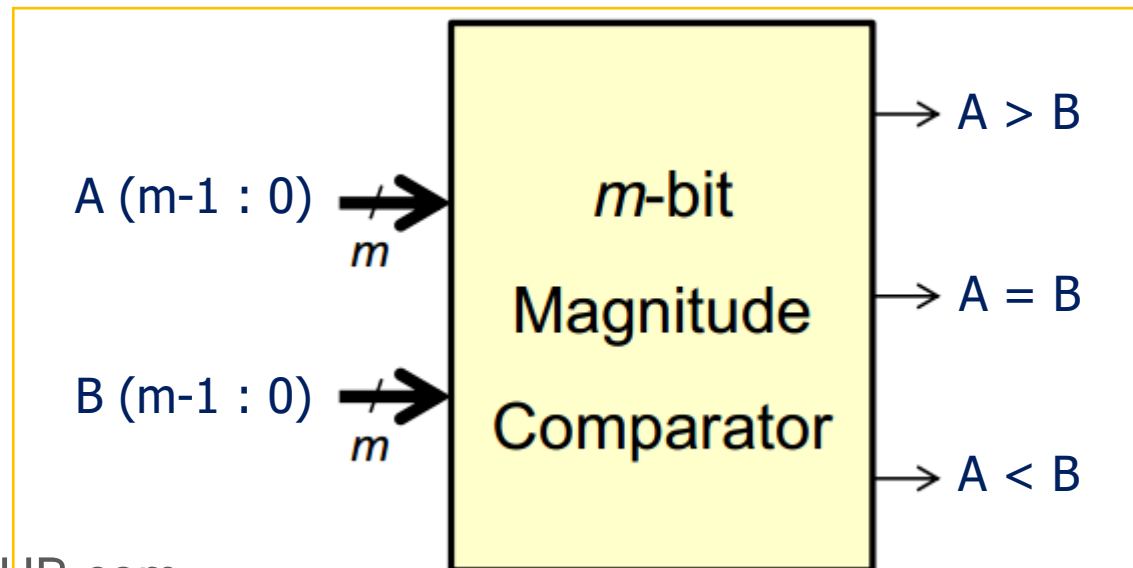**K=4****J=3****12 AND Gates****2 (4-Bit) Adders****7 bits Result**

- 🌀 A magnitude Comparator: a combinational circuit that **compares** two **unsigned** numbers A and B and determines their relative magnitudes.
- 🕒 Two Inputs:
    - 1) Unsigned integer A (m-bit number)
    - 2) Unsigned integer B (m-bit number)
  - 🕒 Three outputs:
    - 1)  $A > B$  (GT output)
    - 2)  $A = B$  (EQ output)
    - 3)  $A < B$  (LT output)
  - 🕒 **Exactly one** of the three outputs must be equal to **1** while the **remaining two** outputs must be equal to **0**



🌀 **Consider:** a circuit to compare two **4-bit** numbers A and B

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

🕒 Input/output: 8 inputs, 3 outputs  $\Rightarrow$  **huge** truth table (256 Rows)

🌀 A better method to design this circuit is to follow the **systematic** way of comparison, where we compare **each pair** of bits starting from the **most significant** bit.

🕒 If **all pairs** are **equal**  $\rightarrow A=B$ .

🕒 If we find a **difference** in the compared bits (i.e. one is 1 and the other is 0),  $\rightarrow$  the number containing the **1** is **larger**

### Case 1 (A = B):

🌟 **All pairs** of bits should be equal


$$(A_i = B_i, i = \{0, 1, 2, 3\})$$

🌟 Equality using **XNOR** operation

$$x_i = A_i B_i + A_i' B_i', i = \{0, 1, 2, 3\}$$

🌟 A = B **only if all**  $x_i$ 's are **1**
 
$$\rightarrow (A = B) = x_3 x_2 x_1 x_0$$



### Case 2 and 3 (A < B or A > B):

🌟 Compare the **most-significant** bits ( $A_3$  &  $B_3$ )

🌟 If the two bits are **equal**, Compare the **next pair** of bits ( $A_2$  &  $B_2$ )

🌟 **Continue** comparing the subsequent pairs of bits if the **previous** comparisons are **equal** ( $A_1$  &  $B_1$ ) and ( $A_0$  &  $B_0$ )

🌟 If  **$A_i \neq B_i$**  at **any** stage, then:


**A < B** if  $A_i = 0$  and  $B_i = 1$  or, simply, if  $A_i' B_i = 1$

OR **A > B** if  $A_i = 1$  and  $B_i = 0$  or, simply, if  $A_i B_i' = 1$

$\rightarrow$  In logical expressions:


$$(A < B) = A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0$$
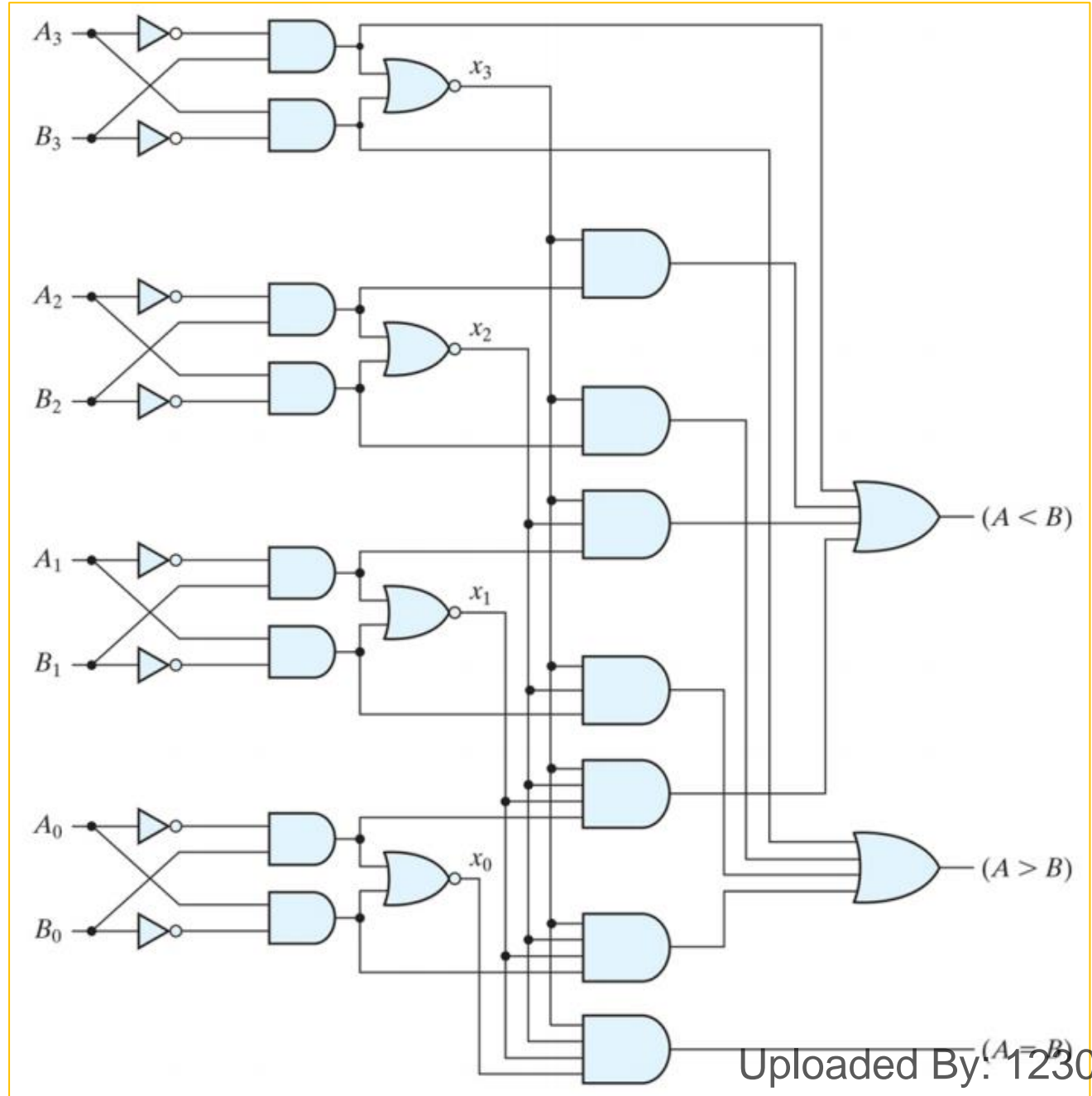
$$(A > B) = A_3 B_3' + x_3 A_2 B_2' + x_3 x_2 A_1 B_1' + x_3 x_2 x_1 A_0 B_0'$$



- Imagine that we have a circuit with a **3-bit** input **A** and a **single-bit** output **X**. The circuit should **indicate** when a particular code of 110 appears at the input. In other words, the circuit should give **X=1** at its **output** when binary number  $A_2A_1A_0 = \mathbf{110}$  occurs at its **inputs**
- This called a **decoding** process as the circuit indicates when a particular code appears at the inputs → that's why we may call it a **decoder**
- This could be extended to consider **all possible** combinations of the **input bits**

- Recall:** A binary code of **n** bits is capable of representing up to **2<sup>n</sup>** **distinct** elements
- A **decoder** is a combinational circuit that **converts** binary information from **n** input lines to a maximum of **2<sup>n</sup>** **unique** output lines
  - This is called an **n-to-m** line decoder. ( $m \leq 2^n$ , with  $m = 2^n$  we call it a Full Decoder)
- The output whose value is **1** represents the **minterm equivalent** to the **binary input**.
- Each **combination** of inputs will activate a **unique** output

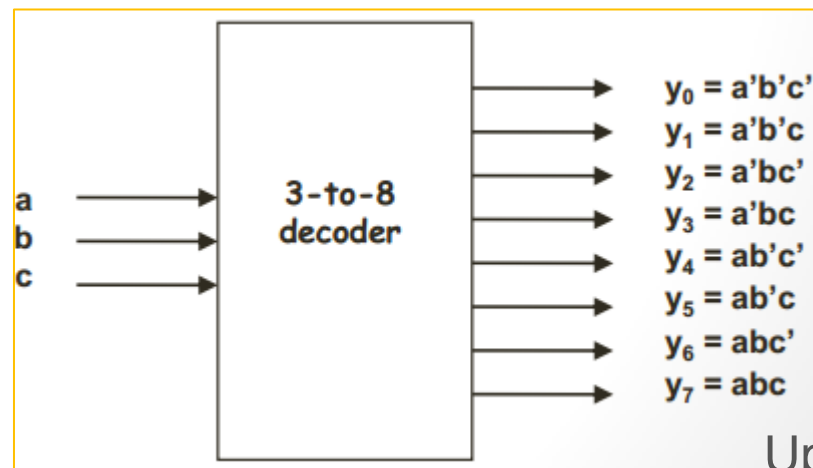

Binary **decoder** has **n** inputs and **2<sup>n</sup>** outputs  
**All 2<sup>n</sup> minterms** are generated



**Example: 3x8 Decoder**

- The 3 inputs are **decoded** into 8 outputs, each representing **one** of the **minterms** of the three input variables (**Minterms Indicator**)
- Could be considered as **Binary-to-Octal** Decoder

Inputs			Outputs							
$x$	$y$	$z$	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1



ONLY **ONE** Output is Activated (=1)

**Example: 3x8 Decoder**

This decoder can be implemented using **three inverters** and **eight AND gates**


Only **one** output is **1** while the **other** seven are **0**

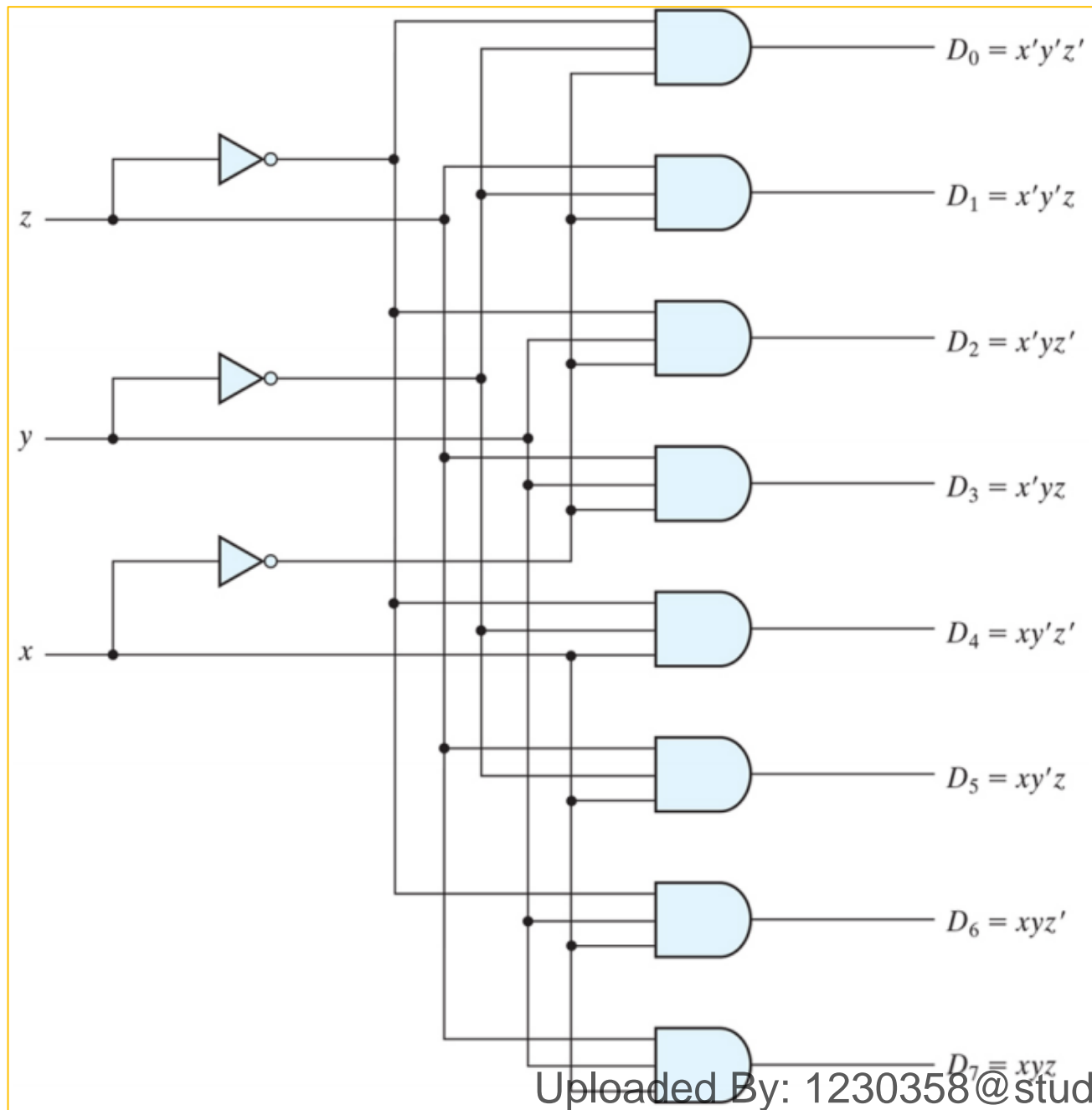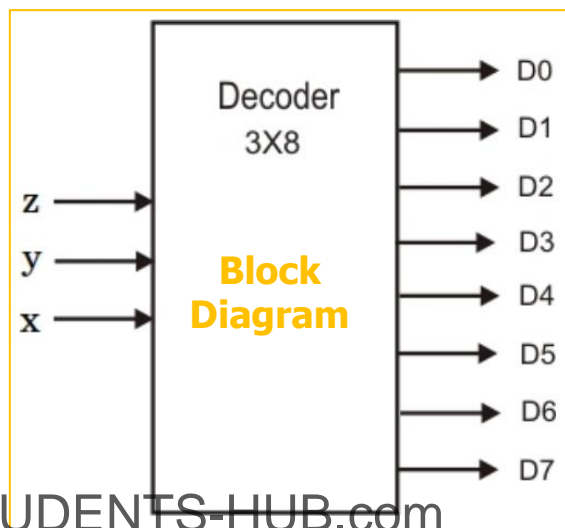The **output** whose value = 1 represents the **minterm** equivalent of the binary number currently **available** in the **input lines**




- Decoders may be constructed using **NAND** gates (**Inverted** Output Decoders)
- Decoders may include one or more **enable** inputs to **control** the circuit operation (**Demultiplexer**)
  - An **enable** is an **extra** input that will **activate** or **shut off** the Decoder

 **Inverted** Output 2 x 4 Decoder with **Enable**



<i>E</i>	<i>A</i>	<i>B</i>	<i>D</i> <sub>0</sub>	<i>D</i> <sub>1</sub>	<i>D</i> <sub>2</sub>	<i>D</i> <sub>3</sub>
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

 


The **bubble** indicates that the decoder is **enabled** when  $E=0$   
Sometime denoted as  $\overline{E}$

**Active High:** When Outputs are **1** (**Normal** Output, **AND** Gates Used)  
**Active Low:** When Outputs are **0** (**Inverted** Output, **NAND** Gates Used)

**Active High** → **minterms Generator**  
**Active Low** → **maxterms Generator**

Decoders with **enable** inputs can be **connected** together to form a **larger** decoder circuit
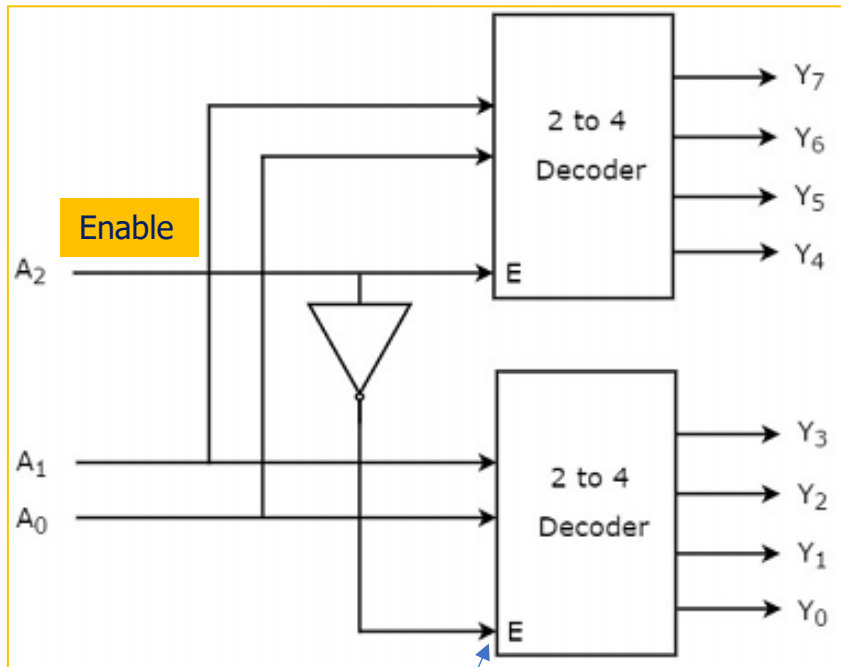
### Active high **3x8** Decoder using **2x4** Decoders



Enable			$A_2$	$A_1$	$A_0$	$Y_7$	$Y_6$	$Y_5$	$Y_4$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	0	0	1	0	0	0
0	1	1	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	0	1	0	0	0	0	0
1	0	1	0	0	0	0	1	0	0	0	0	0	0
1	1	0	0	0	0	1	0	0	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0	0	0

**No bubble** → the decoder is **enabled** when  $E=1$

**Be careful: Don't get confused**  
between **E** and the **input** variable ( $A_2$ )



- ⌘ **Recall:** A decoder provides the  $2^n$  **minterms** of  $n$  input variables.
- ⌘ **Recall:** Any Boolean function can be expressed in **sum-of-minterms** form.
- ⌘ A decoder together with an external OR gate provides a logic implementation of the function
  - ⌘ Since **all** the **minterms** of the function are **available** at the output then there is **NO** need for **simplification**
  - ⌘ **Inputs** to each **OR** gate are selected from the **decoder outputs** according to the **list of minterms** of each function


A combinational circuit with  $n$  inputs and  $m$  outputs can be implemented with an **n-to- $2^n$  decoder** and  **$m$  OR** gates

**Example:** Full Adder Implementation Using Active High (And) Decoders


$x$	$y$	$z$	$C$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S(x, y, z) = \Sigma(1, 2, 4, 7)$$

$$C(x, y, z) = \Sigma(3, 5, 6, 7)$$

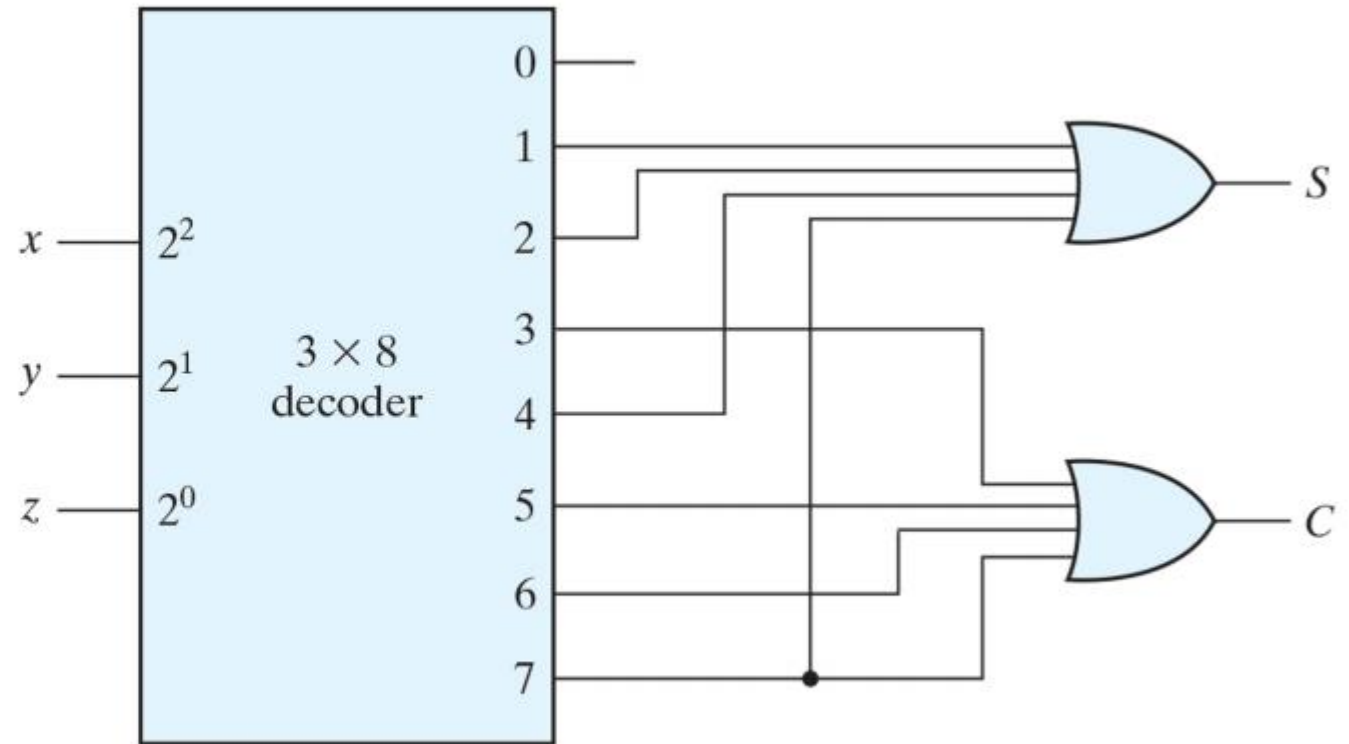


 **Example:** Implementation of  $F = \Sigma(3, 5, 6, 7)$ , Using Active Low (**NAND**) Decoders



**Active High**

$$F = \Sigma(3, 5, 6, 7)$$

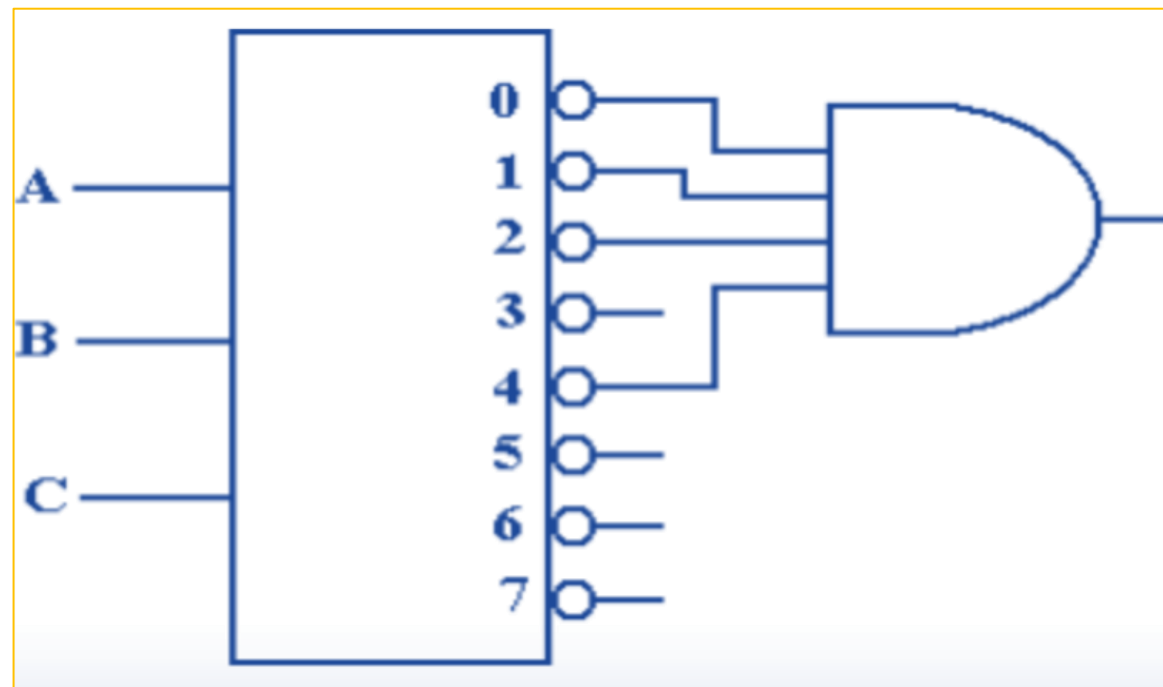

**Active Low**

$$F = \Pi(0, 1, 2, 4)$$

**F=0**, if any of these terms is **selected**  
Remember: **Selected** in Active **Low** → **0**

## General Considerations

- ⊗ A function with a **long** list of **minterms** requires an **OR** gate with a **large** number of inputs.
- ⊗ A function having a list of **k minterms** can be expressed in its **complemented** form **F'** with **( $2^n - k$ ) minterms**
- ⊗ If the number of **minterms** in the function is **greater** than  **$2^n/2$**  → **F'** can be expressed with **fewer minterms**
  - ⊗ Same Applied in the case of **maxterms**
- ⊗ **Recall:** Active-**High** Decoder: **minterm generator** & Active-**Low** Decoder: **maxterm generator**

**Important!!**

## Steps for Optimized Implementation Using Decoders

- 1) Select **Simplest/Minimal** Form:
  - ⊗ Evaluate both **F and F'** → choose the one with the **fewest** terms
- 2) Choose **Decoder and External Gate**
  - ⊗ **Minterm** Generation (Active-**High** Decoder): Use **OR** with **F**, **NOR** with **F'**
  - ⊗ **Maxterm** Generation (Active-**Low** Decoder): Use **AND** with **F**, **NAND** with **F'**
- 3) Optimize with Smaller Decoders (if needed/required)
  - ⊗ Assign the **most significant variable** as an **enable input** for smaller decoders.
  - ⊗ Share **remaining inputs** across the decoders.



## Decoder Type Selection and External Gate Combination

Function Type/Form	Decoder Type	Combining Gate	Explanation
F (fewest <b>minterms</b> )	Active- <b>High</b> (Minterm Generator)	<b>OR Gate</b> to combine minterm outputs (of F)	OR gate groups outputs representing <b>F</b> minterms
F' (fewest <b>minterms</b> )	Active- <b>High</b> (Minterm Generator)	<b>NOR Gate</b> to combine minterm outputs (of F')	NOR gate groups outputs for <b>F'</b> minterms $\rightarrow$ F
F (fewest <b>maxterms</b> )	Active- <b>Low</b> (Maxterm Generator)	<b>AND Gate</b> to combine maxterm outputs (of F)	AND gate groups outputs representing <b>F</b> maxterms
F' (fewest <b>maxterms</b> )	Active- <b>Low</b> (Maxterm Generator)	<b>NAND Gate</b> to combine maxterm outputs (of F')	NAND gate groups outputs for <b>F'</b> maxterms, $\rightarrow$ F

## Summary


Step	Description
1. Simple Form	Determine whether F or F' has <b>fewer</b> terms (minterms/maxterms).
2. Select Decoder	Choose Active- <b>High</b> for <b>minterms</b> , Active- <b>Low</b> for <b>maxterms</b> .
3. Combine with Gate	Use OR/NOR for Active-High (F/F'), AND/NAND for Active-Low (F/F')
4. Smaller Decoders	Enable input used for MSB, others shared among decoders (As Required)

### Example:

$$F_1(A, B, C) = \sum(3, 5)$$


$$F_2(A, B, C) = \sum(2, 4, 5, 6, 7)$$

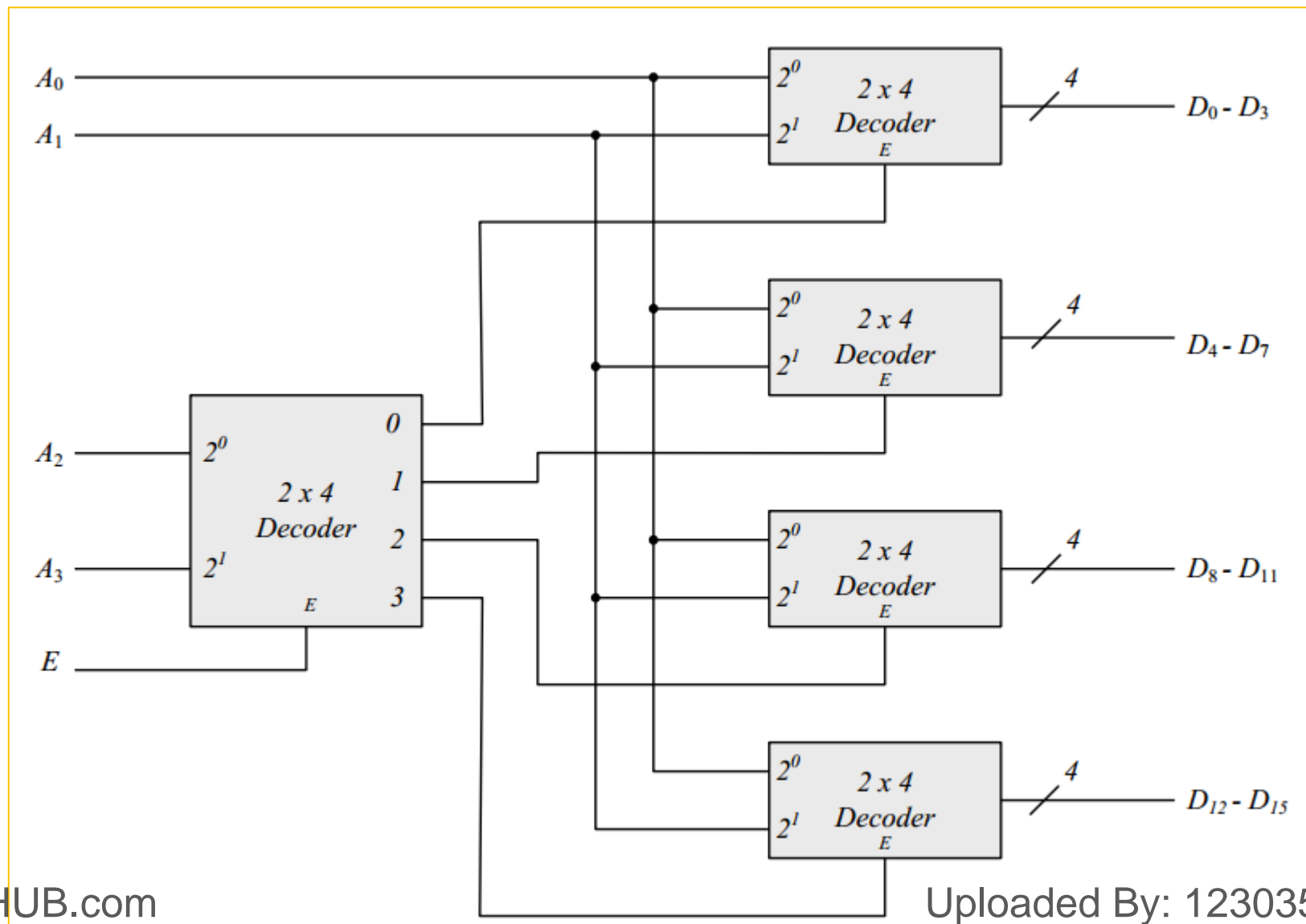**Extra Example:** Construct a **4-to-16** decoder with **Five 2-to-4** decoders with **enable**



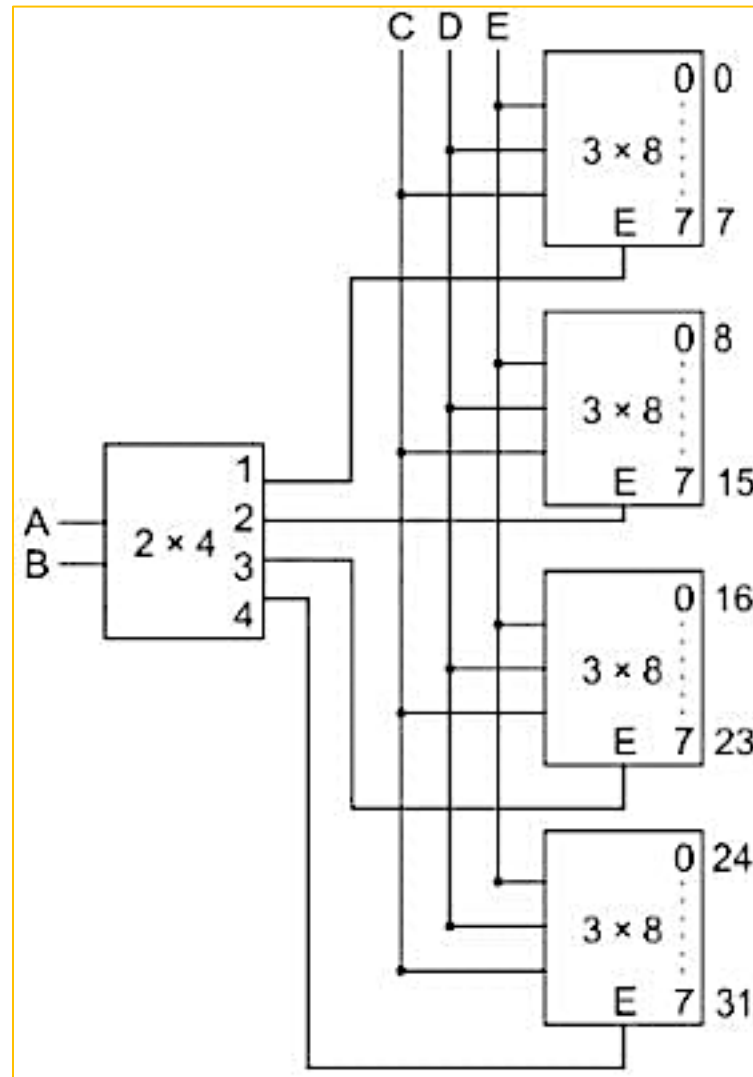
**Extra Example:**

Construct a **5-to-32** decoder with **four 3-to-8** decoders with **enable** and a **2-to-4** decoder



☯ An **Encoder** is a digital circuit that performs the **inverse** operation of a **Decoder**

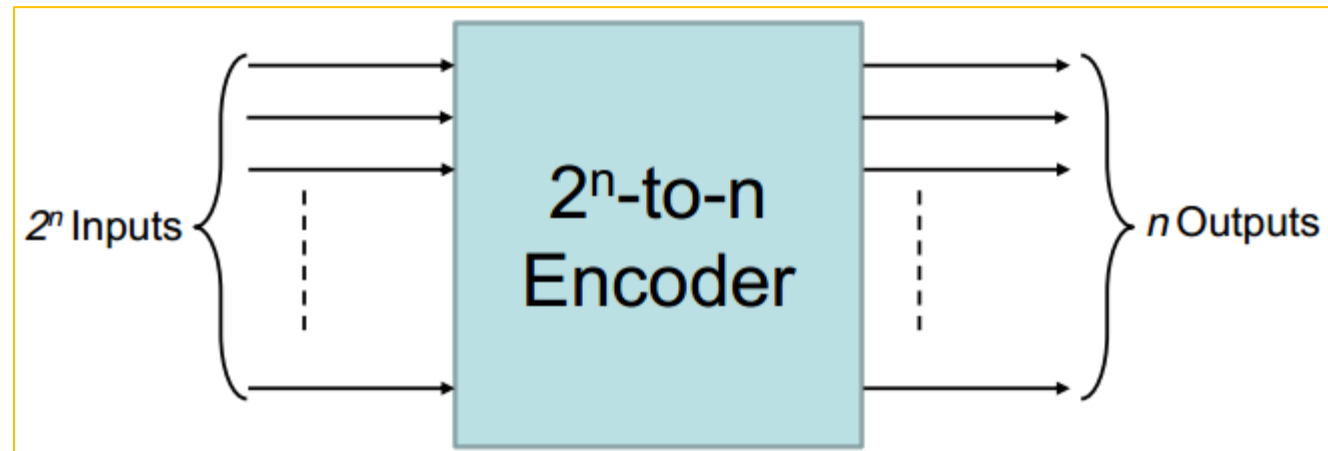- ☯ It has **maximum** of  **$2^n$  input** lines and  **$n$  output** lines
- ☯ **Output** lines give the **binary code** of the **input** lines
- ☯ **Only 1 input** line should be **active** at a time



**Example:** Design an Octal to Binary **Encoder** (8-to-3 Encoder)

Inputs								Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	$x$	$y$	$z$
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$Z = D_1 + D_3 + D_5 + D_7$$

$$Y = D_2 + D_3 + D_6 + D_7$$

$$X = D_4 + D_5 + D_6 + D_7$$

## Limitations

- 1) If **two** inputs are **active simultaneously** (say  $D_3=D_6=1$ ), then the output = 111 which does **NOT** represent either binary 3 or binary 6 (**Wrong Code**)
  - ★ Encoder circuits must establish an **input priority** to ensure that **only one** input is encoded
- 2) If ALL Input = 0s  $\rightarrow$  ALL output = 0s which is the **same** output when  **$D_0=1$** 
  - ★ This discrepancy can be resolved by providing **one more output** to indicate whether at **least** one input is equal to 1

To overcome these limitations, we may use a **priority encoder**

- ⌘ A **priority encoder** is an encoder circuit that includes the **priority** function
- ⌘ if **two or more inputs** are equal to **1** at the same time →
  - ⌘ the **input** having the **highest priority** will take precedence
- ⌘ A **valid** bit (**v**) is introduced at output to indicate the **invalid all 0s** input combination

### 4-to-2 Priority Encoder


Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$x$	$y$	$V$
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

In place of the 'X', you **substitute** '1' then a '0':

X → **2** minterms (0,1)

XX → **4** minterms (00,01,10,11)

 XXX → **8** minterms (000,001,010,011,100,101,110,111)




### 4-to-2 Priority Encoder


$$X = D_2 + D_3$$

$$Y = D_3 + D_1 D_2'$$

$$V = D_0 + D_1 + D_2 + D_3$$


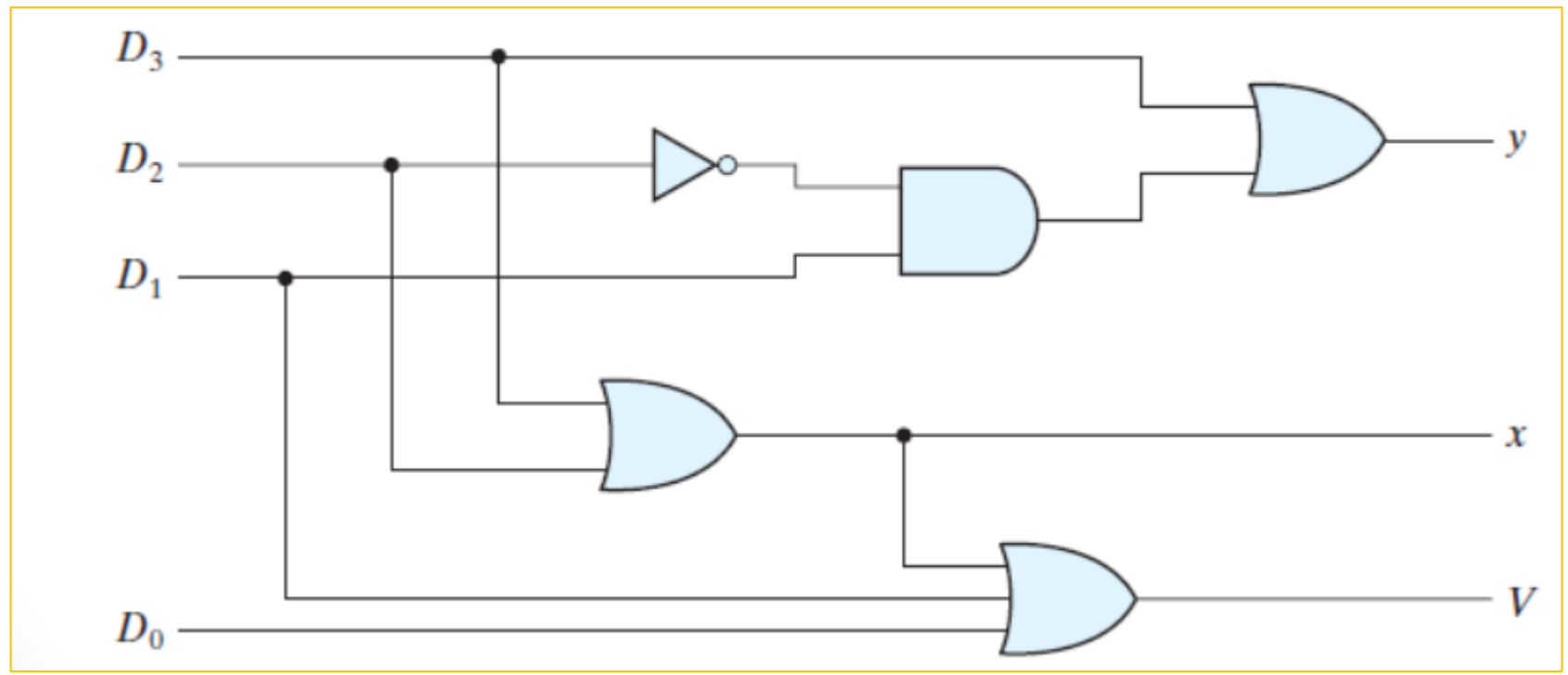
**V** is **0** only when **all** Inputs are 0 (Inactive)



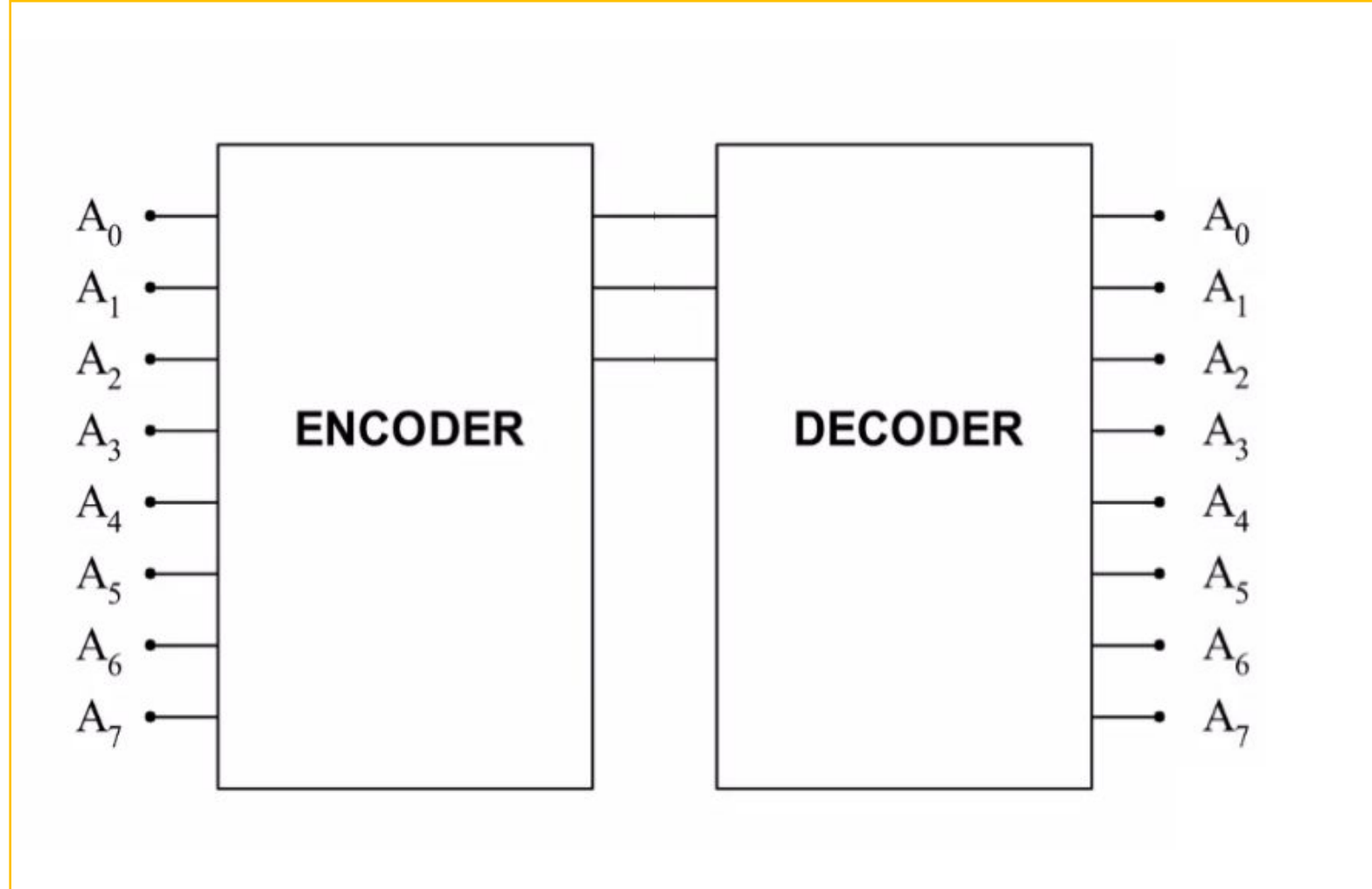



 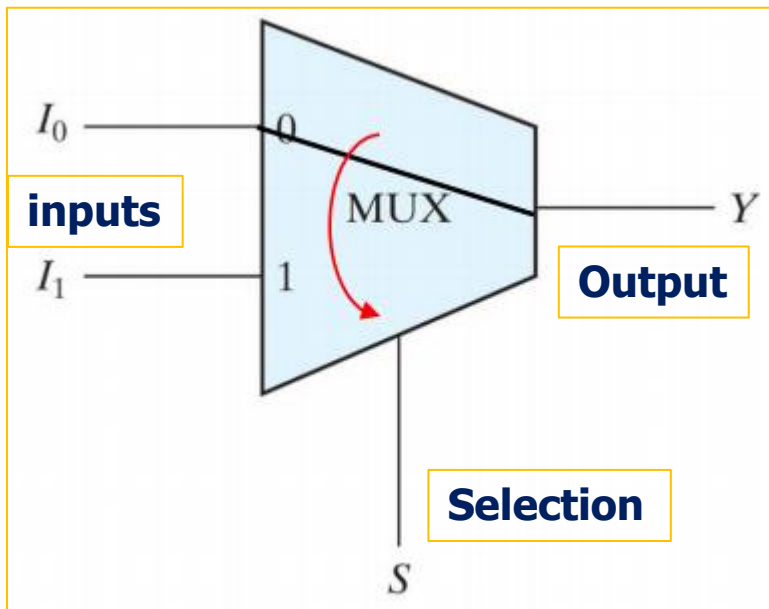
- ⌘ A **multiplexer** (MUX) is a combinational circuit that **selects** binary information from one of **many input lines** and directs it to a **single output line**.
- ⌘ The selection is performed using **selection control lines**.
- ⌘ Normally, there are  **$2^n$  input lines** and  **$n$  selection lines**.
- ⌘ A MUX acts as an electronic **switch** that **selects one** of several sources.





$I_0$  will move to the output  $Y$  when  $S = 0$

$I_1$  will move to the output  $Y$  when  $S = 1$

Applications of MUX

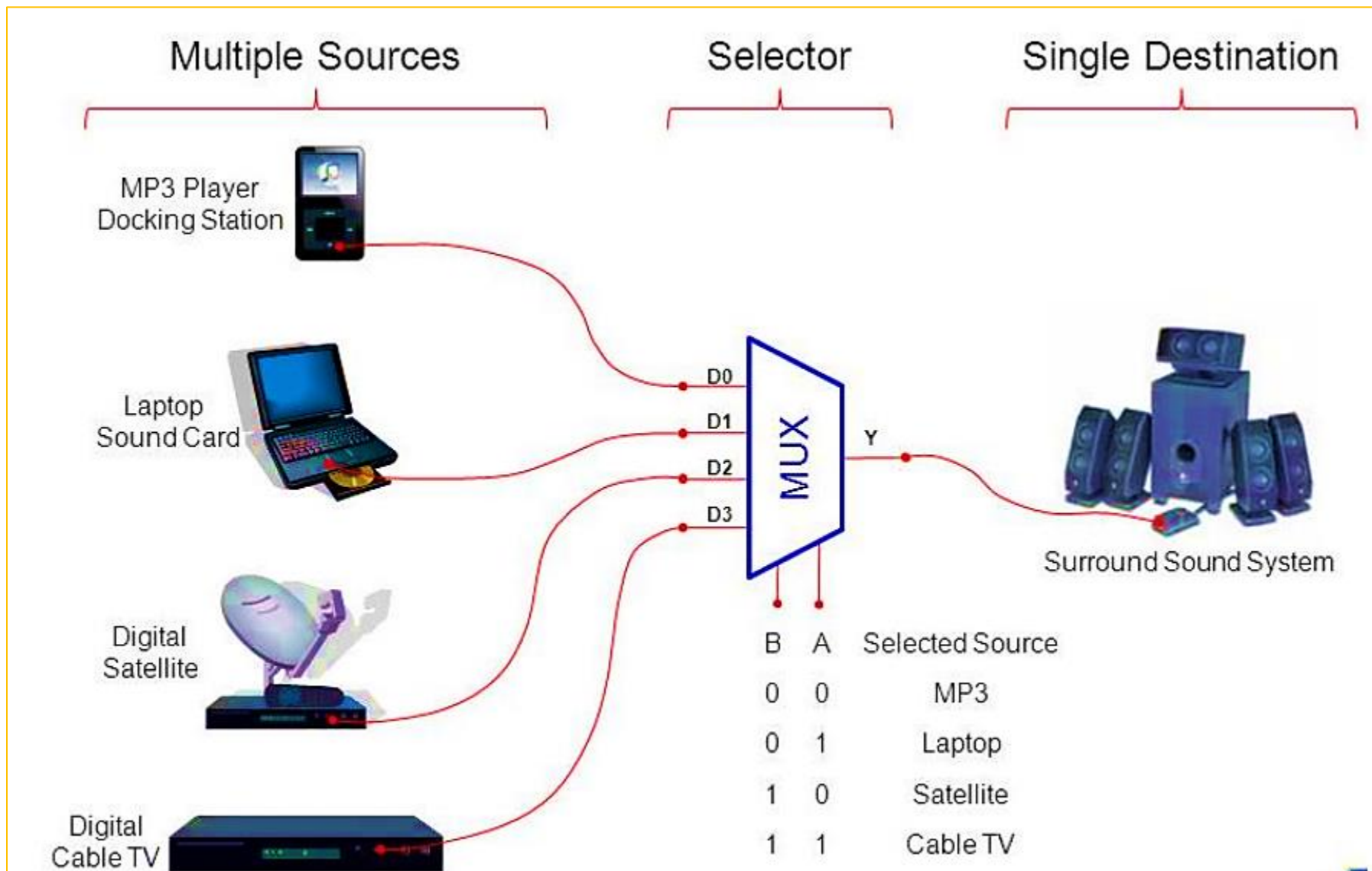

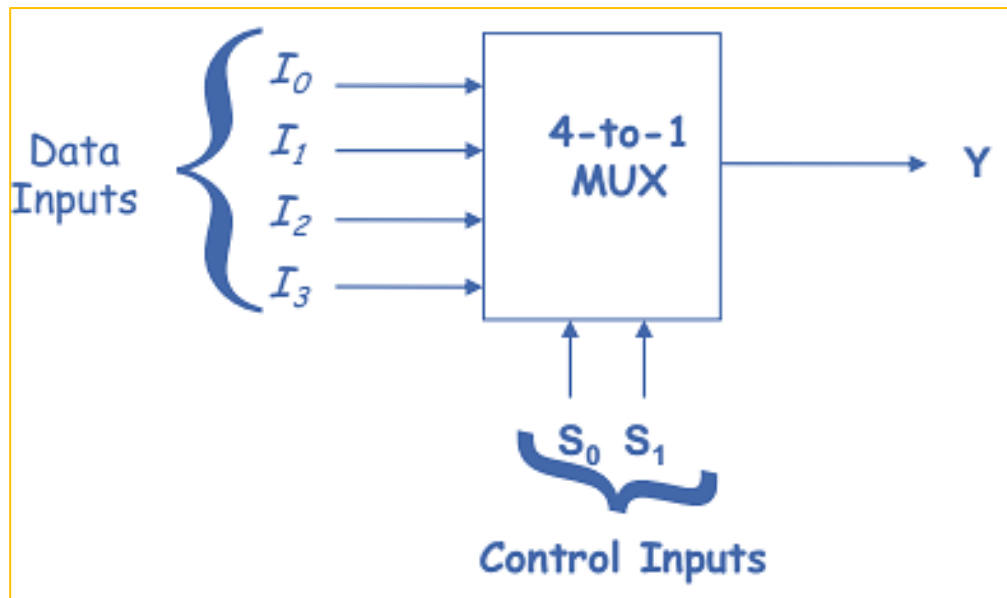 **Example: 4-to-1 MUX****Block Diagram****Logic Diagram**

$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

**Function Table**

$$Y = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$


**Expression**

- ⊗ A **multiplexer** is also called a **data selector**, since it selects one of many inputs and steers the binary information to the **single** output line
- ⊗ The **AND gates and inverters** in the multiplexer resemble a **decoder** circuit, and they decode the selection input lines.
- ⊗ In general, for **2<sup>n</sup>-to-1** multiplexer
  - Ⓜ Data **selection** lines → **n**
  - Ⓜ **Input** lines → **2<sup>n</sup>**
  - Ⓜ **Output** lines → **always 1**
- ⊗ **2<sup>n</sup>-to-1** multiplexer is constructed from
  - Ⓜ **n-to-2<sup>n</sup> Decoder**
  - Ⓜ **2<sup>n</sup>** input lines connected to the **AND** gates.
  - Ⓜ The outputs of the AND gates are applied to a **single OR** gate



$$Y = m_0 I_0 + m_1 I_1 + m_2 I_2 + \dots + m_{2^n-1} I_{2^n-1}$$

**MUX Output  
(General)**

 - Multiplexers may have an **enable** input, similar to decoders, to **control** the **operation** of the unit
- M-bit** (2-to-1) multiplexer is equivalent to **M** parallel mux's **share** a common selection line
  - It is viewed as a circuit that selects **one of two M-bit sets** of data lines





E	S	Y
1	X	All 0's
0	0	Select A
0	1	Select B

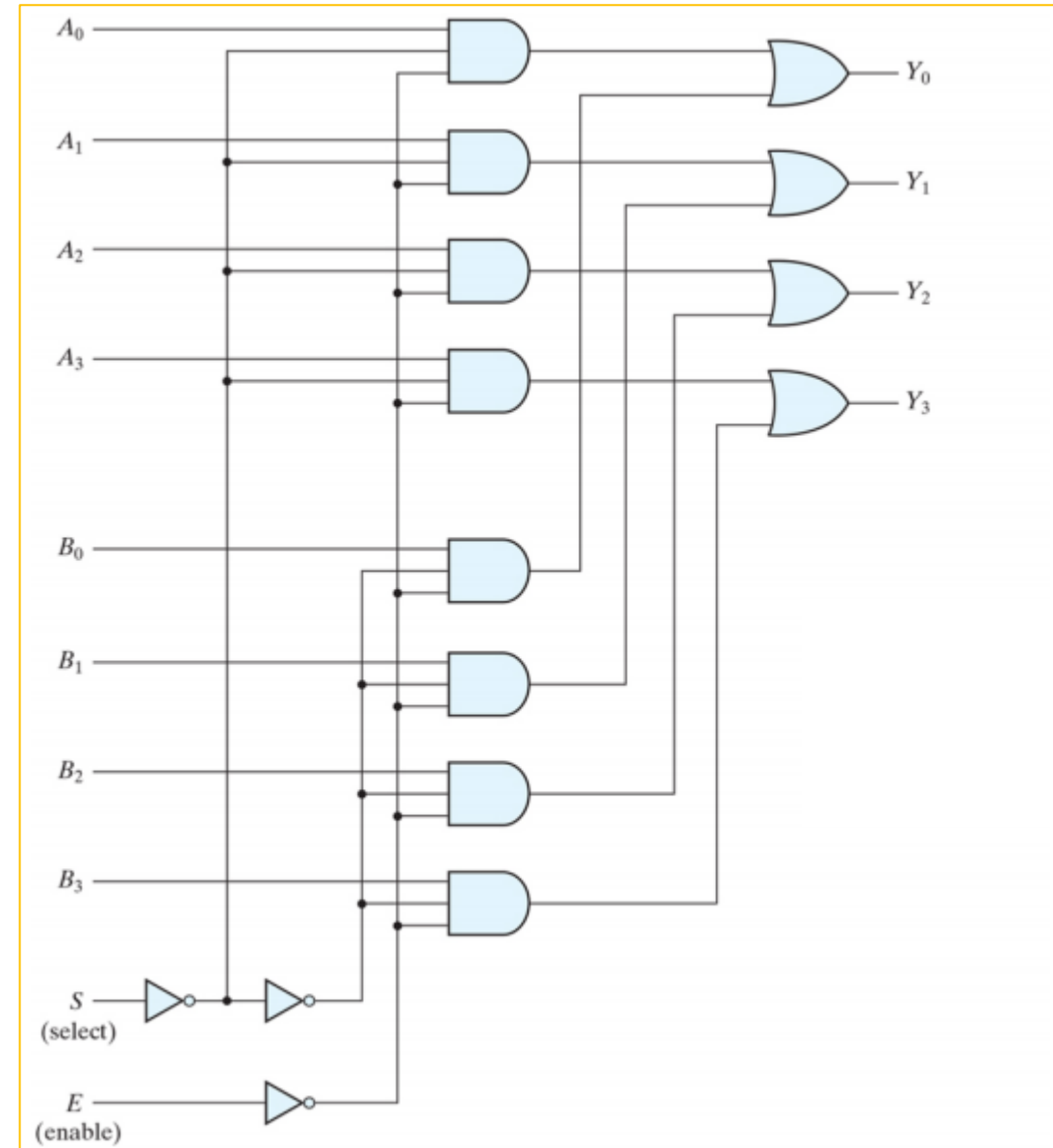 

Remember: The **bubble** indicates that the mux is **enabled** when **E=0**

/ → M-bit

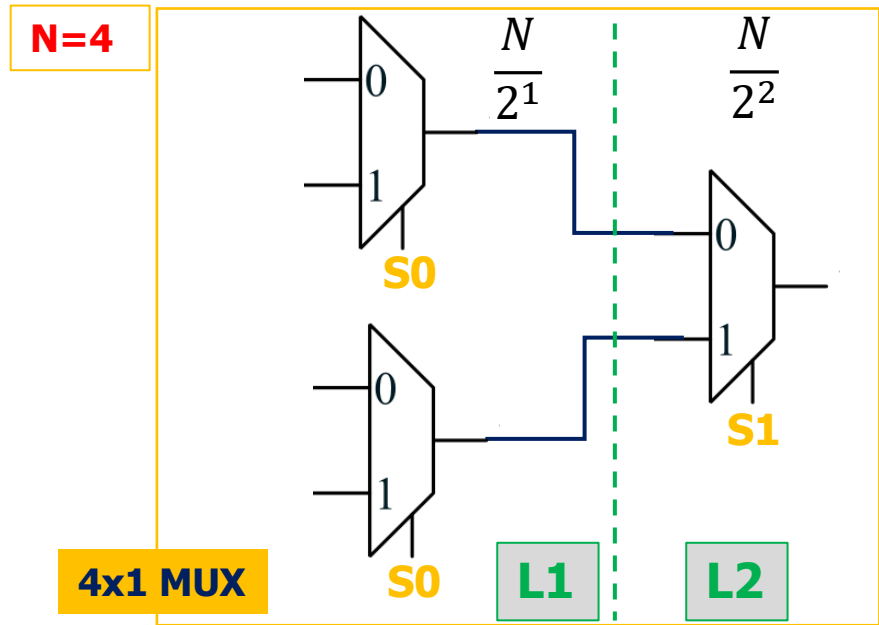
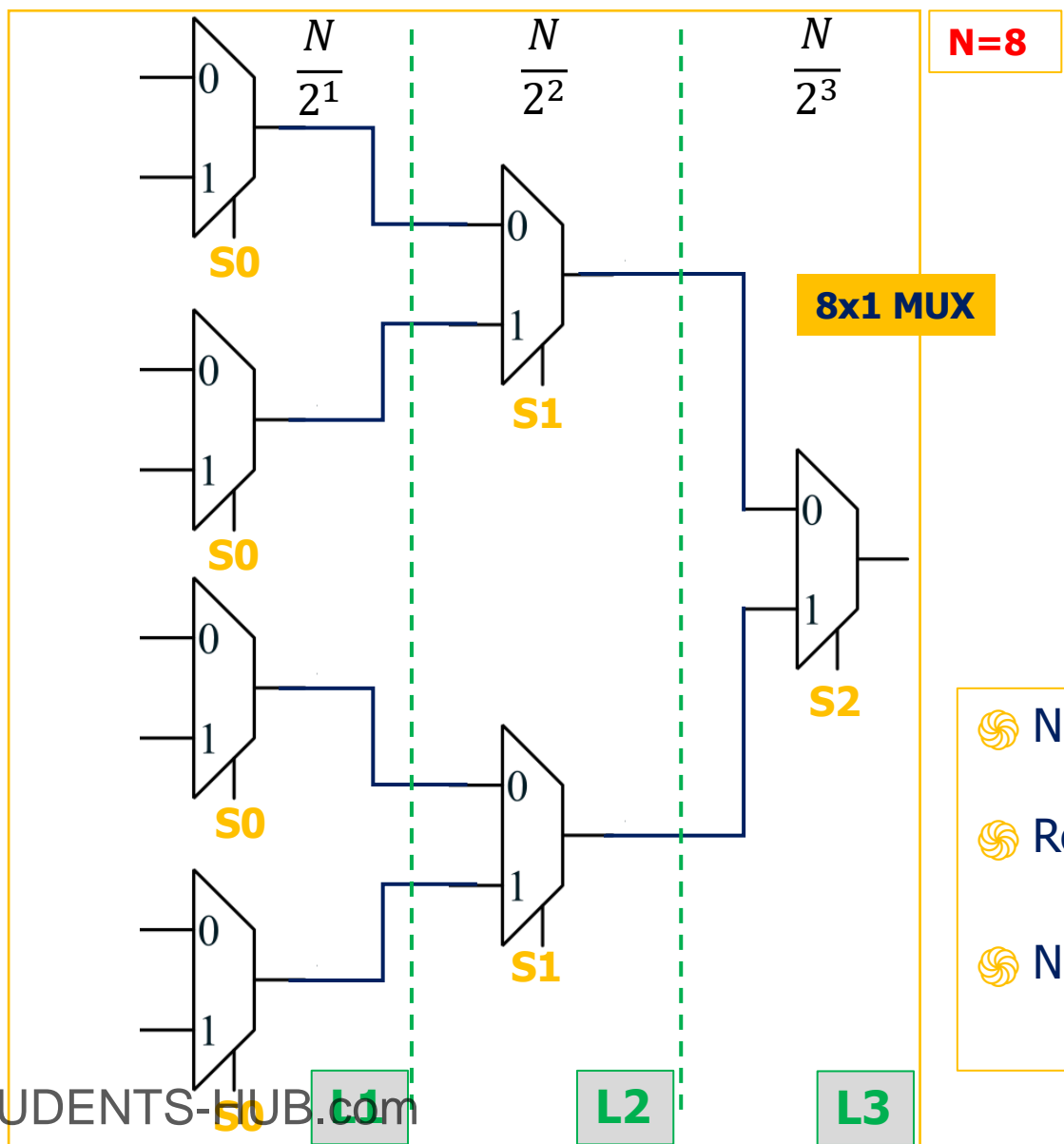
Muxes can be **connected** together to form a **larger** Mux circuit



- N → No. of Inputs ( $2^n$ )
- Required Levels using 2x1 Mux =  $\log_2(N)$
- No. of Muxes in level (i) =  $\frac{N}{2^i}$ ,  $i=0,1,2,\dots$


Muxes can be **connected** together to form a **larger** Mux circuit

**8x1 MUX**

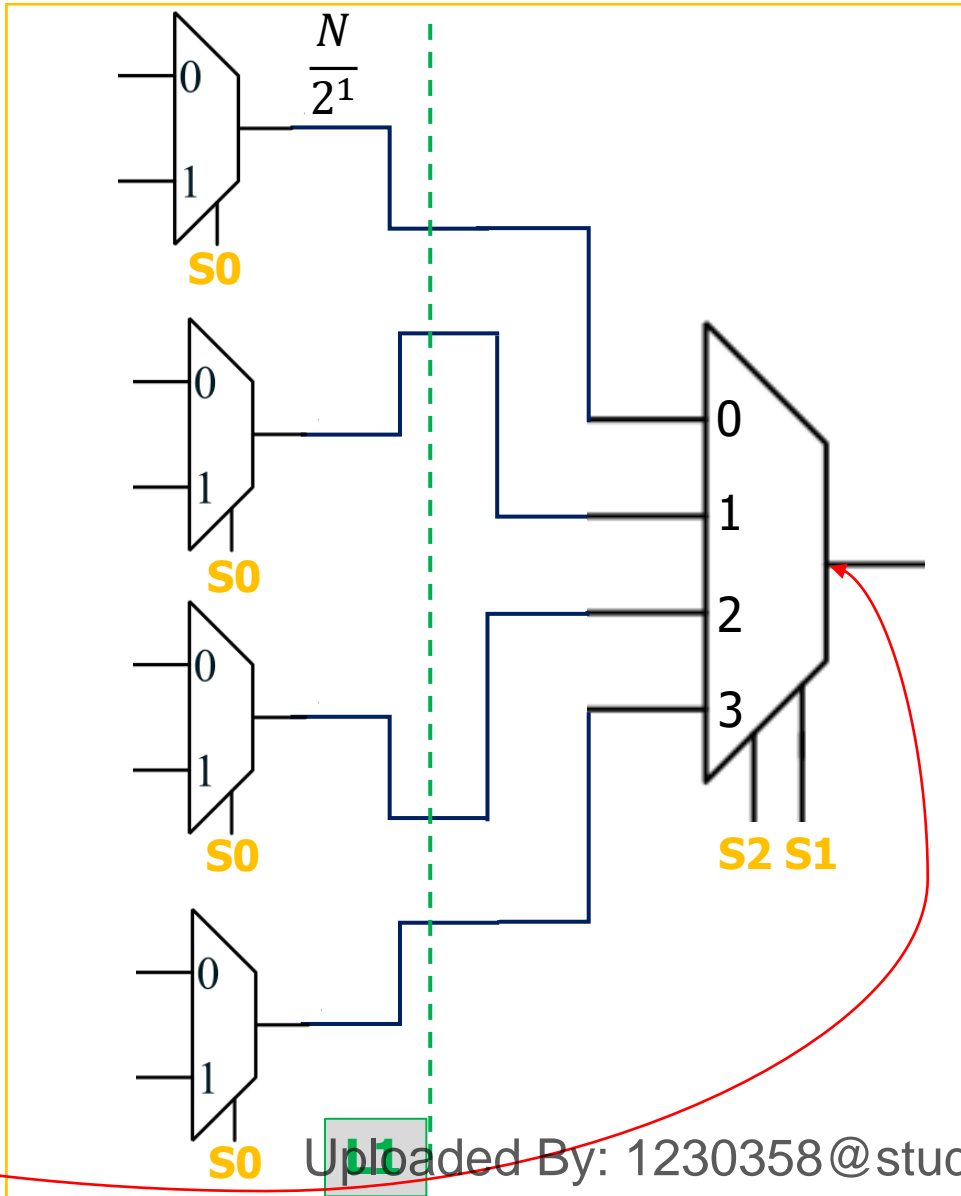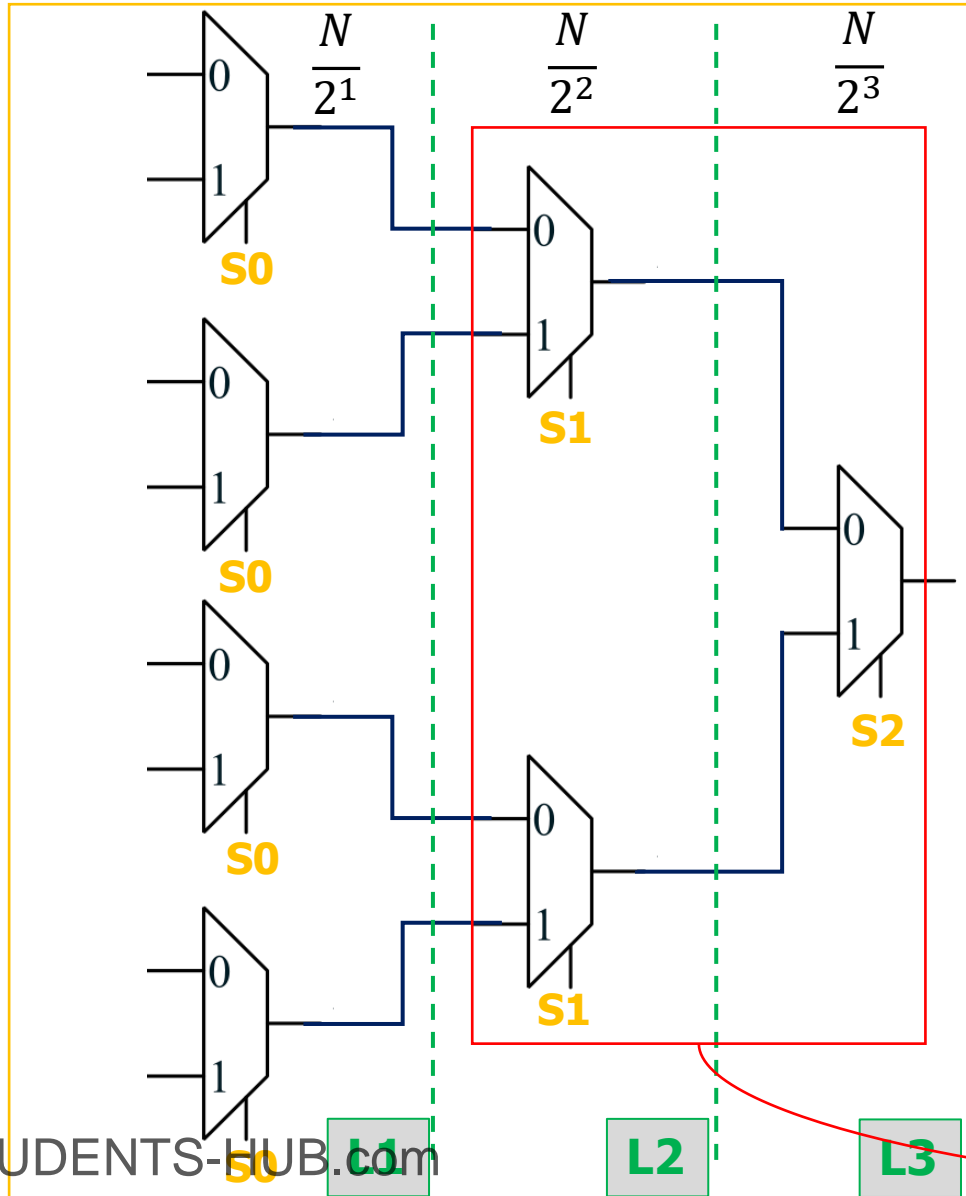

Muxes can be **connected** together to form a **larger** Mux circuit

**8x1 MUX**

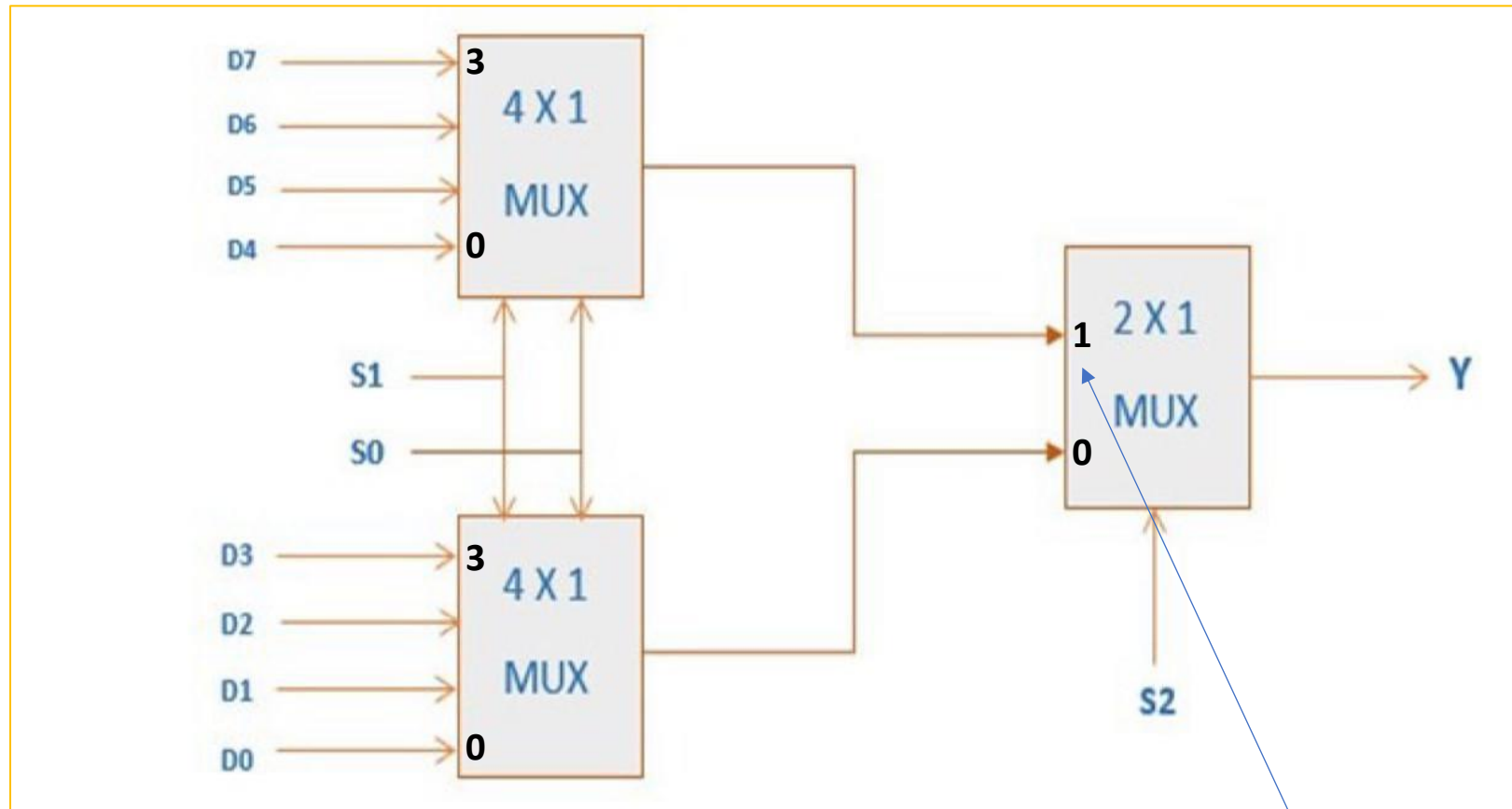


Always Follow/Consider the **internal Labels** To determine **MSB & LSB (Connection Order)**



Muxes can be **connected** together to form a **larger** Mux circuit


**16x1 MUX**

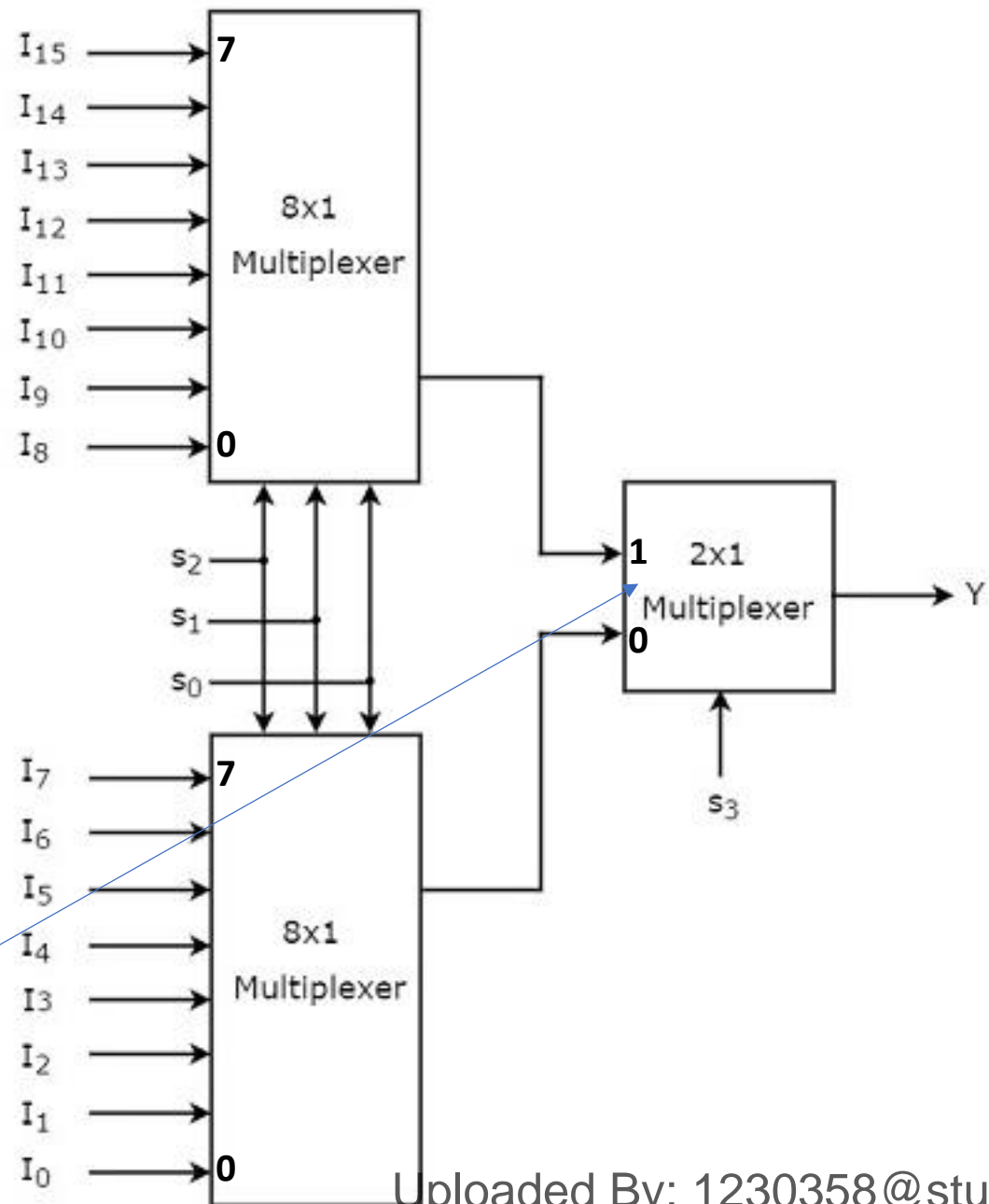

Always Follow/Consider the **internal Labels** To determine **MSB & LSB (Connection Order)**

Muxes can be **connected** together to form a **larger** Mux circuit

**16x1 MUX**

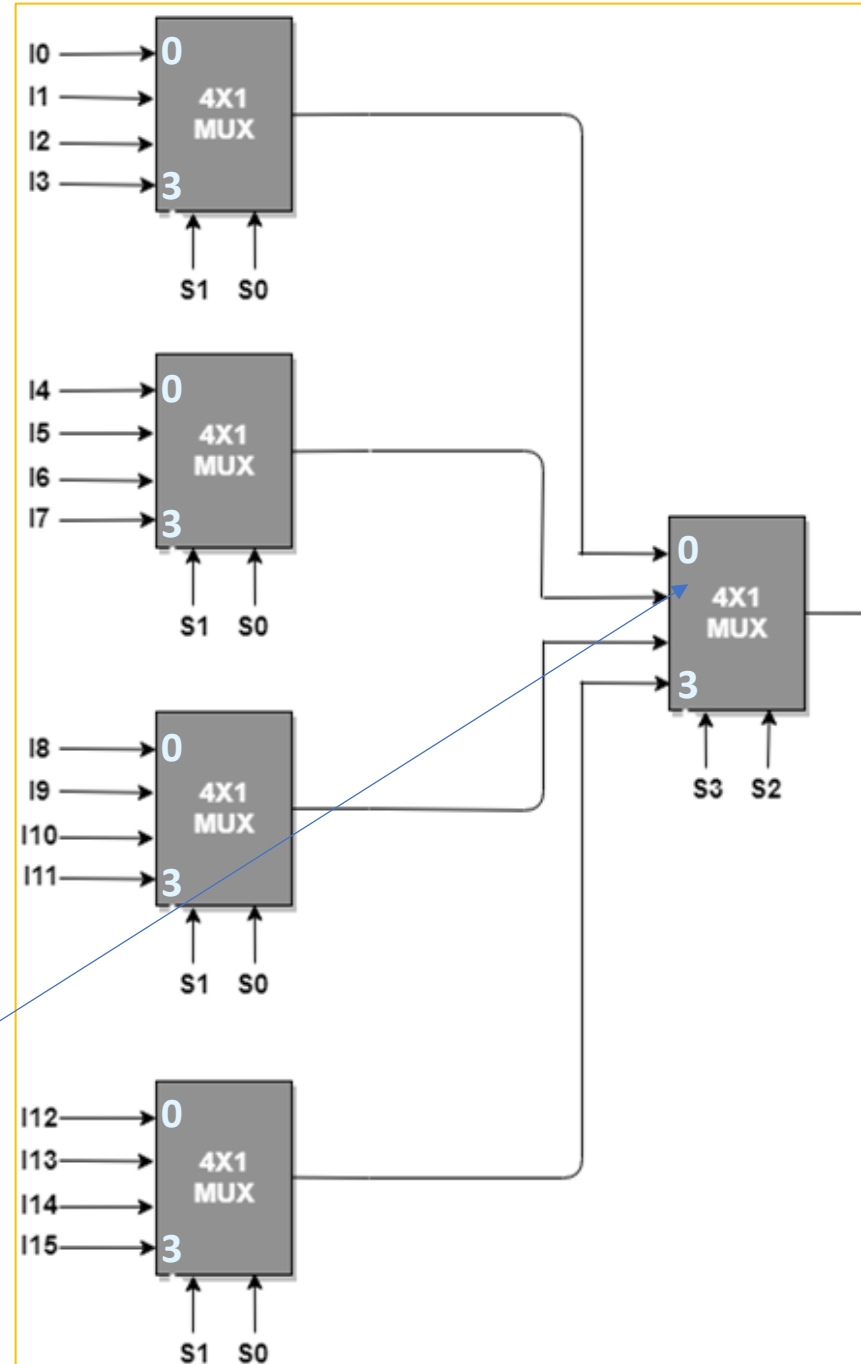


Always Follow/Consider the **internal Labels To** determine **MSB & LSB (Connection Order)**

- 🌀 **RECALL:** We learned how to implement Boolean functions using **decoders**, by adding external **OR** gate
- 🌀 **RECALL:** A multiplexer is a **decoder** and an **OR** gate that provides the output
  - ★ Multiplexer inputs are the **minterms**

We can implement any **n** variable Boolean function using a **MUX** with **n** select lines ( **$2^n$**  input lines)

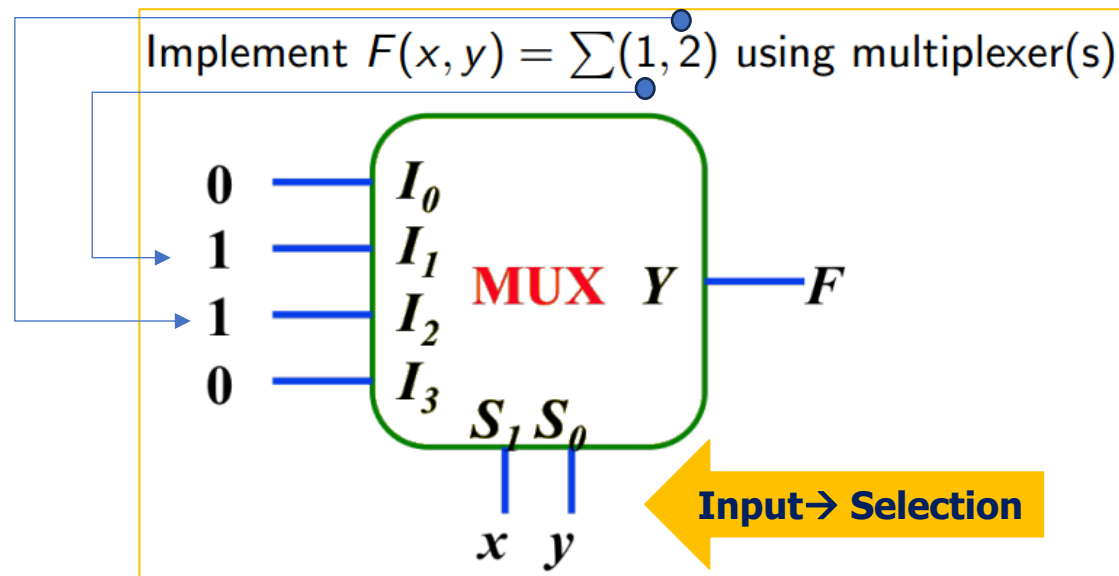
- 🌀 The **n** variables are **connected** to the **n selection** lines.
- 🌀 Each input of the multiplexer is **set to 0 or 1**, depending on which minterm of the function is present.



**Example:** Implement  $F(x,y,z) = \Sigma(1,2,6,7)$  using **8-to-1** multiplexer.

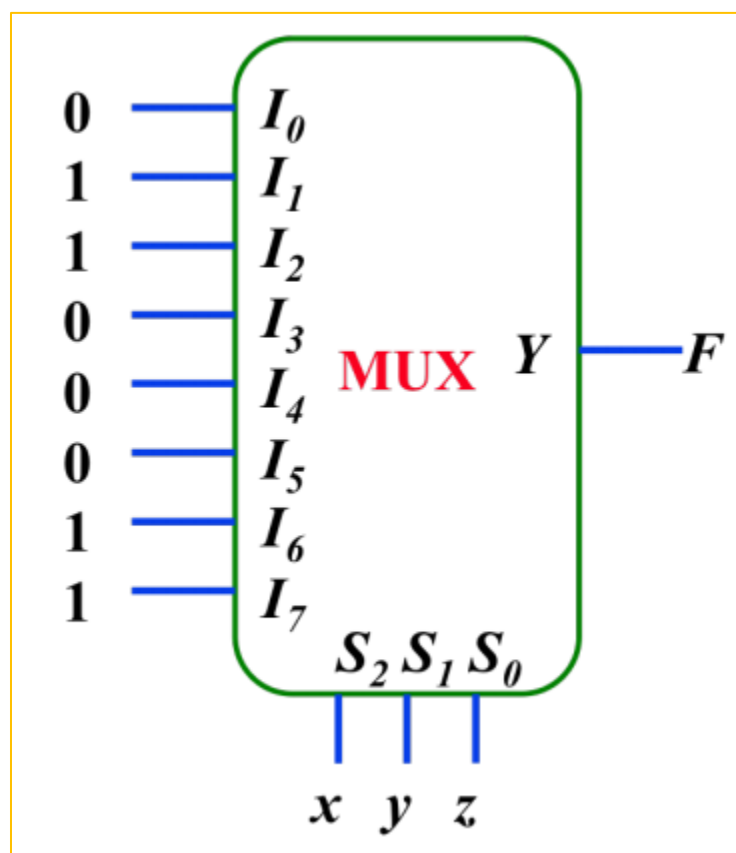**n Variables  $\rightarrow (2^n \times 1)$ Mux**

Solution: Connect the variables  $x, y, z$  to the selection inputs  $S_2, S_1,$  and  $S_0$ . Then set  $I_0 = I_3 = I_4 = I_5 = 0$  and  $I_1 = I_2 = I_6 = I_7 = 1$ .




☉ We can **efficiently** implement any **n** variable Boolean function using a MUX with **(n-1) select** lines ( **$2^{n-1}$**  input lines)

- 1) Connect the first **(n-1)** variables to the **select** lines
- 2) The **remaining single** variable of the function is used for the **data inputs (x, x', 1, 0)**

**Example:**Implement  $F(x,y,z) = \Sigma(1,2,6,7)$  using **4-to-1** multiplexer.**n Variables  $\rightarrow (2^{n-1} \times 1)$  Mux**

x	y	z	F	
0	0	0	0	$F = z$
0	0	1	1	
0	1	0	1	$F = z'$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

 

### Alternative Method : **Implementation Table** [Simpler for $2^{n-1} \times 1$ Mux]

- A. List the **input** of the multiplexer (**z**)
- B. List under it all the **minterms** in (**2**) Rows and (**4**) Columns
- C. The **first half** of the minterms is associated with the **Primed Variable (z')** and the **second half** with the **Normal Variable (z)**
- D. The given function is implemented by circling the minterms of the function and applying the following **rules** to find the values for the inputs of the multiplexer
  - 1) If **both** the minterms in the column are **not** circled, apply **0** to the corresponding input
  - 2) If **both** the minterms in the column are circled, apply **1** to the corresponding input
  - 3) If **the bottom** minterm is circled and the **top is not** circled, apply **z** to the input
  - 4) **If the top** minterm is circled and the **bottom is not** circled, apply **z'** to the input


**No need for TT**  
Could be derived  
**directly from minterms**

Z'	0	2	4	6
Z	1	3	5	7
	Z	Z'	0	1
	I <sub>0</sub>	I <sub>1</sub>	I <sub>2</sub>	I <sub>3</sub>

Don't Get Confused  
It has **NO** relation to K-Map

**Extra Example:**Implement  $F(A,B,C) = \Sigma(3,5,6,7)$  using **4-to-1** multiplexer. **$n$  Variables  $\rightarrow (2^{n-1} \times 1)$  Mux**

A	B	C	F	
0	0	0	0	F=0
0	0	1	0	
0	1	0	0	F=C
0	1	1	1	
1	0	0	0	F=C
1	0	1	1	
1	1	0	1	F=1
1	1	1	1	

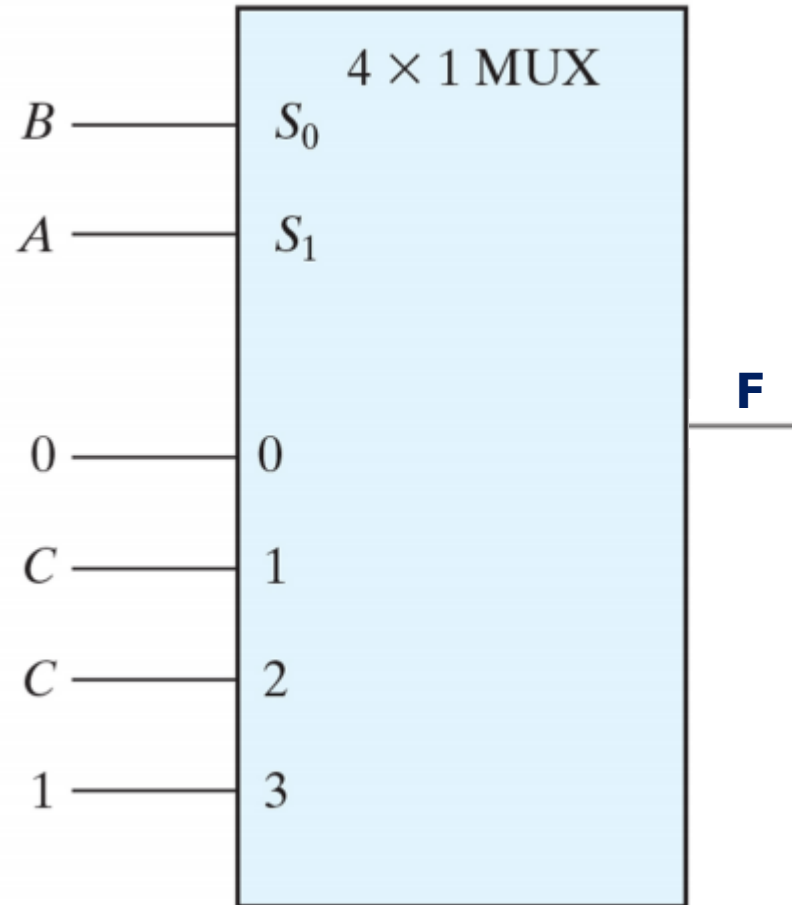


$C'$	0	2	4	6
C	1	3	5	7
	0	C	C	1
	$I_0$	$I_1$	$I_2$	$I_3$

**Extra Example:**

Implement  $F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$  using **8-to-1** multiplexer

ABC	A	B	C	D	F	
0	0	0	0	0	0	$F = D$
	0	0	0	1	1	
1	0	0	1	0	0	$F = D$
	0	0	1	1	1	
2	0	1	0	0	1	$F = D'$
	0	1	0	1	0	
3	0	1	1	0	0	$F = 0$
	0	1	1	1	0	
4	1	0	0	0	0	$F = 0$
	1	0	0	1	0	
5	1	0	1	0	0	$F = D$
	1	0	1	1	1	
6	1	1	0	0	1	$F = 1$
	1	1	0	1	1	
7	1	1	1	0	1	$F = 1$
	1	1	1	1	1	

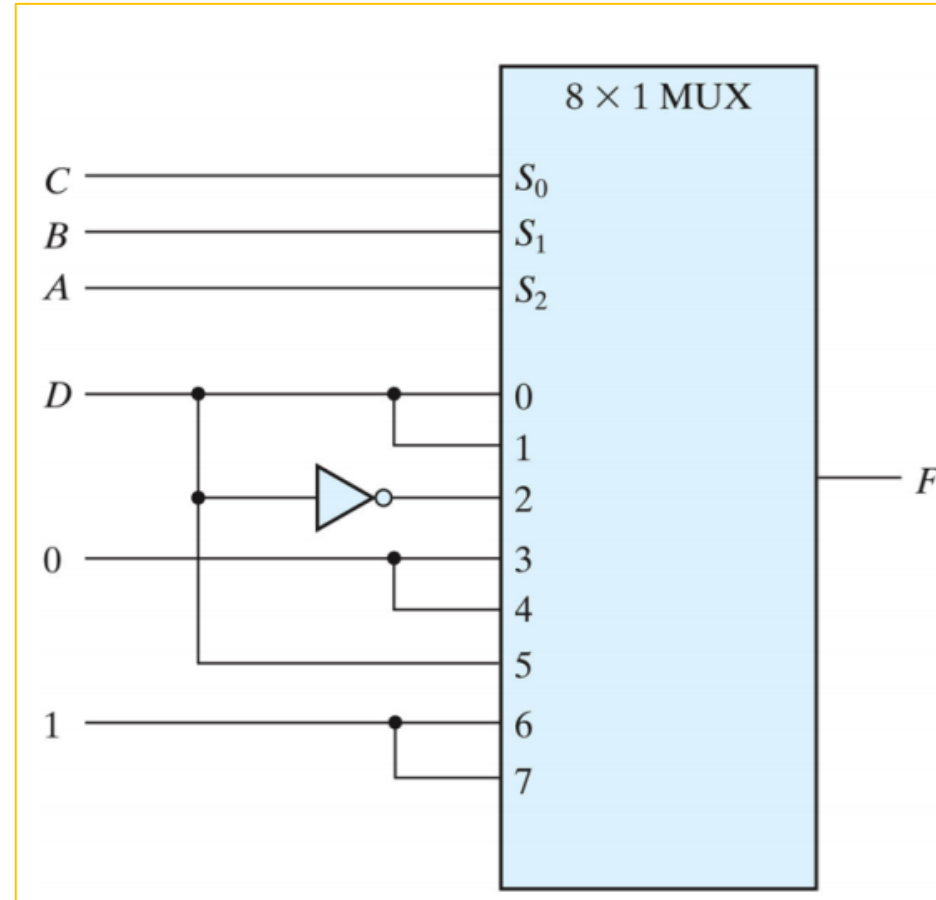

D'	0	2	4	6	8	10	12	14
D	1	3	5	7	9	11	13	15
	D	D	D'	0	0	D	1	1
	I <sub>0</sub>	I <sub>1</sub>	I <sub>2</sub>	I <sub>3</sub>	I <sub>4</sub>	I <sub>5</sub>	I <sub>6</sub>	I <sub>7</sub>



**Extra Example:**

Implement  $F(A, B, C, D) = \Sigma(3, 5, 10, 11, 12, 15) + \Sigma(4, 8, 14)$  using **8-to-1** multiplexer (Use **A,C,D** as selection lines)


A	B	C	D	F	
0	0	0	0	0	$I_0$
0	0	0	1	0	$I_1$
0	0	1	0	0	$I_2$
0	0	1	1	1	$I_3$
0	1	0	0	X	$I_4$
0	1	0	1	1	$I_5$
0	1	1	0	0	$I_6$
0	1	1	1	0	$I_7$
1	0	0	0	X	$I_4$
1	0	0	1	0	$I_5$
1	0	1	0	1	$I_6$
1	0	1	1	1	$I_7$
1	1	0	0	1	$I_4$
1	1	0	1	0	$I_5$
1	1	1	0	X	$I_6$
1	1	1	1	1	$I_7$

Both Values **Similar** → **Constant** (0,1)  
**Different** → Check **B**

**Be Careful about the Order**

B'	0	1	2	3	8	9	10	11
B	4	5	6	7	12	13	14	15
	0	B	0	B'	1	0	1	1
	$I_0$	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$I_7$

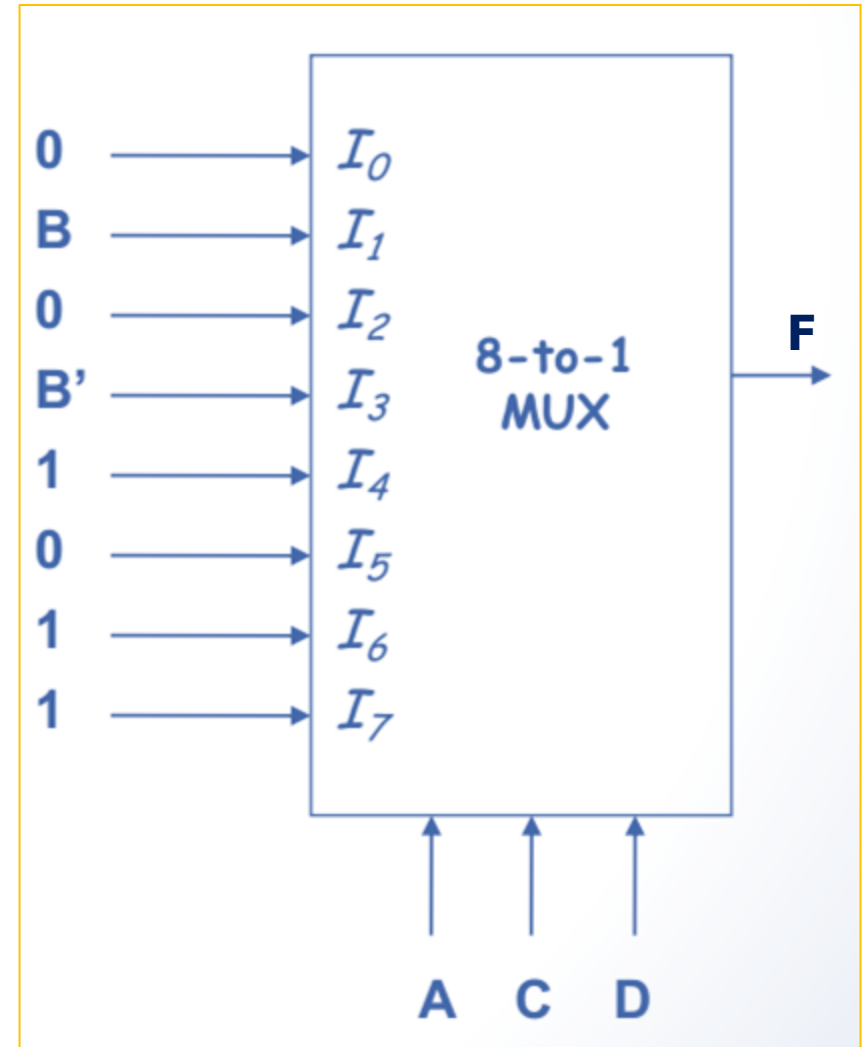**ONLY** Consider **Don't Care**, when **other** circles exist in the **same** Column



**Extra Example:**

Implement  $F(A, B, C, D) = \Sigma(3, 5, 10, 11, 12, 15) + \Sigma(4, 8, 14)$  using **4-to-1** multiplexer (Use **C,D** as selection lines)

A	B	C	D	F	
0	0	0	0	0	$I_0$
0	0	0	1	0	$I_1$
0	0	1	0	0	$I_2$
0	0	1	1	1	$I_3$
0	1	0	0	X	$I_0$
0	1	0	1	1	$I_1$
0	1	1	0	0	$I_2$
0	1	1	1	0	$I_3$
1	0	0	0	X	$I_0$
1	0	0	1	0	$I_1$
1	0	1	0	1	$I_2$
1	0	1	1	1	$I_3$
1	1	0	0	1	$I_0$
1	1	0	1	0	$I_1$
1	1	1	0	X	$I_2$
1	1	1	1	1	$I_3$


Both Values **Similar**  $\rightarrow$  **Constant** (0,1)  
**Different**  $\rightarrow$  Check **A,B**

**A'B**


A	B	C	D	F	
0	0	0	1	0	$I_1$
0	1	0	1	1	$I_1$
1	0	0	1	0	$I_1$
1	1	0	1	0	$I_1$


**A+B'**

A	B	C	D	F	
0	0	1	1	1	$I_3$
0	1	1	1	0	$I_3$
1	0	1	1	1	$I_3$
1	1	1	1	1	$I_3$

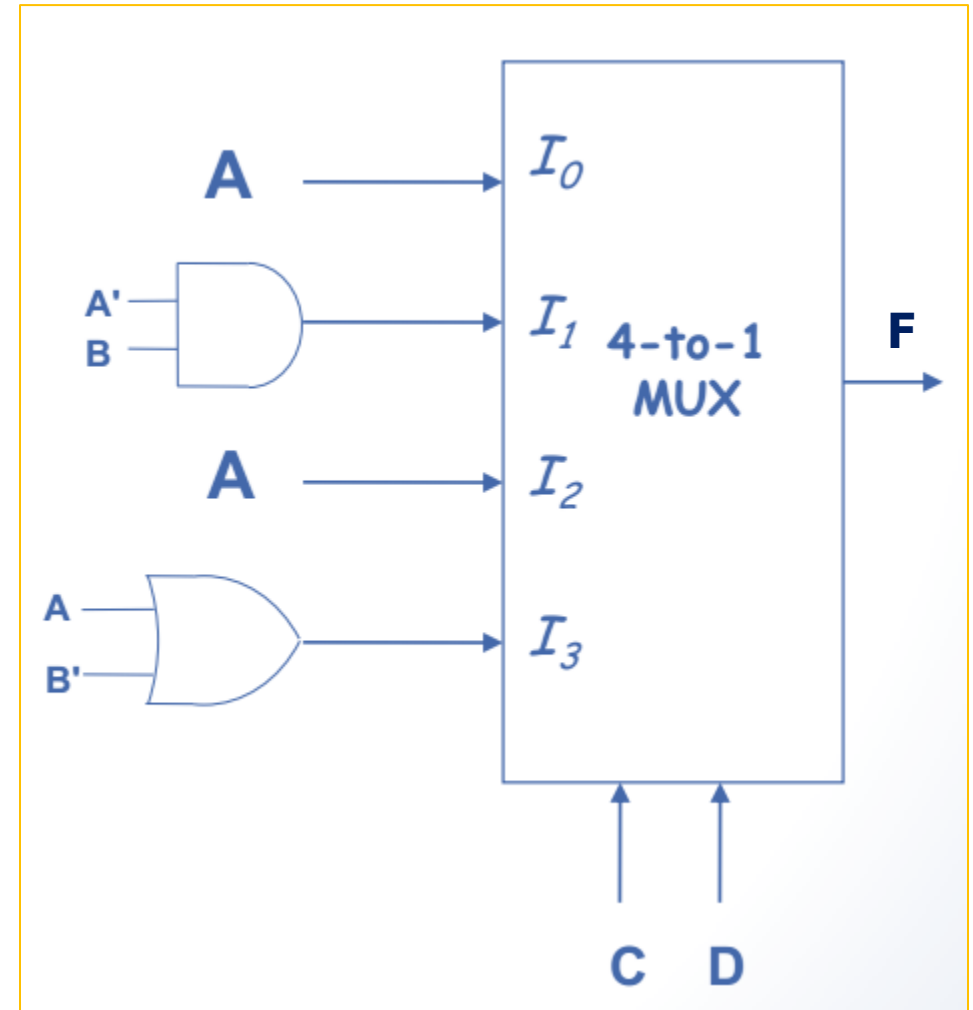

- ☞ **Recall:** A **decoder** with **enable** input can function as a **demultiplexer**
- ☞ **Demultiplexer (Demux):** It is a circuit that receives information from a **single line** and **directs** it to **ONE** of  **$2^n$  output** lines.
- ☞ The **selection** of a **specific output** is controlled by the **bit** combination of  **$n$  selection** lines.
- ☞ A **demultiplexer** of  **$2^n$  outputs** has  **$n$  selection** lines, which are used to **select** which output line to **send** the **input**.
- ☞ A **demultiplexer** is also called a **data distributor**.

 

 


$$Y_0 = \bar{S}_1 \bar{S}_0 I$$

$$Y_1 = \bar{S}_1 S_0 I$$

$$Y_2 = S_1 \bar{S}_0 I$$

$$Y_3 = S_1 S_0 I$$


Select Line		Outputs			
S <sub>1</sub>	S <sub>0</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

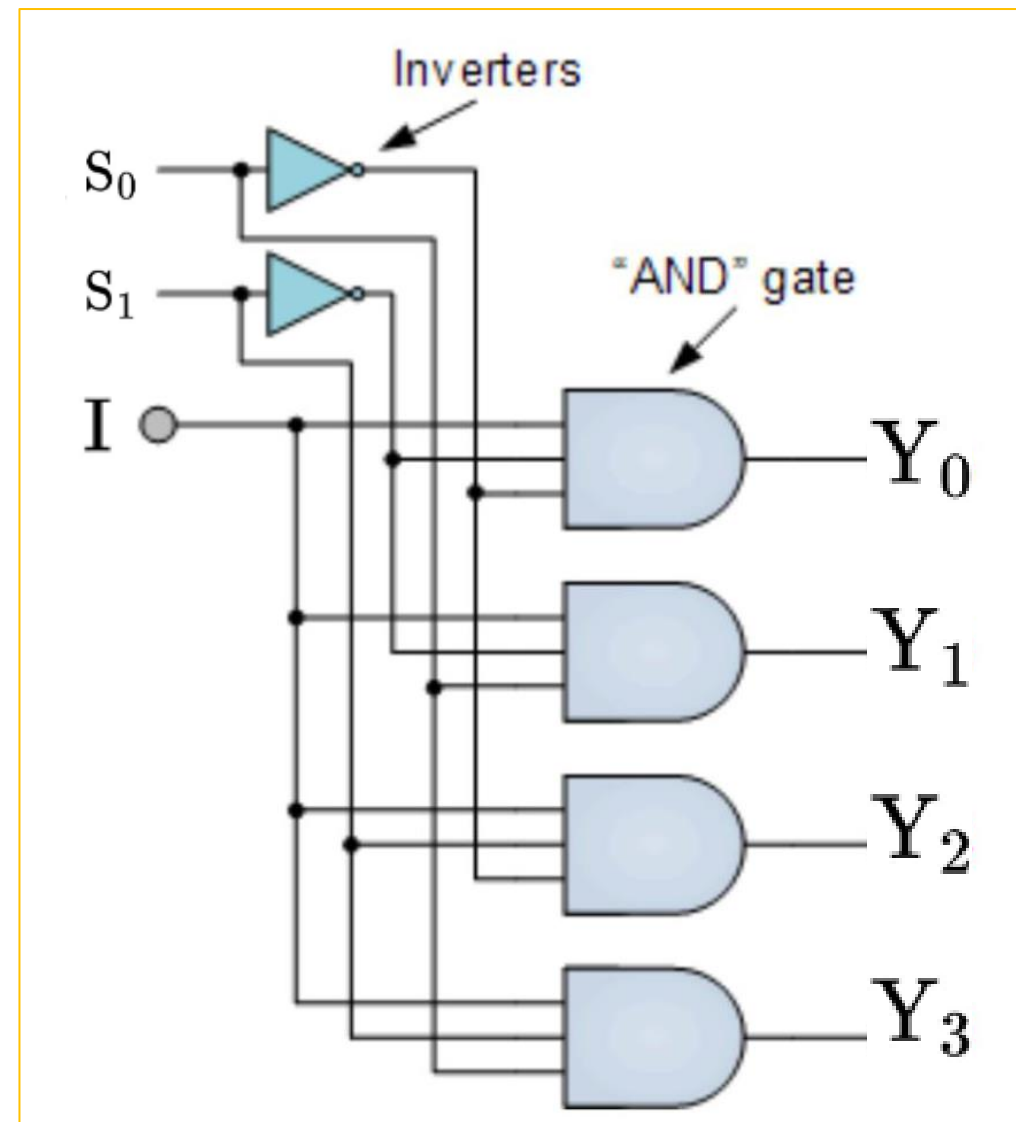

**1:8 DeMux with Enable**

A 1:8 DEMUX takes a single data **input D**, enables it through an **Enable signal E**, and sends the data to one of the eight **outputs**  $Y_0$ - $Y_7$  based on the 3-bit **selection lines**  $S_0, S_1, S_2$

**8 Outputs** → **3 Selection Lines**

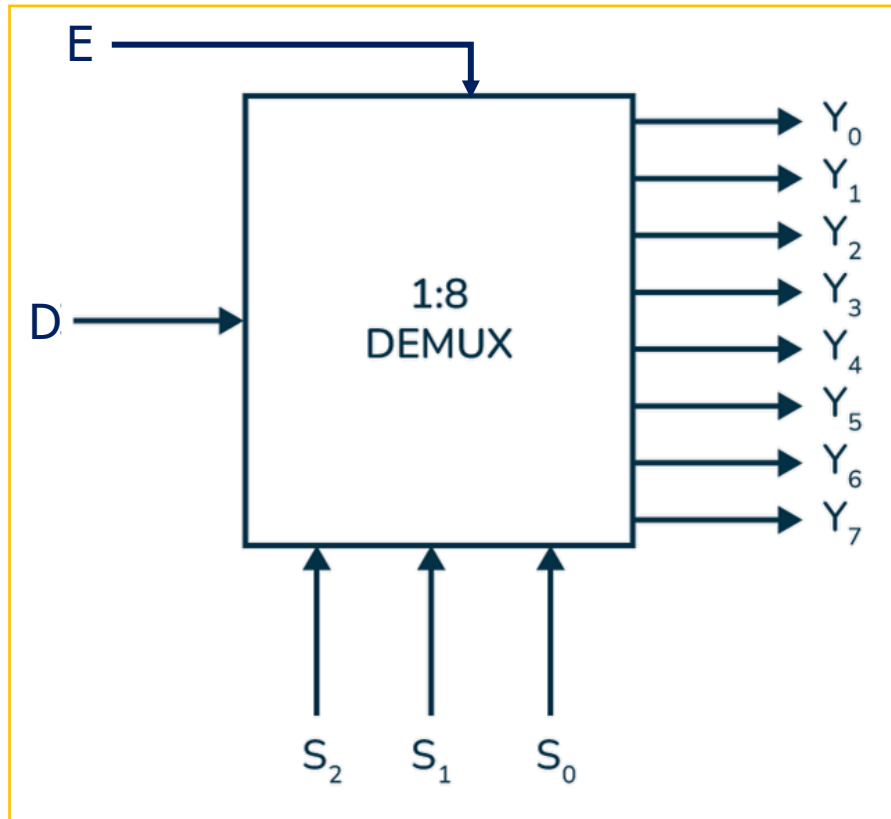


E	S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>	Y <sub>4</sub>	Y <sub>5</sub>	Y <sub>6</sub>	Y <sub>7</sub>
0	X	X	X	0	0	0	0	0	0	0	0
1	0	0	0	<b>D</b>	0	0	0	0	0	0	0
1	0	0	1	0	<b>D</b>	0	0	0	0	0	0
1	0	1	0	0	0	<b>D</b>	0	0	0	0	0
1	0	1	1	0	0	0	<b>D</b>	0	0	0	0
1	1	0	0	0	0	0	0	<b>D</b>	0	0	0
1	1	0	1	0	0	0	0	0	<b>D</b>	0	0
1	1	1	0	0	0	0	0	0	0	<b>D</b>	0
1	1	1	1	0	0	0	0	0	0	0	<b>D</b>


**E = 0:** All outputs are **0**, regardless of selection lines.

**E = 1:** Data **D** is routed to the output **selected** by  $S_2S_1S_0$

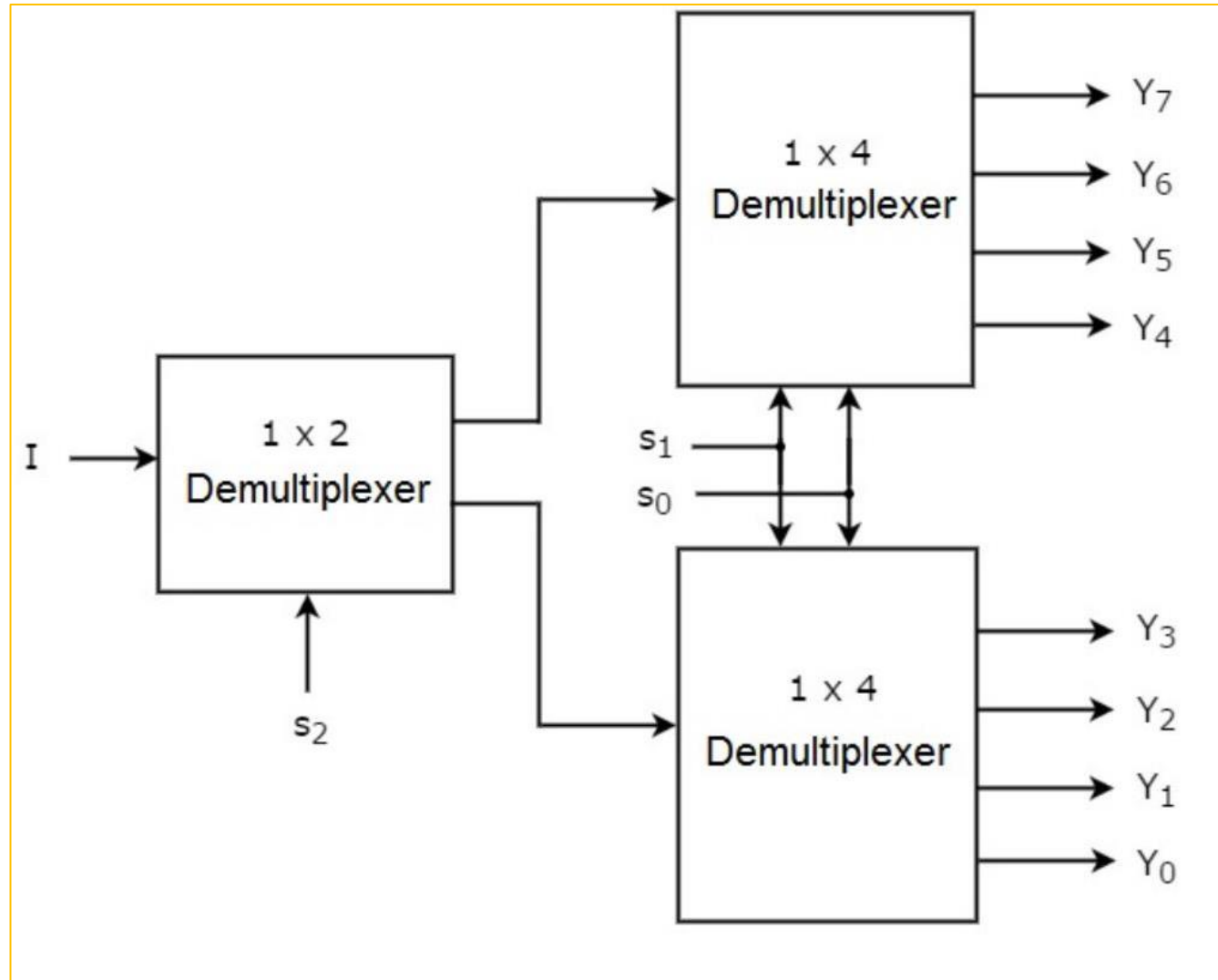
DeMuxes can be **connected** together to form a **larger** DeMux circuit



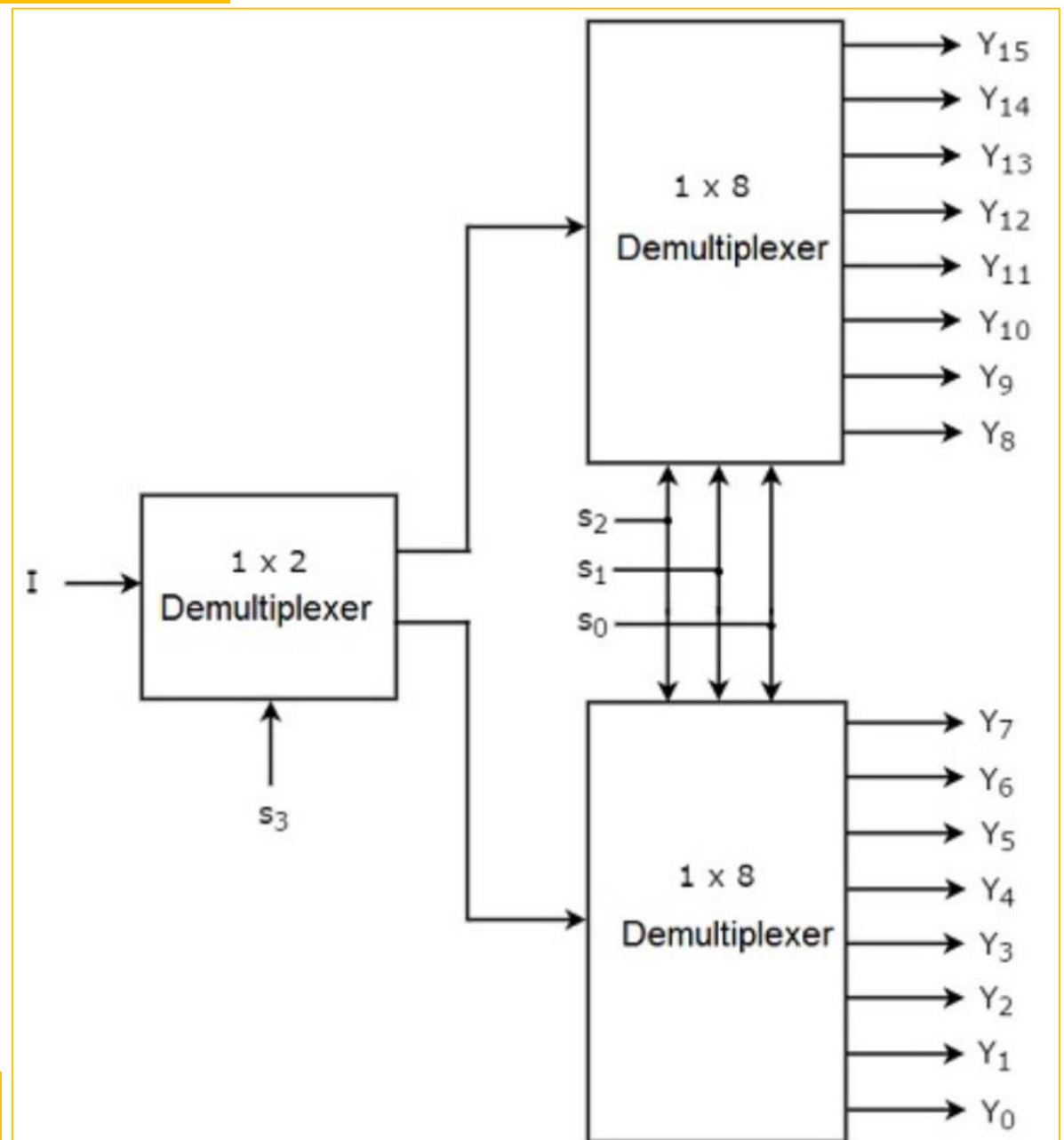DeMuxes can be **connected** together to form a **larger** DeMux circuit




**1x16 DEMUX**

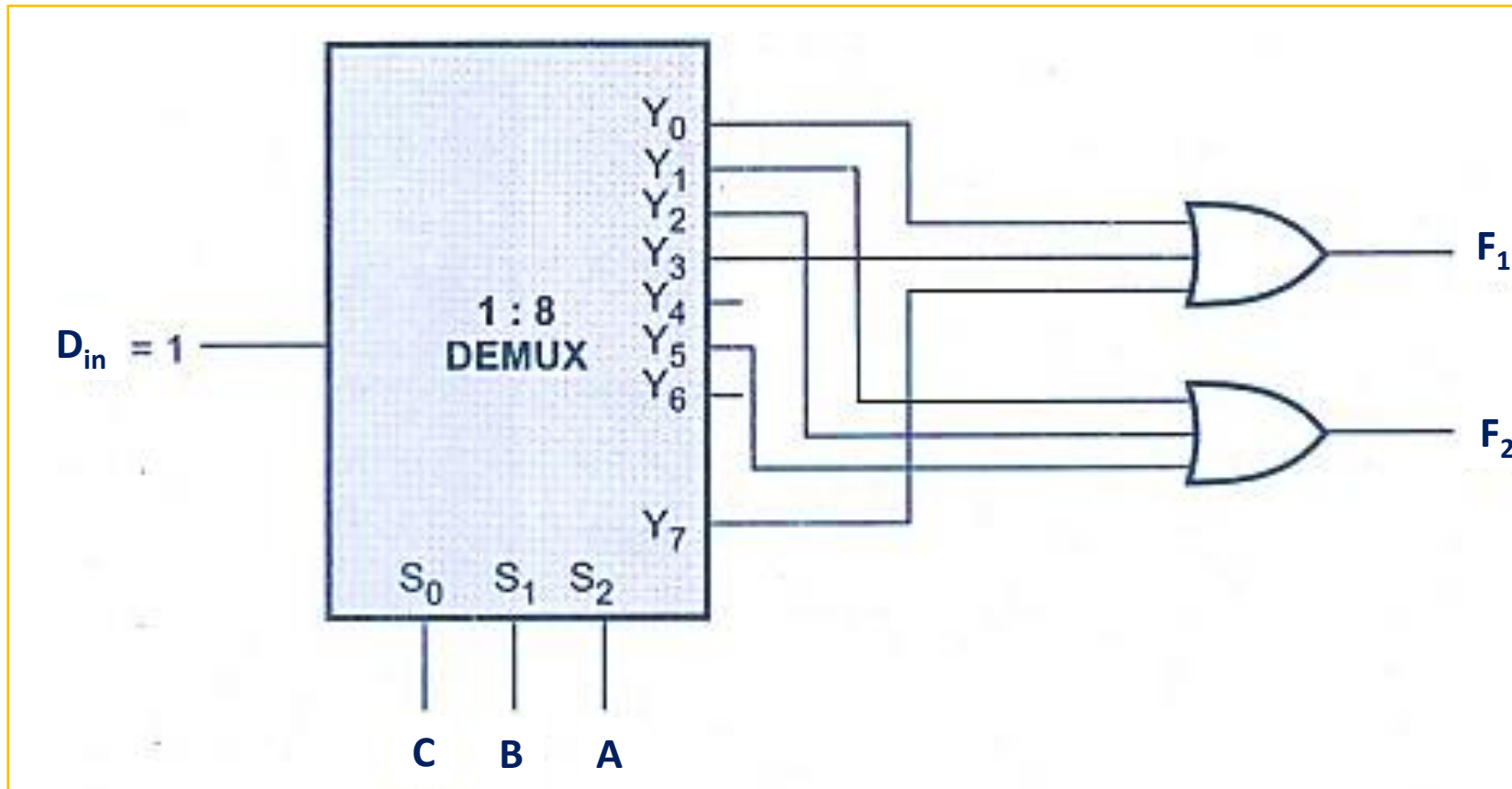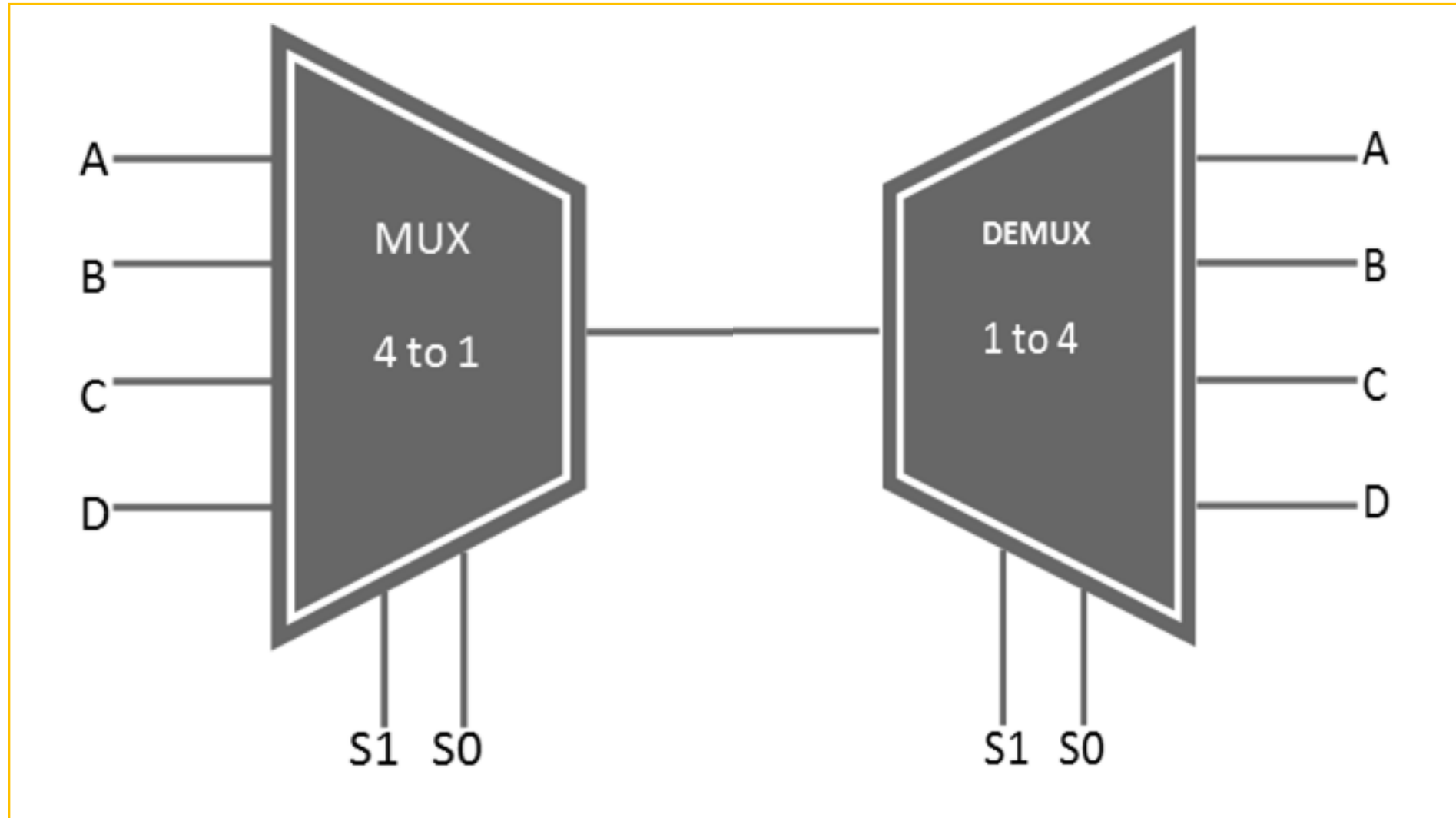**Example:**Implement  $F_1(\mathbf{A},\mathbf{B},\mathbf{C}) = \Sigma(0,3,7)$  ,  $F_2(\mathbf{A},\mathbf{B},\mathbf{C}) = \Sigma(1,2,5)$  using **1-to-8** demultiplexer.**What About Using  
1-to-4 DeMux??**

**Same as Decoder** with:  
Decoder Inputs  $\rightarrow$  Selection Lines  
DeMux Input  $\rightarrow$  1









These gates can be in one of **2 possible states**

    - 1) An **enabled** state where the output may assume one of two possible values (**0, 1**)
- 2) A **disabled** state where the gate output is in a the **Hi-impedance** (Hi-Z) state
  - ✦ The circuit behaves like an **open circuit**, which means that the output appears to be **disconnected**
  - ✦ The circuit has **NO** logic **significance**
  - ✦ The circuit connected to the output of the three-state gate is **NOT** affected by the inputs to the gate


A control input (**C**) is used to **control** the gate into either the **enabled** or **disabled** state.

- ✦ C could be **Normal** (Active **High**) or **Inverted** (Active **Low**)
- ✦ Output could be **Normal** (**Buffer**) or **Complemented** (**Inverter**)




It is possible to implement **multiplexers** using **3-state** buffers

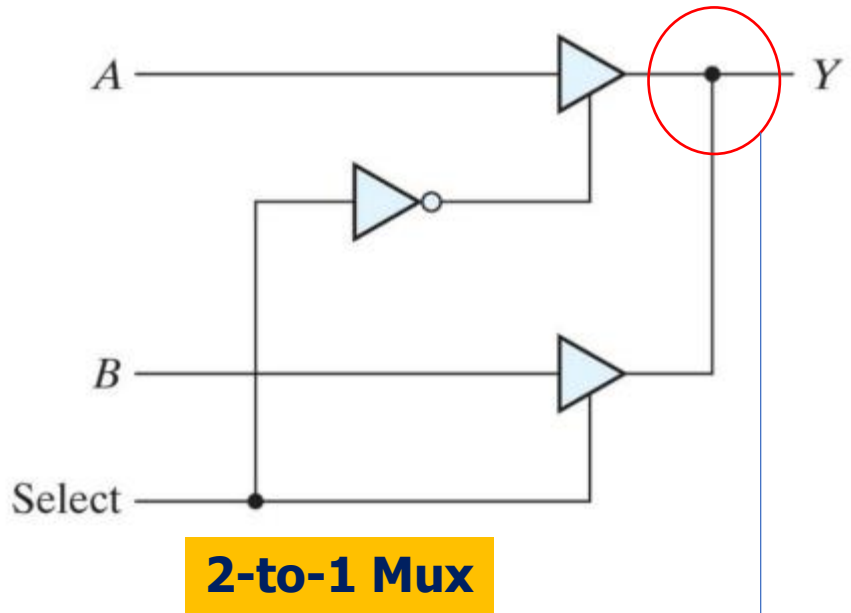A **4-to-1** multiplexer may be constructed using **four 3-state** buffers and a **2-to-4** decoder



**Problem:** Direct Connected/Wired Outputs → Short Circuit → Damage (**Burn**)

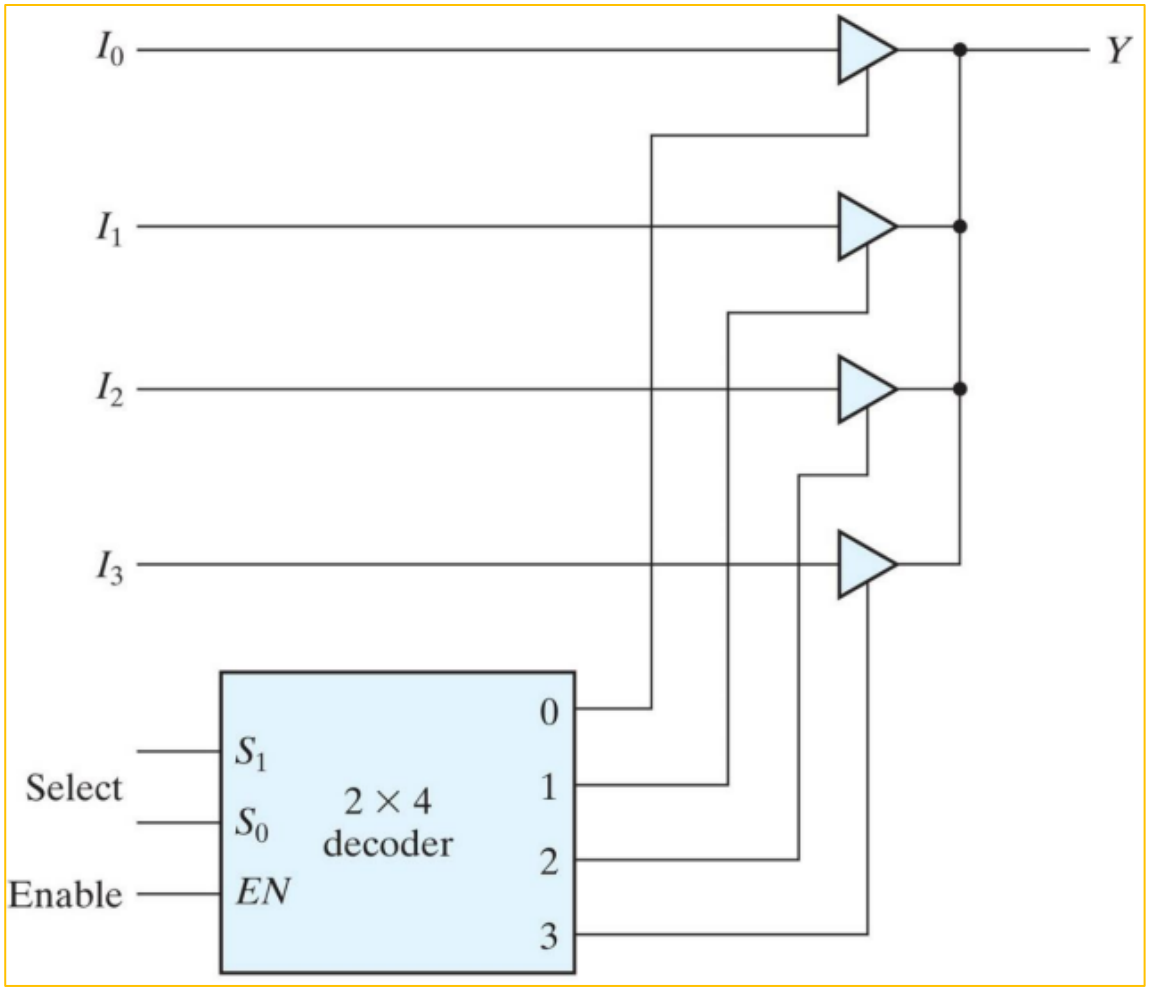**Solution:** Make sure **ONLY ONE** Input is **enabled** by utilizing the **3-States Buffer**



Implement the following Boolean functions (Together): (With minimum number of inputs in the external gates)

$$F_1(A, B, C) = \sum(3, 5)$$
$$F_2(A, B, C) = \sum(2, 4, 5, 6, 7)$$

**Using:**

- A. 3x8 decoder constructed with AND gates.
- B. 3x8 decoder constructed with NAND gates.
- C. 2x4 decoders constructed with NAND gates.

Implement the following Boolean function:

$$F_1(A, B, C, D) = \sum(0, 1, 2, 4, 6, 9, 12, 14)$$

**Using:**

- A. 8-to-1 MUX.
- B. 4-to-1 MUXes, with minimum external gates.

Implement each of the following Boolean functions (**Separately**):

$$F_1(A, B, C) = \sum(0, 1, 3, 5), F_2(A, B, C) = \sum(0, 1, 4, 5)$$

**Using:**

- A. 4-to-1 MUX.
- B. 1-to-4 DEMUX with one external gate.