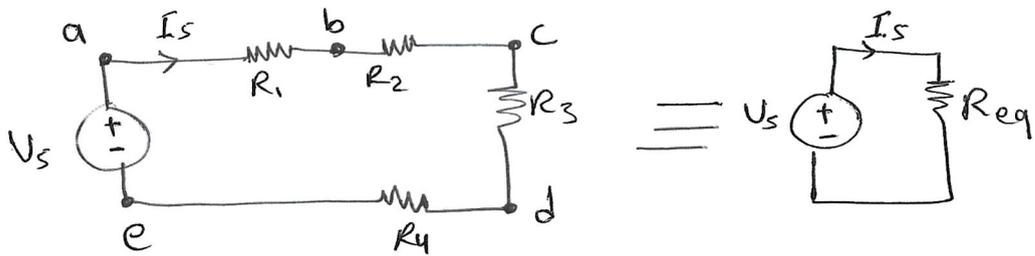


Chapter 3 :- Simple Resistive Circuits


3.1 Resistors in Series :-



$$R_{eq} = R_1 + R_2 + R_3 + R_4$$

$$= \sum_{i=1}^n R_i$$

3.2 Resistors in parallel :-

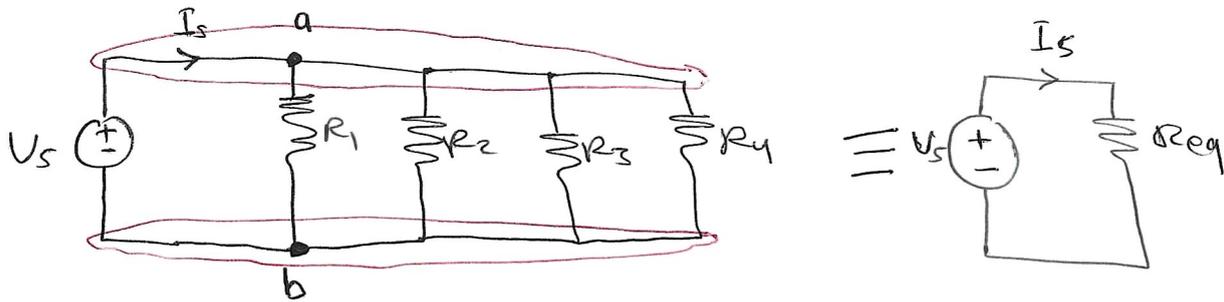


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

Two resistors in parallel

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}, \quad 0.5 \min(R_1, R_2) \leq R_{eq} < \min(R_1, R_2)$$

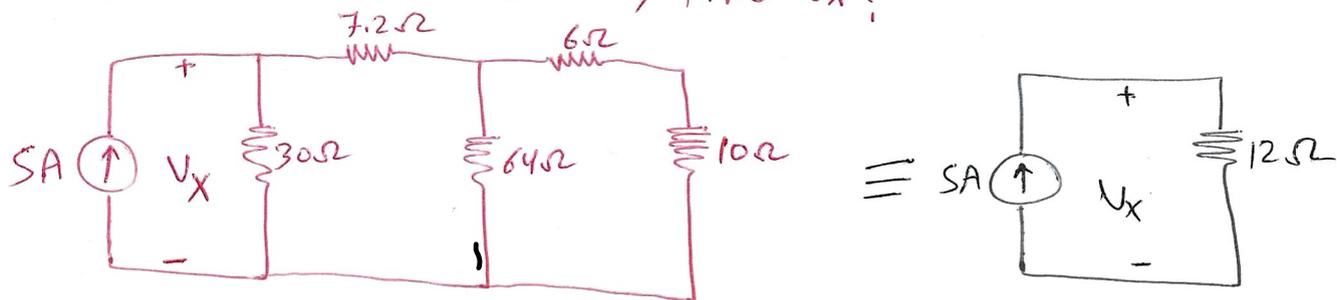Example 8 For the circuit shown, find V_x ?





$$6 + 10 = 16$$

$$16 \parallel 64 = 12.8 \Omega$$

$$20 \Omega \parallel 30 \Omega = 12 \Omega$$

$$V_x = (5)(12) = 60 \text{ V}$$

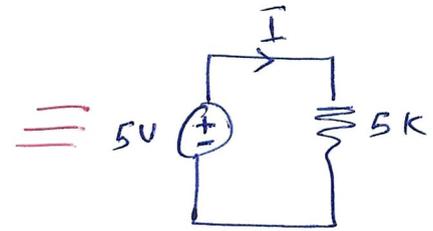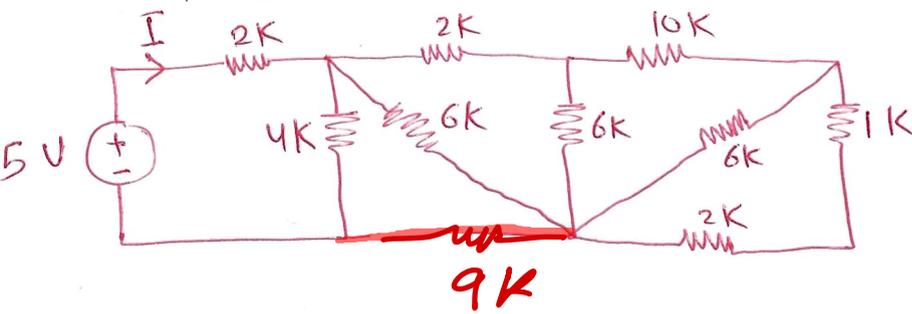
Example - For the following circuit, find I ?



$$\begin{array}{l}
 1+2 = 3K \\
 3K // 6K = 2K \\
 2K + 10K = 12K
 \end{array}
 \left. \vphantom{\begin{array}{l} 1+2 = 3K \\ 3K // 6K = 2K \\ 2K + 10K = 12K \end{array}} \right\}
 \begin{array}{l}
 12 // 6 = 4K \\
 4K + 2K = 6K \\
 6K // 6K = 3K
 \end{array}
 \left. \vphantom{\begin{array}{l} 12 // 6 = 4K \\ 4K + 2K = 6K \\ 6K // 6K = 3K \end{array}} \right\}
 \begin{array}{l}
 3K + 9K = 12K \\
 12K // 4K = 3K \\
 3K + 2K = 5K
 \end{array}
 \left. \vphantom{\begin{array}{l} 3K + 9K = 12K \\ 12K // 4K = 3K \\ 3K + 2K = 5K \end{array}} \right\}
 \begin{array}{l}
 I = \frac{5V}{5K\Omega} \\
 = 1mA
 \end{array}$$

3.3 The voltage-divider and Current-divider Circuits


* Voltage divider -

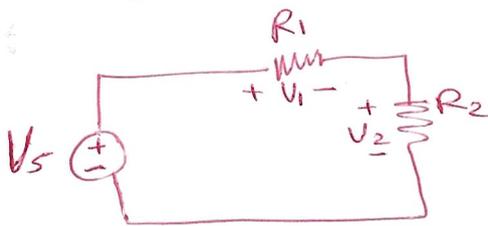

$$V_1 = \frac{V_s R_1}{R_1 + R_2}$$


$$V_2 = \frac{V_s R_2}{R_1 + R_2}$$

* Current divider -

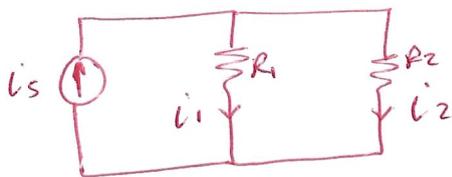



$$i_1 = \frac{i_s R_2}{R_1 + R_2}$$

$$i_2 = \frac{i_s R_1}{R_1 + R_2}$$

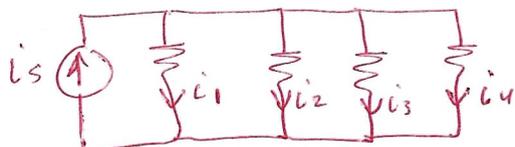



$$i_j = \frac{R_{eq} i_s}{R_j}$$

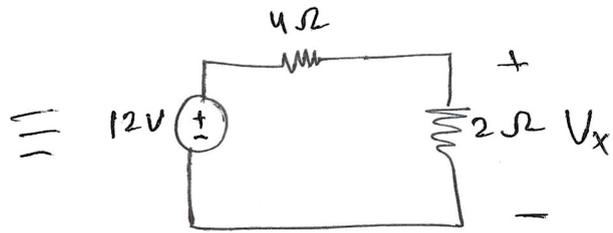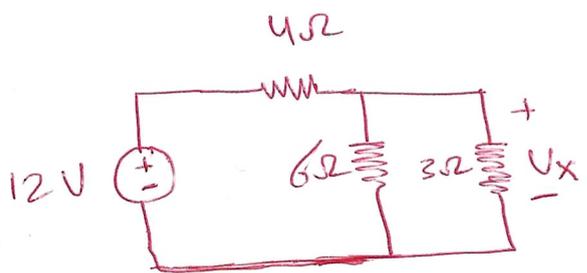Example:- For the circuit shown, find V_x ?



$$V_x = 12 \left(\frac{2}{4+2} \right) = 4V$$

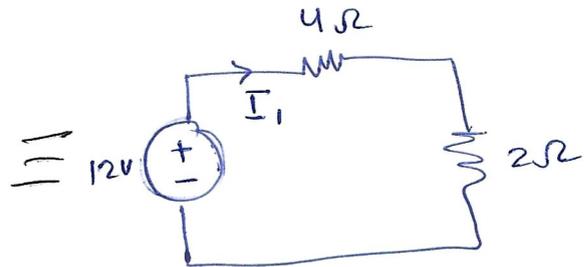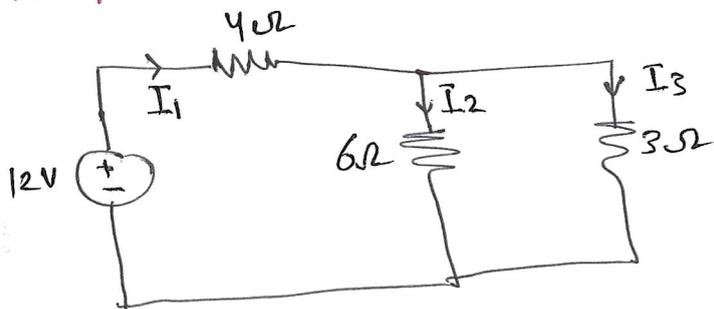
Example:- For the circuit shown, find I_3 ?



$$I_1 = \frac{12}{4+2} = 2A$$

$$I_3 = 2 \left(\frac{6}{6+3} \right) = 1.33A$$


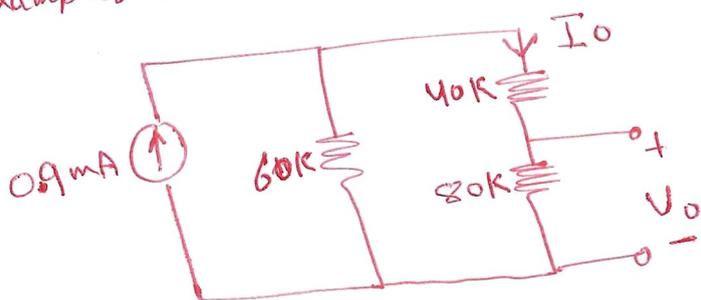
Example:- For the circuit shown, find V_o ?



$$I_o = \frac{0.9mA (60k)}{60k + (40k + 80k)} = 0.3mA$$

$$V_o = 80k(0.3mA) = 24V$$

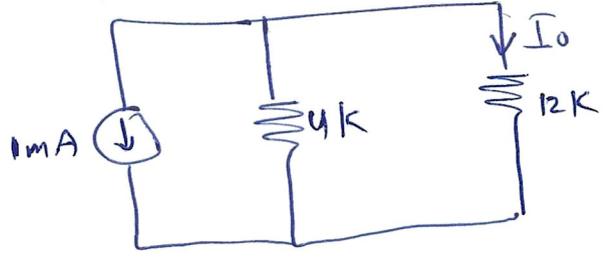
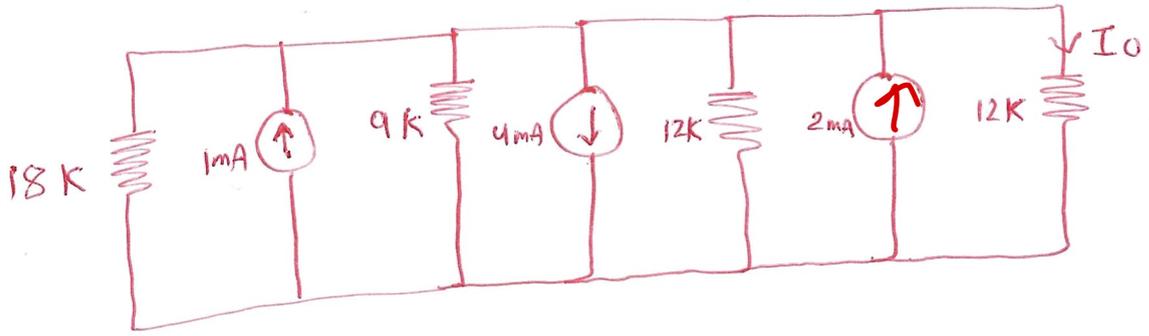
Example: For the circuit shown, find I_0 ?



$$18K // 12K // 9K = 4K$$

$$I_0 = \frac{1mA (4K)}{4K + 12K} = 0.25mA$$

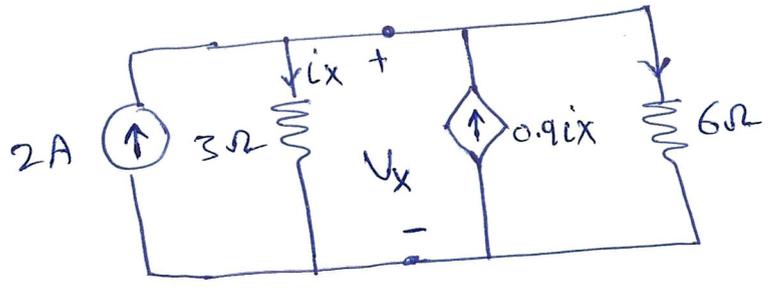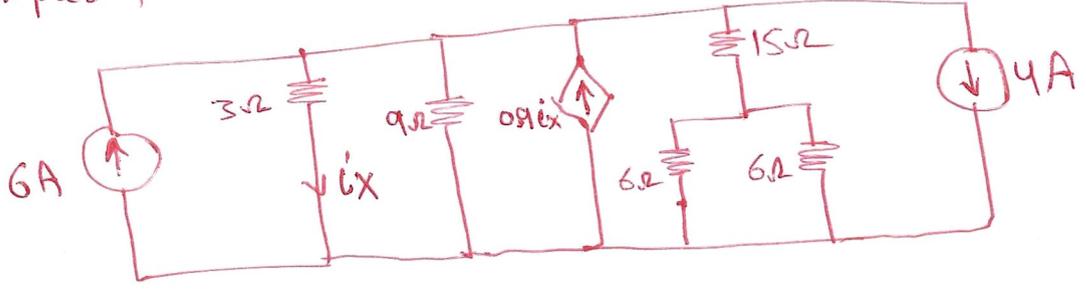Example: for the circuit shown, find the power supplied by $0.9i_x$ source




$$2 + 0.9i_x = i_x + \frac{V_x}{6}, \quad i_x = \frac{V_x}{3}$$


$$\therefore V_x = 10V, \quad i_x = \frac{10}{3}A$$

$$P_{0.9i_x} = -(0.9i_x)V_x = -30W \text{ Supplying}$$

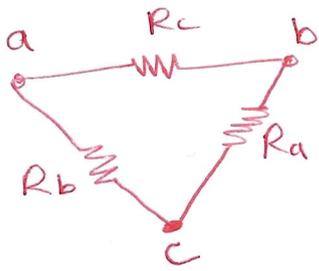3.7 Delta-to-Wye (pi-to-Tee) Transformation




Delta or

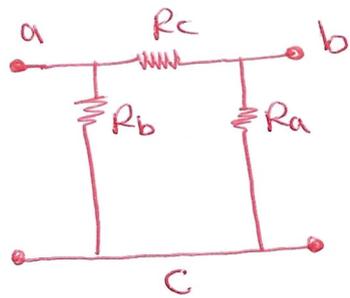


Pi




to

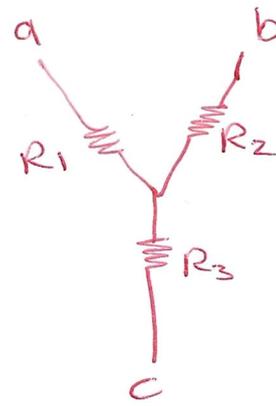

Yee or

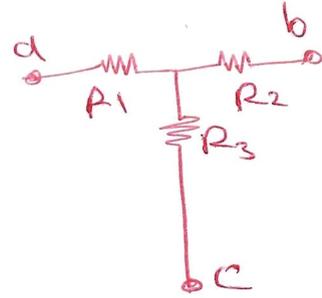

Tee

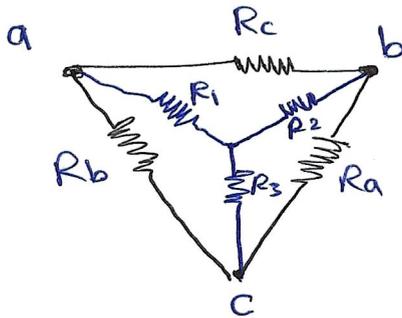

$\Delta - Y$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$Y - \Delta$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$

For the balanced case where


$$R_a = R_b = R_c = R_\Delta$$

$$R_1 = R_2 = R_3 = R_Y$$

$$R_\Delta = 3 R_Y$$

$$R_Y = \frac{1}{3} R_\Delta$$

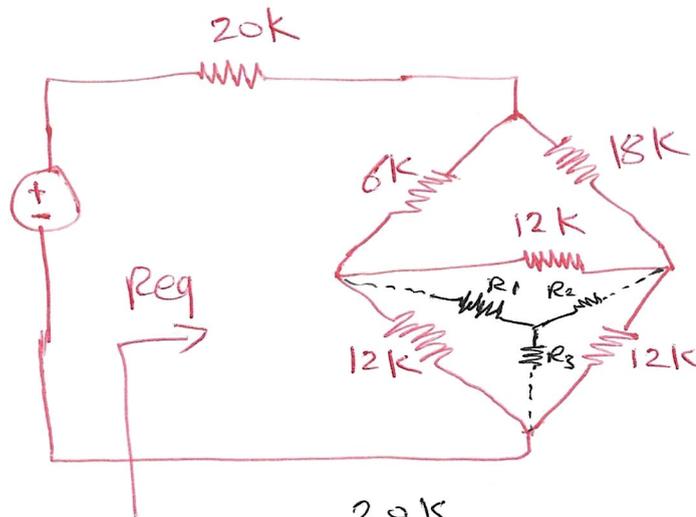Example 9- For the circuit shown, find R_{eq}




$$R_a = R_b = R_c = R_d$$

$$R_{\Delta} = 12K$$

$$R_y = \frac{1}{3} R_{\Delta} = \frac{12K}{3} = 4K$$

$$R_1 = R_2 = R_3 = R_y$$

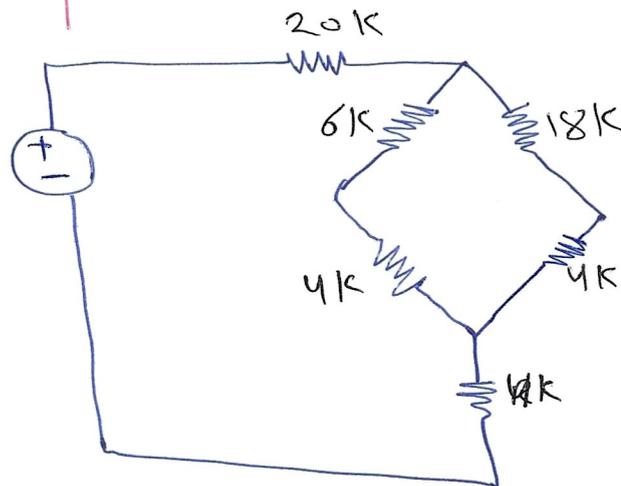


$$R_{eq} = \left[20K + (18K + 4K) \parallel (6K + 4K) + 4K \right]$$

$$= 20 + 22 \parallel 10 + 4$$

$$= 30.88 K\Omega$$

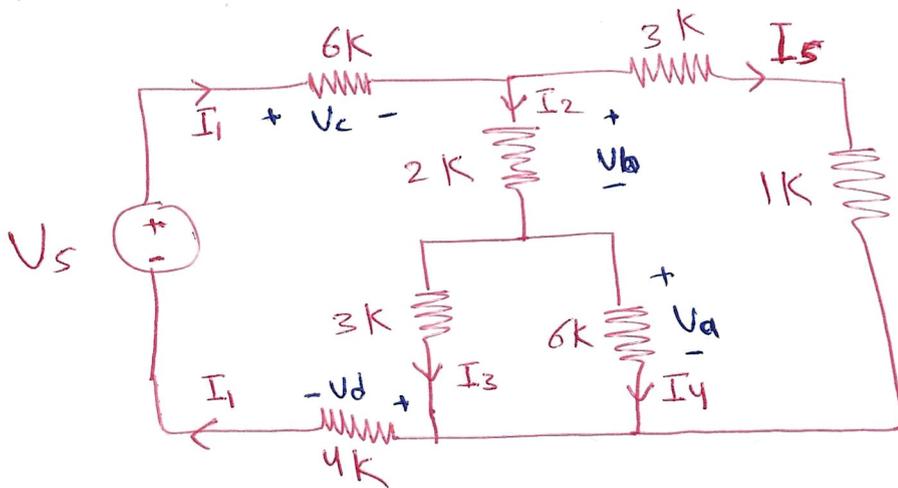Design 8- For the circuit shown, given $I_4 = 0.5 \text{ mA}$, find V_s



$$V_a = (6\text{K})(0.5\text{mA}) = 3\text{V}$$

$$I_3 = \frac{V_a}{3\text{K}} = \frac{3\text{V}}{3\text{K}} = 1\text{mA}$$

$$I_2 = I_3 + I_4 = 1 + 0.5 = 1.5\text{mA}$$

$$V_b = (2\text{K})(1.5\text{mA}) = 3\text{V}$$

$$I_5 = \frac{V_a + V_b}{(3+1)\text{K}\Omega} = \frac{6\text{V}}{4\text{K}} = 1.5\text{mA}$$

$$I_1 = I_2 + I_5 = 3\text{mA}$$

$$V_c = (6\text{K})(3\text{mA}) = 18\text{V}$$

$$V_d = (4\text{K})(3\text{mA}) = 12\text{V}$$

$$-V_s + V_c + V_b + V_a + V_d = 0$$

$$V_s = 18 + 3 + 12 = 33\text{V}$$