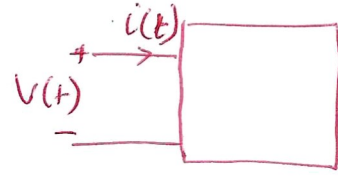


Chapter 10 - Sinusoidal steady state power calculations

10.1 Instantaneous power

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$



$$p(t) = v(t) i(t) \quad i(t) = I_m \cos(\omega t)$$

$$= V_m I_m \cos(\omega t + \theta_v - \theta_i) \cos(\omega t) \quad v(t) = V_m \cos(\omega t + \theta_v - \theta_i)$$

using the identities as in the slides

$$p(t) = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos(2\omega t) - \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin(2\omega t)$$

$$p(t) = P + P \cos(2\omega t) + Q \sin(2\omega t)$$

10.2 Average and Reactive power

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \quad \text{average power (Real power)}$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \quad \text{reactive power}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$X_L = \omega L$$

$$X_C = \frac{-1}{\omega C}$$

for Resistor

$$\theta_v - \theta_i = 0 \quad \text{so} \quad P = \frac{V_m I_m}{2} = V_{rms} I_{rms} = I_{rms}^2 R \quad \text{W}$$

$$Q = 0 \quad \text{VAR} \quad = \frac{I_{rms}^2}{2} R$$

for Inductor

$$\theta_v - \theta_i = 90^\circ \quad \text{so} \quad P = 0 \quad \text{W}$$

$$Q = \frac{V_m I_m}{2} = V_{rms} I_{rms} = I_{rms}^2 X_L \quad \text{VAR}$$


for Capacitor

$$P = 0 \quad \text{W}$$

$$Q = -\frac{V_m I_m}{2} = -V_{rms} I_{rms} = I_{rms}^2 X_C \quad \text{VAR}$$

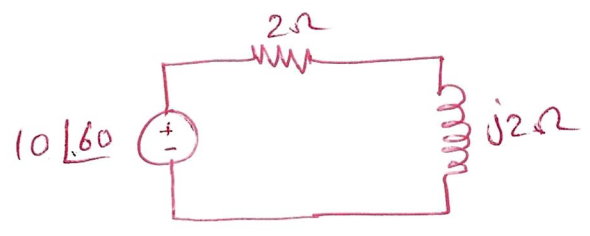Example 8 - Find the average power absorbed by each element

$$I = \frac{10 \angle 60}{2 + j2} = 3.53 \angle 15^\circ \text{ A}$$



$$P_{av} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$P_{av_{j2\Omega}} = 0$$

$$P_{av_{2\Omega}} = \frac{I_m^2 R}{2} = I_{rms}^2 R$$

$$= \frac{(3.53)^2 \cdot 2}{2} = 12.5 \text{ W}$$

$$P_{av_{V_s}} = -\frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$= -\frac{(10)(3.53)}{2} \cos(60 - 15)$$


$$= -12.5 \text{ watt supplied}$$

Example 8 - Determine the average power absorbed by each resistor

$$I_1 = \frac{12 \angle 45}{4\Omega} = 3 \angle 45^\circ \text{ A}$$

$$I_2 = \frac{12 \angle 45}{2 - j1} = 5.36 \angle 71.57^\circ \text{ A}$$
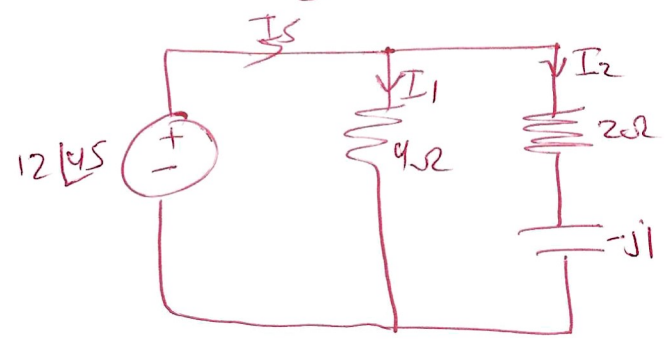
$$I_s = I_1 + I_2 = 8.15 \angle 62.1^\circ \text{ A}$$



$$P_{4\Omega} = \frac{I_{m1}^2 \cdot 4}{2} = 18 \text{ W}$$

$$P_{2\Omega} = \frac{I_{m2}^2 \cdot 2}{2} = 28.7 \text{ W}$$

$$P_{ov} = -(12)(8.16) \cos(45 - 62.1) = -46.7 \text{ W} = - (18 + 28.7)$$

supplied


Example 2 - Determine average power supplied or absorbed by each element

$$I_2 = \frac{12 \angle 30^\circ}{2} = 6 \angle 30^\circ \text{ A}$$

$$I_3 = \frac{12 \angle 30^\circ - 6 \angle 0^\circ}{j1} = 7.43 \angle -36.19^\circ \text{ A}$$

$$I_1 = I_2 + I_3 = 11.29 \angle -7.07^\circ \text{ A}$$
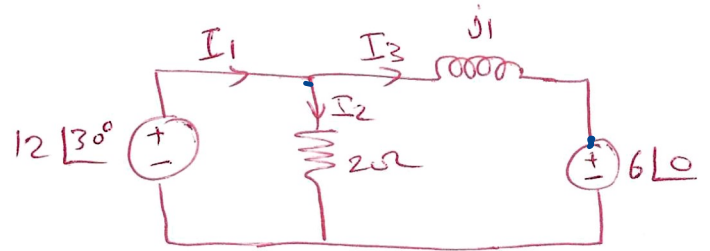
$$P_{2\Omega} = \frac{I_{2m}^2 \cdot 2}{2} = 36 \text{ W}$$



$$P_{12\angle 30^\circ} = -\frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$= -\frac{(12)(11.29)}{2} \cos(30^\circ - -7.07^\circ)$$

$$= -54 \text{ W supply}$$

$$P_{6\angle 0^\circ} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$= \frac{(6)(7.43)}{2} \cos(0^\circ - -36.19^\circ)$$

$$= 18 \text{ W absorbed}$$

$$* V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$P_{av} = V_{rms} I_{rms} \cos(\theta_v - \theta_i) \text{ W}$$

$$P_{apparent} = V_{rms} I_{rms} \text{ VA}$$

$$P_{pf} = \text{Power Factor} = \cos(\theta_v - \theta_i) \Rightarrow P_{av} = P_a \cdot pf$$

For Resistor

$$\theta_v - \theta_i = 0$$

$$\therefore \text{PF} = 1$$

For Inductor

$$\theta_v - \theta_i = 90$$

$$\theta_i < \theta_v$$

$$\therefore \text{PF} = 0$$

For Capacitor

$$\theta_v - \theta_i = -90$$

$$\theta_i > \theta_v$$

$$\therefore \text{PF} = 0$$

For Inductive Load

$$90^\circ > \theta_v - \theta_i > 0$$

$$1 > \text{PF} > 0$$

Lagging Power factor
Current lags voltage

For Capacitive Load


$$-90 < \theta_v - \theta_i < 0$$

$1 > \text{PF} > 0$ Leading power factor
Current leads voltage

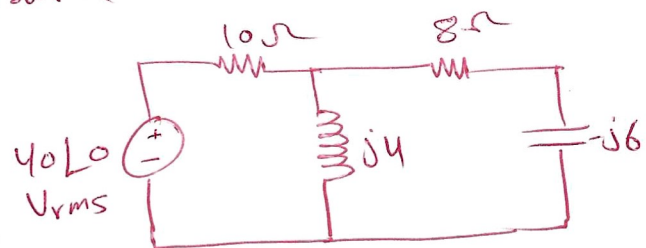Example :- Calculate the power factor seen by the source and the average power supplied by the source

$$Z = (10 + j4) \parallel (8 - j6)$$
$$= 12.69 \angle 20.62^\circ \Omega$$

$$I_s = \frac{40 \angle 0^\circ}{12.69 \angle 20.62^\circ} = 3.152 \angle -20.62^\circ \text{ A}_{\text{rms}}$$



$$\theta_v = 0^\circ$$

$$PF = \cos(\theta_v - \theta_i)$$

$$= \cos(20.62)$$

$$= 0.936 \text{ lagging (Inductive load)}$$

The average power supplied by the source equals to the average power absorbed by the circuit

$$P_{\text{av source}} = -(40)(3.152) \cos(0 - (-20.62))$$

$$= -118 \text{ W supplied.}$$

Example: An Industrial load consumes 11 kW at 0.5 pf lagging from a 220 Vrms line. The transmission line resistance from the power company to the plant is 0.2Ω

1) Determine the power average that must be supplied by the power company

$$P_{\text{av Load}} = V_{\text{rms}} I_{\text{rms}} \cdot PF$$


$$\therefore I_{\text{rms}} = \frac{P_{\text{av Load}}}{V_{\text{rms}} \cdot PF}$$

$$= \frac{11 \text{ kW}}{(220)(0.5)} = 100 \text{ A rms}$$

$$P_{\text{loss}} = (I_{\text{rms}}^2)(0.2) = 2 \text{ kW}$$

$$\therefore P_{\text{sup}} = P_{\text{av Load}} + P_{\text{av Loss}}$$


$$= 11 + 2 = 13 \text{ kW}$$

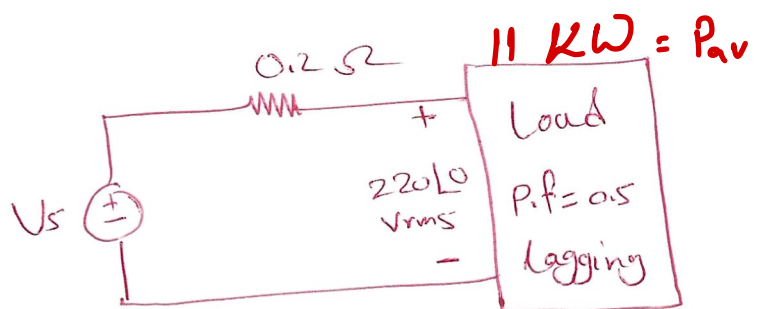

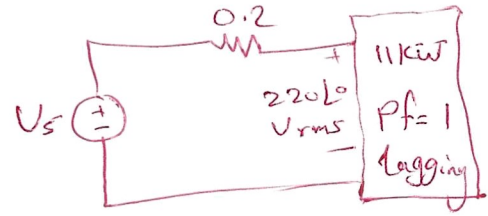2) Repeat ① if the power factor is changed to unity

$$P_{av \text{ Load}} = V_{rms} I_{rms} \cdot pf$$

$$\therefore I_{rms} = \frac{P_{av}}{V_{rms} \cdot pf} = 50 \text{ Arms}$$



$$P_{Loss} = I_{rms}^2 R = (50)^2 (0.2) = 0.5 \text{ kW}$$

$$P_{av \text{ sup.}} = 0.5 + 11 = 11.5 \text{ kW}$$

10.4 Complex Power



The complex power is the complex sum of the real power and the reactive power

$$S = P + jQ$$

S = complex power

P = average power

Q = reactive power

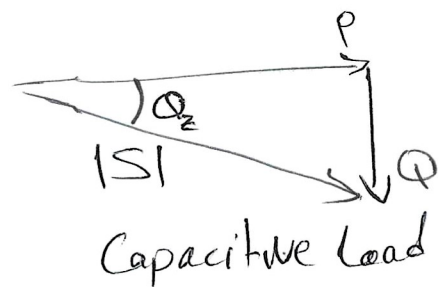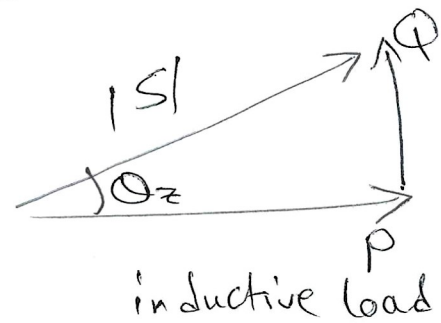

$$Q = \tan^{-1} \frac{Q}{P} = \cos^{-1}(P.F.)$$

$$\therefore \theta_z = \theta_v - \theta_i$$

$$Q = P \tan \theta \Rightarrow P = \frac{Q}{\tan \theta}$$

$$|S|_{\text{apparent power}} = \sqrt{P^2 + Q^2}$$

$$= V_{rms} I_{rms} \angle \theta_v - \theta_i$$


$$= V_{rms} I_{rms}^*$$

where I_{rms}^* is the conjugate of the rms phasor.

Example:- what are the VARs consumed by the circuit?

$$P = V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$

$$I_1 = \frac{V_s}{Z}$$

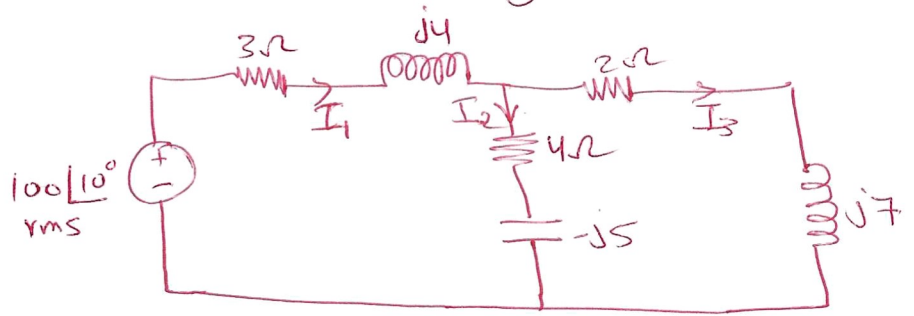

$$Z = 3 + j4 + (4 - j5) \parallel (2 + j7)$$

$$= 10.35 + j4.55 = 11.3 \angle 23.7^\circ$$

$$\therefore I_1 = \frac{100 \angle 10^\circ}{11.3 \angle 23.7^\circ} = 8.84 \angle -13.7^\circ \text{ A}_{rms}$$

$$\therefore Q = (100)(8.84) \sin(10 - (-13.7))$$

$$= 355 \text{ VAR}$$


$$P_{av_T} = P_{av_1} + P_{av_2} + \dots + P_{av_n}$$

$$Q_T = Q_1 + Q_2 + \dots + Q_n$$

$$S_T = S_1 + S_2 + \dots + S_n$$

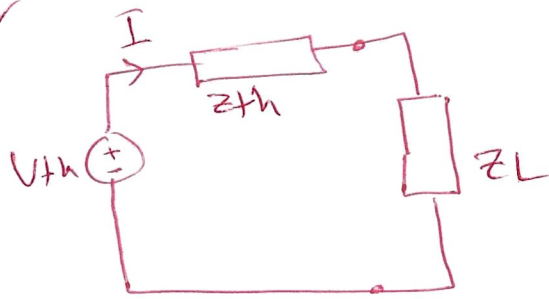10.6 Maximum Power Transfer

For Maximum power transfer, Z_L must equal to conjugate of the Thevenin impedance



$$Z_L = Z_{th}^*$$


For maximum power

$$P_{max} = \frac{1}{4} \frac{V_{th_{rms}}^2}{R_L} \quad V_{rms}$$

$$= \frac{1}{8} \frac{V_{th_{m}}^2}{R_L} \quad V_m$$

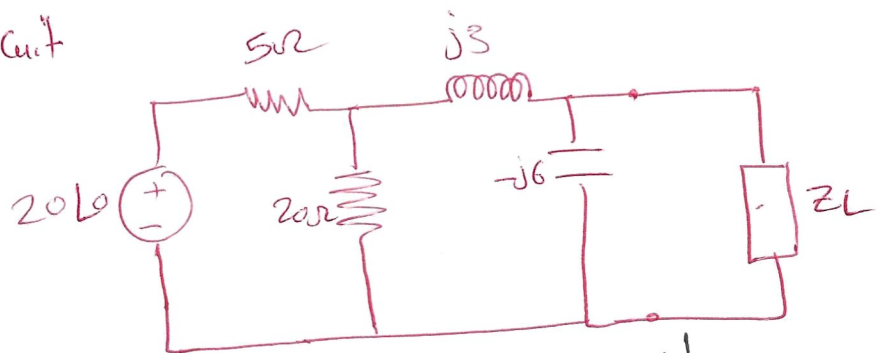Example 2 - for the circuit

shown, determine the impedance Z_L that results in maximum power transfer to Z_L






② what is the maximum average power transferred to the load impedance determined in ①

$$V_{th} = \frac{16 \angle 0}{4 + j3 - j6} \quad (-j6)$$


$$= 19.2 \angle 53.13$$

$$= 11.52 - j15.36 \text{ V}$$

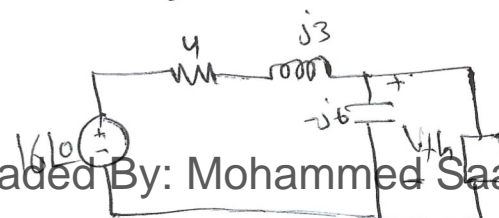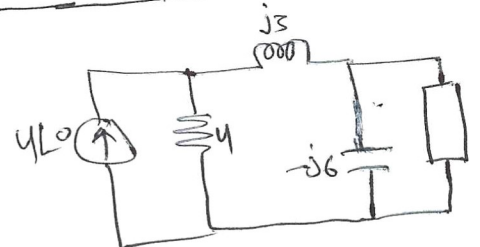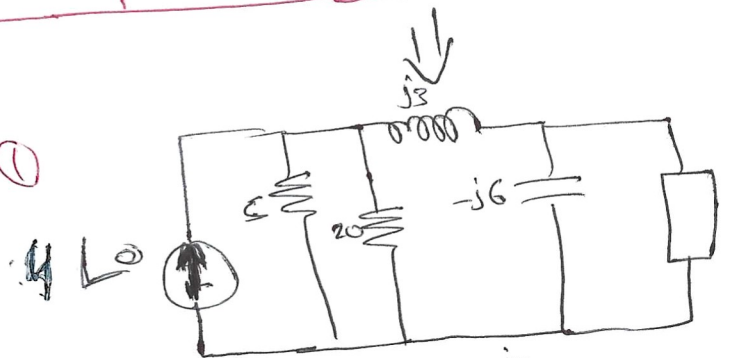

$$Z_{eq} = \frac{(-j6)(4 + j3)}{4 + 3j - j6}$$

$$= 5.76 - j1.68 \Omega$$

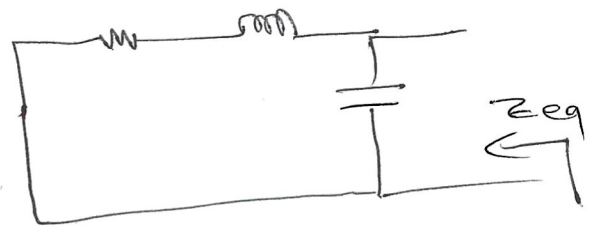

∴ For maximum power transfer $Z_L = 5.76 + j1.68 \Omega$

$$P_{\text{aw maximum}} = \frac{V_{th}^2}{8 R_L}$$

$$= \frac{(19.2)^2}{8(5.76)}$$

$$= 8 \text{ W}$$





$$P_{\text{max}} = \frac{V_{th}^2}{4 R_L} \quad (V_{\text{rms}})$$



$$P_{\text{max}} = \frac{V_{th}^2}{8 R_L} \quad (V_m)$$

Power factor Correction

Power factor correction is the process of increasing the power factor without altering the voltage or the current to the original load. It is necessary for economic reasons.

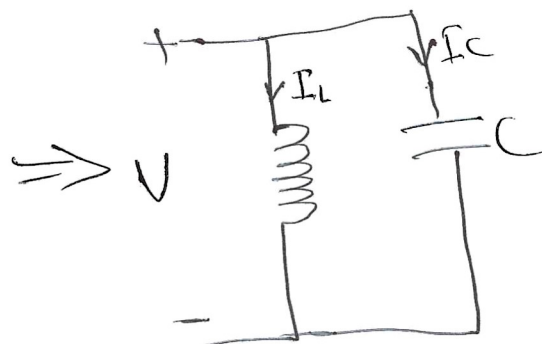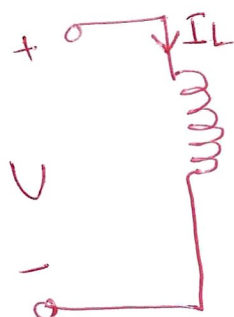To improve the power factor we must decrease the reactive power. For inductive circuit, we add a capacitor in parallel to the load.



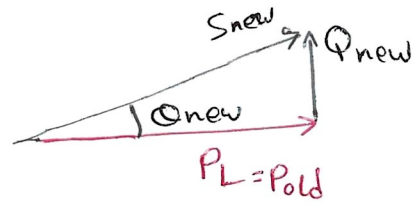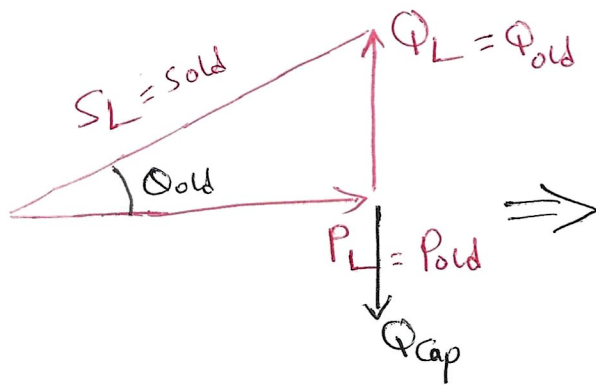

$$S_{old} = P_{old} + Q_{old}$$

$$S_{new} = P_{old} + Q_{new}$$


$$Q_{new} = Q_{old} + Q_{Cap}$$

$$Q_{Cap} = Q_{new} - Q_{old}$$

$$= -\omega C V_{rms}^2$$

$$\therefore C = -\frac{Q_{Cap}}{\omega V_{rms}^2}$$

Example 8

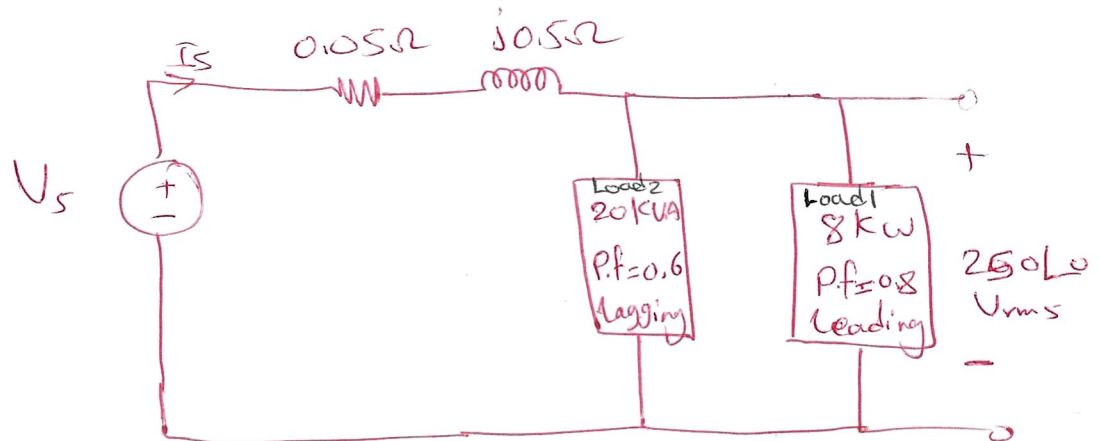

1) Determine the power factor of the two loads in parallel

$$P_{av} = 8 \text{ kW given}$$


$$\frac{Q}{P} = \tan \theta$$

$$\theta = \cos^{-1} \text{p.f.} = \cos^{-1}(0.8) \text{ Leading} = 37^\circ$$


$$Q = -P \tan(\cos^{-1}(0.8)) = -6000 \text{ VAR} = 6000 \text{ VAR}$$

$$\therefore \underline{S_1} = P + jQ$$

$$= 8000 - j6000$$

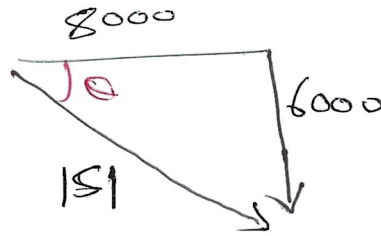

For Load 2

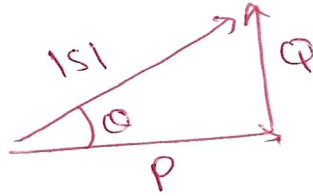

$$|S_2| = 20000 \text{ VA given}$$

$$\theta = \cos^{-1}(\text{PF}) = \cos^{-1}(0.6)$$

$$P_{av} = |S_2| \cos \theta$$

$$= |S_2| \cdot \text{PF}$$

$$= (20000)(0.6) = 12000 \text{ W}$$

$$Q = |S_2| \sin \theta$$

$$= P_{av} \tan(\cos^{-1}(\text{PF}))$$

$$= 12000 \tan(\cos^{-1}(0.6)) = 16000 \text{ VAR}$$

$$S_2 = 12000 + j16000 \text{ VA}$$

$$S_T = S_1 + S_2$$

$$= 20000 + j10000 \text{ VA}$$

$$= 22360 \angle 26.565^\circ$$

$$\therefore \text{pf}_{\text{two loads}} = \cos(26.565) = 0.8944 \text{ lagging}$$

2) Determine the apparent power required to supply the loads, the magnitude of the current I_s , the average power loss in the transmission line.

$$S_T = \sum_{\text{two loads}} = 20000 + j10000$$

$$= 22360 \angle 26.565^\circ$$

$$S_T = V_{\text{rms}} I_{\text{rms}}^*$$

$$\therefore I_{\text{rms}}^* = \frac{S_T}{V_{\text{rms}}} = \frac{22360 \angle 26.565^\circ}{250 \angle 0^\circ} = 89.44 \angle 26.565^\circ$$

$$\therefore I_{\text{rms}} = 89.44 \angle -26.565^\circ$$

$$P_{\text{apparent}} = P_a = |S_T| = 22360 \text{ VA}$$

$$P_{\text{ave loss}} = I_s^2 (0.05)$$

$$= 400 \text{ W}$$

3) Compute the value of the capacitor that would correct the power factor to 1 placed in parallel with two loads, $\omega = 377 \text{ rad/sec}$

$$\theta_{\text{new}} = \cos^{-1}(1) = 0^\circ$$

$$Q_{\text{new}} = 0$$

$$Q_{\text{old}} = 10000 \text{ VAR}$$

$$\therefore Q_{\text{cap}} = Q_{\text{new}} - Q_{\text{old}} = 0 - 10000 = -10000$$

$$C = \frac{-Q_{\text{cap}}}{\omega V_{\text{rms}}^2} = \frac{10000}{(377)(250)^2} = 424.4 \mu\text{F}$$