

①


سار، د. جابر Principles of physics (10th edition)

phy 132

CH 27: circuits

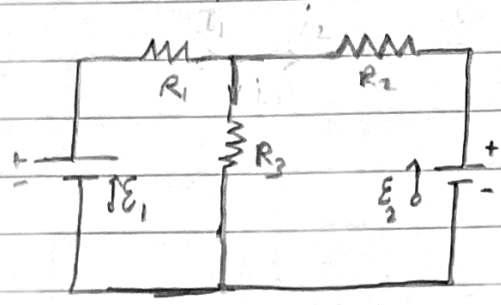Problems: 3, 8, 15, 18, 30, 62, 69

P₃: In Fig 27-18 $\mathcal{E}_1 = 1.00 \text{ V}$, $\mathcal{E}_2 = 3.00 \text{ V}$, $R_1 = 4.00 \Omega$, $R_2 = 2.00 \Omega$, $R_3 = 5.00 \Omega$ and both batteries are ideal. What is the rate at which energy is dissipated in (a) R_1 , (b) R_2 and (c) R_3 ? What is the power of (d) battery 1 and (e) battery 2? Is energy being absorbed or provided in (f) battery 1 and (g) battery 2?




sol:

$$\mathcal{E}i = 0$$

$$i_1 = i_2 + i_3 \rightarrow \textcircled{1}$$

$$\sum \mathcal{U}_i = 0$$

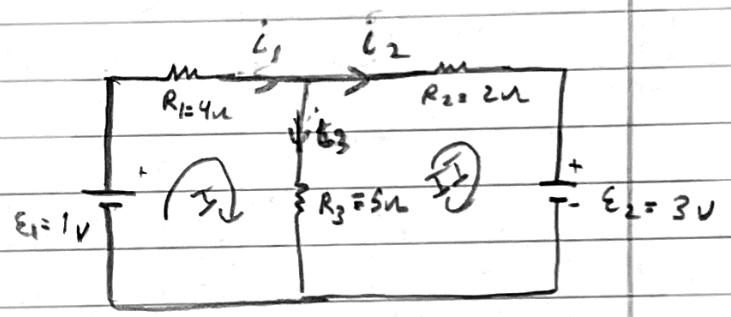

for $\textcircled{1}$: $\mathcal{E}_1 - i_1 R_1 - i_3 R_3 = 0$

$$1 - 4i_1 - 5i_3 = 0 \rightarrow \textcircled{2}$$

for $\textcircled{2}$: $i_3 R_3 - i_2 R_2 - \mathcal{E}_2 = 0$

$$5i_3 - 2i_2 - 3 = 0 \rightarrow \textcircled{3}$$

Sub $\textcircled{1}$ in $\textcircled{2}$

$$1 - 4(i_2 + i_3) - 5i_3 = 0$$

$$1 - 4i_2 - 4i_3 - 5i_3 = 0$$

$$1 - 4i_2 - 9i_3 = 0 \quad \textcircled{4}$$

(2)

حل المعادلتين (3) و (4) بطريقة الكرف ساره بخار

$$5i_3 - 2i_2 - 3 = 0 \quad (3)$$

$$1 - 4i_2 - 9i_3 = 0 \quad (4)$$

اضرب طرفي المعادله (3) بـ -2

$$-10i_3 + 4i_2 + 6 = 0 \quad (5)$$

اجمع المعادلتين (4) و (5)

$$1 - 4i_2 - 9i_3 - 10i_3 + 4i_2 + 6 = 0$$

$$7 - 19i_3 = 0$$

$$i_3 = \frac{7}{19} A$$

$$i_3 = 0.368 A$$

sub i_3 in eq (4)

$$1 - 4i_2 - 9(0.368) = 0$$

$$4i_2 = 1 - 9(0.368)$$

$$4i_2 = -2.315$$

$$i_2 = -0.579 A$$

يعني عكس الاتجاه الذي افترضناه

$$i_1 = i_2 + i_3$$

$$i_1 = -0.579 + 0.368$$

$$i_1 = -0.211 A$$

ايضاً عكس الاتجاه المفترض

3

سارو بخار

$$a) P_1 = i_1^2 R_1 = (-0.211)^2 (4) = 0.178 \text{ watt}$$

$$b) P_2 = i_2^2 R_2 = (-0.579)^2 (2) = 0.670 \text{ watt}$$


$$c) P_3 = i_3^2 R_3 = (0.368)^2 (5) = 0.677 \text{ watt}$$

$$\text{or } \left(\frac{7}{19}\right)^2 (5) = 0.6786 \text{ watt} \\ \approx 0.679 \text{ watt}$$

$$d) P \text{ for } \epsilon_1 = i_1 \epsilon_1 = (-0.211)(1) = -0.211 \text{ watt}$$

$$e) P \text{ for } \epsilon_2 = i_2 \epsilon_2 = (0.579)(5) = 1.737 \approx 1.74 \text{ watt}$$

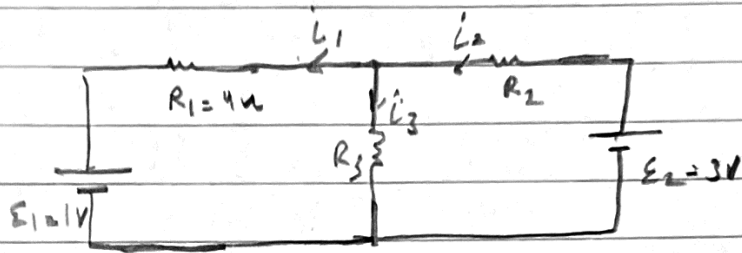لأنه من اتجاه البطارية ϵ_2 إلى اتجاه التيار i_2



اتجاه i_2 مع اتجاه البطارية ϵ_2 أي أنها توفر الطاقة وليست مستهلكة


f) battery 1 absorbing

g) battery 2 providing

(4)

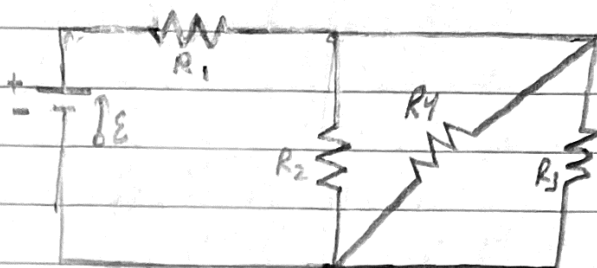Q. 8, Lw

P8: In Fig 27-23, $R_1 = 100 \Omega$, $R_2 = R_3 = 50.0 \Omega$, $R_4 = 75.0 \Omega$ and the ideal battery has emf $\mathcal{E} = 12.0 \text{ V}$ (a) what is the equivalent resistance? what is i in (b) resistance 1 (c) resistance 2 (d) resistance 3 and (e) resistance 4?




sol:

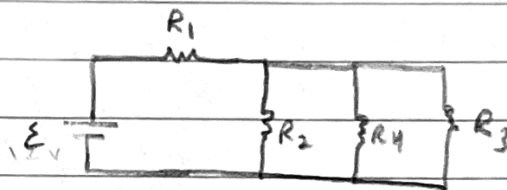a) R_2, R_4, R_3 in parallel


$$\frac{1}{R} = \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$= \frac{1}{75} + \frac{1}{50} + \frac{1}{50}$$



$$\frac{1}{R} = 0.053$$

$$R = 18.75 \Omega$$

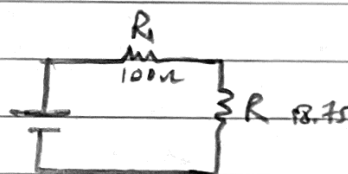

R_1, R in series

$$R_{eq} = R_1 + R$$

$$= 100 + 18.75$$

$$R_{eq} = 118.75 \Omega$$

$$b) i_{tot} = \frac{V}{R_{eq}} = \frac{12}{118.75} = 0.101 \text{ A}$$

$$i_{R_1} = i_{tot} = 0.101 \text{ A}$$

c) $V_R = V_{R_2} = V_{R_3} = V_{R_4}$

سارہ بخار

$$V_R = iR$$

$$= 0.101 \times 18.75$$

$$= 1.89 \text{ volt}$$

e $i_2 = \frac{V_{R_2}}{R_2} = \frac{1.89}{50} = 0.0378 \text{ A}$

d) $i_3 = \frac{V_{R_3}}{R_3} = \frac{1.89}{50} = 0.0378 \text{ A}$

or $i_2 = i_3 = 0.0378 \text{ A}$ since they have the same V, R

e) $i_4 = \frac{V_{R_4}}{R_4} = \frac{1.89}{75} = 0.0252 \text{ A}$

P15: What multiple of time constant τ gives the time taken by an initially uncharged capacitor in an RC series circuit to be charged to 89.0% of its final charge?

sol:

During charging the charge on the positive plate of the capacitor is given by

$$q = C\mathcal{E}(1 - e^{-t/\tau})$$

$$q = q_0(1 - e^{-t/\tau})$$

, q_0 : equilibrium or final charge

$$0.89 q_0 = q_0(1 - e^{-t/\tau})$$

$$0.89 = (1 - e^{-t/\tau})$$

$$e^{-t/\tau} = 1 - 0.89$$

$$e^{-t/\tau} = 0.11$$

6

لإزالة
Taking the natural logarithm of both sides, we obtain

$$\ln(e^{-t/\tau}) = \ln(0.11)$$

$$\frac{-t}{\tau} = -2.207$$

$$\frac{t}{\tau} = 2.207$$

$$t = 2.207\tau$$

$$t \approx 2.21\tau$$

So t is 2.21 multiple of time constant τ

P18: A capacitor with an initial potential difference of 80.0V is discharged through a resistor when a switch between them is closed at $t=0$. At $t=10.0$ s, the potential difference across the capacitor is 1.00 V. (a) What is the time constant of the circuit? (b) What is the potential difference across the capacitor at $t=17.0$ s?

Sol : a) $\mathcal{E}_0 = 80.0$ V At $t=10$ $\mathcal{E} = 1$ volt

$$q = q_0 e^{-t/RC}$$

for discharging capacitor

$$\frac{q}{c} = \frac{q_0}{c} e^{-t/\tau}$$

$$\mathcal{E} = \mathcal{E}_0 e^{-t/\tau}$$

$$1 = 80 e^{-10/\tau}$$

$$\frac{1}{80} = e^{-10/\tau}$$

$$0.0125 = e^{-10/\tau}$$

(7)

سارو فار

$$\ln(0.0125) = \ln e^{-10/\tau}$$

$$-4.38 = \frac{-10}{\tau}$$

$$4.38 = \frac{10}{\tau}$$

$$\tau = \frac{10}{4.38}$$

$$\tau = 2.28 \text{ se}$$

b) $\mathcal{E}(t=17\text{ms}) = \mathcal{E}_0 e^{-t/\tau}$

$$\mathcal{E}(t=17) = 80 e^{-17/2.28}$$

$$= 80 e^{-7.46}$$

$$\mathcal{E} = 0.0462 \text{ Volt}$$

P30: A capacitor with initial charge q_0 is discharged through a resistor. What multiple of time constant τ gives the time the capacitor takes to lose (a) the first 25% of the charge and b) 50% of its charge?

Sol: during the discharging, the charge stored in the capacitor at time t is given by

$$q = q_0 e^{-t/\tau}$$

a) When 25% of the charge is lost then the charge in the capacitor is $100\% - 25\% = 75\%$ of the charge

$$q = q_0 - 0.25q_0 = 0.75 q_0$$

$$\Rightarrow 0.75 q_0 = q_0 e^{-t/\tau}$$

8

$$0.75 = e^{-t/\tau}$$

سوال ۸

$$\ln 0.75 = \frac{-t}{\tau}$$

$$-0.288 = \frac{-t}{\tau}$$

$$0.288 = \frac{t}{\tau} \Rightarrow t = 0.288 \tau$$

$$b) \quad q = q_0 - 0.50 q_0 = 0.50 q_0$$

$$q = q_0 e^{-t/\tau}$$

$$0.50 q_0 = q_0 e^{-t/\tau}$$

$$0.5 = e^{-t/\tau}$$

$$\ln(0.5) = \frac{-t}{\tau}$$

$$-0.693 = \frac{-t}{\tau}$$

$$0.693 = \frac{t}{\tau} \Rightarrow t = 0.693 \tau$$

P62: A 1.0 MF capacitor with an initial stored energy of 0.60 J is discharged through a 1.0 M Ω resistor. (a) What is the initial charge on the capacitor? (b) What is the current through the resistor when the discharge starts? Find an expression that gives, as a function of time t (c) the potential difference V_C across the capacitor (d) the potential difference V_R across the resistor and (e) the rate at which thermal energy is produced in the resistor?

(9)

ساره جبار

Sol: $C = 1.0 \mu\text{F}$, $E = 0.60\text{J}$, $R = 1.0\text{M}\Omega$

a) $E = \frac{Q_0^2}{2C}$, Q_0 : initial charge on the capacitor

$$Q_0^2 = 2EC$$

$$Q_0 = \sqrt{2EC}$$

$$= \sqrt{2 \times 0.60 \times 1 \times 10^{-6}}$$

$$Q_0 = 1.095 \times 10^{-3} \text{ C}$$

b) $q = Q_0 e^{-t/RC}$

$$i = \frac{dq}{dt} = -\frac{Q_0}{RC} e^{-t/RC}$$

$$i = -\frac{Q_0}{\tau} e^{-t/RC}$$

$$i = -i_0 e^{-t/RC}$$

$$i_0 = \frac{Q_0}{\tau} = \frac{1.095 \times 10^{-3}}{1 \times 10^6 \times 1 \times 10^{-6}} = 1.095 \times 10^{-3} \text{ A}$$

(The current through the resistor when discharge start)

$$\Rightarrow i = -1.095 \times 10^{-3} e^{-t/\tau}$$

but $\tau = RC = 1 \times 10^6 \times 1 \times 10^{-6}$

$$\Rightarrow \boxed{i = -1.095 \times 10^{-3} e^{-t}}$$

The expression as a function of time t

(10)

c) $V_c = V_0 e^{-t/RC}$ or $\epsilon = \epsilon_0 e^{-t/RC}$ ساره جيار

$$= \frac{q_0}{C} e^{-t/RC}$$

$$= \frac{1.095 \times 10^{-3}}{1 \times 10^{-6}} e^{-t/(1 \times 10^{-6} \times 1 \times 10^6)}$$

$$\tau = RC = 1$$

$$V_c = 1.095 \times 10^3 e^{-t}$$

d) $V_R = -\frac{q_0}{C} e^{-t/RC}$

$$\Rightarrow V_R = -1.095 \times 10^3 e^{-t}$$

e) $P = i^2 R$

$$= (-1.095 \times 10^{-3} e^{-t})^2 \times 1 \times 10^6$$

$$= 1.199 \times 10^{-6} e^{-2t} \times 10^6$$

$$P = 1.199 e^{-2t}$$

OR $P = i^2 R$


$$= \left(\frac{q_0}{RC} e^{-t/RC} \right)^2 R$$

$$= \frac{q_0^2}{R^2 C^2} R e^{-2t/RC}$$

$$P = \frac{q_0^2}{R C^2} e^{-2t/RC} = \frac{(1.095 \times 10^{-3})^2}{1 \times 10^6 \times 1 \times 10^{-6}} e^{-2t} = 1.199 e^{-2t}$$

B.O.L.W

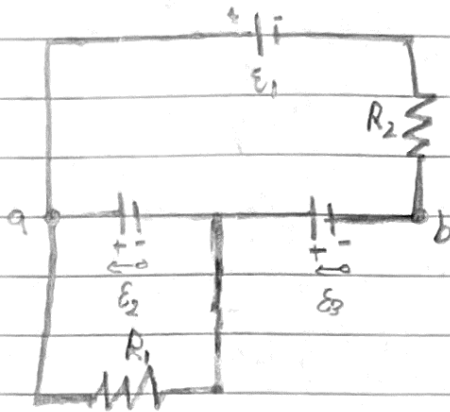P 69: In Fig 27-60, $R_1 = 100 \Omega$, $R_2 = 50 \Omega$ and the ideal batteries have emfs $\mathcal{E}_1 = 6.0 \text{ V}$, $\mathcal{E}_2 = 10 \text{ V}$ and $\mathcal{E}_3 = 4.0 \text{ V}$. Find (a) the current in resistor 1, (b) the current in resistor 2 and (c) the potential difference between points a and b.



Sol:

a) (I)

$$\mathcal{E}_2 - i_1 R_1 = 0$$

$$\mathcal{E}_2 = i_1 R_1$$

$$i_1 = \frac{\mathcal{E}_2}{R_1}$$


$$i_1 = \frac{10}{100}$$

$$i_1 = 0.1 \text{ A}$$

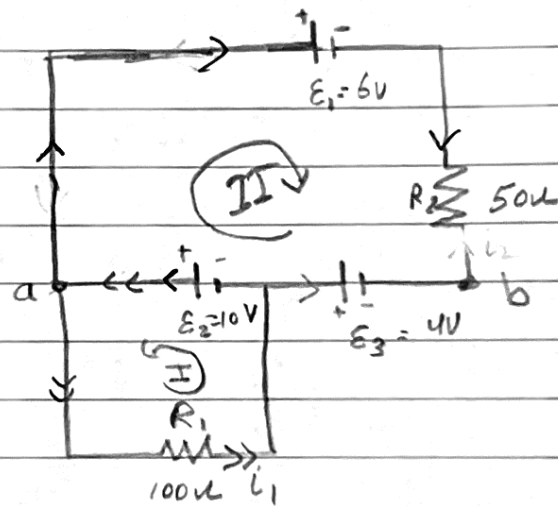b) (II)

$$\mathcal{E}_2 - \mathcal{E}_1 + \mathcal{E}_3 - i_2 R_2 = 0$$

$$\mathcal{E}_2 - \mathcal{E}_1 + \mathcal{E}_3 = i_2 R_2$$



(12)

سارو جا

$$i_2 = \frac{\varepsilon_2 - \varepsilon_1 + \varepsilon_3}{R_2} = \frac{10 - 6 + 4}{50} = \frac{8}{50} = 0.16 \text{ A}$$

c) $V_a = V_b + \varepsilon_3 + \varepsilon_2$

$$\begin{aligned} V_a - V_b &= \varepsilon_3 + \varepsilon_2 \\ &= 4 + 10 \\ &= 14 \text{ volt} \end{aligned}$$

