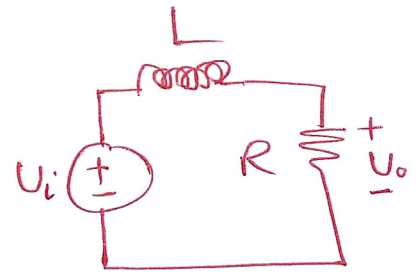


Chapter 14^o - Introduction to frequency selective circuits

14.2 Low-pass filters (LPF)


①-RL $V_o(s) = \frac{R (U_i(s))}{sL + R} \div \frac{L}{L}$



$$\frac{V_o(s)}{U_i(s)} = H(s) = \frac{R/L}{s + R/L}$$

$$s = j\omega$$
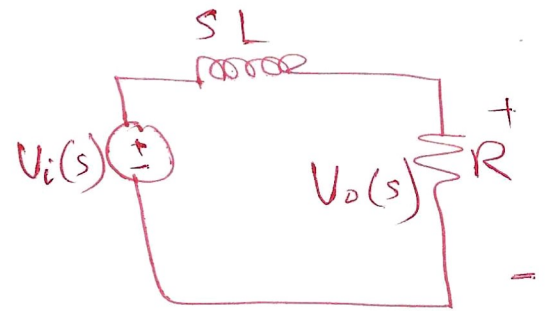
$$H(j\omega) = \frac{R/L}{j\omega + R/L}$$



$$|H(j\omega)|^2 = \frac{R/L}{j\omega + R/L} \cdot \frac{R/L}{-j\omega + R/L}$$

$$= \frac{(R/L)^2}{\omega^2 + (R/L)^2}$$

$$\therefore |H(j\omega)| = \frac{\overbrace{(R/L)}^{\omega_c}}{\sqrt{\omega^2 + (R/L)^2}}$$

$$\omega_c = \frac{R}{L} = 2\pi f_c$$

② RC (LPF) $H(s) = \frac{1/sC}{1/sC + R} = \frac{\overbrace{1/RC}^{\omega_c}}{s + 1/RC}$




$$\omega_c = \frac{1}{RC}$$

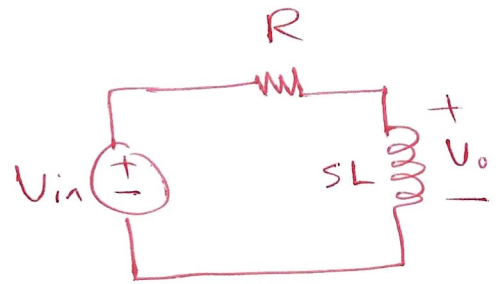14.3 High-pass filters

① RL (HPF)


$$H(s) = \frac{sL}{sL + R} = \frac{s}{s + \left(\frac{R}{L}\right) \omega_c}$$



$$\omega_c = \frac{R}{L}$$

② RC (HPF)
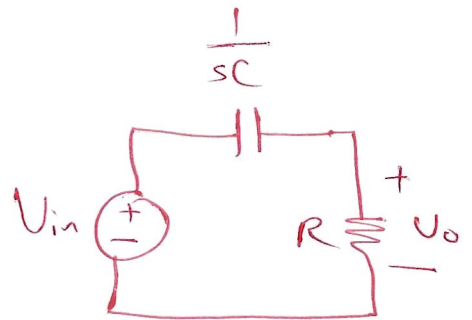
$$H(s) = \frac{R}{R + \frac{1}{sC}} = \frac{s}{s + \frac{1}{RC}}$$




$$\omega_c = \frac{1}{RC}$$

14.4 Band-pass Filters (BPF)

① series RLC (BPF)

$$H(s) = \frac{R}{R + sL + \frac{1}{sC}} = \frac{R}{\frac{sCR + s^2LC + 1}{sC}}$$
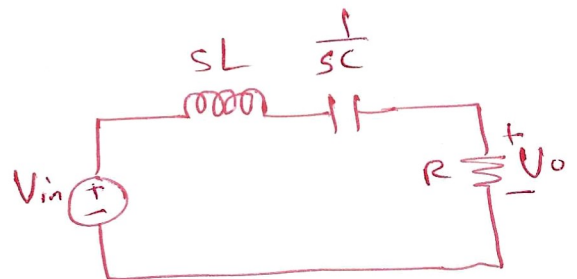
$$= \frac{sRC/LC}{s^2 + \frac{sRC}{LC} + \frac{1}{LC}}$$



$$= \frac{s\left(\frac{R}{L}\right)}{s^2 + s\left(\frac{R}{L}\right) + \frac{1}{LC}} = \frac{\beta s}{s^2 + \beta s + \omega_0^2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\beta = \frac{R}{L} = \omega_{c2} - \omega_{c1}$$

$$\omega_0 = \sqrt{\omega_{c1}\omega_{c2}}$$

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$Q = \frac{\omega_0}{\beta} = \sqrt{\frac{L}{CR^2}}$$

$$\omega_{c2} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$


② Parallel RLC - band pass filter (BPF)

$$H(s) = \frac{Z_{eq}}{Z_{eq} + R}$$

$$= \frac{s}{RC}$$

$$s^2 + \frac{s}{RC} + \frac{1}{LC}$$
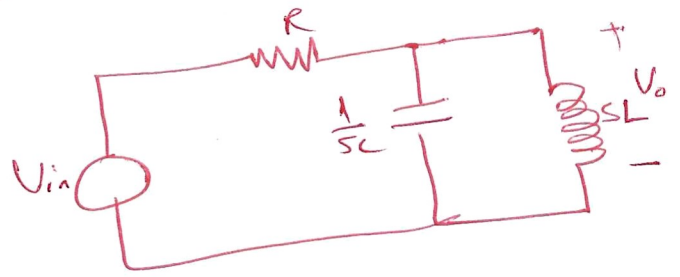
$$\equiv \frac{Bs}{s^2 + Bs + \omega_0^2}$$



$$\omega_{c1} = -\frac{1}{RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c2} = \frac{1}{RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\omega_0 = \sqrt{\omega_{c1} \omega_{c2}} = \frac{1}{\sqrt{LC}}$$


$$B = \omega_{c2} - \omega_{c1} = \frac{1}{RC}$$

$$Q = \frac{\omega_0}{B} = \frac{1/\sqrt{LC}}{1/RC} = \sqrt{\frac{R^2 C}{L}}$$

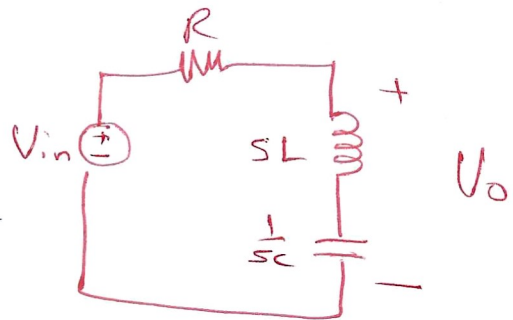14.5 Band-reject filters (BRF)

① Series RLC


$$H(s) = \frac{s^2 + \left(\frac{1}{LC}\right)}{s^2 + s\left(\frac{R}{L}\right) + \frac{1}{LC}} \equiv \frac{s^2 + \omega_0^2}{s^2 + Bs + \omega_0^2}$$



$\omega_{c1}, \omega_{c2}, \omega_0, B$ and Q as in series RLC bandpass

② Parallel RLC BRF
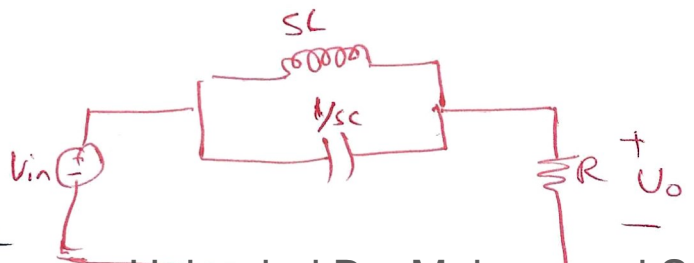
$$H(s) = \frac{s^2 + \left(\frac{1}{LC}\right)}{s^2 + s\left(\frac{1}{RC}\right) + \frac{1}{LC}}$$



$\omega_0, \omega_{c1}, \omega_{c2}, B$ and Q as in parallel RLC BPF