



BIRZEIT UNIVERSITY

كلية العلوم Faculty of Science

دائرة الفيزياء Department of Physics

Phys111 Report

Experiment #4: DC Circuit

Name:	Malek Zeghari	ID #:	1230358
Partner:	////////////////////	ID #:	////////////////////
Section:	W01		
Date:	26\12\2023		

(1) Abstract:

- Aim of the experiment:

To calculate the value of an unknown resistance and to find if it ohmic or non-ohmic, and to find the value of R , R_s and R_p .

- The main results are:

$$R = 100 \pm 11 \Omega$$

$$R_s = 300 \pm 50 \Omega$$

$$R_p = 62 \pm 14 \Omega$$

(2) Data:

Part A: One resistor circuit

	1.	2.	3.	4.	5.	6.
I (mA)	5mA	10mA	15mA	20mA	25mA	30mA
V (volts)	0.5v	1.0v	1.5v	2.0v	2.5v	3.0v

$$\Delta I = 1\text{mA}$$

$$\Delta V = 0.1\text{v}$$

Part B: Two resistors in series

$$I_s = 16\text{mA}$$

$$V_s = 5\text{v}$$

$$\Delta I_s = 1\text{mA}$$

$$\Delta V_s = 0.5\text{v}$$

Part C: Two resistors in parallel

$$I_p = 80\text{mA}$$

$$V_p = 5\text{v}$$

$$\Delta I_p = 10\text{mA}$$

$$\Delta V_p = 0.5\text{v}$$

Note: the result of V, I in ΔR is the average of my readings in the experiment.

$$V_{\text{average}} = 1.75 \Omega$$

$$I_{\text{average}} = 17.5 \Omega$$

(3) Calculations:

Part A: One resistor circuit

From the Graph :(in the last page)

From Graph	$R = 100 \Omega$	From Color code	$R = 100 \Omega$
	$\Delta R = 11.42857143 \Omega$		$\Delta R = 5 \Omega$

To find ΔR I need to Derivation ($R = \frac{V}{I}$) $\rightarrow \Delta R = R \times (\frac{\Delta V}{V} + \frac{\Delta I}{I}) = 100 \times (\frac{0.1}{1.75} + \frac{1}{17.5}) = 11.42857143$

Resistance form color code

Brown	Black	Brown	Gold
$R_1 = 100 \pm 5 \Omega$			

Red	Black	Brown	Gold
$R_2 = 200 \pm 10 \Omega$			

Part B: Two resistors in series

From Experiment	$R_s = \frac{V_s}{I_s} = \frac{5}{16 \times 10^{-3}} = 312.5 \Omega$	From Color code	$R_s = R_1 + R_2 = 100 + 200 = 300 \Omega$
	$\Delta R_s = 50.78125 \Omega$		$\Delta R_s = \Delta R_1 + \Delta R_2 = 5 + 10 = 15 \Omega$

*To find ΔR_s I need to Derivation ($R_s = \frac{V_s}{I_s}$) $\rightarrow \Delta R_s = R_s (\frac{\Delta V_s}{V_s} + \frac{\Delta I_s}{I_s}) = 312.5 (\frac{0.5}{5} + \frac{1}{16}) =$

Part B: Two resistors in series

From Experiment	$R_p = \frac{V_p}{I_p} = \frac{5}{80 \times 10^{-3}} = 62.5 \Omega$	From Color code	$R_p = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{100 \times 200}{100 + 200} = 66.6667 \Omega \approx 70 \Omega$
	$\Delta R_p = 14.0625 \Omega$		$\Delta R_p = 10.000005 \Omega$

*To find ΔR_p I need to Derivation ($R_p = \frac{V_p}{I_p}$) $\rightarrow \Delta R_p = R_p (\frac{\Delta V_p}{V_p} + \frac{\Delta I_p}{I_p}) = 62.5 (\frac{0.5}{5} + \frac{10}{80}) =$

(4) Results:

$R = 100 \pm 11 \Omega$
$R_s = 310 \pm 50 \Omega$
$R_p = 62 \pm 14 \Omega$

*** I want to suppose: $A = R_1 \times R_2$, $B = R_1 + R_2 \rightarrow A = 100 \times 200 = 20000$ // $B = 100 + 200 = 300$

diff. A, B \rightarrow

$$\Delta A = R_1 \times \Delta R_2 + R_2 \times \Delta R_1 \quad ; \quad \Delta B = \Delta R_1 + \Delta R_2 \rightarrow \Delta A = 100 \times 10 + 200 \times 5 = 20000 \quad // \quad \Delta B = 10 + 5 = 15$$

*To find ΔR_p I need to Derivation ($R_p = \frac{R_1 \times R_2}{R_1 + R_2}$) $= \Delta R_p = (\frac{A}{B})$

$$\Delta R_p = R_p \times (\frac{\Delta A}{A} + \frac{\Delta B}{B}) = 66.6667 (\frac{20000}{20000} + \frac{15}{300}) =$$

(5) Conclusions:

After I did the readings and calculations in the experiment, if I want to know if the results are acceptable or not, I need to make the **range test** for each resistance:

Part (A): R

Range Test : exp 4 :-

→ Part (A) :- R from measurement = $100 \pm 11 \Omega$
R from the color code = $100 \pm 5 \Omega$

according to Rang Test :-

R → color code
 $(R - \Delta R), (R + \Delta R) \rightarrow (100 - 5), (100 + 5)$
 $= (95, 105)$

R → measurement:
 $(R - \Delta R), (R + \Delta R) \rightarrow (100 - 11), (100 + 11)$
 $= (89, 111)$

⇒ It's accepted because there's common area between R from measurement and R from color code (95, 105).

Part(B): R_s

$$\text{Part (B): } R_s \text{ from measurement} = 300 \pm 50 \Omega$$

$$R_s \text{ from color code} = 300 \pm 15 \Omega$$


according to Range Test \Rightarrow

$$R_s \text{ color code} \rightarrow (R_s - \Delta R_s), (R_s + \Delta R_s) \rightarrow (300 - 15), (300 + 15)$$

$$= (285, 315)$$

$$R_s \text{ measurement} \rightarrow (R_s - \Delta R_s), (R_s + \Delta R_s) \rightarrow (300 - 50), (300 + 50)$$

$$= (250, 350)$$

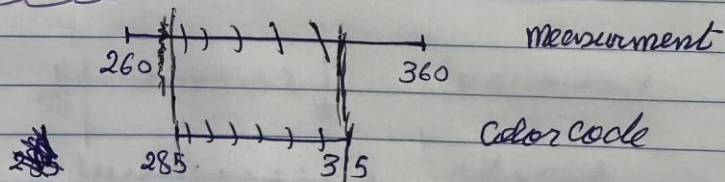

\Rightarrow it's accepted because there's common area between R_s from measurement and R_s from color code (285, 315).

Part (C) : R_p


Part (C) : R_p from measurement = $62 \pm 14 \Omega$

R_p from color code = $70 \pm 10 \Omega$

according to Range Test :-

$R \rightarrow$ measurement $\rightarrow (R_p - DR_p), (R_p + DR_p) \rightarrow (62 - 14), (62 + 14)$
 $= (48, 76)$

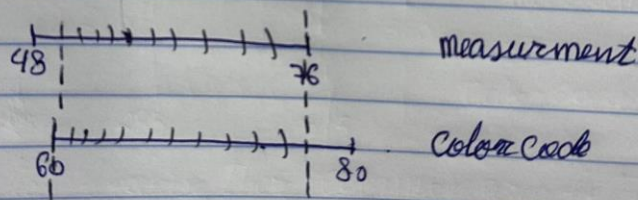$R \rightarrow$ color code $\rightarrow (R_p - DR_p), (R_p + DR_p) \rightarrow (70 - 10), (70 + 10)$
 $= (60, 80)$



\Rightarrow it's accepted because there's common area between R_p from measurement and R_p from color code $(60, 76)$

Malek Zeghari, 1230358 Exp 4

0.25" Quad Ruled Graph Paper

$$R(\text{Graph}) = \text{slope} = \frac{\Delta V}{\Delta I} = \frac{V(6) - V(1)}{I(6) - I(1)}$$

$$= \frac{3.5 - 0.5}{(30 - 5) \times 10^{-3}} = 100 \Omega$$

$(\times 10^{-3})$ jeil r seb c.e A r mA r voltag k pait *

V VS I

