


# DC Power supply :

Mohammed Sa'leh

## 1) Transformer

$$V_2 = \frac{1}{n} V_1$$

$$i_2 = n i_1$$

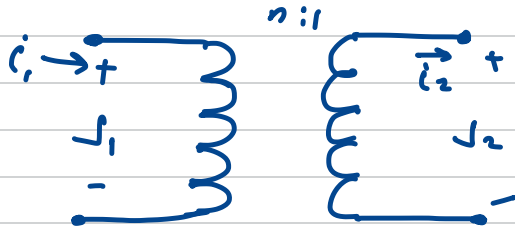

## 2) Rectifier

### A) Half Wave rectifier

$$V_{o,av} = \frac{V_m}{\pi}$$

$$T = T_0$$

$$I_{o,av} = \frac{V_m}{\pi R_L}$$

$$f = f_0$$

$$I_{FM} = \frac{V_m}{\pi R_L}$$

$$PIV = V_{RM} = -V_m$$

### B) Full Wave rectifier

#### 1) Center-tapped transformer Full-Wave rectifier

$$V_{o,av} = \frac{2V_m}{\pi}$$

$$T = \frac{1}{2} T_0$$

$$I_{o,av} = I_{FM} = \frac{2V_m}{\pi R_L}$$

$$f = 2f_0$$

$$PIV = V_{RM} = -2V_m$$

## ② Bridge Full-Wave rectifier

$$V_{o,av} = \frac{2V_m}{\pi} \quad T = \frac{1}{2}T_0$$

$$I_{o,av} = I_{FM} = \frac{2V_m}{\pi R_L} \quad f = 2f_0$$

$$PIV = V_{RM} = -V_m$$

## ③ Filter

$$\text{Ripple Factor } r = \frac{RMS}{\text{Average Value of output signal}} \times 100\%$$

$$\text{For triangular signal } RMS = \frac{\text{Peak Value}}{\sqrt{3}}$$

$$\text{or } RMS = \frac{\text{Peak-to-Peak Value}}{2\sqrt{3}} = \frac{V_{Lr,p-p}}{2\sqrt{3}}$$

$$r = \frac{\frac{V_{Lr,p-p}}{2\sqrt{3}}}{V_{L,dc}}$$

$$V_{L,dc} = V_{L,av} = V_m - \frac{1}{2} V_{Lr,p-p}$$

for Half-wave rectifier

$$V_{Lr, p-p} = \frac{V_m}{f_0 RC}$$

$$\Rightarrow r = \frac{1}{\sqrt{3}(2f_0 RC - 1)} \times 100\%$$

For Full-wave rectifier

$$V_{Lr, p-p} = \frac{V_m}{2f_0 RC}$$


$$\Rightarrow r = \frac{1}{\sqrt{3}(4f_0 RC - 1)} \times 100\%$$

4) Regulator with Zener diode:

Zener in the Break down region:

$$I_{Z(\min)} < I_Z < I_{Z(\max)}$$

Design for  $R_s$

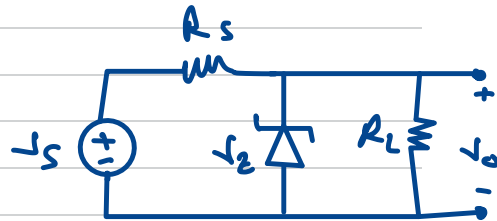

$$\frac{V_{s(\max)} - V_z}{I_{L(\min)} + I_{Z(\max)}} \leq R_s \leq \frac{V_{s(\min)} - V_z}{I_{L(\max)} + I_{Z(\min)}}$$

# AC Small Signal analysis for diodes

$$i_D(t) = I_{DQ} + i_d(t)$$

↑                      ↑  
DC component      AC component

$$v_D(t) = V_{DQ} + v_d(t)$$

↑                      ↑  
DC component      AC component


$$v_d = \frac{i_d}{r_d} \quad , \quad r_d = \frac{V_T}{I_{DQ}} \quad ; \quad V_T = 25.69 \text{ mV}$$

# BJT

npn type



pnp type

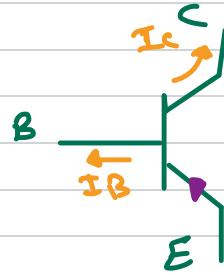

In active region

$$I_C = \alpha I_E$$

$$I_C = \beta I_B$$

$$I_E = I_C + I_B = (\beta + 1) I_B$$

$$\beta = \frac{\alpha}{1 - \alpha} \quad ; \quad \alpha = \frac{\beta}{\beta + 1}$$

For npn  $\rightarrow V_{BE} = 0.7 \text{ Volt.}$

For pnp  $\rightarrow V_{BE} = -0.7 \text{ Volt.}$

To verify that BJT in active region

For npn  $\rightarrow V_{CE} > V_{CE, \text{sat}} = 0.2 \text{ Volt}$

For pnp  $\rightarrow V_{CE} < V_{CE, \text{sat}} = -0.2 \text{ Volt}$

In cutoff region

$$I_C = I_B = I_E = 0$$

In saturation region

For npn :  $V_{CE} = V_{CE, \text{sat}} = 0.2 \text{ Volt}$   
 $V_{BE} = 0.8 \text{ Volt.}$

For pnp :  $V_{CE} = V_{CE, \text{sat}} = -0.2 \text{ Volt}$   
 $V_{BE} = -0.8 \text{ Volt.}$

To verify that BJT in saturation region

$$I_B(\text{min}) = \frac{I_C, \text{sat}}{\beta}$$

$I_B > I_B(\text{min})$  BJT in saturation region

$I_B < I_B(\text{min})$  BJT in active region

AC Small Signal analysis

$$h_{fe} = \beta, \quad h_{ie} = \frac{\sqrt{I}}{I_B}; \quad \sqrt{I} = 25.69 \text{ mV}$$

$$h_{fb} = \alpha, \quad h_{ib} = \frac{\sqrt{I}}{I_E}$$

# OP-Amp

$$i(+)=i(-)=0$$

## ① Linear region

→ there is negative feedback.

$$V_d = V(+)-V(-) = 0$$

1) Inverting Amplifier  $V_o = -\frac{R_F}{R_i} V_s$

2) Inverting Adder  $V_o = -\left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3\right)$

3) Non-Inverting Amplifier  $V_o = \left(1 + \frac{R_F}{R_i}\right) V(+)$

4) Subtraction  $V_o = \left(1 + \frac{R_F}{R_i}\right) V(+)-\frac{R_F}{R_i} V_2$

5) Instrumentation Amplifier  $V_o = \left(1 + \frac{2}{a}\right) (V_1 - V_2)$

## ② Non-Linear (comparator)

→ there is neither negative nor positive feedback.

When  $V_d > 0 \rightarrow V(+)>V(-) \rightarrow V_o = +V_{sat}$

When  $V_d < 0 \rightarrow V(+)<V(-) \rightarrow V_o = -V_{sat}$

## ③ Schmitt trigger

→ there is positive feedback

Find  $V_{UT}$  and  $V_{LT}$  by assume:

1)  $V_o = +V_{sat} \rightarrow V_d > 0$

2)  $V_o = -V_{sat} \rightarrow V_d < 0$

# Voltage Regulator

## 1) Simple Discrete Regulator


$$V_o = \left(1 + \frac{R_1}{R_2}\right) V_z$$

For current limiting  $R_{sc} = \frac{0.7}{I_{L(max)}}$
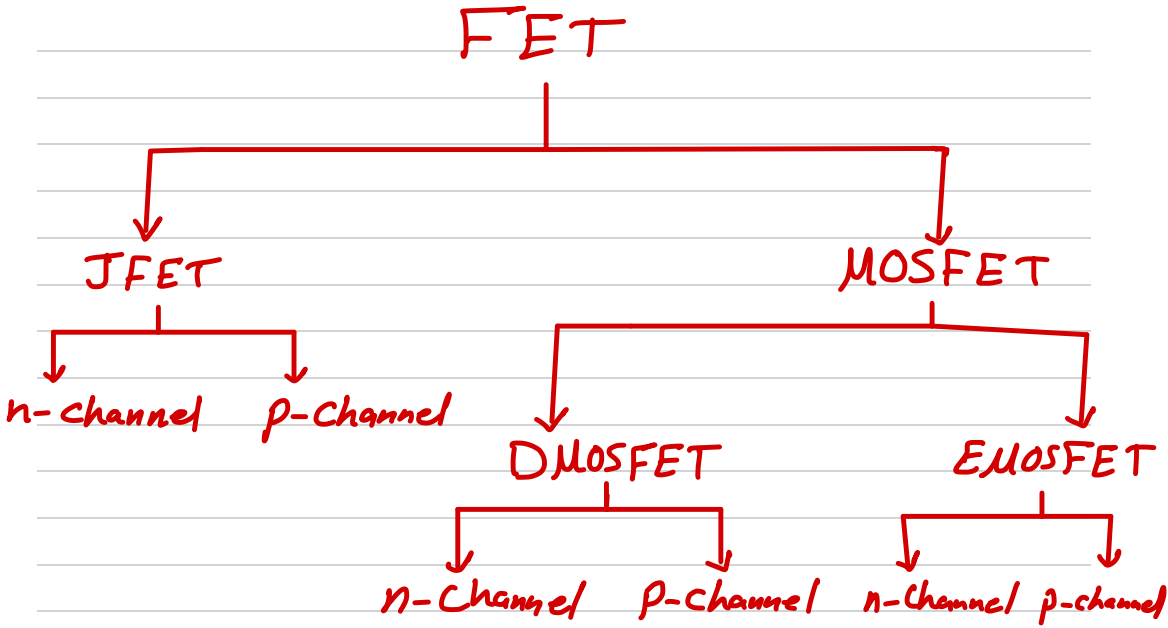
## 2) IC Regulator

$$V_o = V_{REG} \left(1 + \frac{R_2}{R_1}\right) + R_2 I_Q$$






## 1) JFET

$$I_{Ds} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$I_{Ds} \leq I_{DSS}$$

A) n-channel

$V_P, V_{GS}$  negative

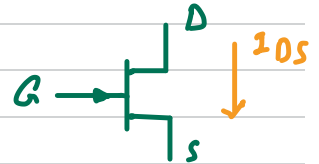

Pinch off region

$$V_P < V_{GS} \leq 0$$

$$|V_{Ds}| > |V_P| - |V_{GS}|$$

B) p-channel

$V_P, V_{GS}$  positive



Pinch off region


$$0 \leq V_{GS} < V_P$$

$$|V_{Ds}| > |V_P| - |V_{GS}|$$

## ② DMOSFET


$$I_{Ds} = I_{Dss} \left( 1 - \frac{V_{Gs}}{V_p} \right)^2$$

A) n-channel  
 $V_p$  negative

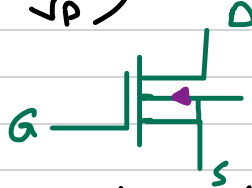

Pinch off regio  $\begin{cases} V_{Gs} > V_p \\ V_{Ds} > V_{Gs} - V_p \end{cases}$

B) p-channel  
 $V_p$  positive

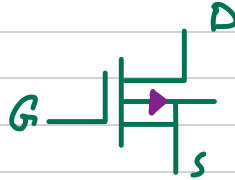


pinch off region  $\begin{cases} V_{Gs} < V_p \\ V_{Ds} < V_{Gs} - V_p \end{cases}$

## ③ EMOSFET


$$I_{Ds} = K_n (V_{Gs} - V_T)^2$$

A) n-channel  
 in pinch off region

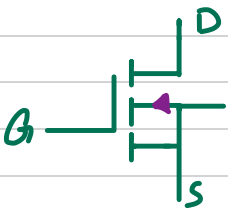

$V_{Gs} > V_T$  positive

B) p-channel  
 in pinch off region

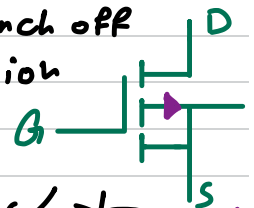

$V_{Gs} < V_T$  negative

For both:  $|V_{Ds}| > |V_{Gs} - V_T|$

## AC Small Signal analysis :

⇒ For JFET and DMOSFET

$$g_m = \frac{-2 I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right)$$

⇒ For EMOSFET

$$g_m = 2 k_n (V_{GS} - V_T)$$

$$g_m = 2 \sqrt{k_n I_{DS}}$$

## Drain equivalent circuit :

- What's in the Drain stay the same
- What's in the Source multiply By  $(\mu+1)$
- $V_g$  multiply By  $\mu$ . ←  $\mu$   $\frac{I_{D(on)}}{I_{D(0V)}}$

## Source equivalent circuit.

- What's in the Source stay the same.
- What's in the Drain divide By  $(\mu+1)$
- $V_g$  multiply B  $\frac{\mu}{\mu+1}$

$$\mu = g_m r_{ds}$$

$$* k_n = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(0V)})^2}$$