

Operational Amplifiers


The Operational Amplifier

Very high voltage gain ; 200,000



Very High input impedance ; 10M ohm

Very small output impedance ; 75ohm

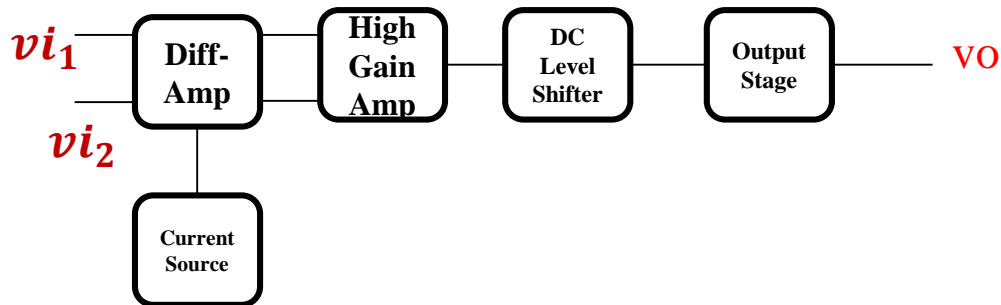
Designed to do mathematical operations such as addition , subtraction



Operational Amplifiers

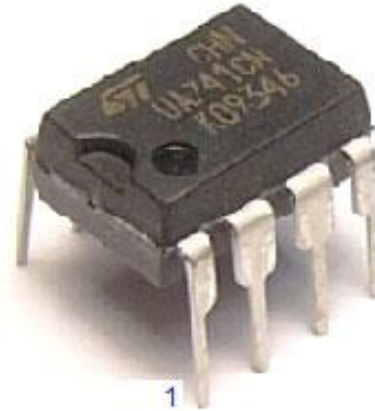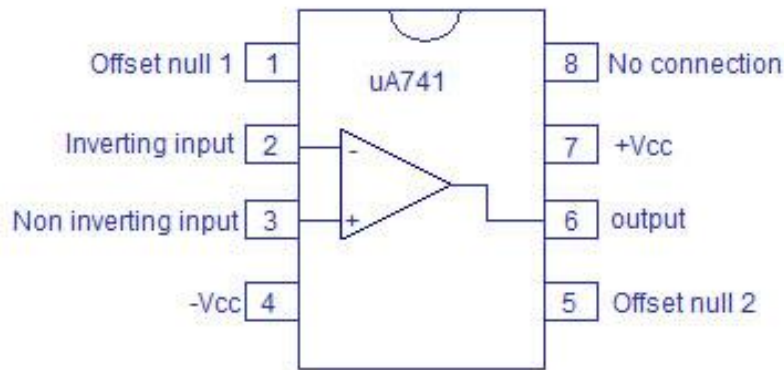

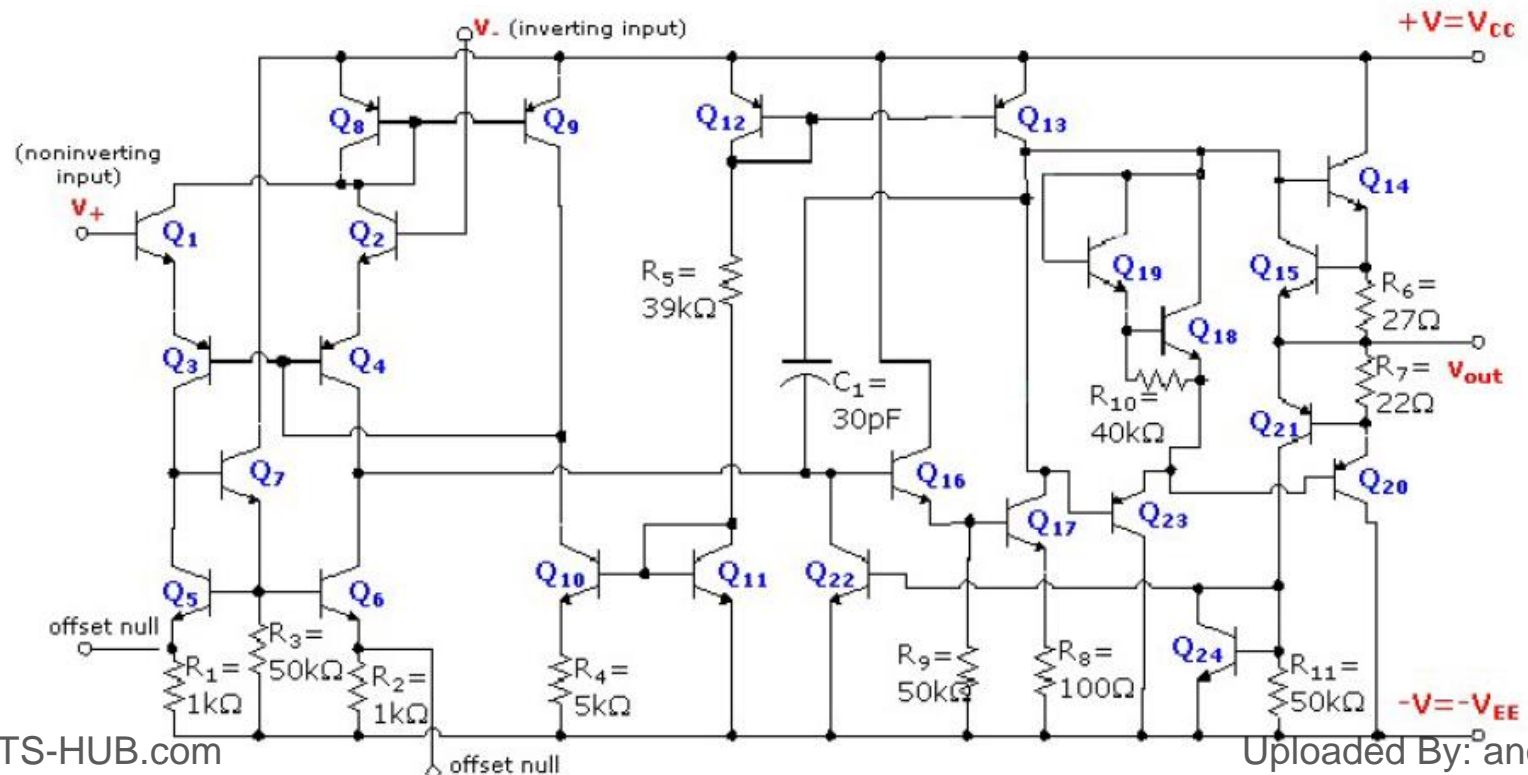
uA741 opamp Pinout and External appearance




Operational Amplifier



Transfer characteristic Curve:
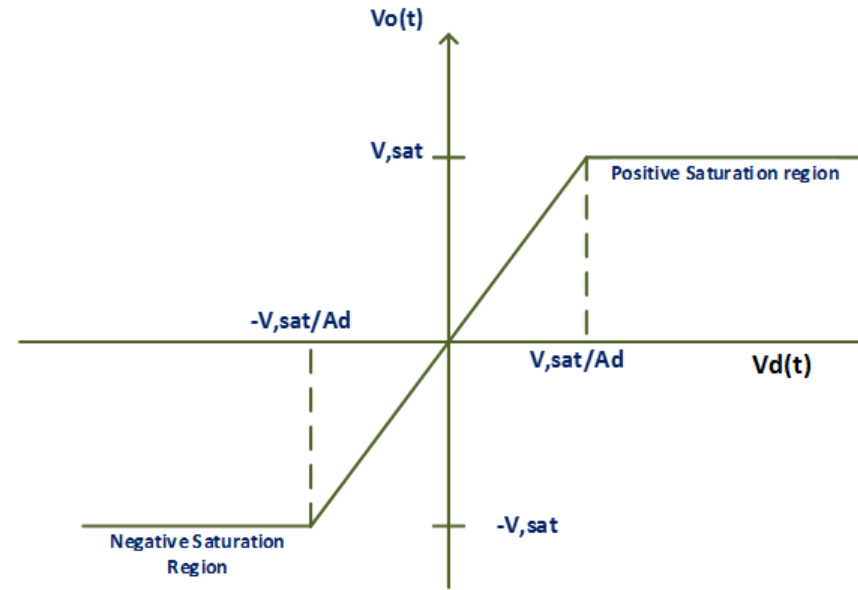
$$V_o = \begin{cases} +V_{sat} & vd > \frac{V_{sat}}{A_d} \\ A_d v_d & \frac{V_{sat}}{A_d} > vd > -\frac{V_{sat}}{A_d} \\ -V_{sat} & vd < -\frac{V_{sat}}{A_d} \end{cases}$$



$$vd = V(+)-V(-)$$

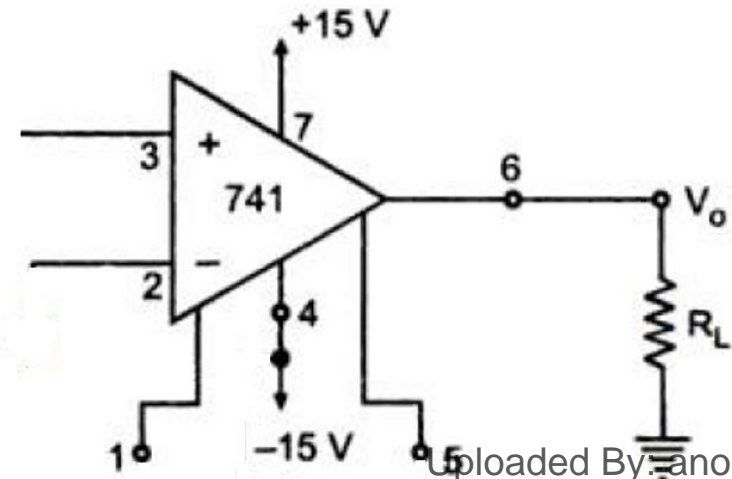

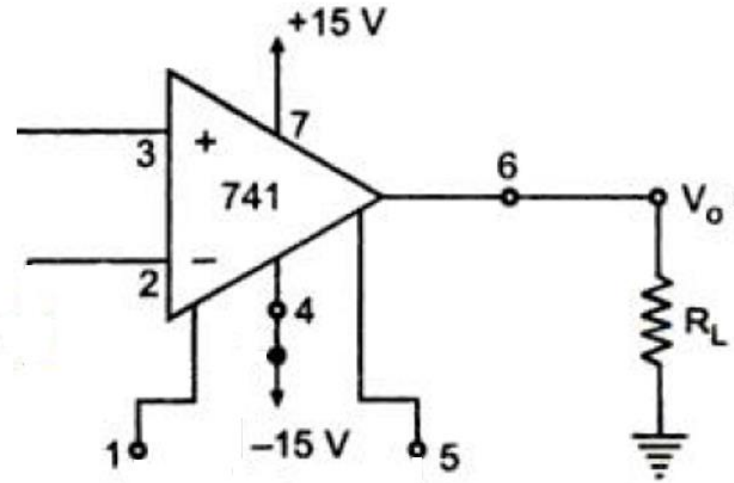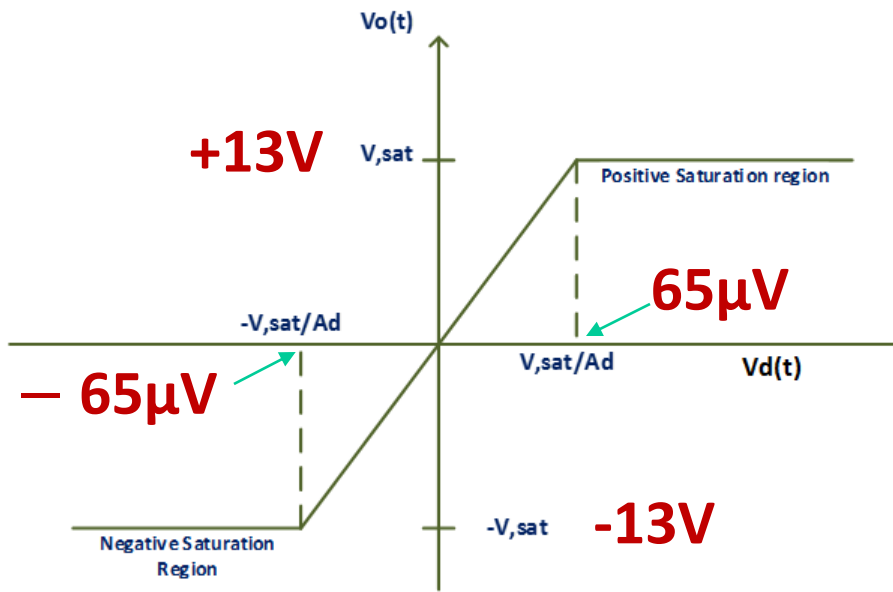

Let $\pm V_{cc} = \pm 15V$; $A_d = 200,000$


$$\therefore \pm V_{sat} = \pm 13V$$

\therefore If $V_d > 65\mu V$; $V_o = +13V$

\therefore If $V_d < -65\mu V$; $V_o = -13V$

Op-amp Model in the Linear Region:


If the Op-Amp is in the Linear Region:

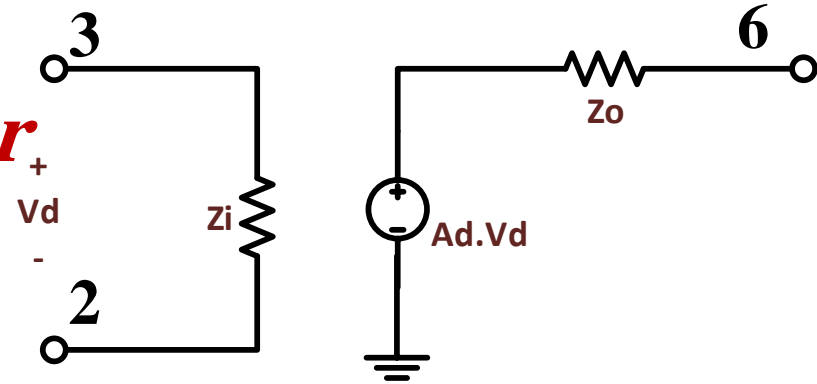

If the Op-Amp is IDEAL and in the Linear Region:

1) $V_d \cong 0 \Rightarrow V(+)=V(-)$

2) $i(+)=i(-)=0$

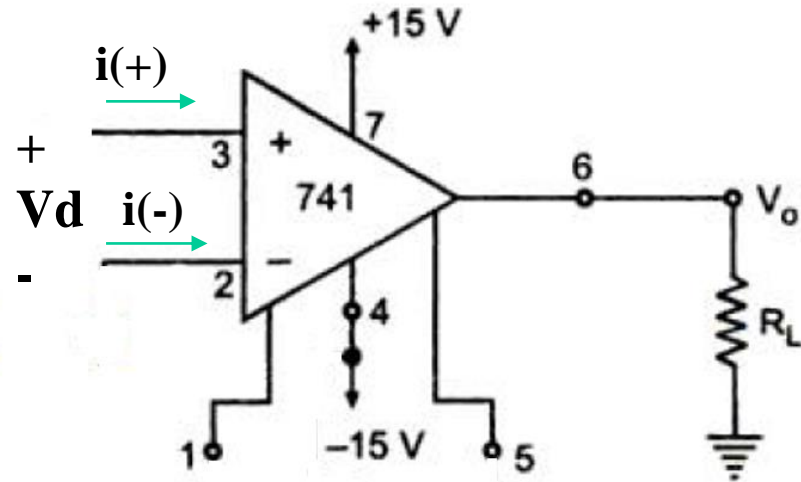

Op-amp Linear Applications:

1. Inverting Amplifier

Op-Amp is ideal


a) Since $V(+)=0$; $\therefore V(-)=0$

And $i_s = \frac{v_s}{R_i}$ (Virtual ground)

b) Since $i(-)=0$; $\therefore i_F = i_s$

c) $V_O = -R_F i_F$



$V_O = -R_F i_s$

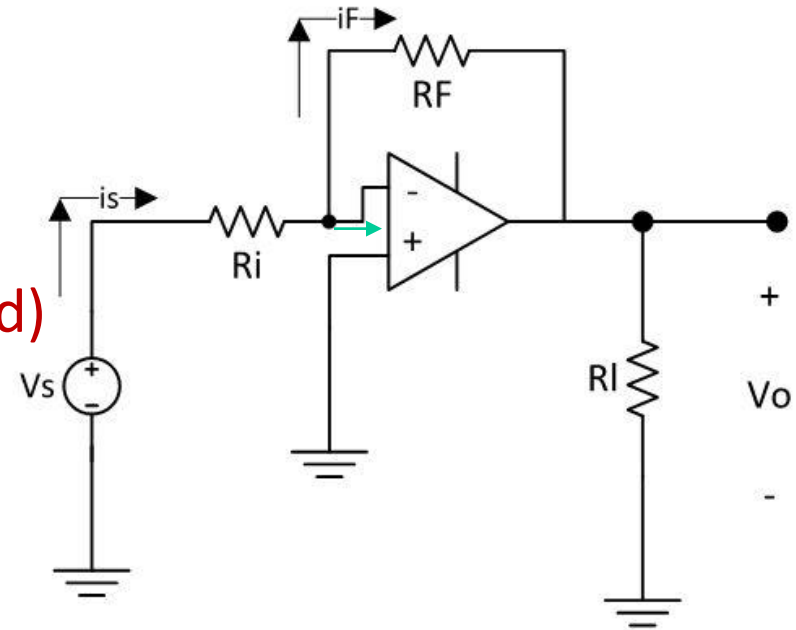



$$V_O = -\frac{R_F}{R_i} V_S$$

$$\therefore A_{CL} = -\frac{R_F}{R_i}$$

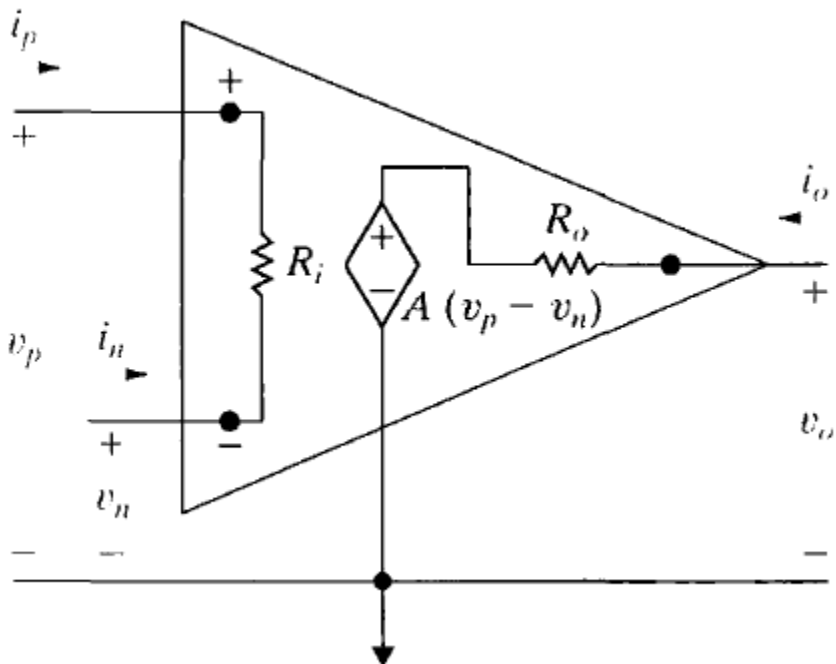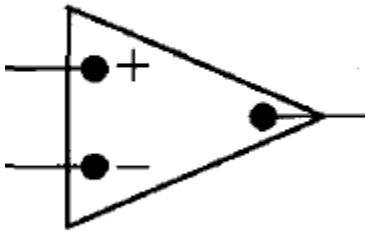
Analysis of an Inverting-Amplifier Circuit Using the More Realistic Op Amp Model



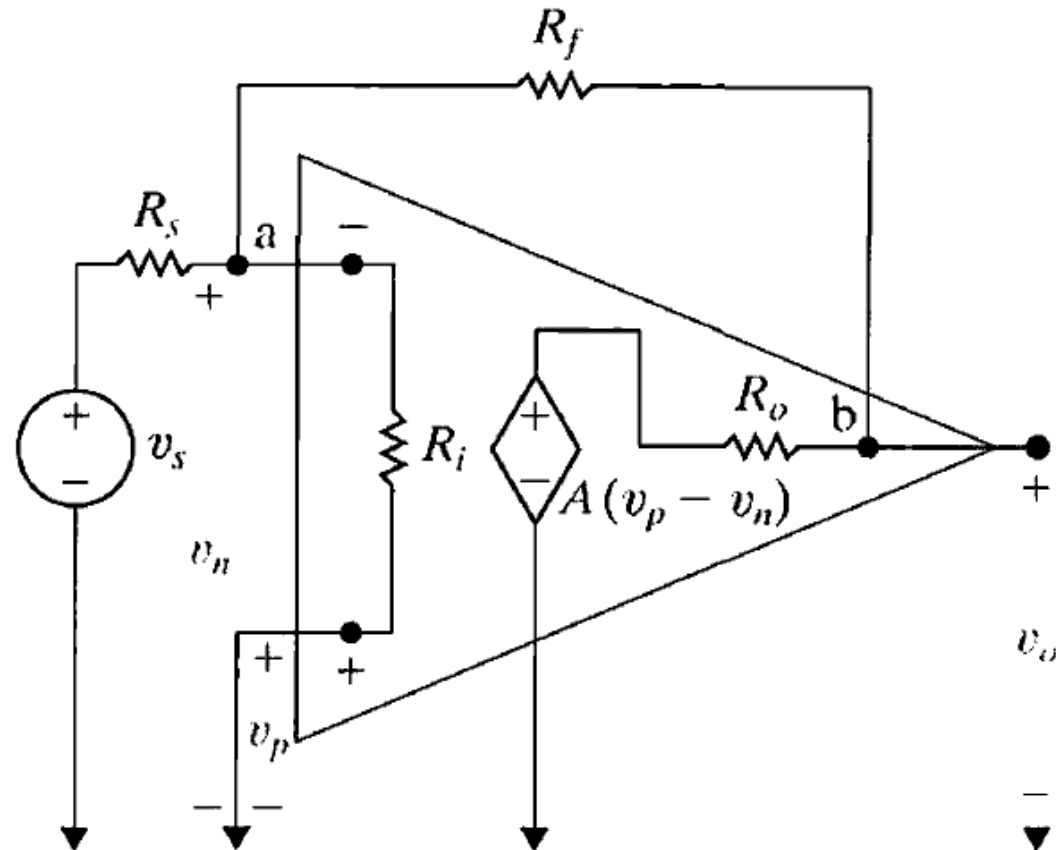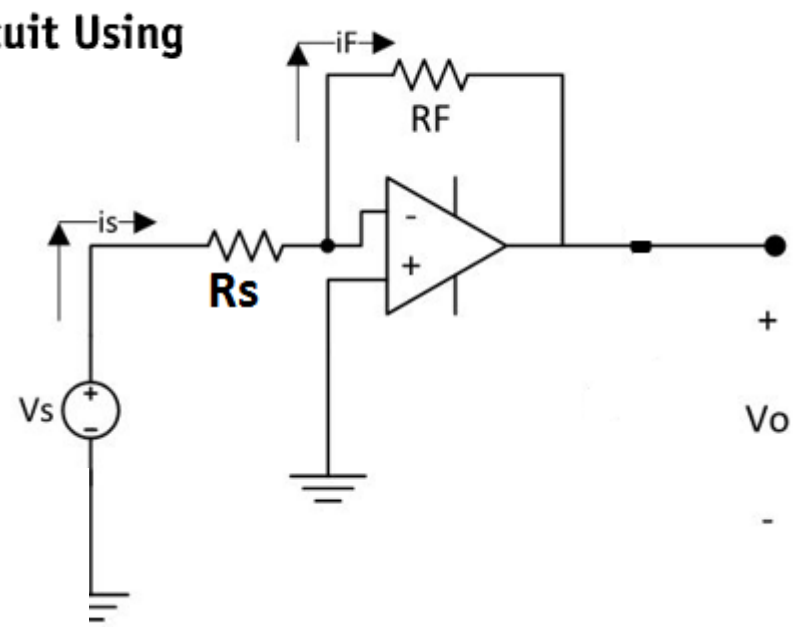Analysis of an Inverting-Amplifier Circuit Using the More Realistic Op Amp Model



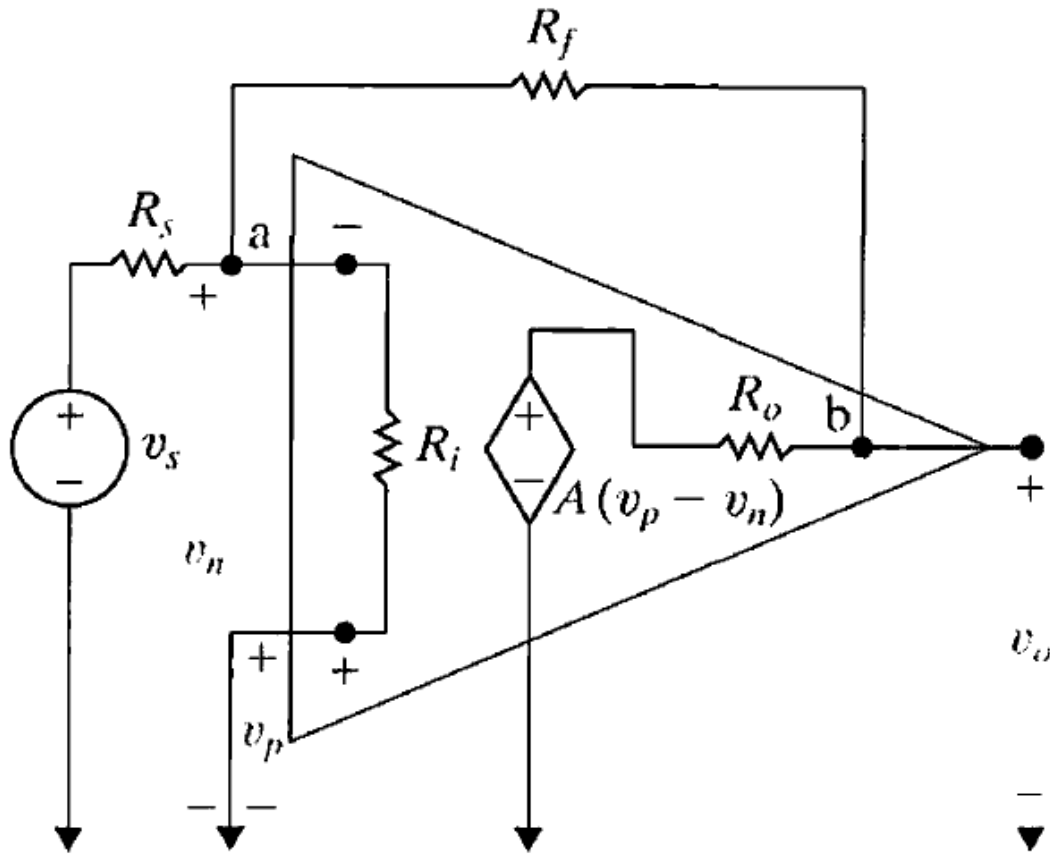Analysis of an Inverting-Amplifier Circuit Using the More Realistic Op Amp Model



$$\text{node a: } \frac{v_n - v_s}{R_s} + \frac{v_n}{R_i} + \frac{v_n - v_o}{R_f} = 0.$$

$$\text{node b: } \frac{v_o - v_n}{R_f} + \frac{v_o - A(-v_n)}{R_o} = 0.$$

$$\left(\frac{1}{R_s} + \frac{1}{R_i} + \frac{1}{R_f}\right)v_n - \frac{1}{R_f}v_o = \frac{1}{R_s}v_s$$


$$\left(\frac{A}{R_o} - \frac{1}{R_f}\right)v_n + \left(\frac{1}{R_f} + \frac{1}{R_o}\right)v_o = 0.$$

$$v_o = \frac{-A + (R_o/R_f)}{\frac{R_s}{R_f}\left(1 + A + \frac{R_o}{R_i}\right) + \left(\frac{R_s}{R_i} + 1\right) + \frac{R_o}{R_f}}v_s$$

$R_o \rightarrow 0$, $R_i \rightarrow \infty$, and $A \rightarrow \infty$

$$v_o = \frac{-R_f}{R_s}v_s$$

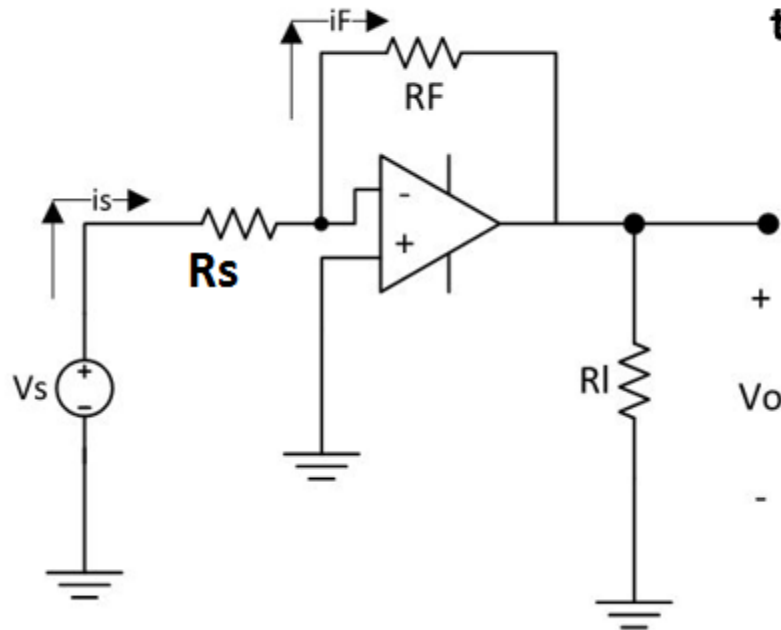Analysis of an Inverting-Amplifier Circuit Using the More Realistic Op Amp Model



$$v_o = \frac{-A + (R_o/R_f)}{\frac{R_s}{R_f} \left(1 + A + \frac{R_o}{R_i} + \frac{R_o}{R_L} \right) + \left(1 + \frac{R_o}{R_L} \right) \left(1 + \frac{R_s}{R_i} \right) + \frac{R_o}{R_f}} v_s$$

$$R_o \rightarrow 0, R_i \rightarrow \infty, \text{ and } A \rightarrow \infty$$

$$v_o = \frac{-R_f}{R_s} v_s$$

Op-Amp Linear Applications:


1. Inverting Amplifier

Design an inverting amplifier to provide $A_{CL} = -200$

Solution :

$$A_{CL} = -\frac{R_F}{R_i} = -200$$

$$\therefore \frac{R_F}{R_i} = 200$$

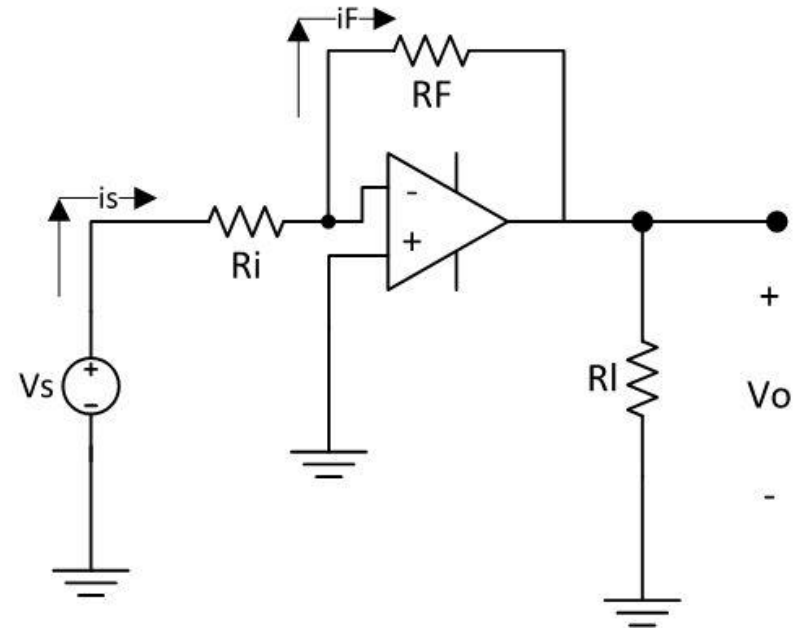


Let $R_i = 20K$

$$\therefore R_F = 4000K$$

Op-amp Linear Applications:

2. Inverting Adder

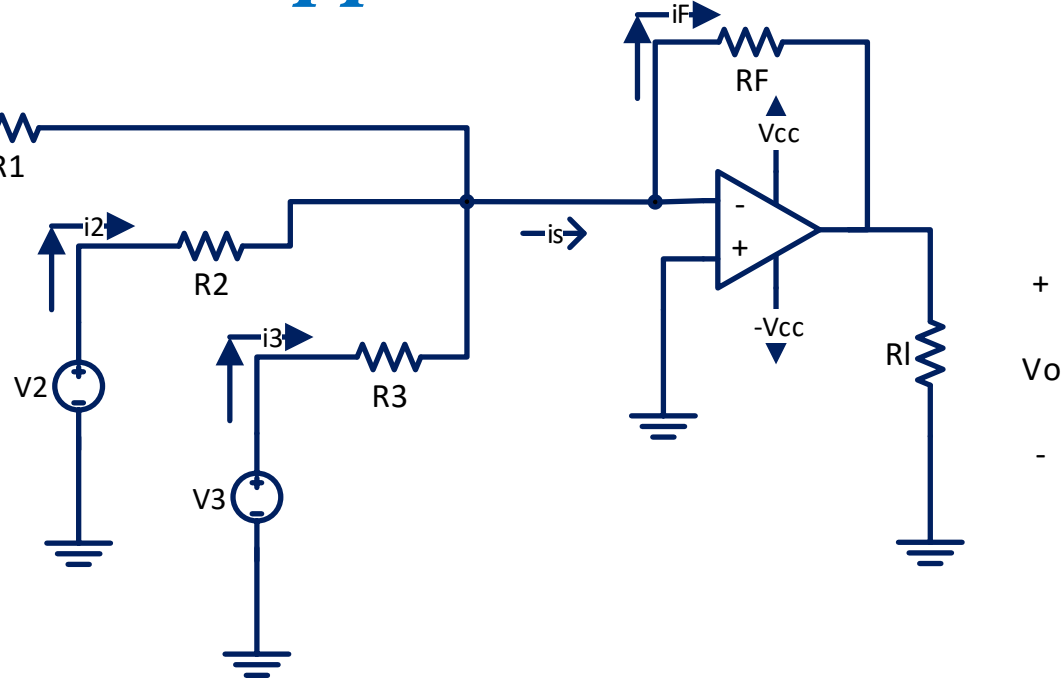

1- Since $V(+)=0$;

$\therefore V(-)=0$

$$i_1 = \frac{v_1}{R_1} ; \quad i_2 = \frac{v_2}{R_2} ;$$

$$i_3 = \frac{v_3}{R_3}$$

$$i_s = i_1 + i_2 + i_3$$

$$V_O = - \left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3 \right)$$

If $R_1 = R_2 = R_3 = R_F = R$


$$V_O = - (V_1 + V_2 + V_3)$$

2- Since $i(-)=0$; $\therefore i_F = i_s$

3- $V_O = -R_F i_F$

Op-amp Linear Applications:

2. Inverting Adder

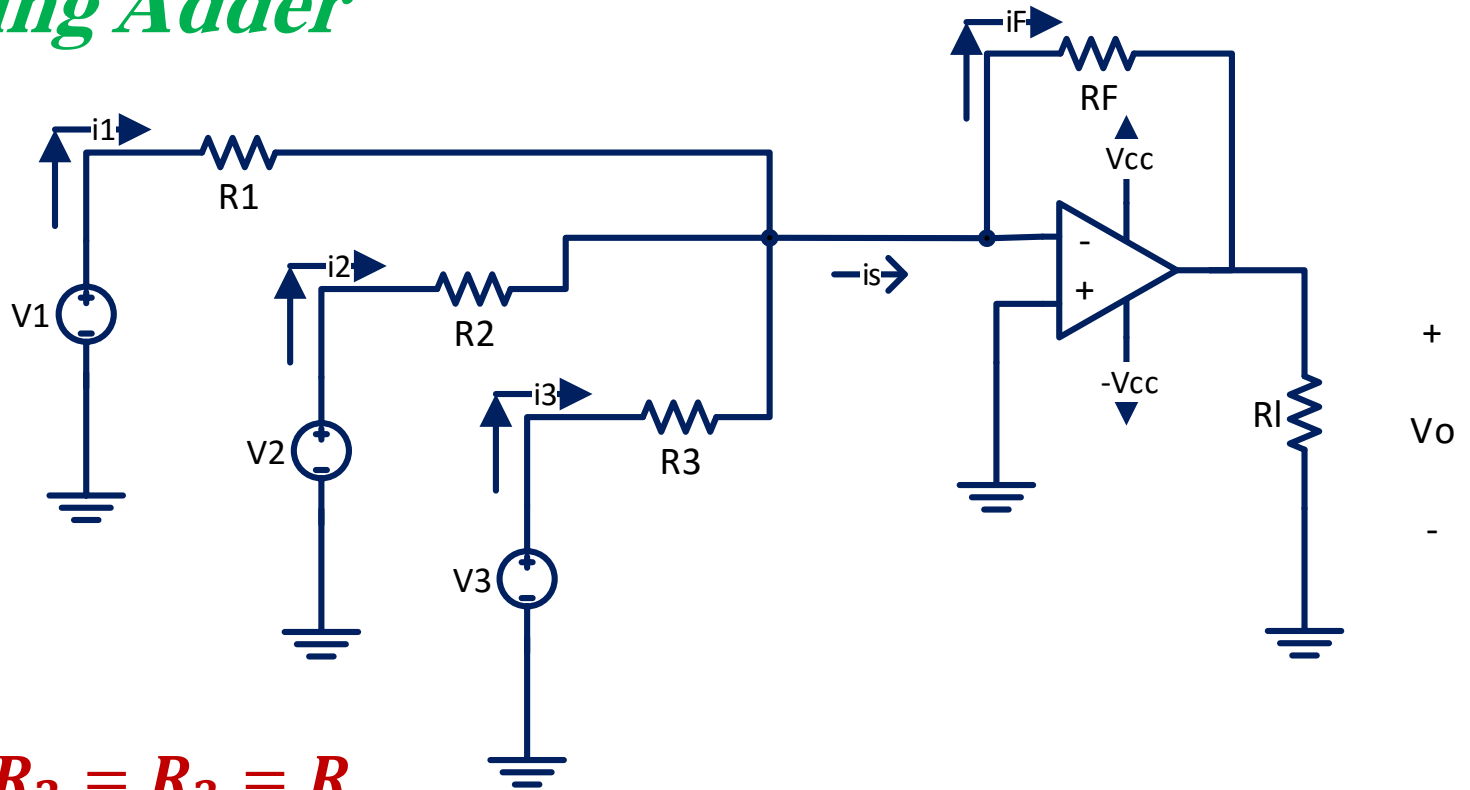

If $R_1 = R_2 = R_3 = R$

And $R_F = \frac{R}{n} = \frac{R}{3}$



average

$$\therefore V_O = -\left(\frac{V_1 + V_2 + V_3}{3}\right)$$

Op-amp Linear Applications:

3. Non Inverting Amplifier

1- Since $V(+)=V_s$


$\therefore V(-)=V_s$

$\therefore i_i = \frac{V_s}{R_i}$

2- Since $i(-) = 0$;

$\therefore i_F = i_i$

3 - $V_O = R_F i_F + R_i i_i$

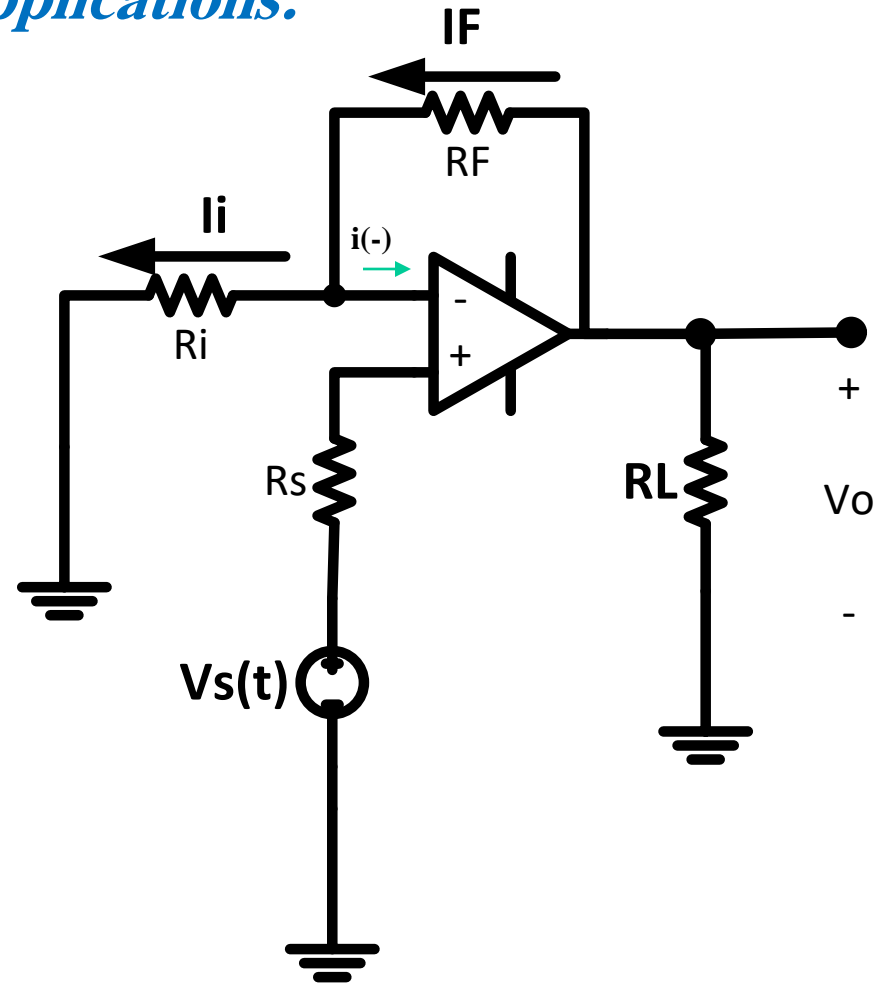

$\rightarrow V_O = \left(1 + \frac{R_F}{R_i}\right) V_s$

Op-amp Linear Applications:

Non Inverting Amplifier

Design a non inverting amplifier to provide $A_{CL} = 100$


Solution :

$$A_{CL} = 1 + \frac{R_F}{R_i} = 100$$



$$\therefore \frac{R_F}{R_i} = 99$$


$$\text{Let } R_i = 10\text{K}$$

$$\therefore R_F = 990\text{K}$$

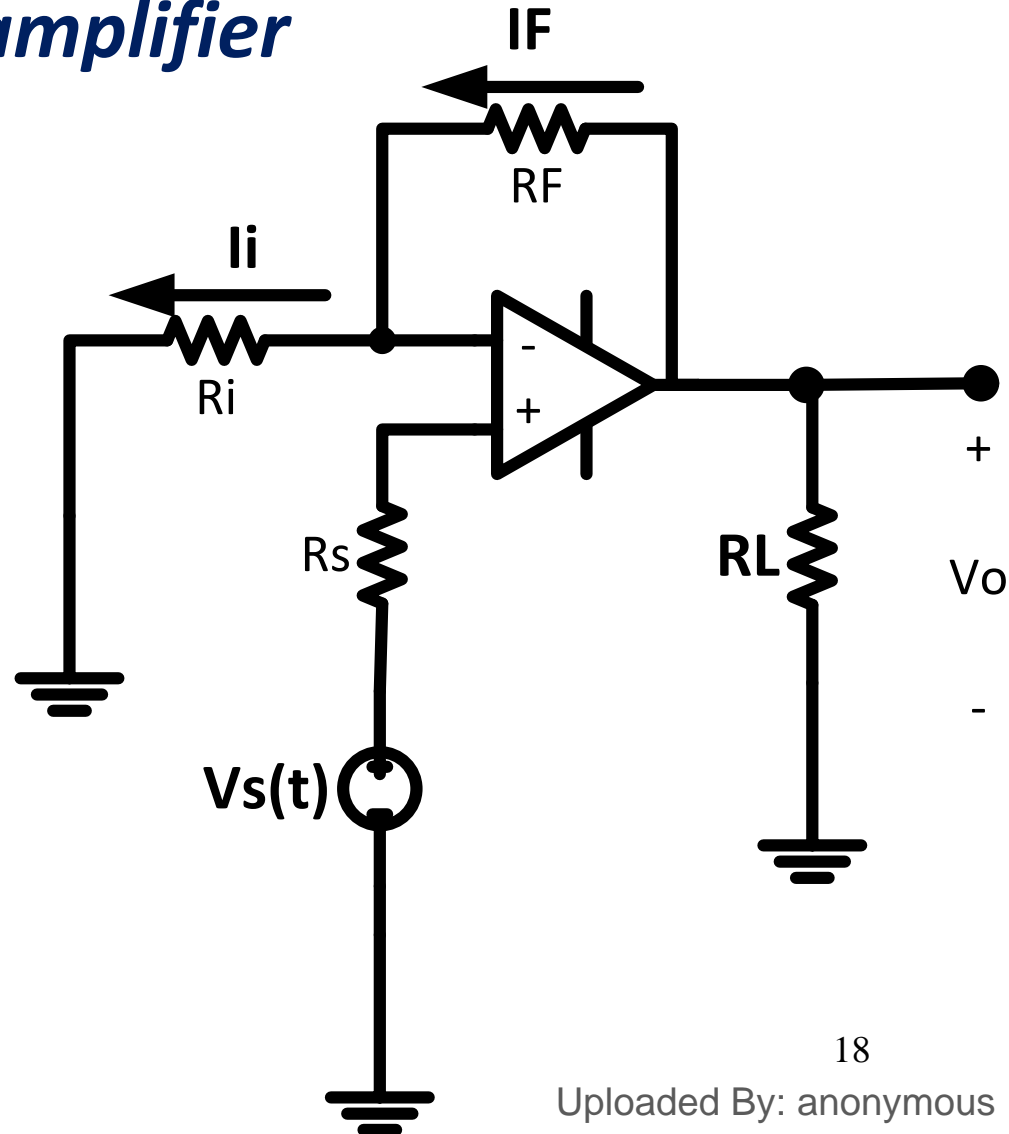

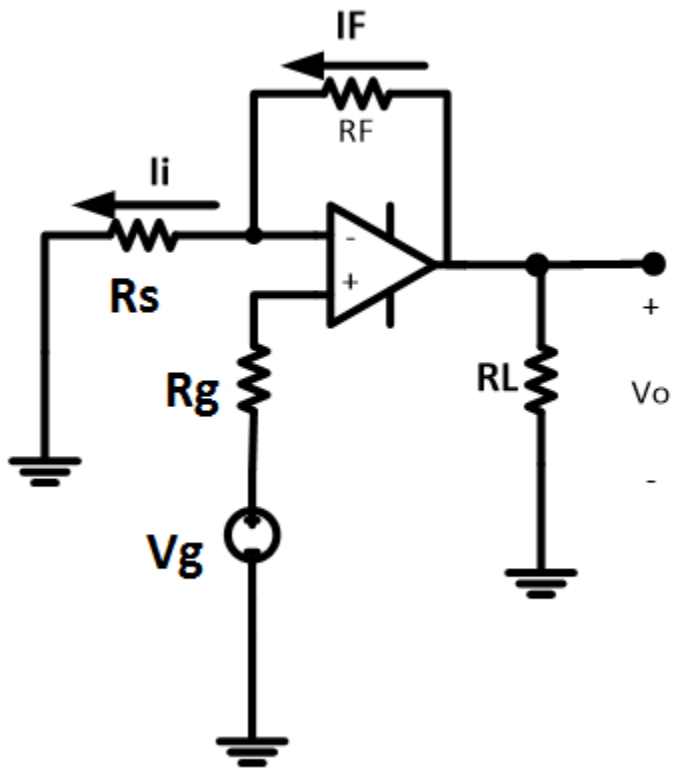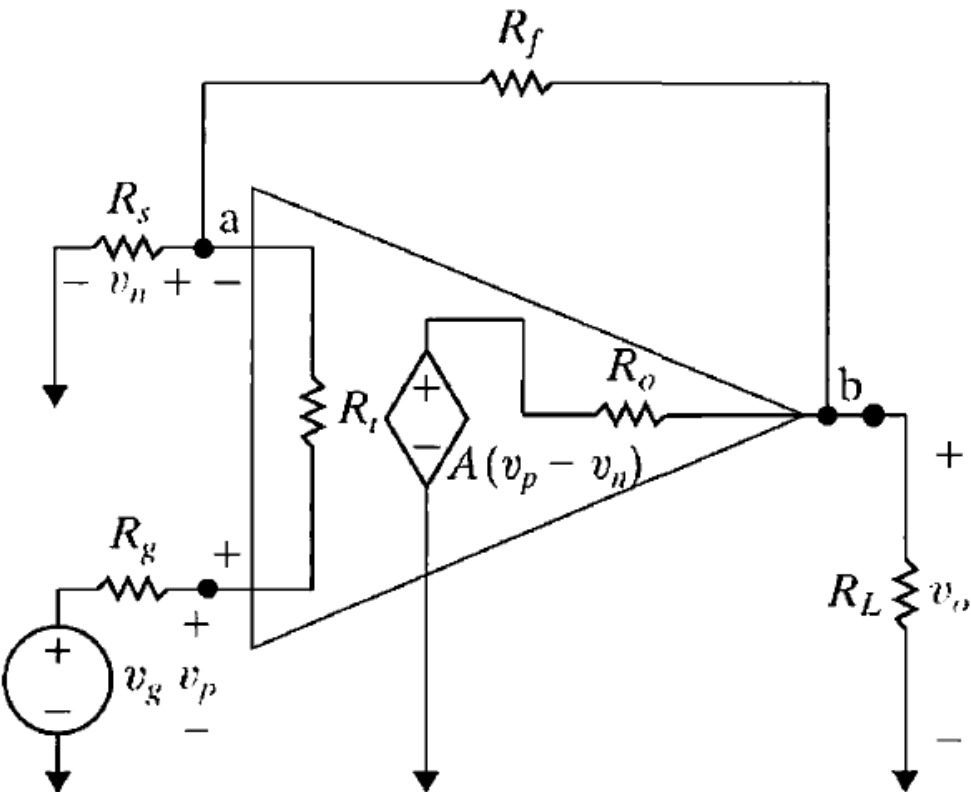Analysis of a Noninverting-Amplifier Circuit Using the More Realistic Op Amp Model



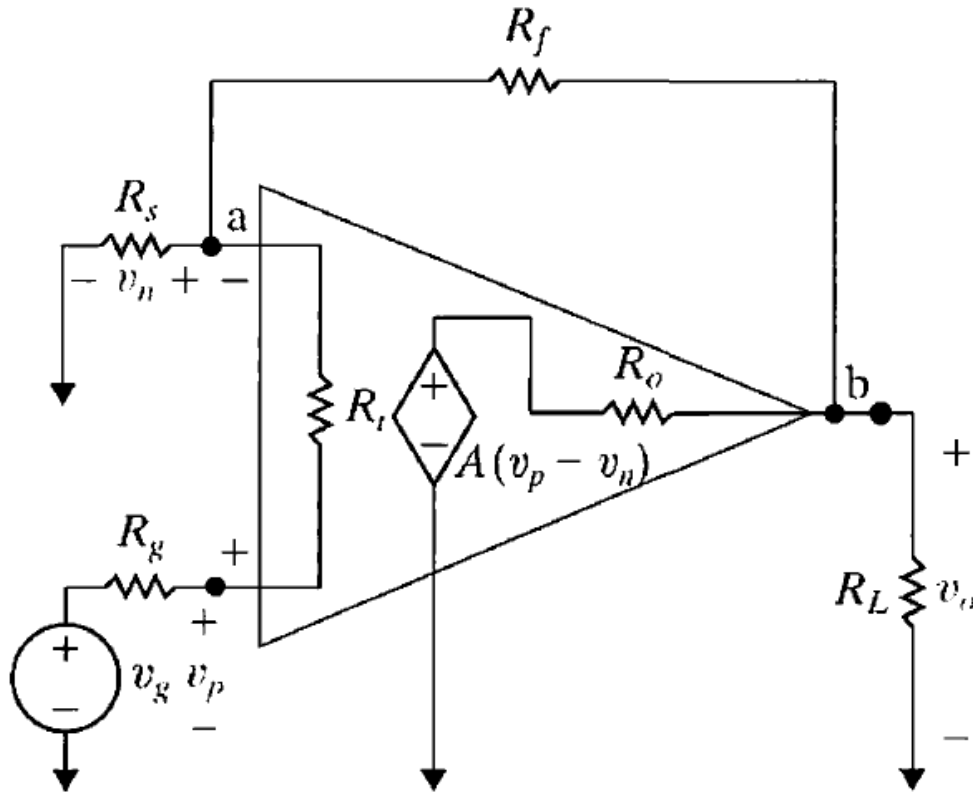

$$\frac{v_p - v_g}{R_g} = \frac{v_n - v_g}{R_i + R_g}$$

At node a

$$\frac{v_n}{R_s} + \frac{v_n - v_g}{R_g + R_i} + \frac{v_n - v_o}{R_f} = 0.$$

at node b

$$\frac{v_o - v_n}{R_f} + \frac{v_o}{R_L} + \frac{v_o - A(v_p - v_n)}{R_o} = 0$$

$$v_o = \frac{[(R_f + R_s) + (R_s R_o / A R_i)]v_g}{R_s + \frac{R_o}{A}(1 + K_r) + \frac{R_f R_s + (R_f + R_s)(R_i + R_g)}{A R_i}}$$

where

$$K_r = \frac{R_s + R_g}{R_i} + \frac{R_f + R_s}{R_L} + \frac{R_f R_s + R_f R_g + R_g R_s}{R_i R_L}$$

$R_o \rightarrow 0$, $R_i \rightarrow \infty$, and $A \rightarrow \infty$

$$v_o = \frac{R_s + R_f}{R_s} v_g$$

Op-amp Linear Applications:

4. Buffer, Unity Gain



1- Since $V(+)=V_s$; $\therefore V(-)=V_s$

2- $V_o = V(-) = V_s$

Buffer is a special Case of
non inverting amplifier for which:


$$R_i = \infty$$


$$R_F = 0$$

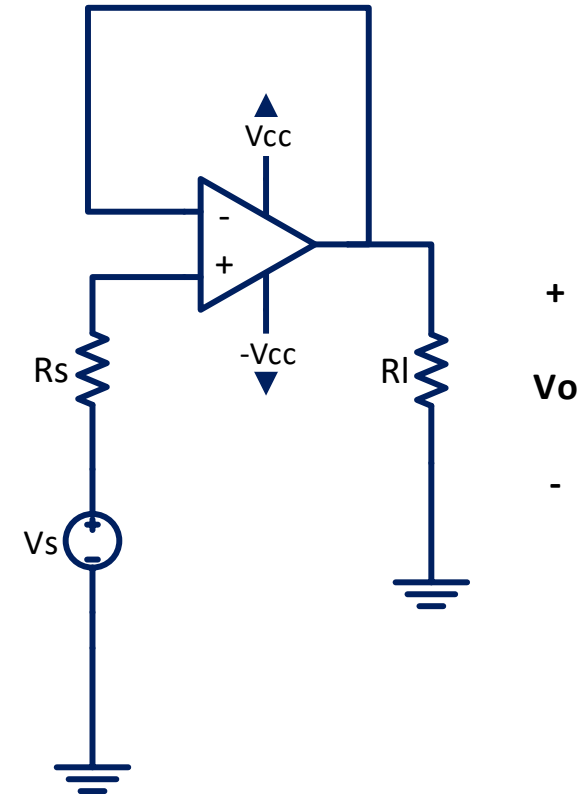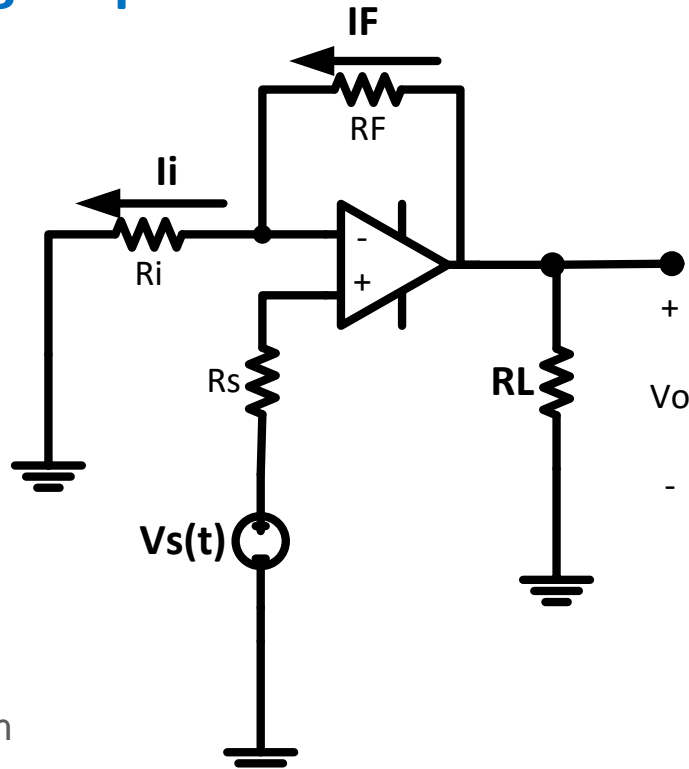

Op-amp Linear Applications:

5. Non-inverting Adder

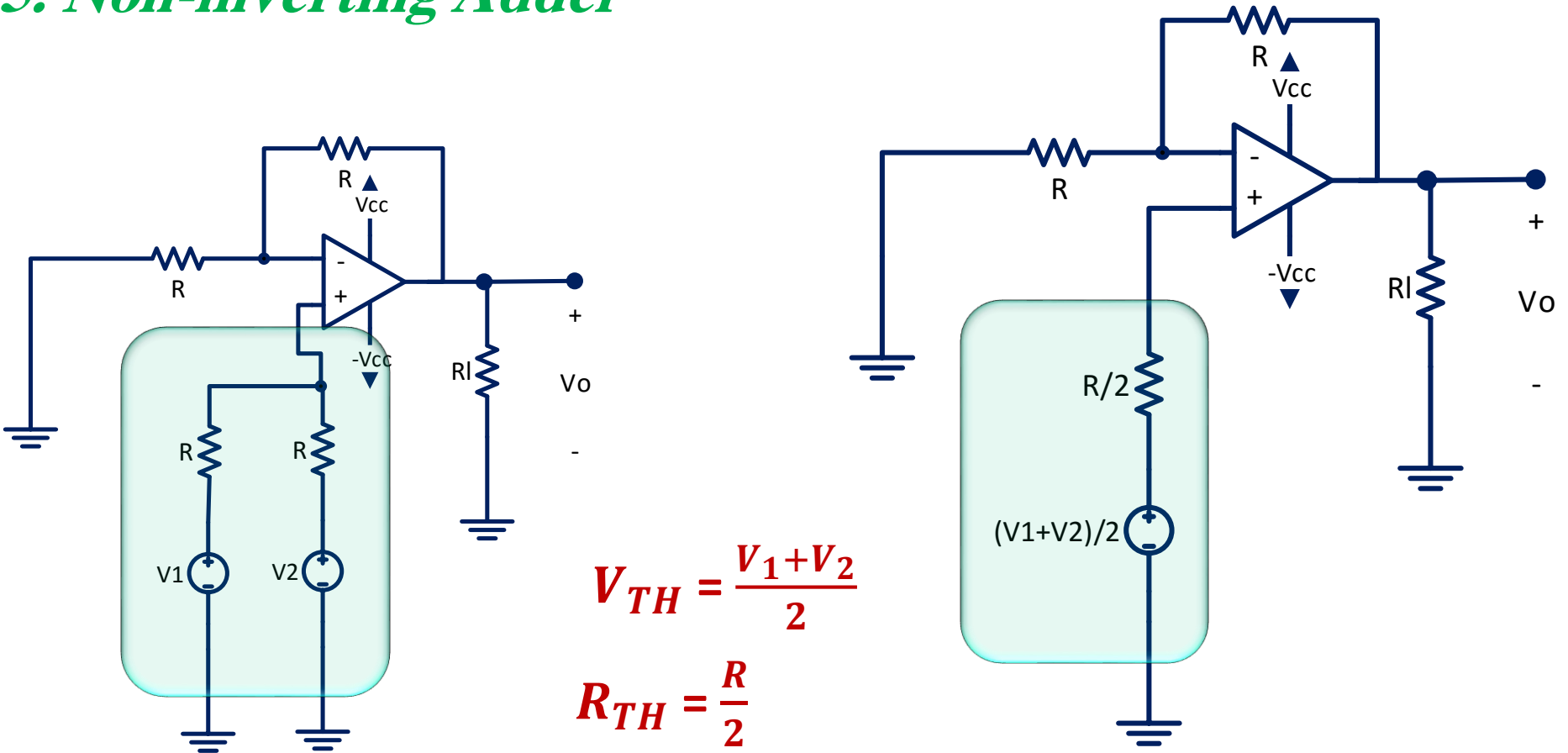

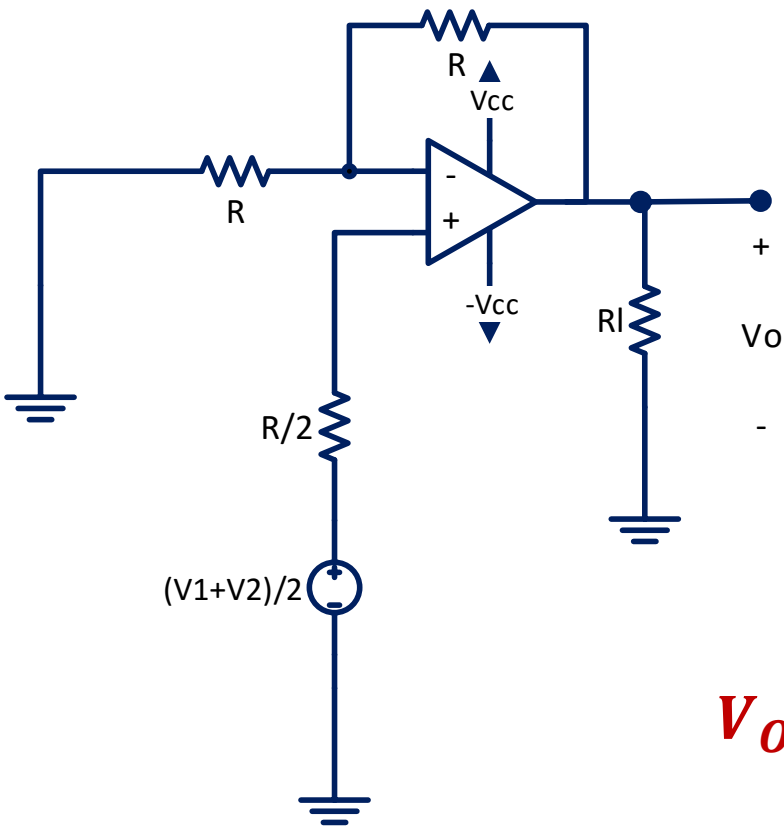

$$V_O = \left(1 + \frac{R}{R}\right) \left(\frac{V_1 + V_2}{2}\right) = V_1 + V_2$$

If we have n signal :

$$\text{let } R_F = (n-1)R$$

$$V_O = V_1 + V_2 + \dots + V_N$$

Op-amp Linear Applications:

6. Voltage Subtraction

Using superposition

a) Let $V_1 = 0$



$$\therefore V_{o1} = -\frac{R_4}{R_3} V_2 \quad (\text{Inverting amplifier})$$


b) Let $V_2 = 0$

$$\therefore V_{o2} = \left(1 + \frac{R_4}{R_3}\right) \left(\frac{R_2}{R_1 + R_2}\right) V_1$$

(non inverting amplifier)
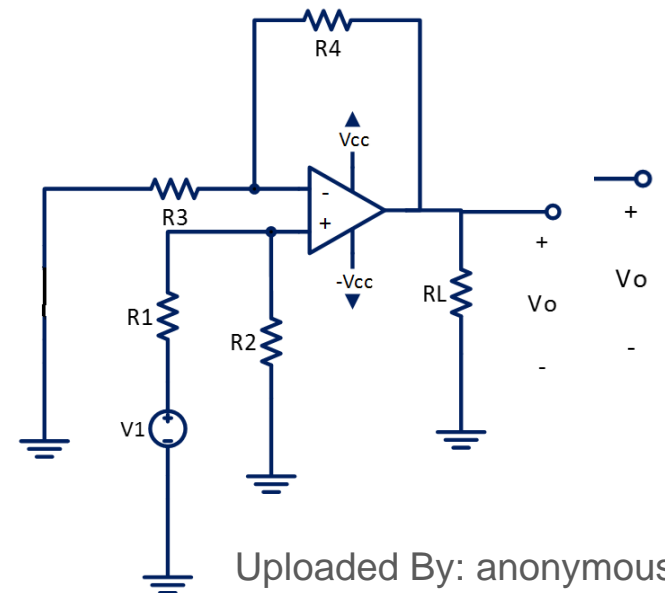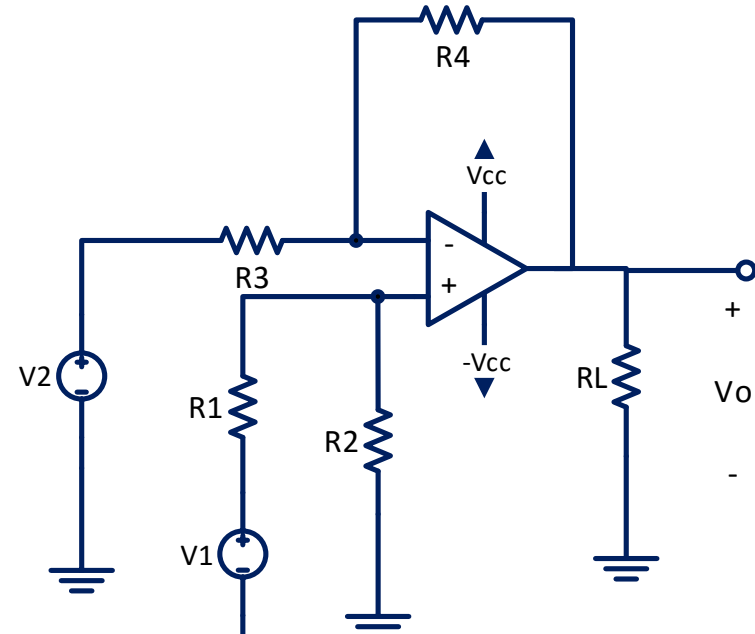
$$\therefore V_O = \left(1 + \frac{R_4}{R_3}\right) \left(\frac{R_2}{R_1 + R_2}\right) V_1 - \frac{R_4}{R_3} V_2$$



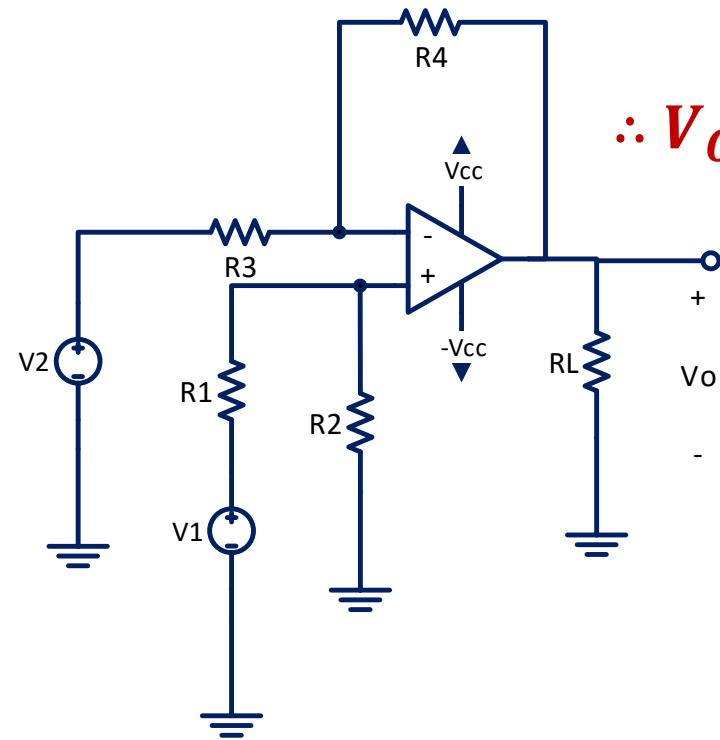

$$\therefore V_O = \left(1 + \frac{R_4}{R_3}\right) \left(\frac{R_2}{R_1 + R_2}\right) V_1 - \frac{R_4}{R_3} V_2$$

$$V_O = aV_1 - bV_2$$

If $R_1 = R_3 = R$
and $R_2 = R_4 = mR$

$$V_O = m(V_1 - V_2)$$

Basic Difference Amplifier

Op-amp Linear Applications:

Basic Difference Amplifier


$$V_O = m(V_1 - V_2)$$


$$Z_{i1} = R + mR$$

$$Z_{i2} = R$$


***It has low input impedance**

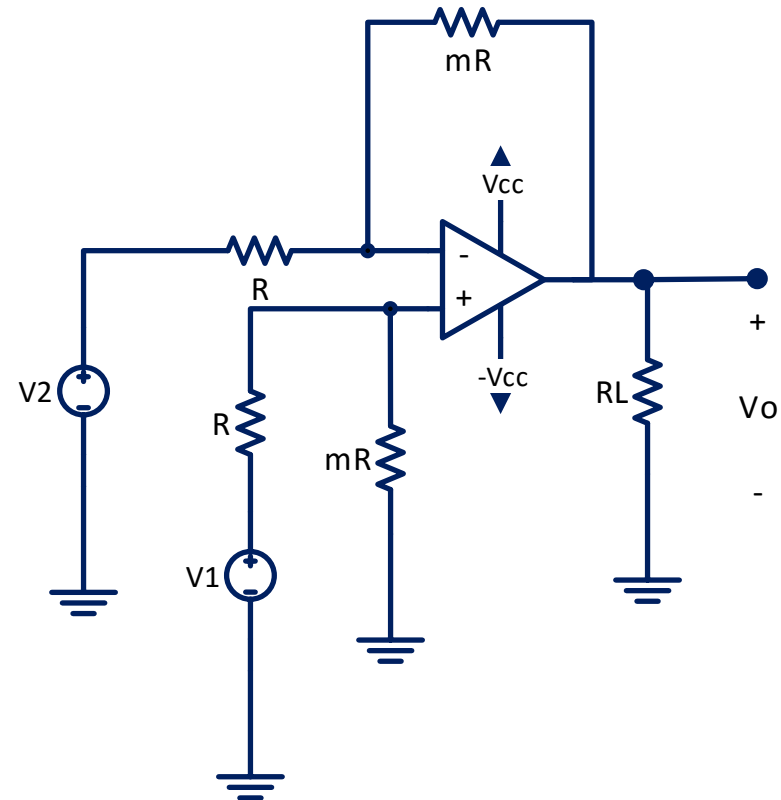***To Change the gain, we must change two resistors.**



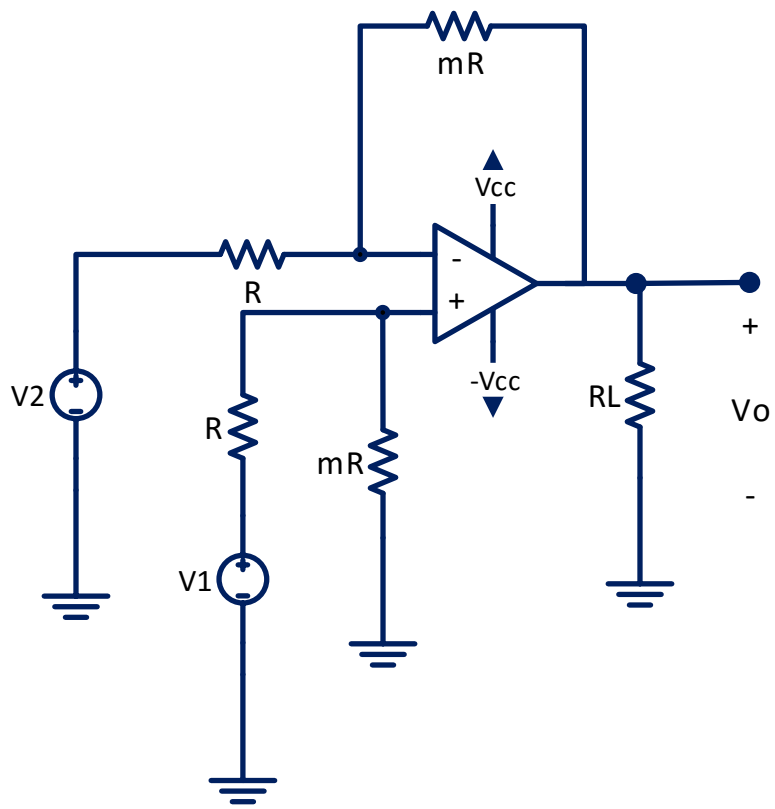

$$V_o = m(V_1 - V_2)$$

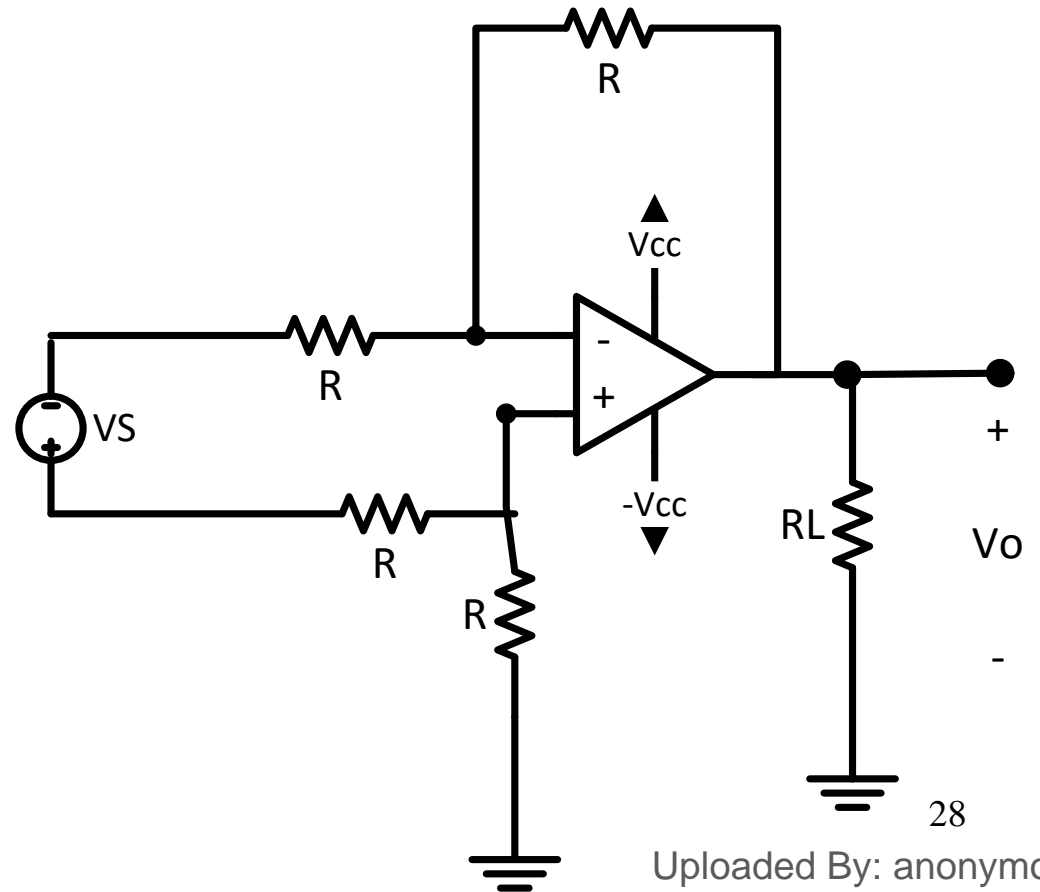

prove that $V_o = V_s$

$m = 1$

Instrumentation Amplifier:

$$I = \frac{V_1 - V_2}{aR}$$

$$V_{o1} = (R + aR + R)I$$

$$V_{o1} = \left(1 + \frac{2}{a}\right) (V_1 - V_2)$$


$$V_o = V_{o1} = \left(1 + \frac{2}{a}\right) (V_1 - V_2)$$

$$Z_{i1} = \infty$$

$$Z_{i2} = \infty$$

To change the gain \rightarrow
change a

$$a \ll 1$$

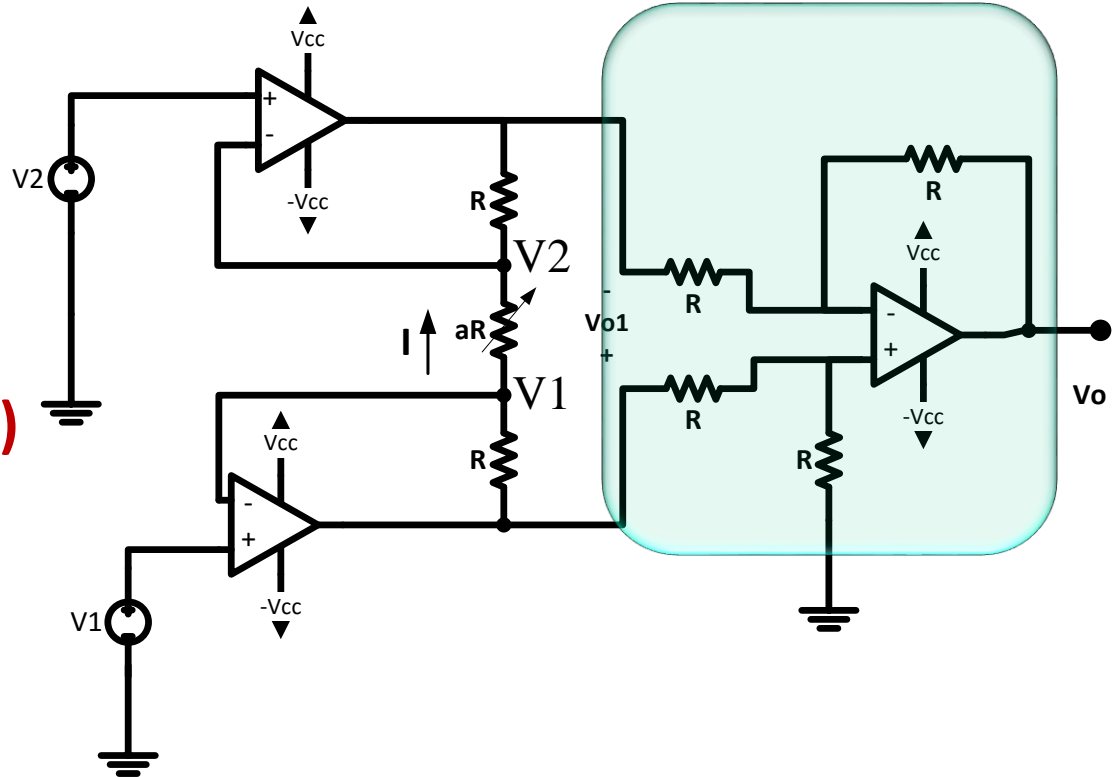

Measuring small resistance change

$$E_1 = \frac{R_1}{R_1 + R_1} E = \frac{E}{2}$$

$$E_2 = \frac{R}{R + R + \Delta R} E = \frac{R}{2R + \Delta R} E$$

$$V_o = \left(1 + \frac{2}{a}\right) (E_1 - E_2).$$

$$E_1 - E_2 = \frac{E}{2} \left(\frac{\Delta R}{2R + \Delta R}\right)$$

ΔR is very small


$$E_1 - E_2 = \frac{E \Delta R}{2 \cdot 2R}$$

$$V_o = \left(1 + \frac{2}{a}\right) (E_1 - E_2).$$

$$\text{Let } \left(1 + \frac{2}{a}\right) = 400$$

$$V_o = (400) \left(\frac{\Delta R}{4R}\right) E$$
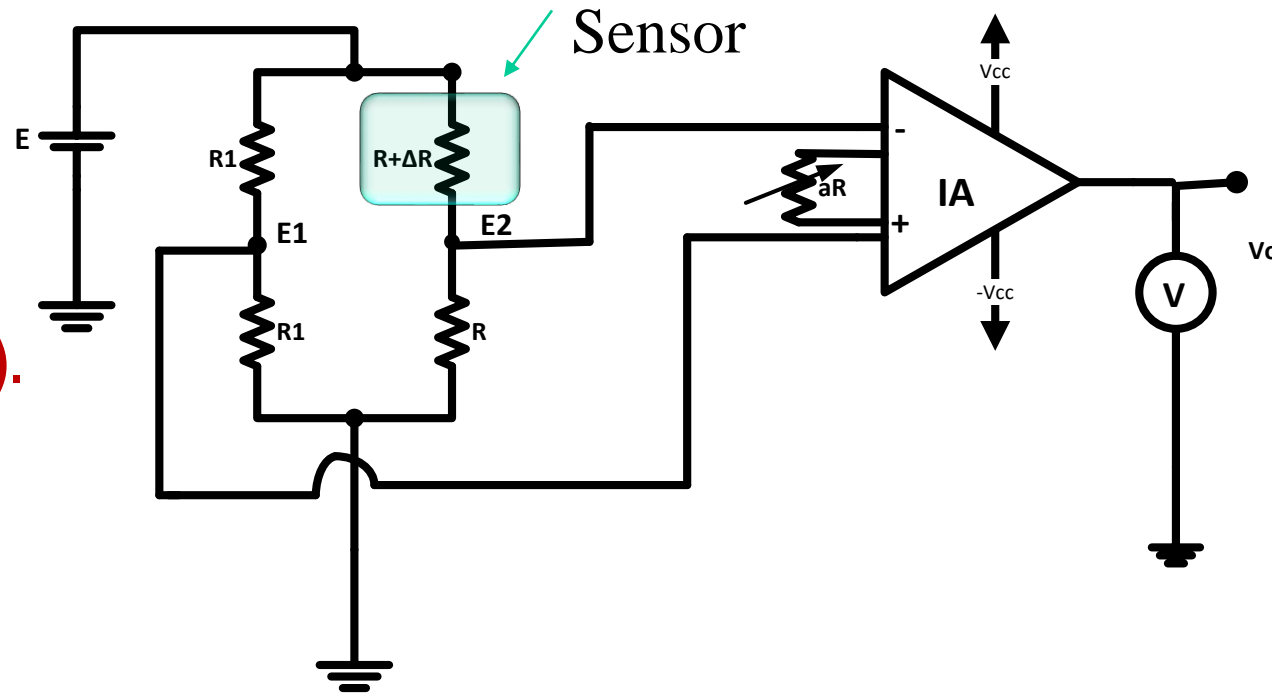
$$V_o = 100 E \left(\frac{\Delta R}{R}\right)$$



Measuring small resistance change

$$V_o = 100 E \left(\frac{\Delta R}{R} \right)$$

If $R = 10K$

$\Delta R = 0.1K$


$E = 1V$

$\frac{\Delta R}{R} = 1\%$ change

$V_o = 1V$

$\therefore 1V$ per 1%

change in resistance

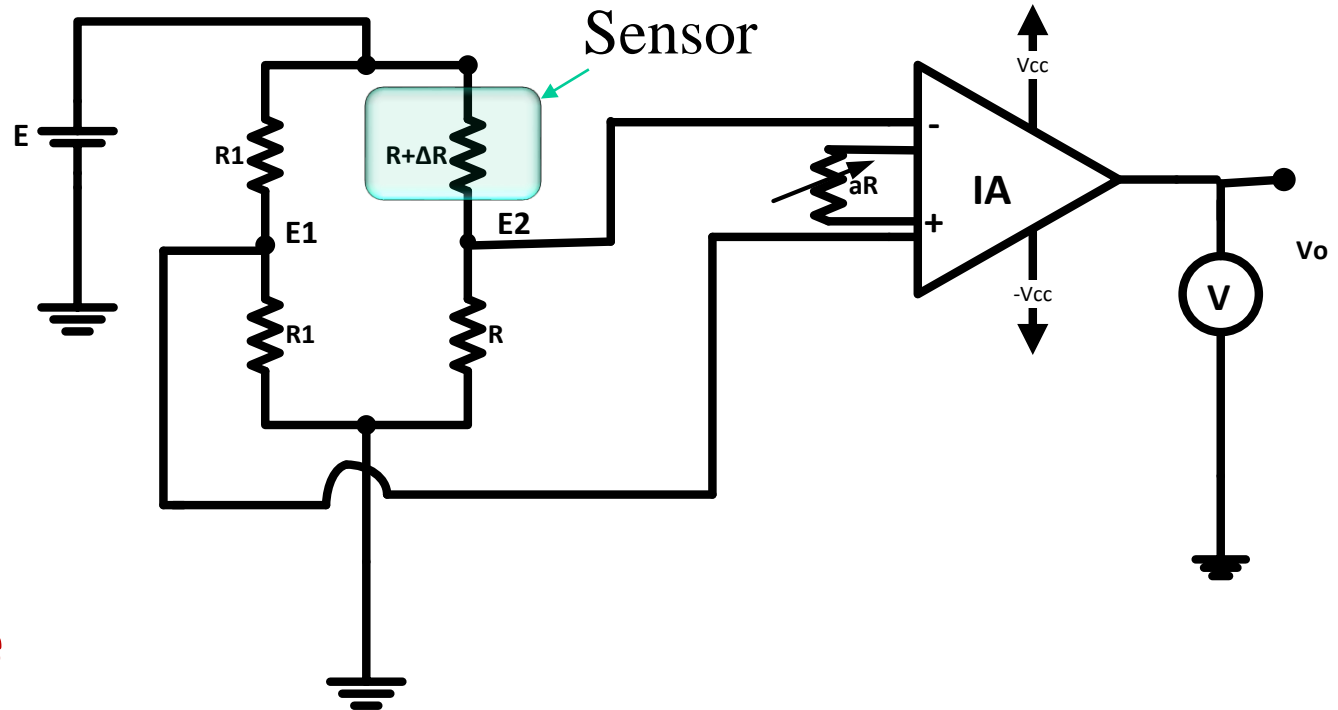


If $V_o = 2V$ \Rightarrow $\Delta R = 0.2K$

If $V_o = 0.1V$ \Rightarrow $\Delta R = 0.01K$

If $V_o = 0.01V$ \Rightarrow $\Delta R = 0.001K$

If $V_o = 1mV$ \Rightarrow $\Delta R = 0.0001K$

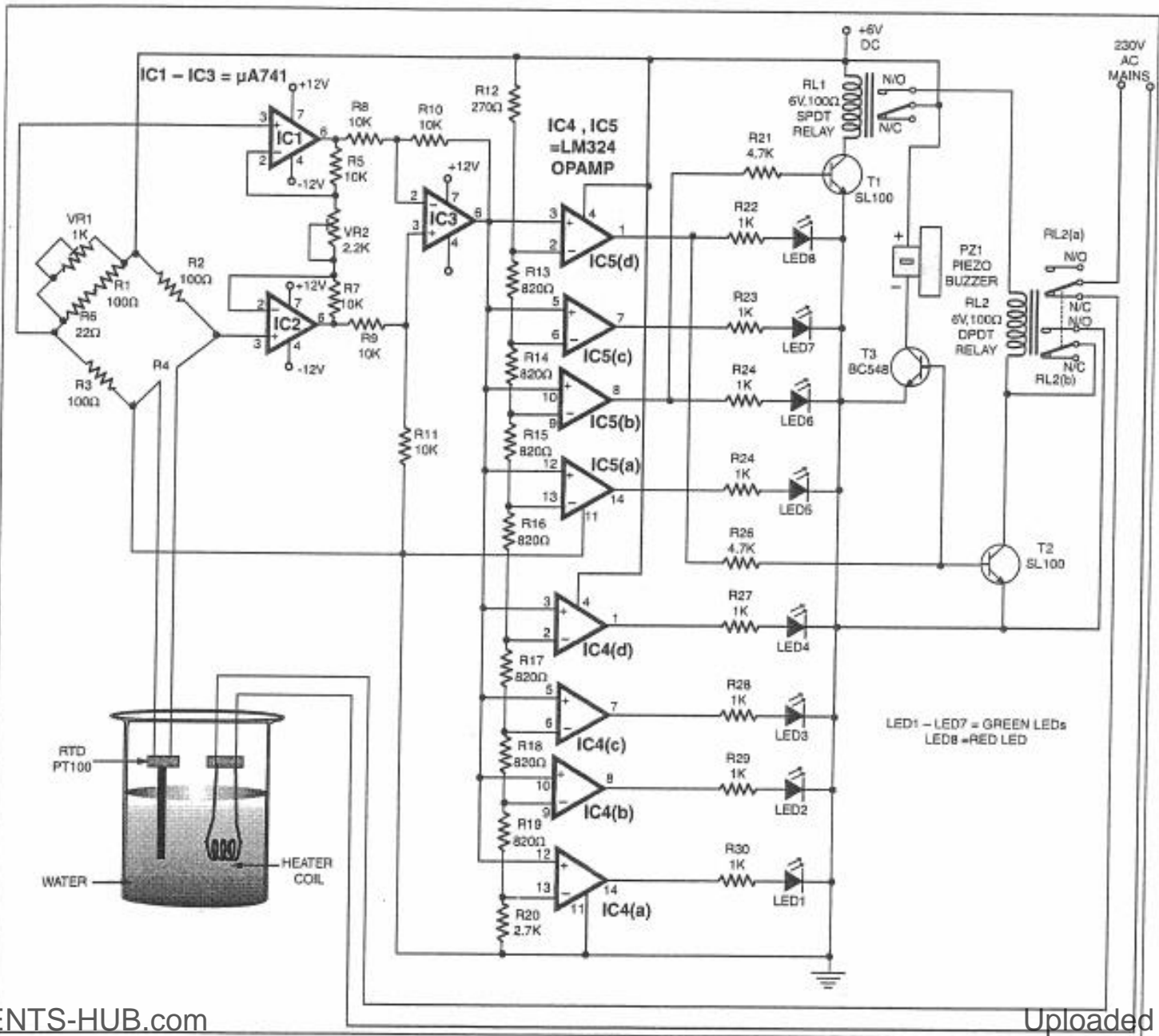ENEE3304 Project#1 :Water Temperature Controller




°C	Ohms	°C	Ohms	°C	Ohms	°C	Ohms
-11	95.69	51	119.78	114	143.80	177	167.35
-10	96.09	52	120.16	115	144.17	178	167.72
-9	96.48	53	120.55	116	144.55	179	168.09
-8	96.87	54	120.93	117	144.93	180	168.46
-7	97.26	55	121.32	118	145.31	181	168.83
-6	97.65	56	121.70	119	145.68	182	169.20
-5	98.04	57	122.09	120	146.06	183	169.57
-4	98.44	58	122.47	121	146.44	184	169.94
-3	98.83	59	122.86	122	146.81	185	170.31
-2	99.22	60	123.24	123	147.19	186	170.68
-1	99.61	61	123.62	124	147.57	187	171.05
0	100.00	62	124.01	125	147.94	188	171.42
1	100.39	63	124.39	126	148.32	189	171.79
2	100.78	64	124.77	127	148.70	190	172.16
3	101.17	65	125.16	128	149.07	191	172.53
4	101.56	66	125.54	129	149.45	192	172.90
5	101.95	67	125.92	130	149.82	193	173.26
6	102.34	68	126.31	131	150.20	194	173.63
7	102.73	69	126.69	132	150.57	195	174.00
8	103.12	70	127.07	133	150.95	196	174.37
9	103.51	71	127.45	134	151.33	197	174.74
10	103.90	72	127.84	135	151.70	198	175.10
11	104.29	73	128.22	136	152.08	199	175.47
12	104.68	74	128.60	137	152.45	200	175.84
13	105.07	75	128.98	138	152.83	201	176.21
14	105.46	76	129.37	139	153.20	202	176.57
15	105.85	77	129.75	140	153.58	203	176.94
16	106.24	78	130.13	141	153.95	204	177.31
17	106.63	79	130.51	142	154.32	205	177.68
18	107.02	80	130.89	143	154.70	206	178.04
19	107.40	81	131.27	144	155.07	207	178.41
20	107.79	82	131.66	145	155.45	208	178.78
21	108.18	83	132.04	146	155.82	209	179.14
22	108.57	84	132.42	147	156.19	210	179.51
23	108.96	85	132.80	148	156.57	211	179.88
24	109.35	86	133.18	149	156.94	212	180.24
25	109.73	87	133.56	150	157.31	213	180.61
26	110.12	88	133.94	151	157.69	214	180.97
27	110.51	89	134.32	152	158.06	215	181.34
28	110.90	90	134.70	153	158.43	216	181.71
29	111.28	91	135.08	154	158.81	217	182.07
30	111.67	92	135.46	155	159.18	218	182.44
31	112.06	93	135.84	156	159.55	219	182.80
32	112.45	94	136.22	157	159.93	220	183.17
33	112.83	95	136.60	158	160.30	221	183.53
34	113.22	96	136.98	159	160.67	222	183.90
35	113.61	97	137.36	160	161.04	223	184.26
36	113.99	98	137.74	161	161.42	224	184.63
37	114.38	99	138.12	162	161.79	225	184.99
38	114.77	100	138.50	163	162.16	226	185.36
39	115.15	101	138.88	164	162.53	227	185.72
40	115.54	102	139.26	165	162.90	228	186.09
41	115.93	103	139.64	166	163.27	229	186.45
42	116.31	104	140.02	167	163.65	230	186.82
43	116.70	105	140.39	168	164.02	231	187.18
		106	140.77	169	164.39		

To detect the temperature of water, commonly used resistance-temperature detector (RTD) PT100 is used. It is connected to one of the arms of a Wheatstone bridge as shown in the figure. RTD PT100 has a resistance of 100 ohms

Before using this circuit, the following adjustments have to be made. First, immerse the RTD in ice water (0°C) and adjust preset VR1 such that the bridge becomes balanced and the output of IC3 becomes 0V. Next, immerse the RTD in boiling water and slightly adjust preset VR2 such that the output of IC3 becomes 6V.


Water Temperature Controller

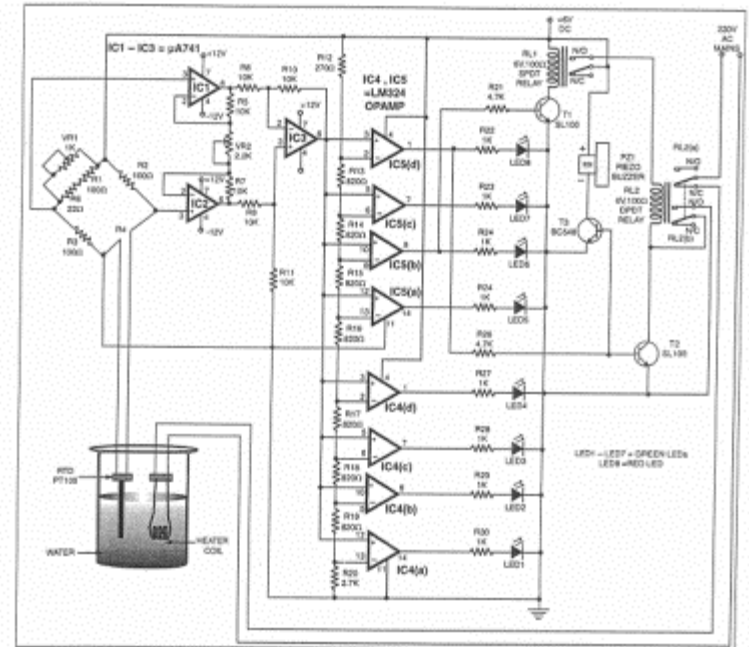

Basic Bridge Amplifier

Prove that
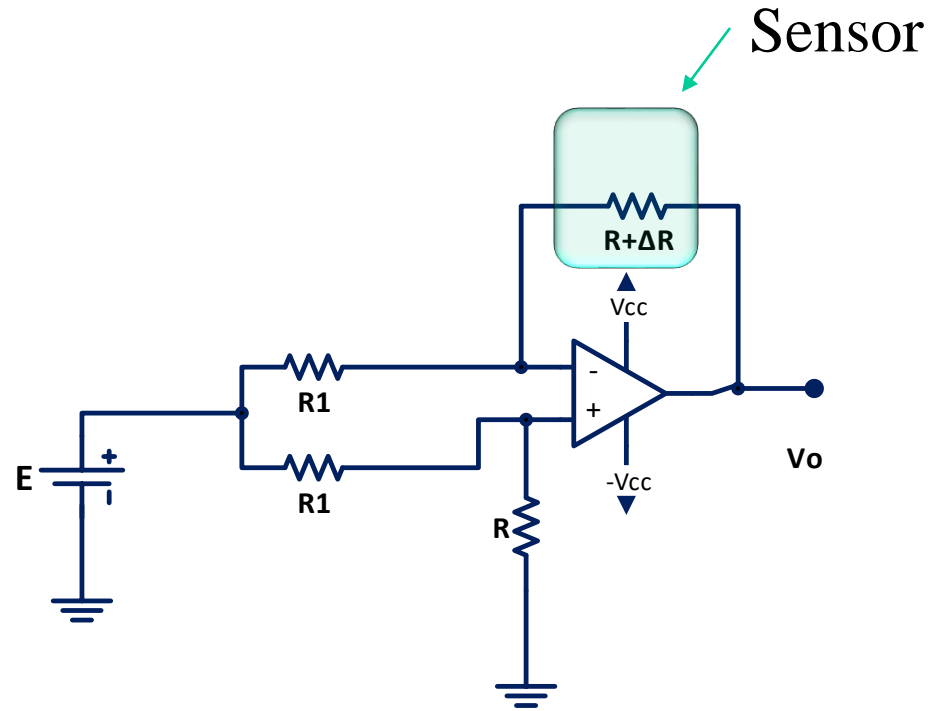
$$V_o = -E \left(\frac{\Delta R}{R_1 + R} \right)$$



This is a sensor(thermistor)

Electronic Thermometer


$$V_o = - E \left(\frac{\Delta R}{R_1 + R} \right)$$

$$E = -15v$$

$$R_1 = 10K$$

$$R = 5K$$


$$V_o = \Delta R$$

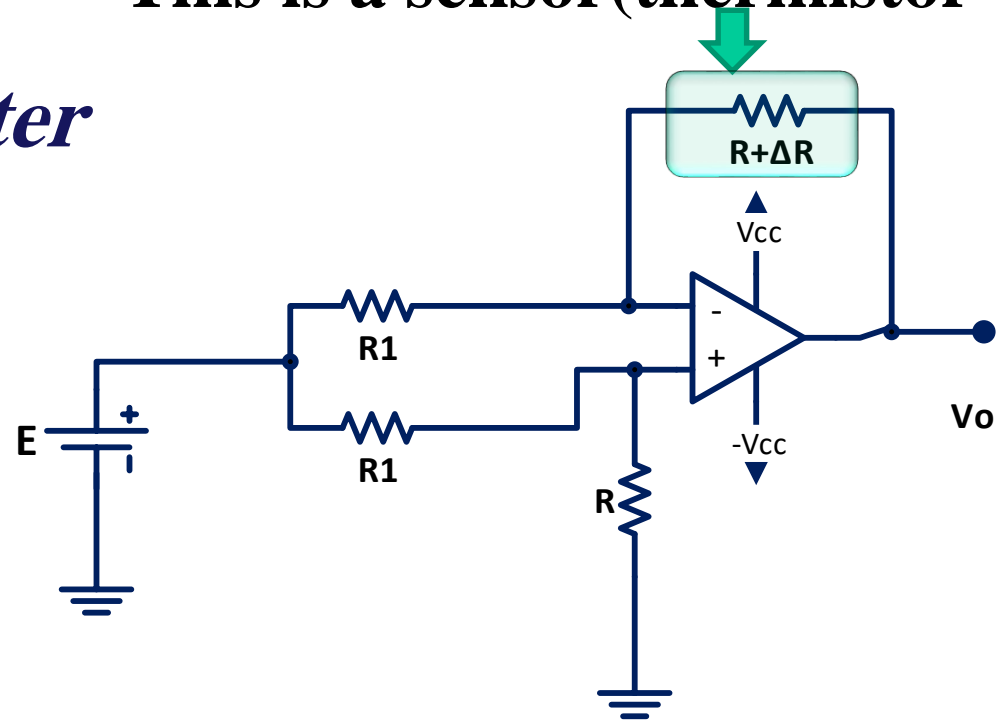


Place the circuit in the reference temperature
(T=100F) and measure the total resistance of the
thermistor(R=5k)

Electronic Thermometer

Voltmeter

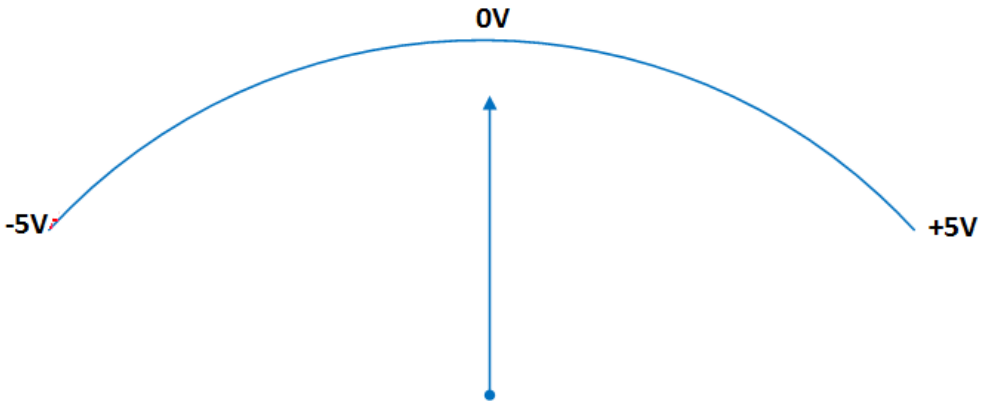

<u>Temp</u>	<u>RT</u>	ΔR	<u>Vo</u>
<u>0</u>	<u>10k</u>	<u>5k</u>	<u>5V</u>
<u>50</u>	<u>7.5k</u>	<u>2.5k</u>	<u>2.5V</u>
<u>100</u>	<u>5k</u>	<u>0k</u>	<u>0V</u>
<u>150</u>	<u>2.5k</u>	<u>-2.5k</u>	<u>-2.5V</u>
<u>200</u>	<u>0k</u>	<u>-5k</u>	<u>-5V</u>

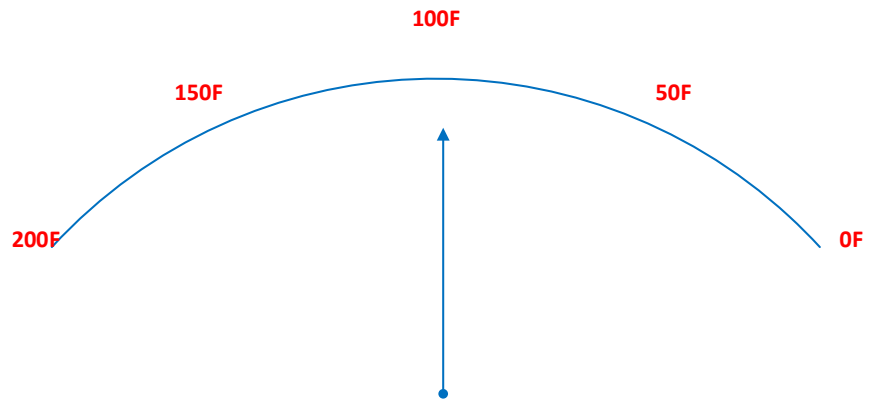

Voltage to current Converter


a) Floating load

Since $V(+)=V_i$

$$\therefore V(-)=V_i$$

$$I_i = \frac{V_i}{R_i}$$

$$I_L = I_i = \frac{V_i}{R_i}$$

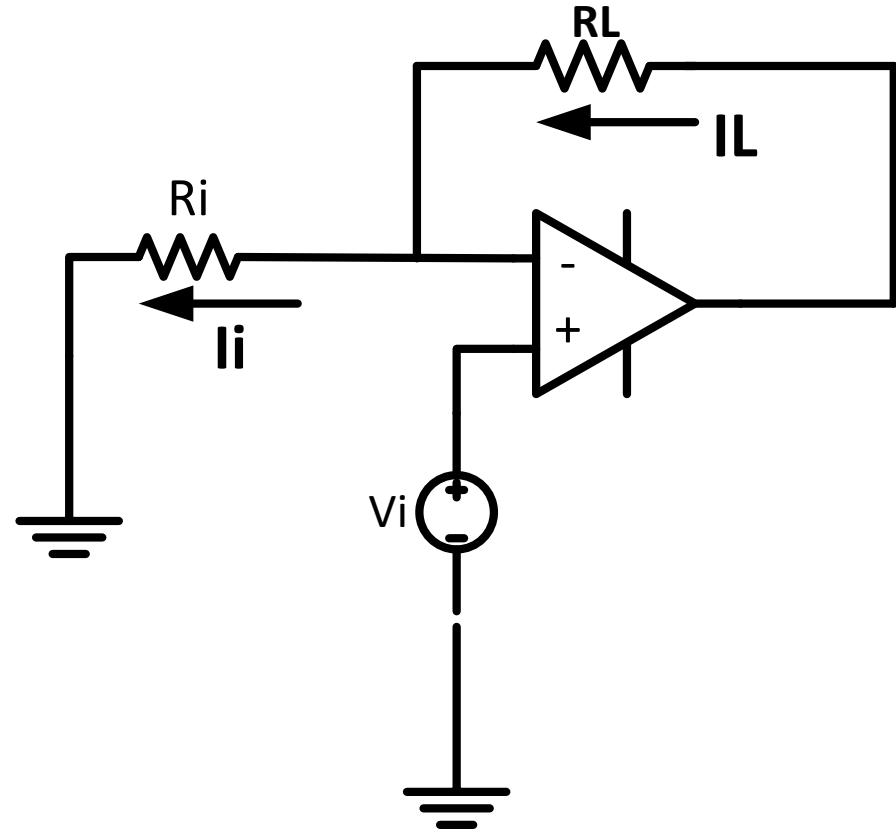

High-Resistance DC Voltmeter

$$I_m = I_i = \frac{V_i}{R_i}$$

If $V_i = +1 \rightarrow I_m = +1\text{mA}$

$$R_i = 1\text{k}$$

If $V_i = -1 \text{ v} \rightarrow I_m = -1\text{mA}$


$$R_i = 1\text{k}$$

If $V_i = +10 \text{ v} \rightarrow I_m = +1\text{mA}$

$$R_i = 10\text{k}$$

If $V_i = -10 \text{ v} \rightarrow I_m = -1\text{mA}$

$$R_i = 10\text{k}$$

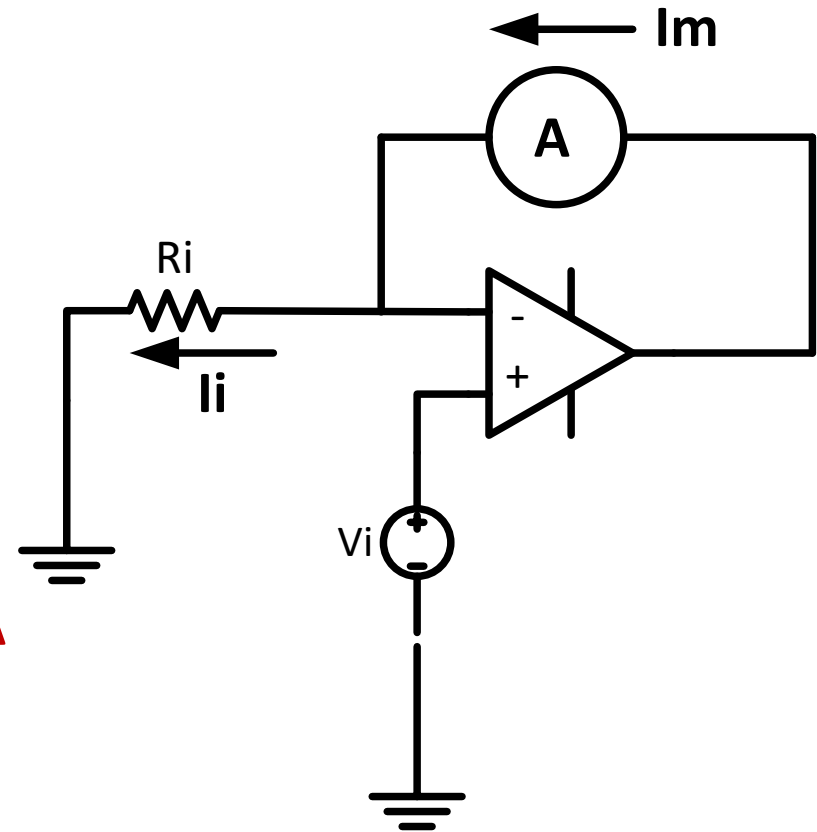

Voltage to current Converter


b) Grounded load

$$V_L = V(-) = \frac{1}{2} V_o$$

$$I_L = I_1 + I_2$$

$$I_L = \frac{V_o - V_L}{R} + \frac{E - V_L}{R}$$

$$\therefore I_L = \frac{E}{R}$$

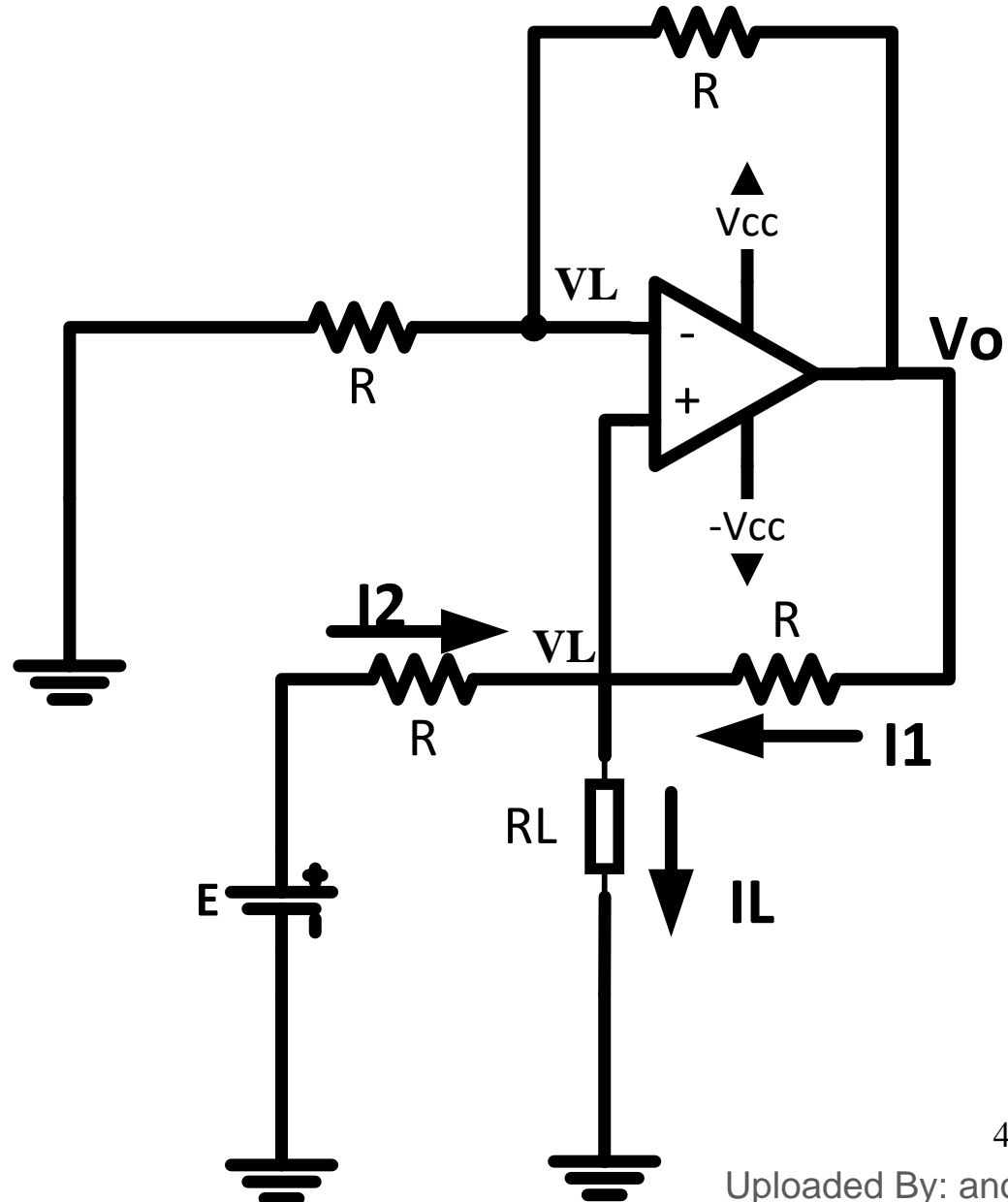


Current to Voltage Converter

$$V(+)=R I$$

$$V_o = \left(1 + \frac{R}{R}\right) V(+)$$

$$V_o = \left(1 + \frac{R}{R}\right) R I$$

$$V_o = K I$$

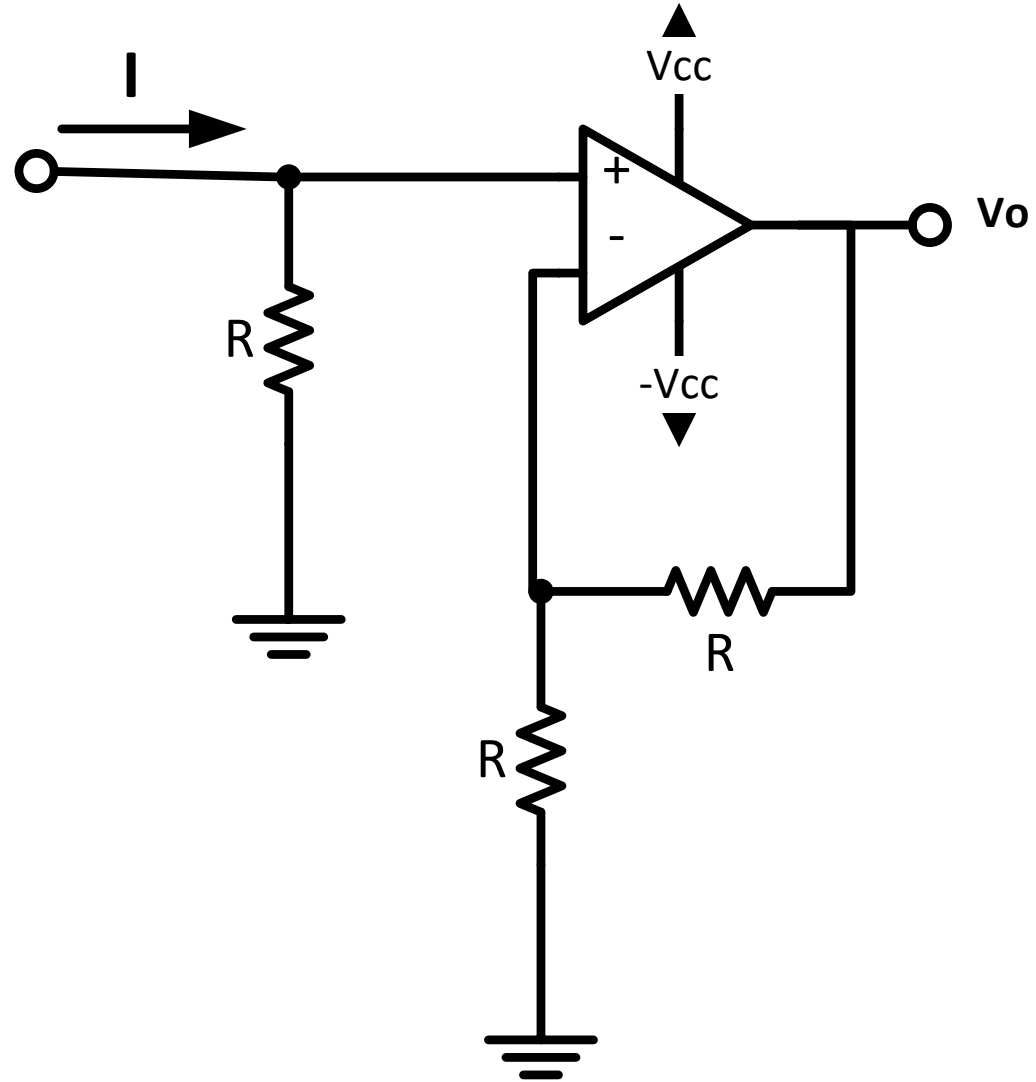




Current to Voltage Converter Application

$$I = \frac{E_i}{R}$$

$$V(+)=RI = E_i$$

$$V_o = V(+)$$

$$\therefore V_o = E_i$$

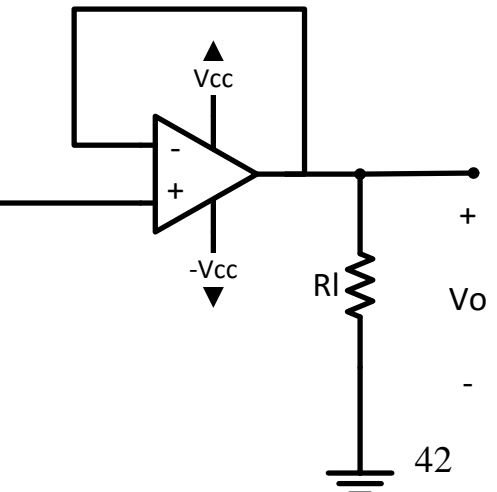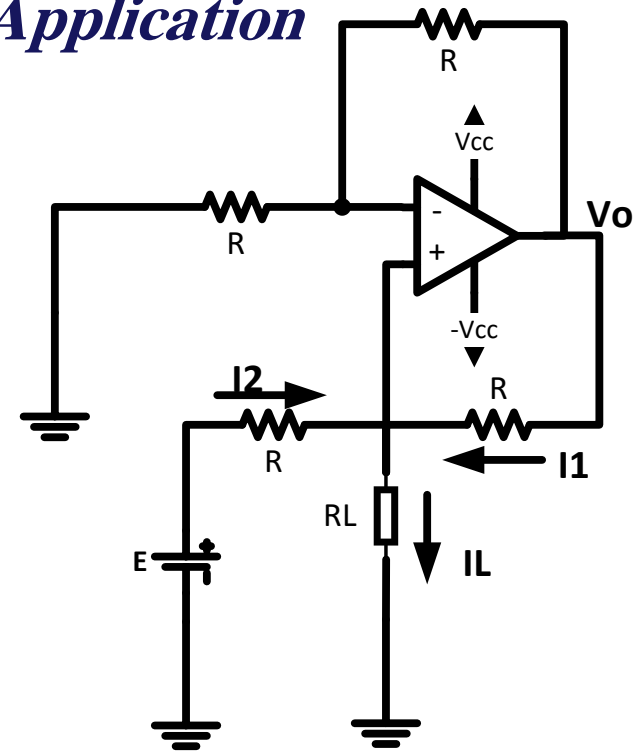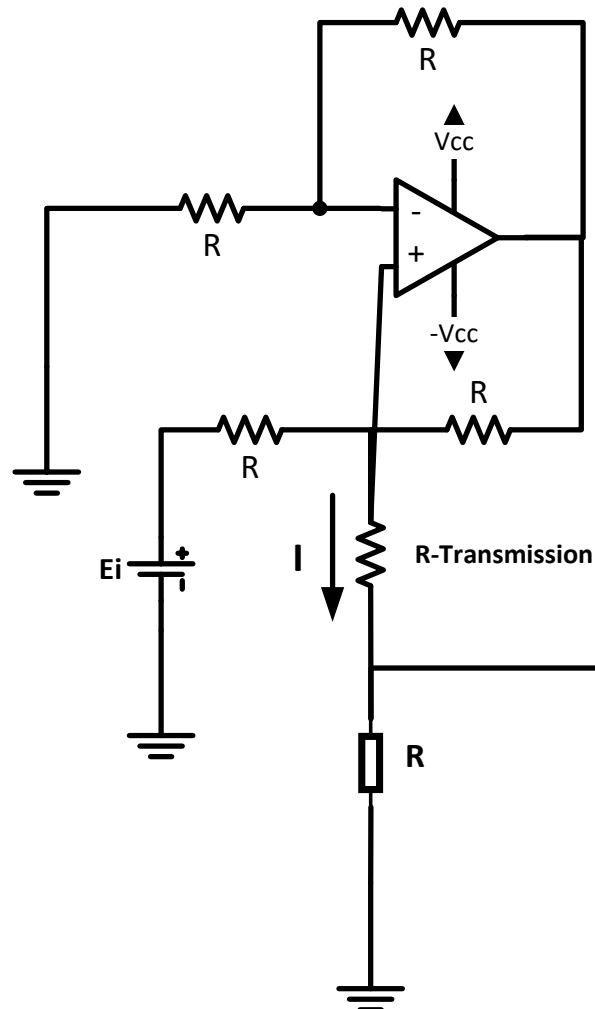

Constant High Current Source


$$I_R = \frac{V_Z}{R} = 1A$$

$$I_R = I_E$$

$$I_E \approx I_L$$

and since $\beta = 100$


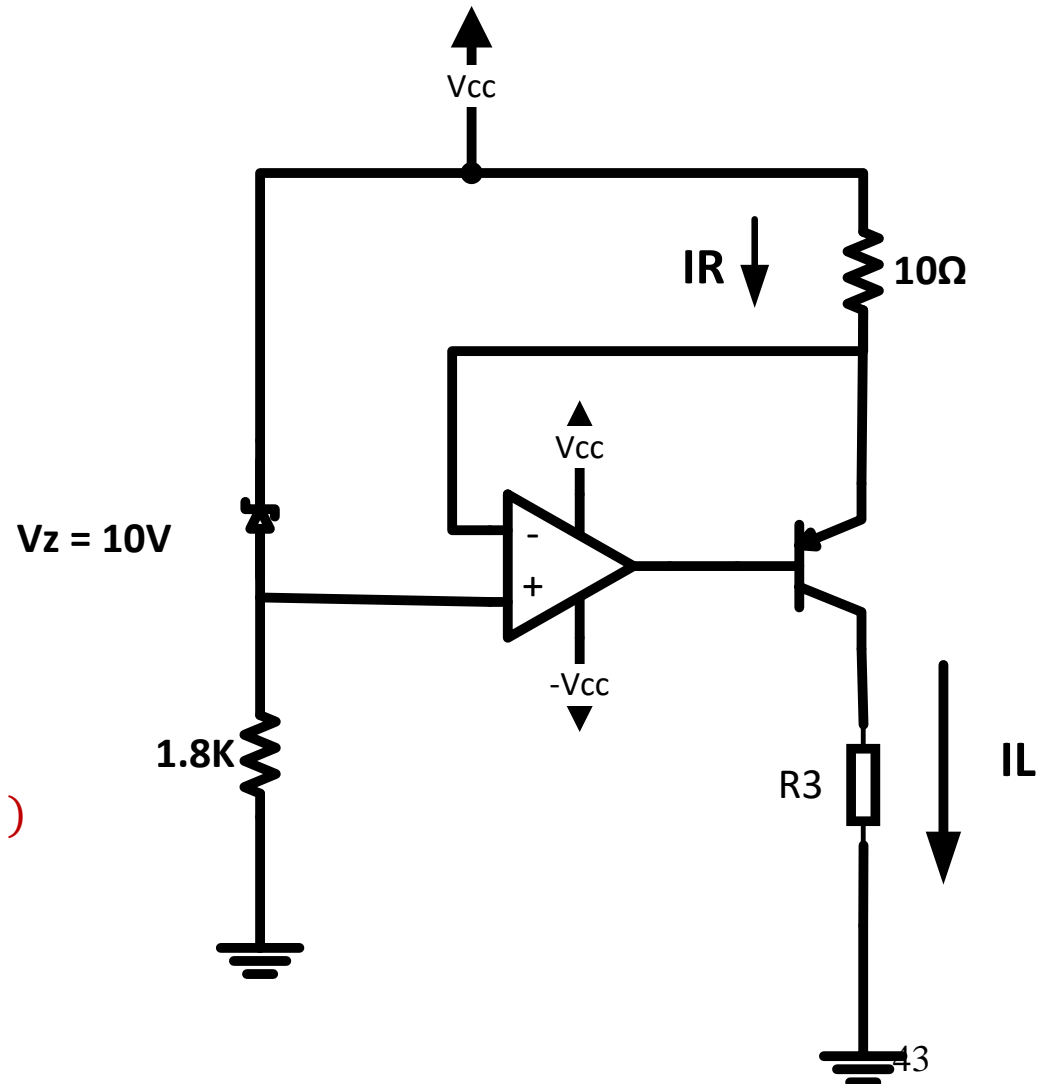
$$I_B = \frac{1A}{100} = 10mA < I_{O(max)}$$



Single Supply Op-amp


If $\pm V_{CC} = \pm 15\text{v}$

$V_{\text{sat}} = \pm 13\text{v}$

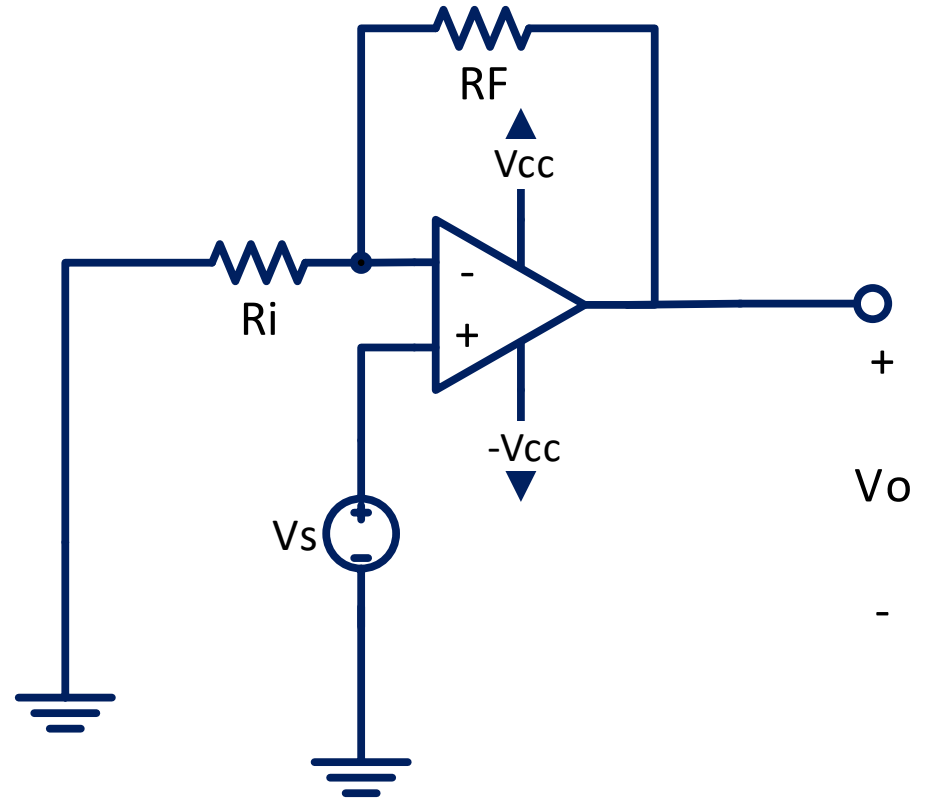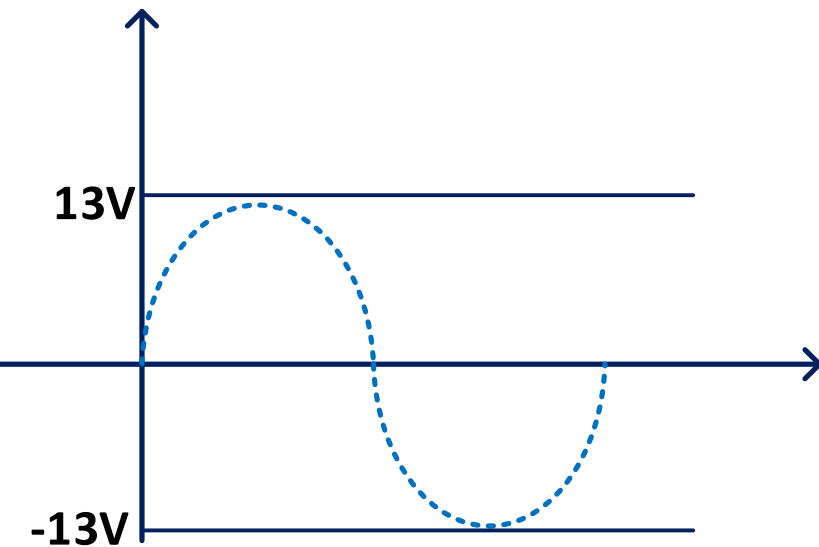


The Maximum possible swing = 26V peak to peak

Single Supply Op-amp

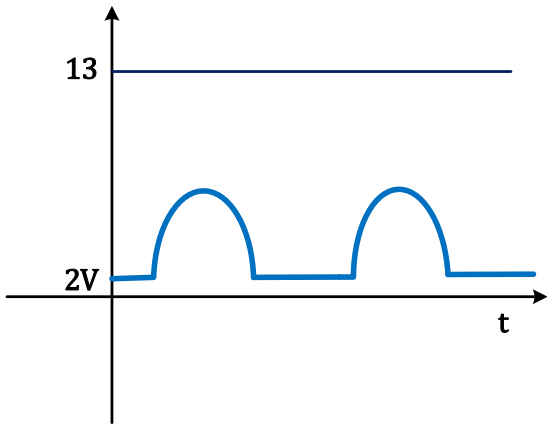


Distortion

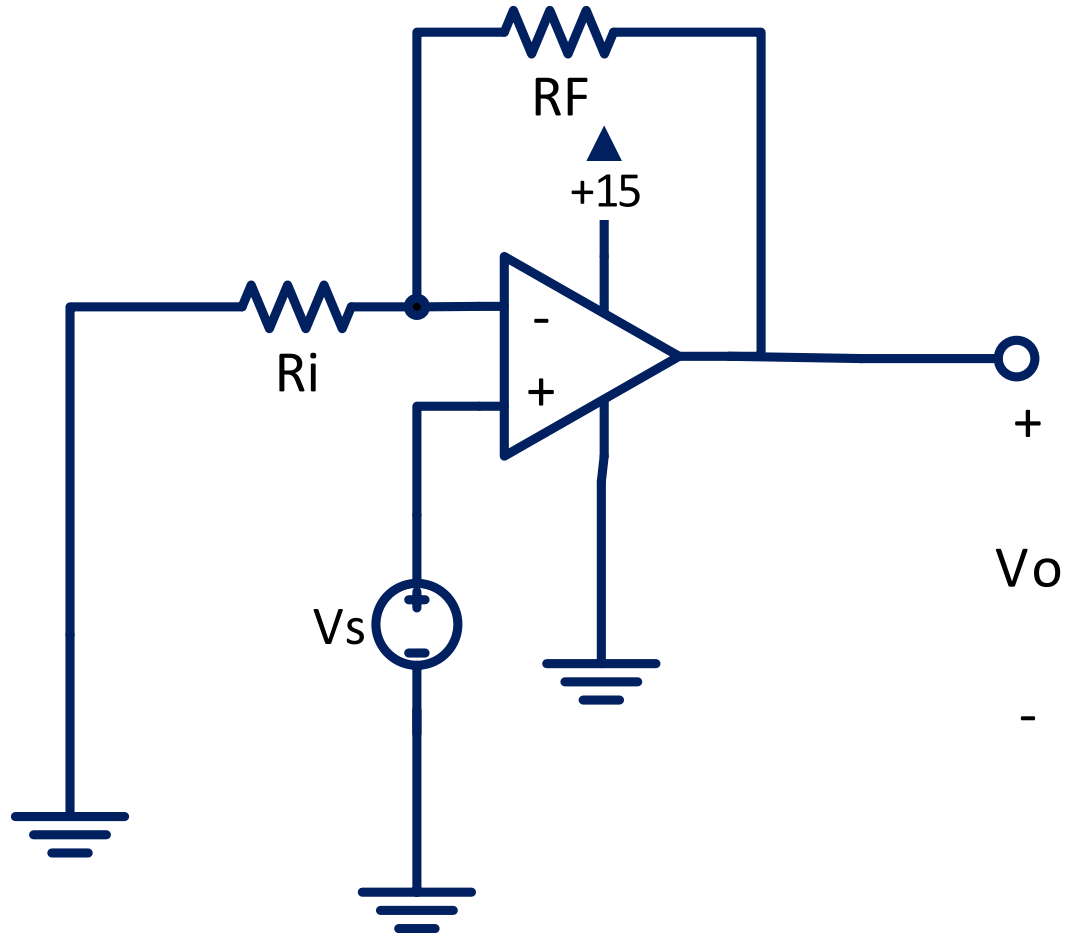


Single Supply Op-amp

DC Equivalent ckt:

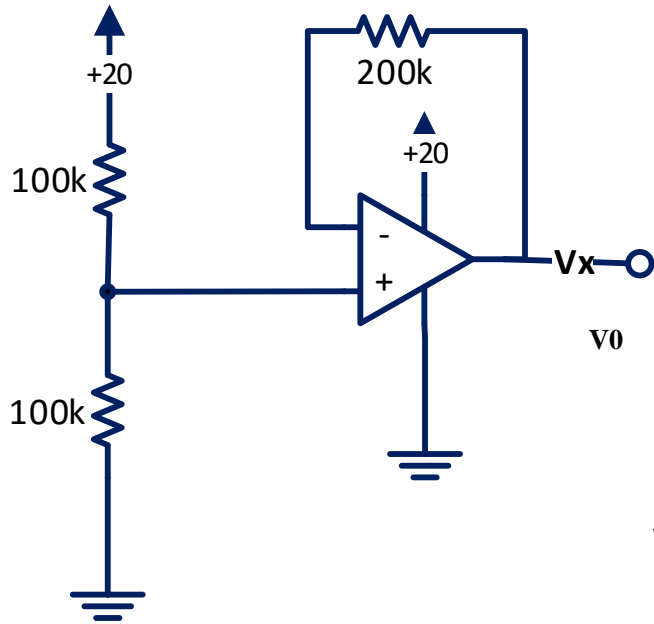



$$V_x = V(+) = 10v$$

$$V_o = 0$$

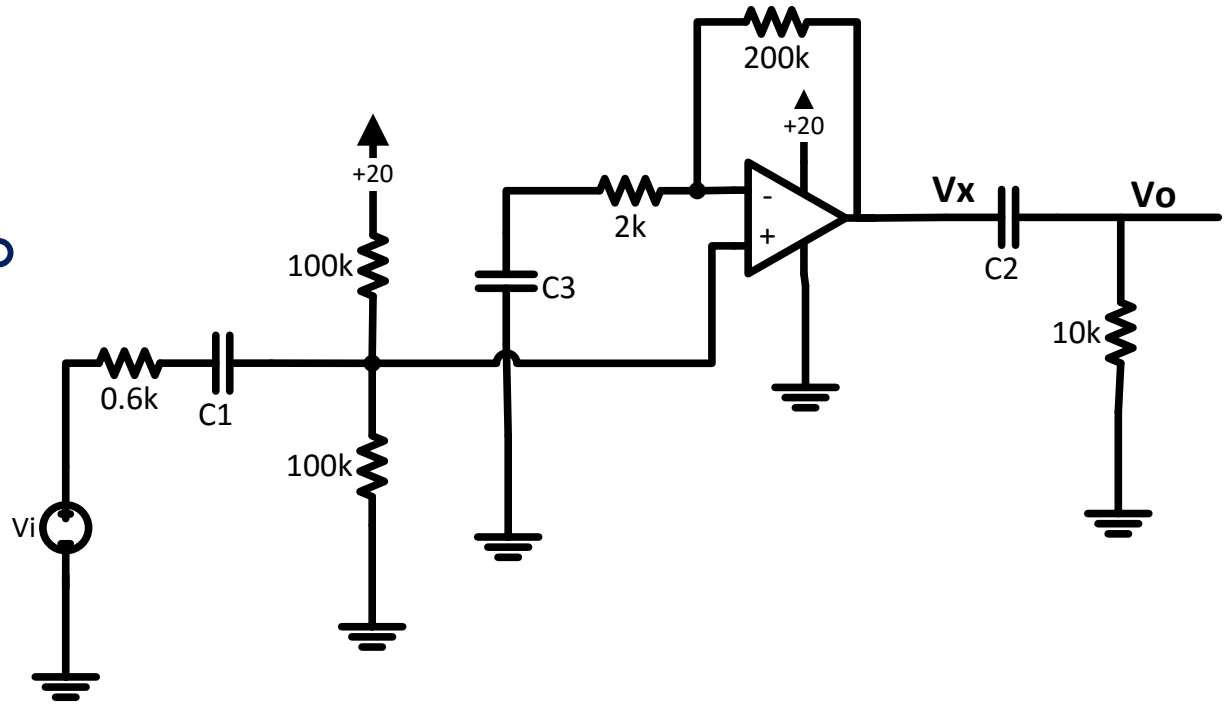

Single Supply Op-amp


AC small signal equivalent ckt:

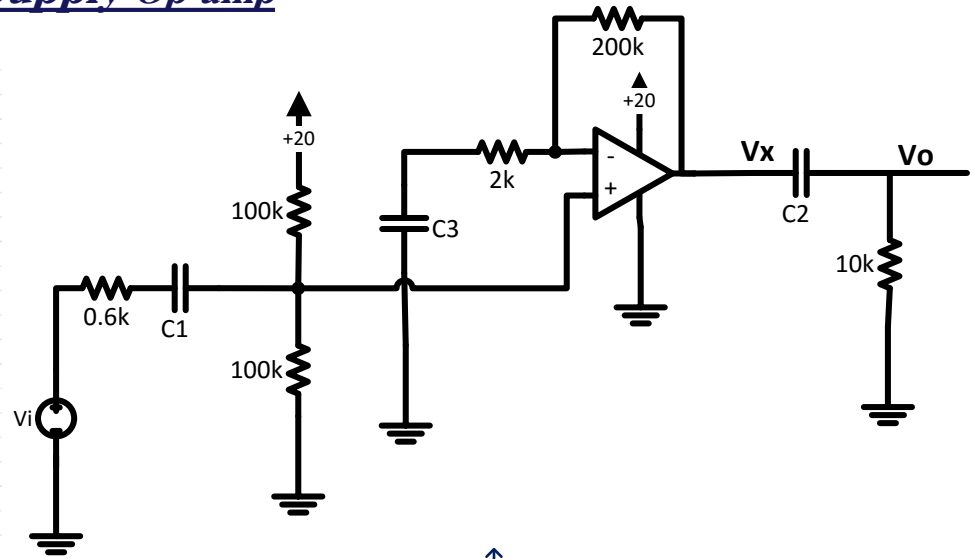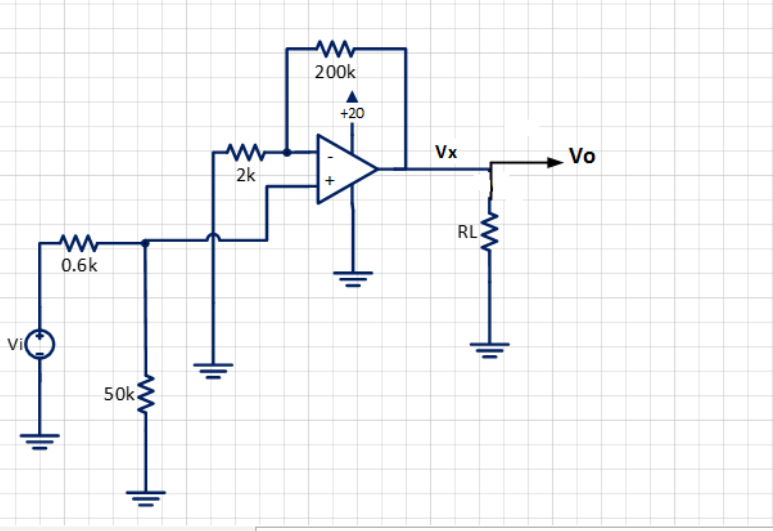



$$V (+) = \frac{50K}{50K+0.6K} V_i \approx V_i$$

$$V_X = V_O = \left(1 + \frac{200K}{2K}\right) (V (+))$$

$$V_X = V_O \cong 101 V_i$$

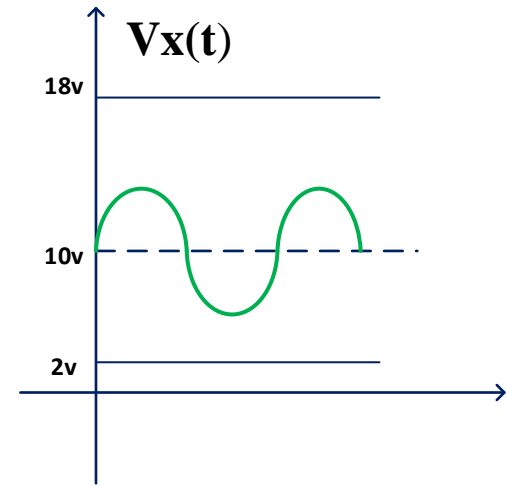

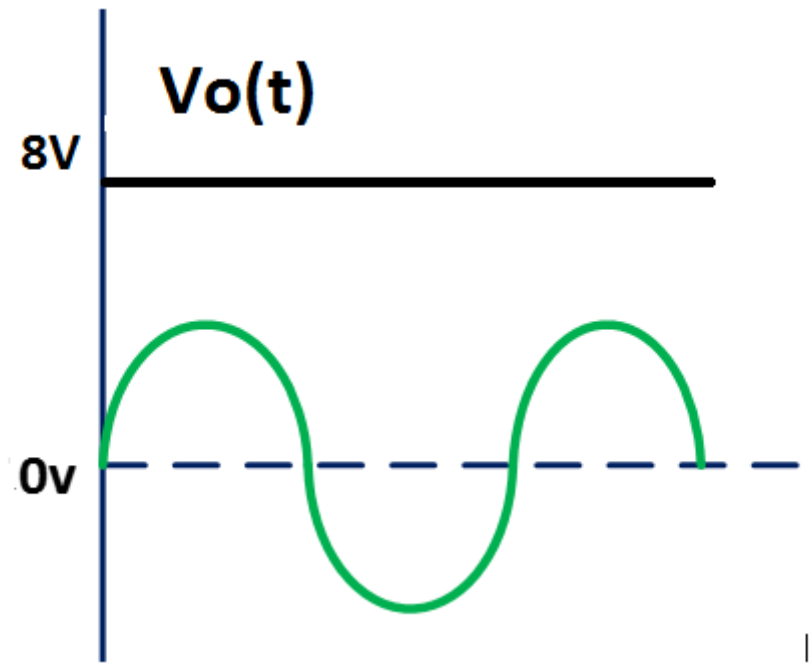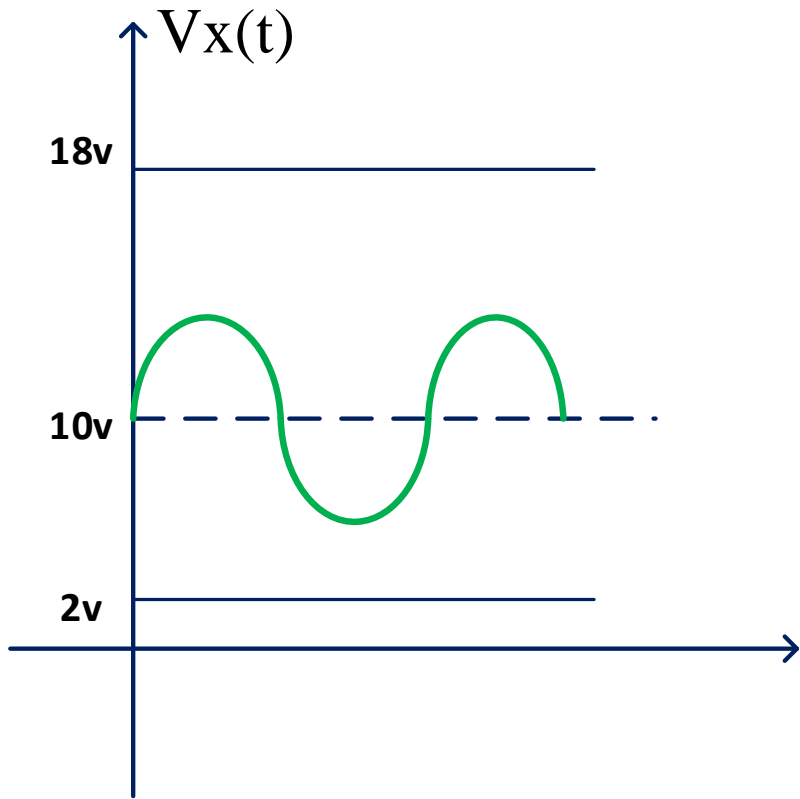The Maximum possible swing = 16V peak to peak



Comparator : Zero -Level detector

Exact analysis:


When $v_d > 65\mu\text{V}$; $V_O = +V_{sat}$

When $v_d < -65\mu\text{V}$; $V_O = -V_{sat}$

Approximate analysis

When $v_d > 0\text{V}$; $V_O = +V_{sat}$



When $v_d < 0\text{V}$; $V_O = -V_{sat}$

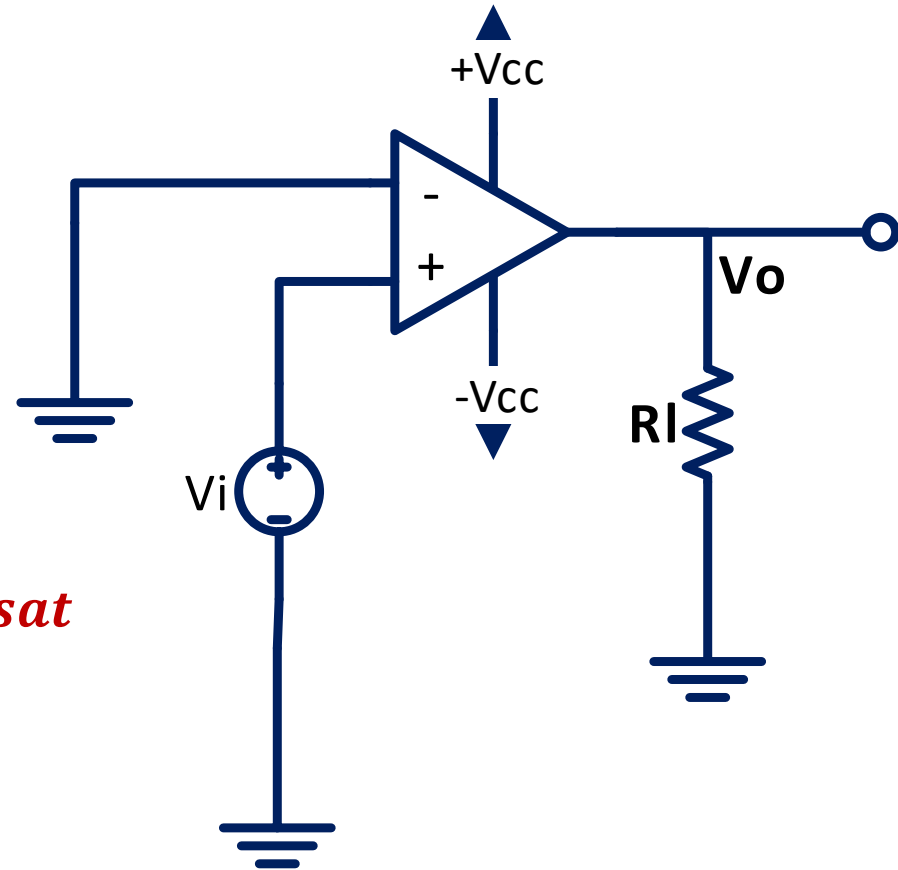

Comparator : Zero -Level detector

$$V_i(t) = 5 \sin \omega t \text{ v}$$

$$\pm V_{sat} = \pm 13 \text{ v}$$

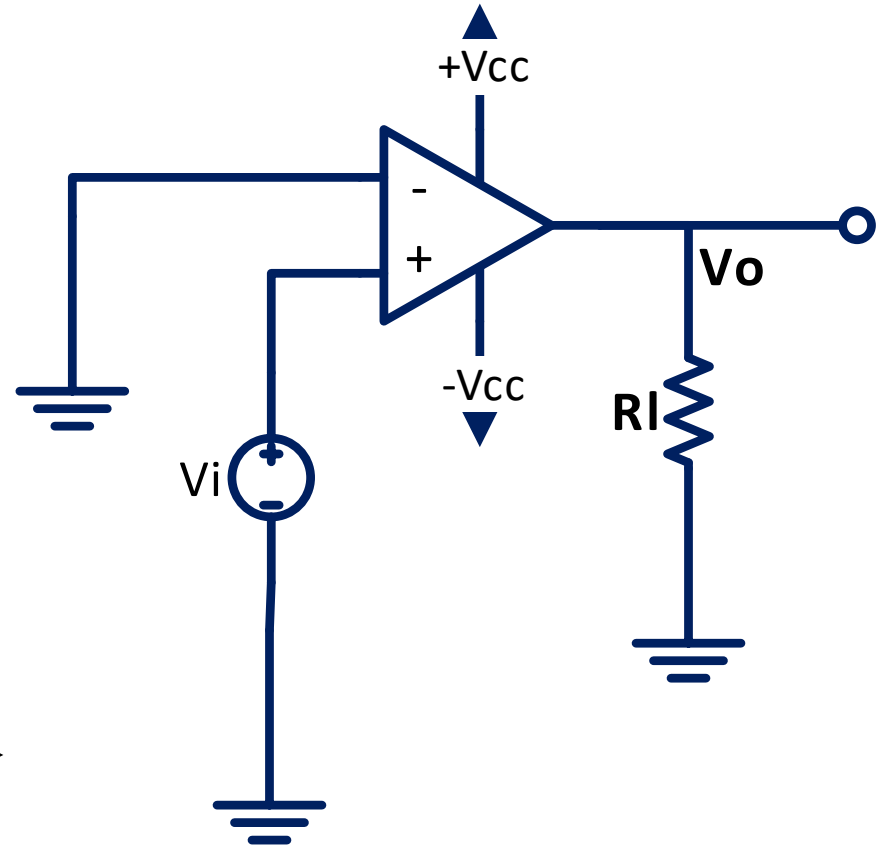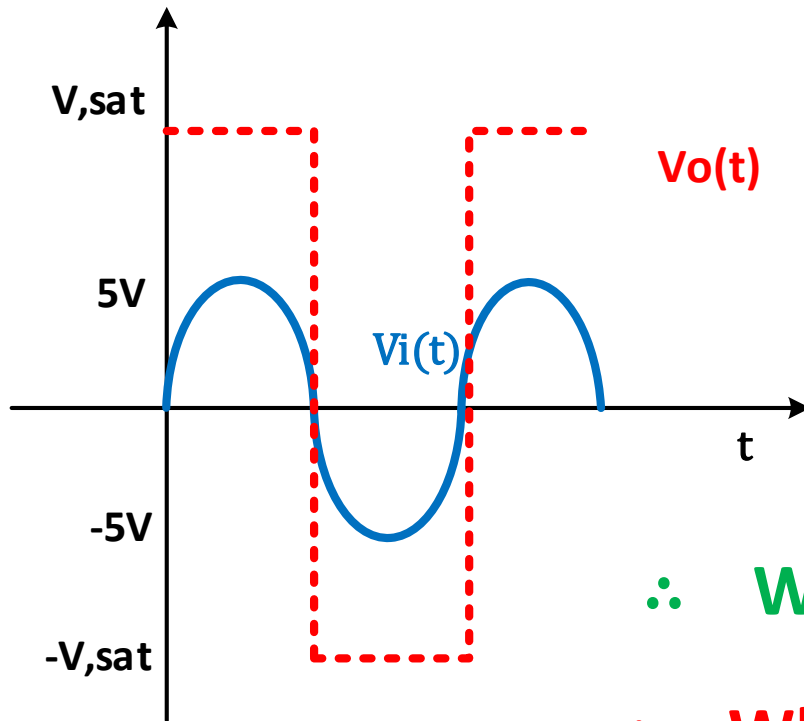

\therefore When $V_i > 0V$; $V_O = +V_{sat}$

\therefore When $V_i < 0V$; $V_O = -V_{sat}$



Non Zero -Level detector

$$V_i(t) = 5 \sin \omega t \text{ v}$$

$$\pm V_{sat} = \pm 13 \text{ v}$$

When $V_i > 2\text{V}$; $V_O = +V_{sat}$

When $V_i < 2\text{V}$; $V_O = -V_{sat}$

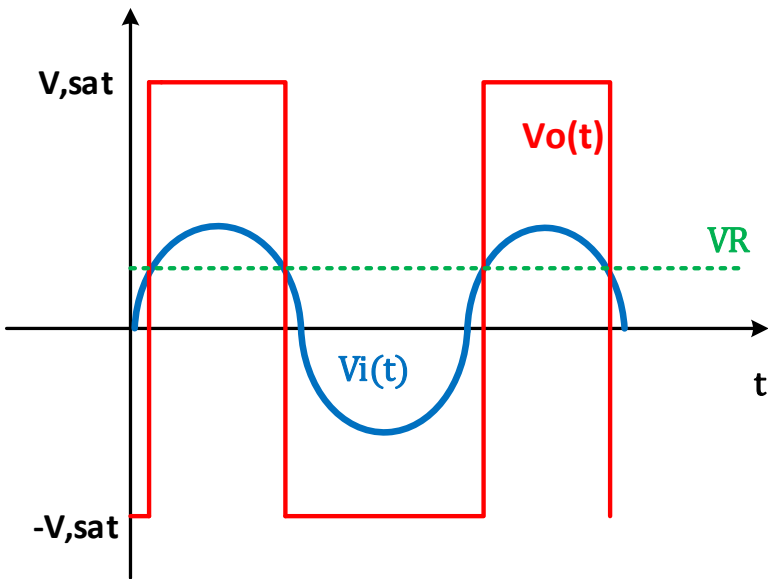
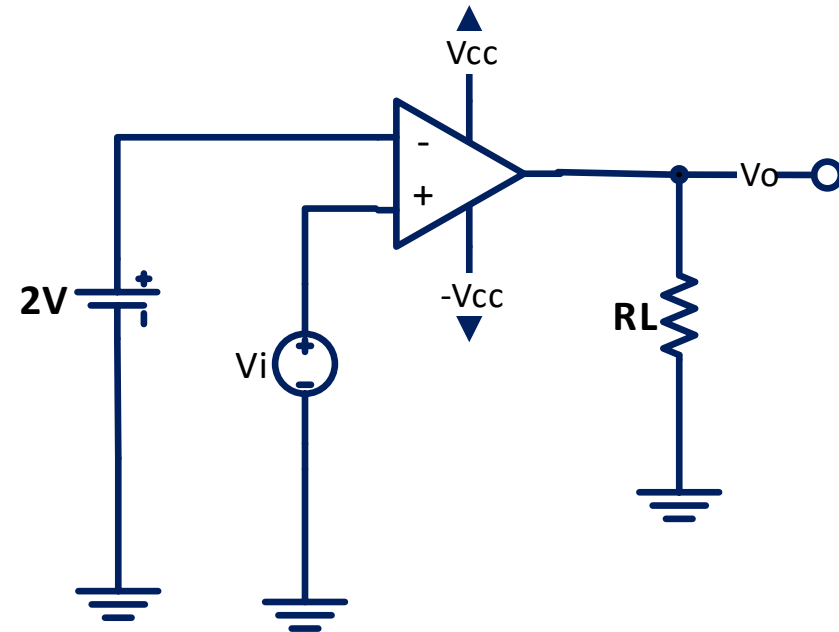


When $v_d > 0\text{V}$; $V_O = +V_{sat}$

When $v_d < 0\text{V}$; $V_O = -V_{sat}$

Practical Non Zero –Level detector

Application

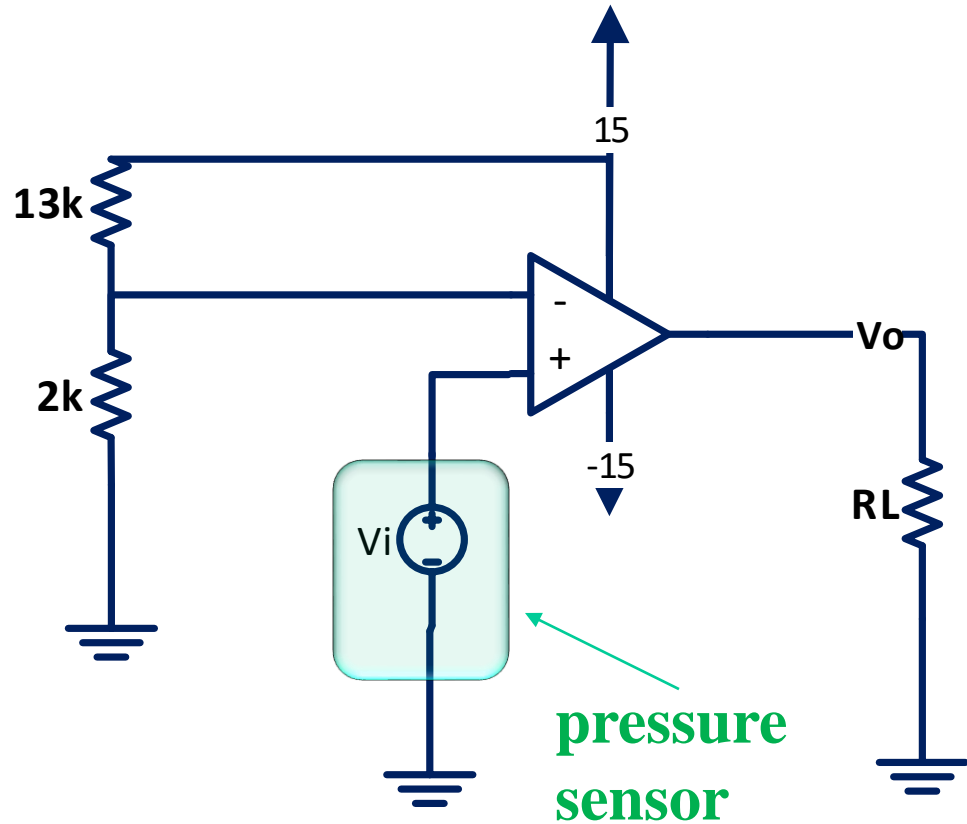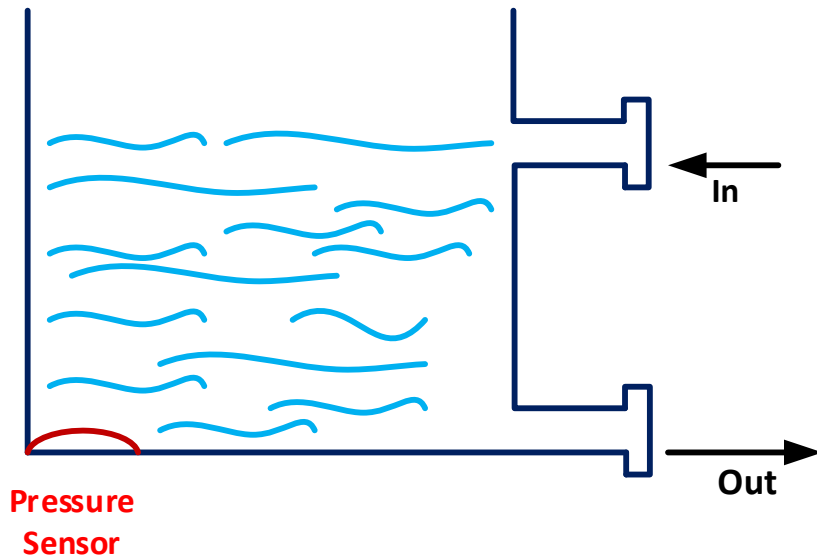

The pressure sensor generates a voltage proportional to the water level in the tank

When water level reaches the maximum allowable level

→ $V_i = 2V$

$$V(-) = 2V$$

When $V_i > 2V$; $V_o = +V_{sat}$

When $V_i < 2V$; $V_o = -V_{sat}$

Voltage-Level detector with LEDs:

When $V_i > 2V$; $V_o = +V_{sat}$


∴ Red LED is ON

∴ green LED is OFF

When $V_i < 2V$; $V_o = -V_{sat}$

∴ green LED is ON

∴ Red LED is OFF

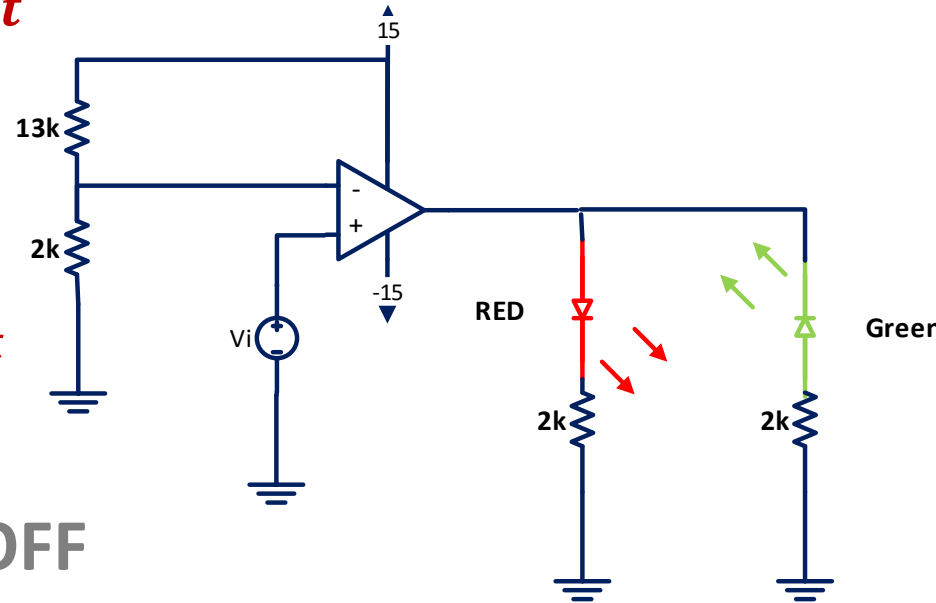

When $V_i = 2V$; $V_o = 0$

∴ green LED and the Red LED are OFF

Over Temperature sensing Circuit



$R1 \uparrow$ as $T \downarrow$

R1 = Resistance of the thermistor.

R2 is set equal to the resistance of the thermistor at the critical temp.

R = 100k

This is the thermistor

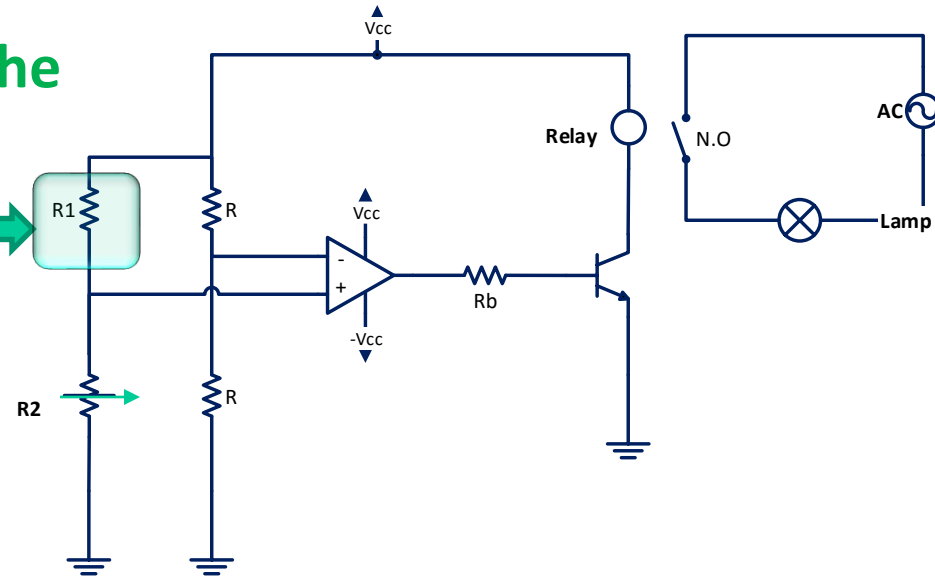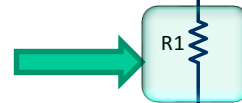

1) At Normal temperature ($T < T_c$)

$$R_1 > R_2$$

$$V(+)=\frac{R_2}{R_1+R_2} V_{CC} < \frac{1}{2} V_{CC}$$

$$V(-)=\frac{1}{2} V_{CC}$$

$$\therefore V(-) > V(+), \therefore V_{op} = -V_{sat}$$

\therefore transistor is cut OFF ; $I_C = 0$

\therefore Relay is denergized

\therefore switch is open

\therefore Lamp is OFF

Over Temperature sensing Circuit

2) When $T = T_c$

$$R_1 = R_2$$

$$V(+)=V(-)=\frac{1}{2}V_{cc}$$

$$\therefore V_{op} = 0$$


\therefore transistor is in cut OFF ;

$$I_C = 0$$

\therefore Relay is denergized

\therefore switch is open

\therefore Lamp is OFF

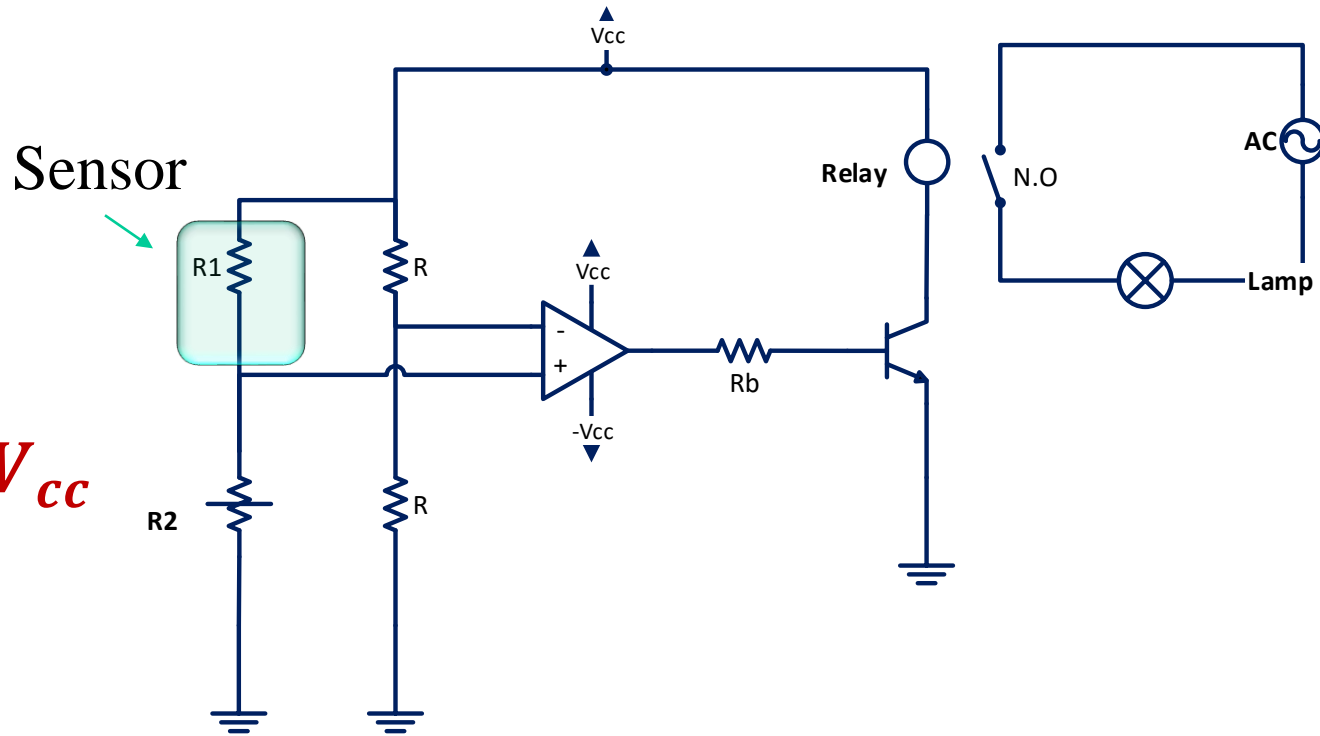

Over Temperature sensing Circuit

3- When $T > T_c$

$$R_1 < R_2$$

$$V(+)=\frac{R_2}{R_1+R_2} V_{cc} > \frac{1}{2} V_{cc}$$


$$V(-)=\frac{1}{2} V_{cc}$$



$$\therefore V_{op} = +V_{sat}$$

\therefore transistor is conducting

\therefore Relay is energized

\therefore Lamp is on

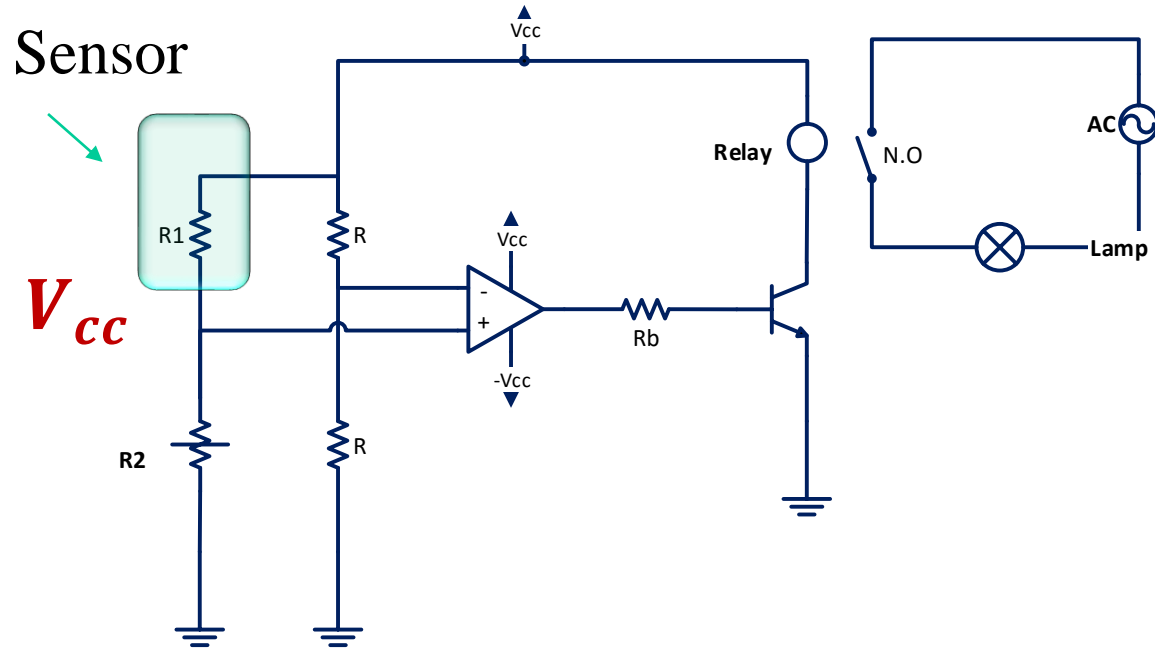

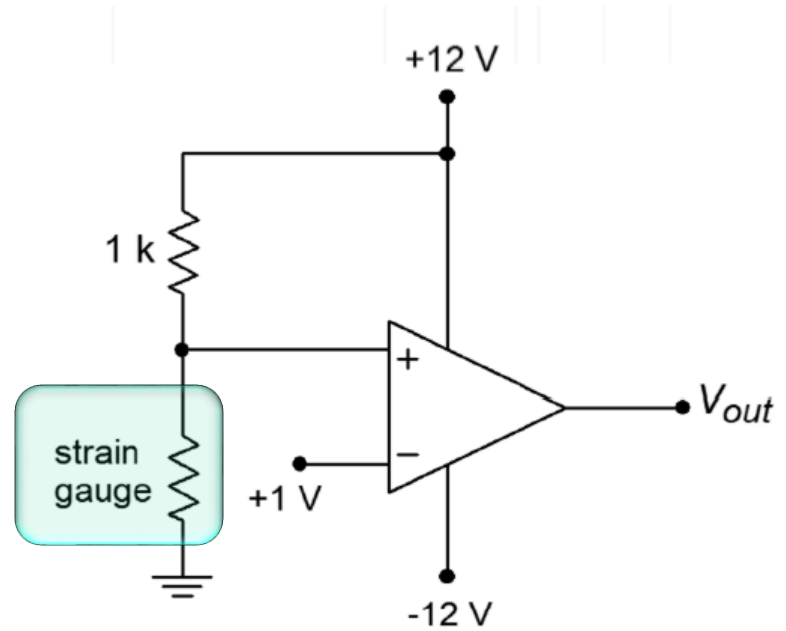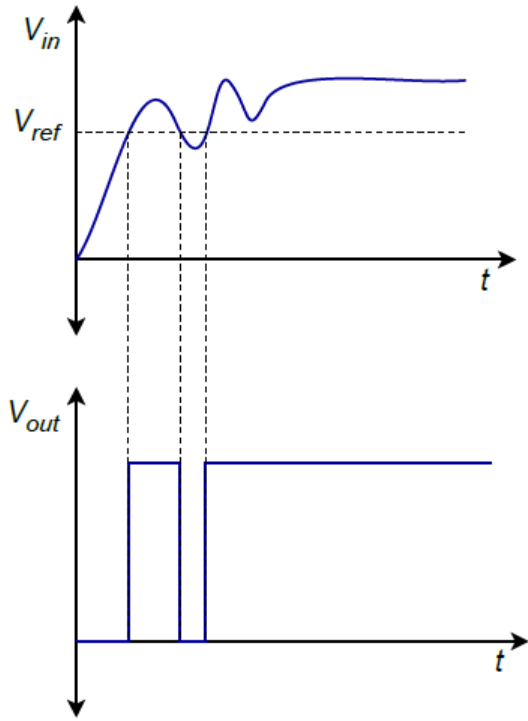

The signal V_i is noisy


The noise will produce a false turn off spike

The solution is *Schmitt Trigger Comparator*

We must have two references

When $V_i > V_{ref(U)}$  V_o switch to **+ V_{sat}**

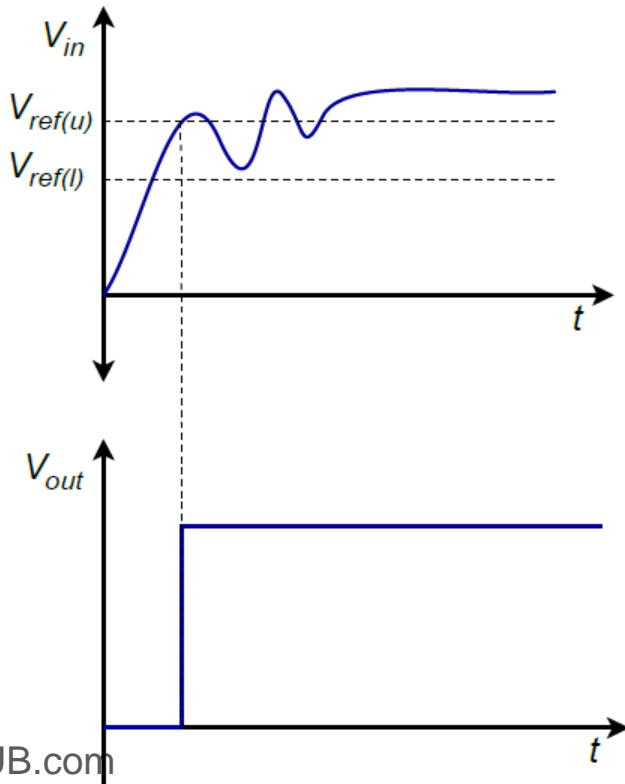When $V_i < V_{ref(L)}$  V_o switch to **- V_{sat}** **(This case should not happen in this application)**



Schmitt Trigger Comparator

1. Assume $V_O = +V_{sat}$

$$V(-) = V_i$$

$$V(+) = \frac{R_2}{R_1 + R_2} (+V_{sat}) = V_{UT}$$

$$v_d > 0$$

$$\frac{R_2}{R_1 + R_2} (+V_{sat}) - V_i > 0$$


$$\therefore V_i < \frac{R_2}{R_1 + R_2} (+V_{sat})$$

$$\therefore \text{as long as } V_i < \frac{R_2}{R_1 + R_2} (+V_{sat})$$


$$V_O = +V_{sat}$$

$$\text{But when } V_i > \frac{R_2}{R_1 + R_2} (+V_{sat})$$

V_O switch to $(-V_{sat})$

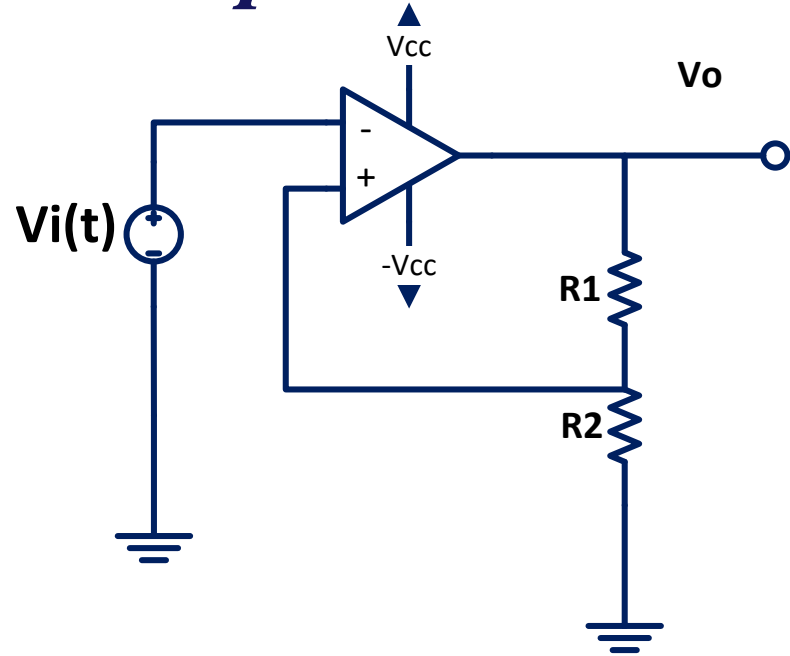

Inverting Schmitt trigger comparator

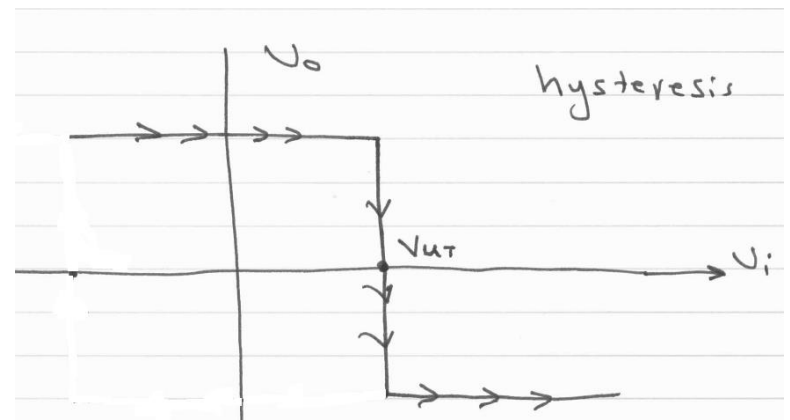

Schmitt Trigger Comparator

2. Assume $V_O = -V_{sat}$

$$V(-) = V_i$$

$$V(+) = \frac{R_2}{R_1 + R_2} (-V_{sat}) = V_{LT}$$

$$v_d < 0$$

$$\frac{R_2}{R_1 + R_2} (-V_{sat}) - V_i < 0$$



$$\therefore V_i > \frac{R_2}{R_1 + R_2} (-V_{sat})$$

$$\therefore \text{as long as } V_i > \frac{R_2}{R_1 + R_2} (-V_{sat})$$

$$V_O = -V_{sat}$$

$$\text{But when } V_i < \frac{R_2}{R_1 + R_2} (-V_{sat})$$

$$V_O \text{ switch to } (+V_{sat})$$

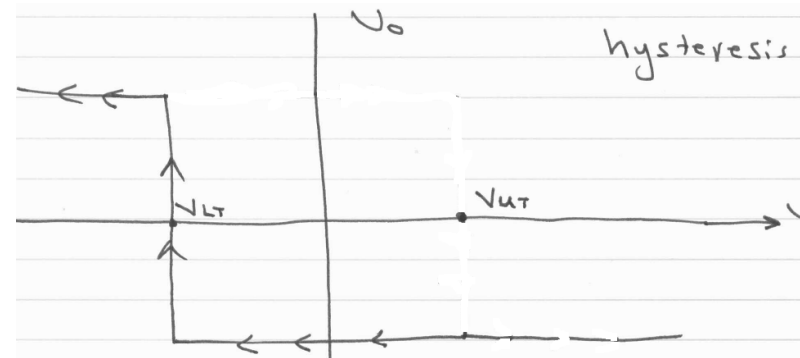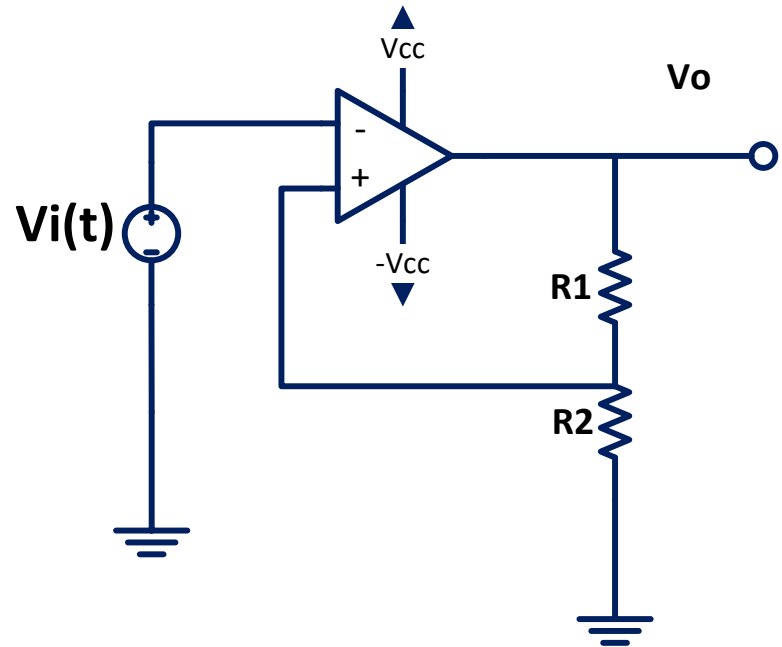

Schmitt Trigger Comparator


Hysteresis voltage $\equiv V_H = V_{UT} - V_{LT}$

$V_{UT} \equiv$ *Upper Threshold voltage*

$$V_{UT} = \frac{R_2}{R_1 + R_2} (+V_{sat})$$


$V_{LT} \equiv$ *Lower Threshold voltage*
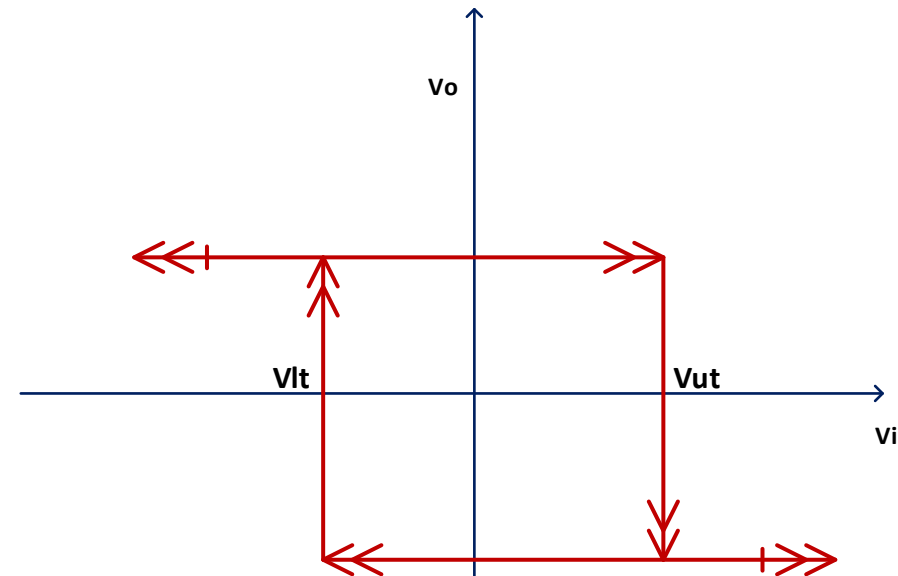
$$V_{LT} = \frac{R_2}{R_1 + R_2} (-V_{sat})$$



Schmitt Trigger Comparator

Signal Wave form

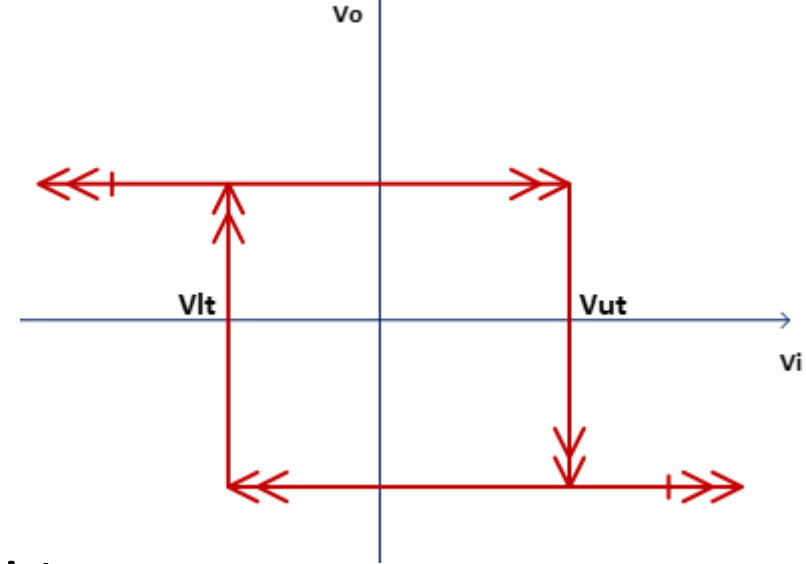


when $V_i < \frac{R_2}{R_1 + R_2} (-V_{sat})$

V_o switch to $(+V_{sat})$

when $V_i > \frac{R_2}{R_1 + R_2} (+V_{sat})$

V_o switch to $(-V_{sat})$

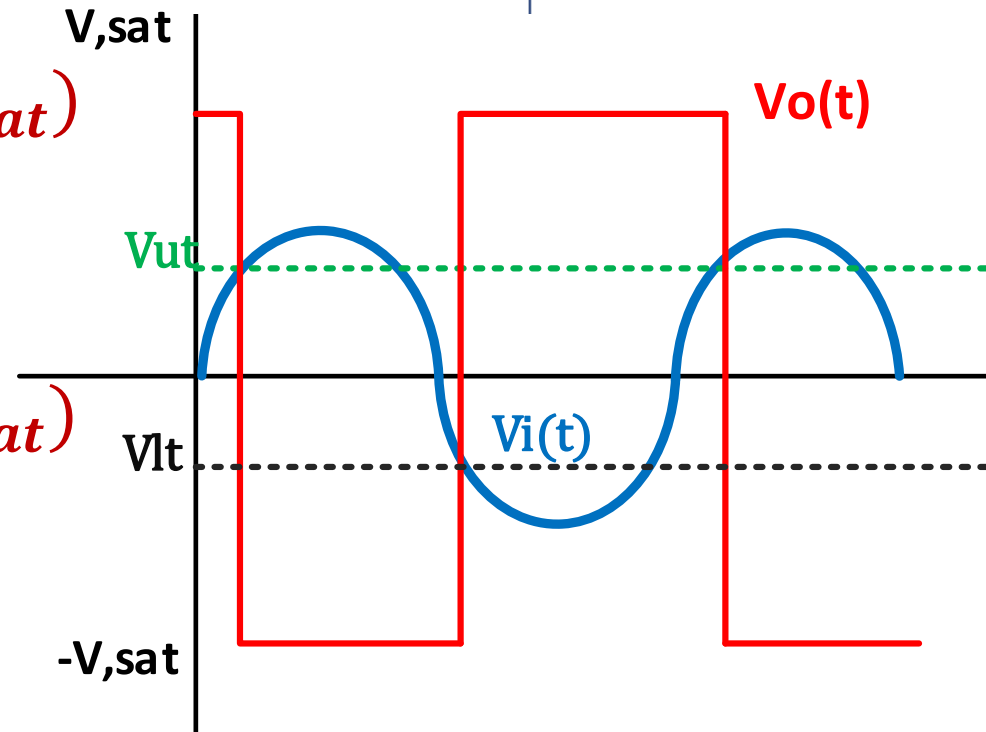

Room Thermostat

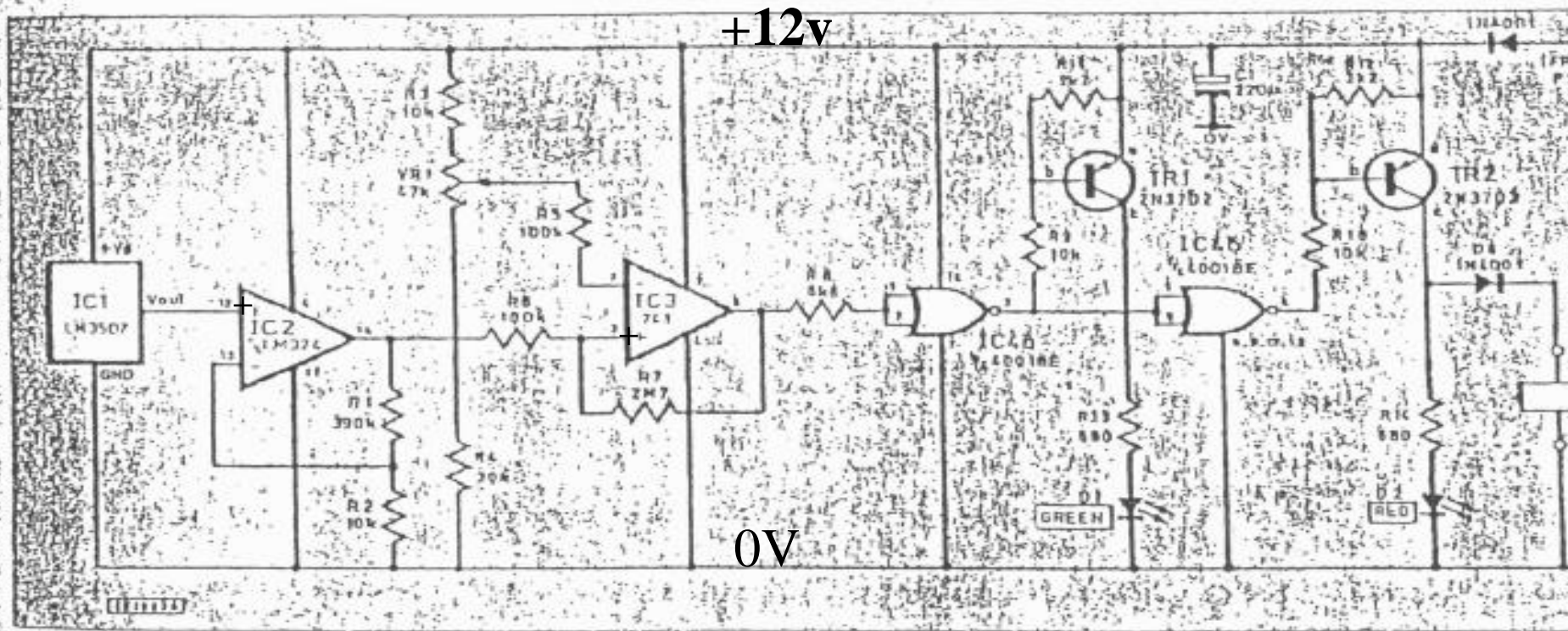


Fig. 2. Complete circuit diagram for the Room Thermostat. The connections to the "relay" are for the low voltage only.

IC1 = LM3507

IC2 = LM324

IC3 = 741

IC4 = 4001B

TR1 = 2N3702

TR2 = 2N3702

R1 = 390K

R2 = 10K

R3 = 10K

VR1 = 47K

R4 = 30K

R5 = 100K

R6 = 100K

R7 = 2.7MΩ

R8 = 6.8K

R9 = 10K

R10 = 10K


R11 = 2.2K

R12 = 2.2K

R13 = 0.68K


Schmitt Trigger Comparator

Room Thermostat

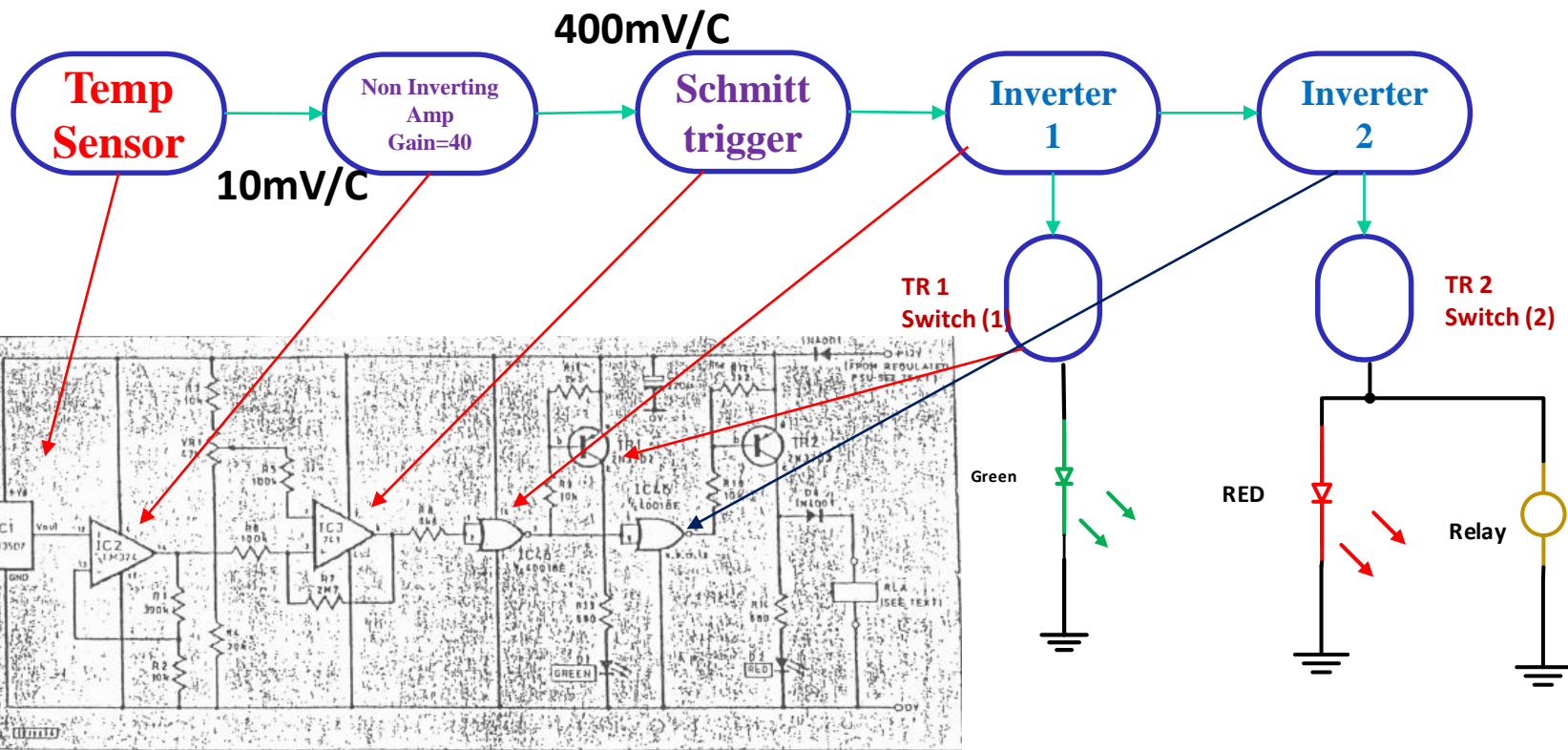

Schmitt Trigger Comparator

Room Thermostat

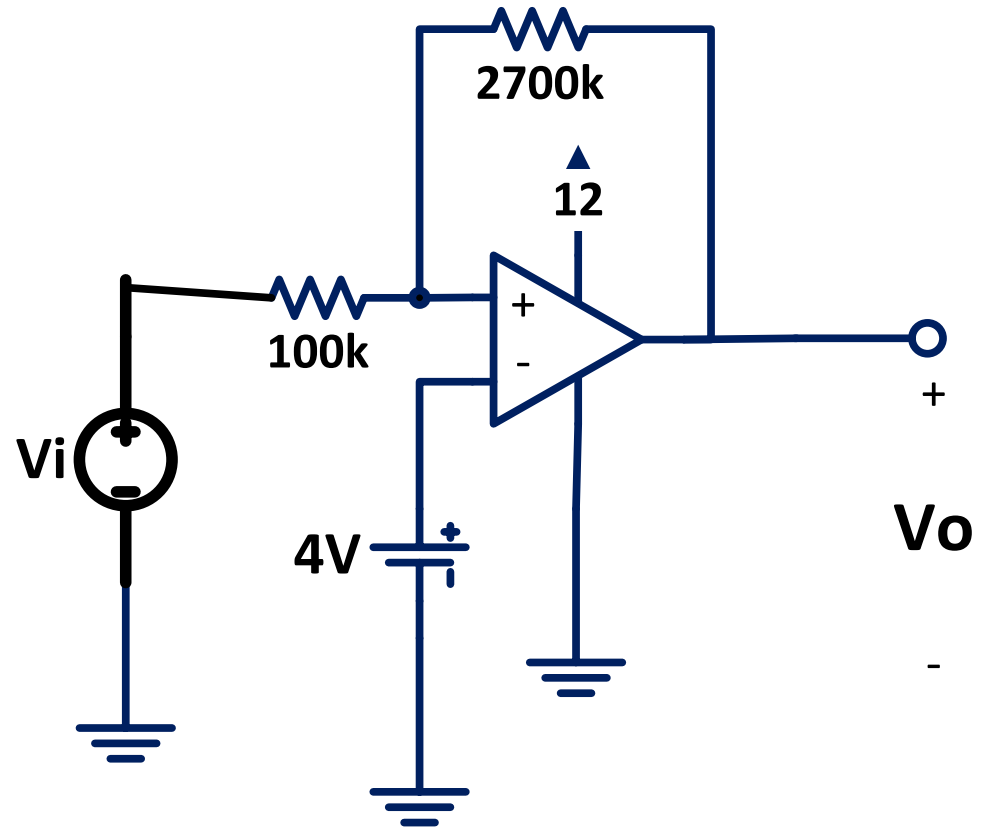

$$V_i = 400\text{mV/C}$$

$$1. \text{ Let } V_o = +V_{sat} = +10$$

$$v_d > 0$$

$$V(-) = 4\text{v}$$


$$V(+)= \frac{100\text{K}}{100\text{K}+2700\text{K}} (+V_{sat}) + \frac{2700\text{K}}{2700\text{K}+100\text{K}} V_i$$

$$\text{For } v_d > 0 ; V_i > 3.777\text{V}$$

$$\therefore \text{ As long as } V_i > 3.777\text{V} ; V_o = +V_{sat}$$

$$\text{But when } V_i < 3.777\text{V} ; V_o \text{ switch to } (-V_{sat})$$

Schmitt Trigger Comparator

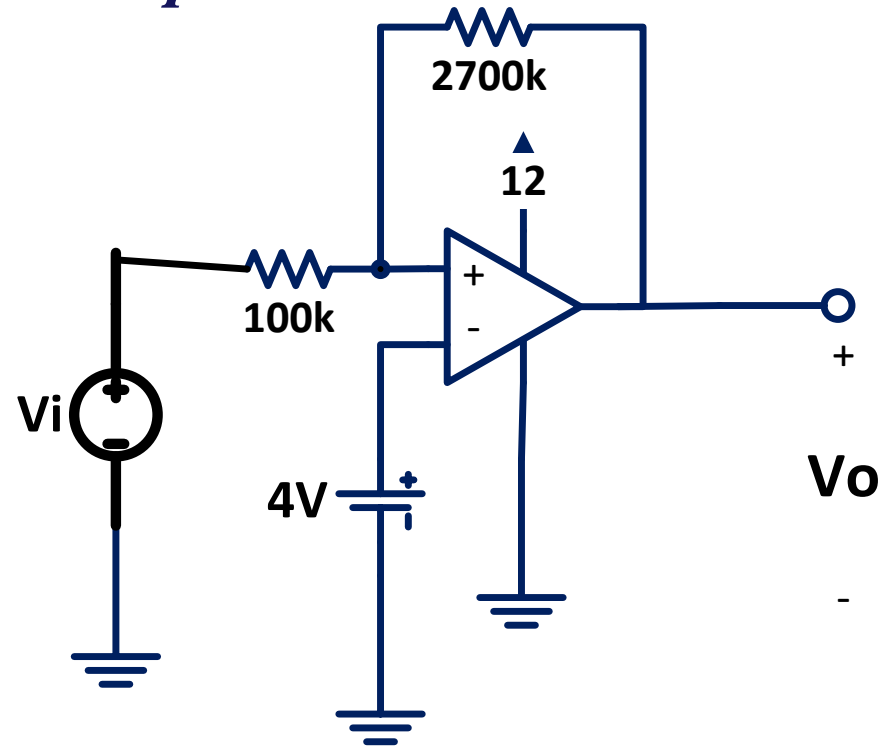

2. Let $V_O = -V_{sat} = +2$

$v_d < 0$

$V(-) = 4V$

$$V(+)= \frac{100K}{100K+2700K} (-V_{sat}) + \frac{2700K}{2700K+100K} V_i$$

For $v_d < 0$; $V_i < 4.072V$


\therefore As long as $V_i < 4.072V$; $V_O = -V_{sat}$

But when $V_i > 4.072V$; V_O switch to $(+V_{sat})$

Schmitt Trigger Comparator

1) When $T > 10.37\text{ C}$, $V_o = +V_{sat}$
Transistor (2) is Off, Relay is
denergized and Heater is Off.


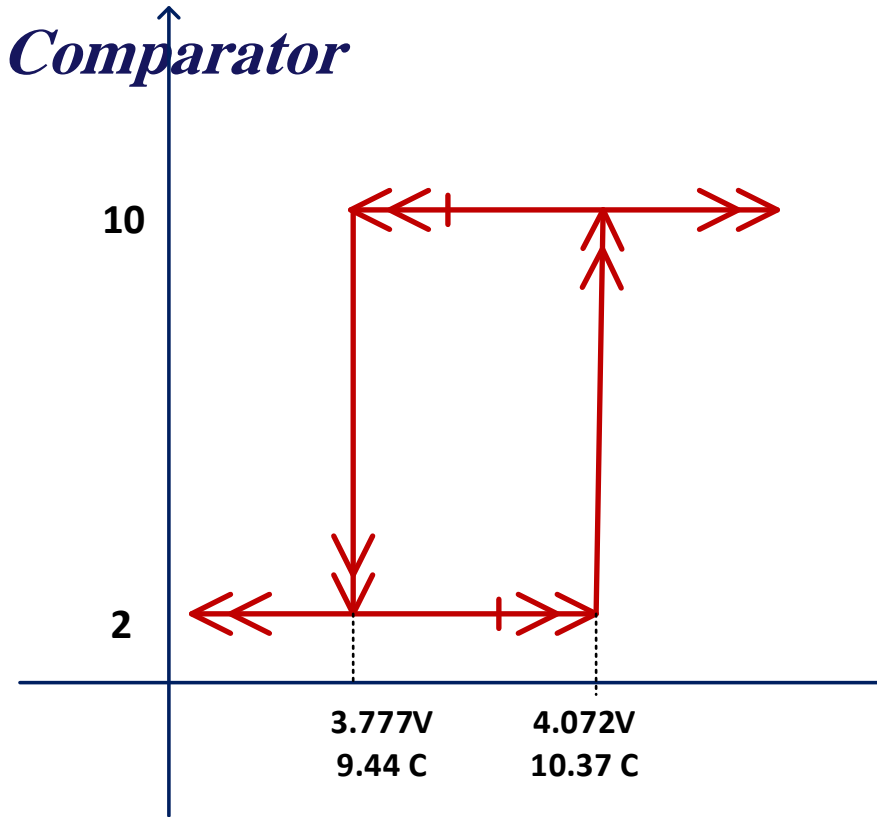
2) Then $T < 9.44\text{ C}$, $V_o = -V_{sat}$
Transistor (2) is On, Relay is
energized
and Heater is on.



Output offset Voltage


Inverting Amplifier

Let $V_i = 0$

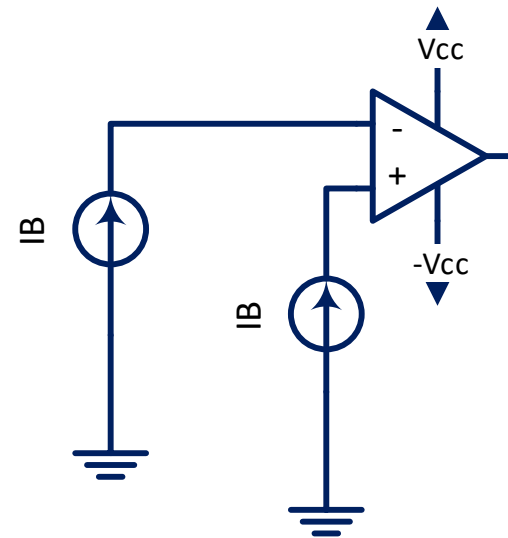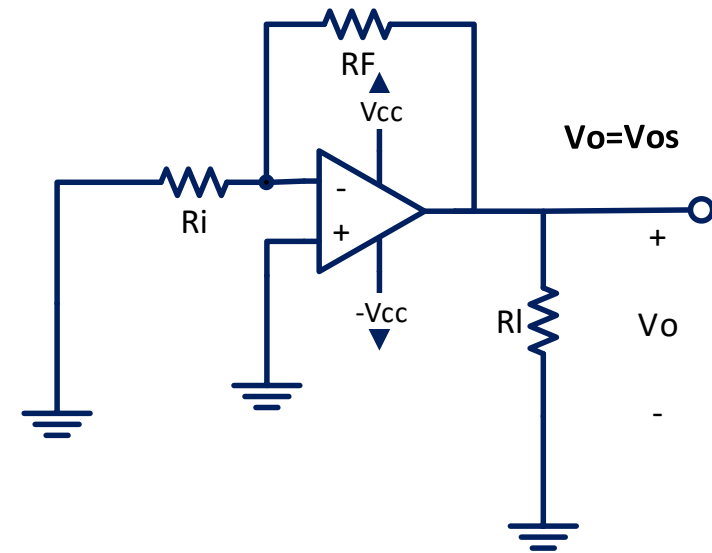

$V_{OS} \equiv$ the output voltage when $V_i = 0$

Output offset Voltage

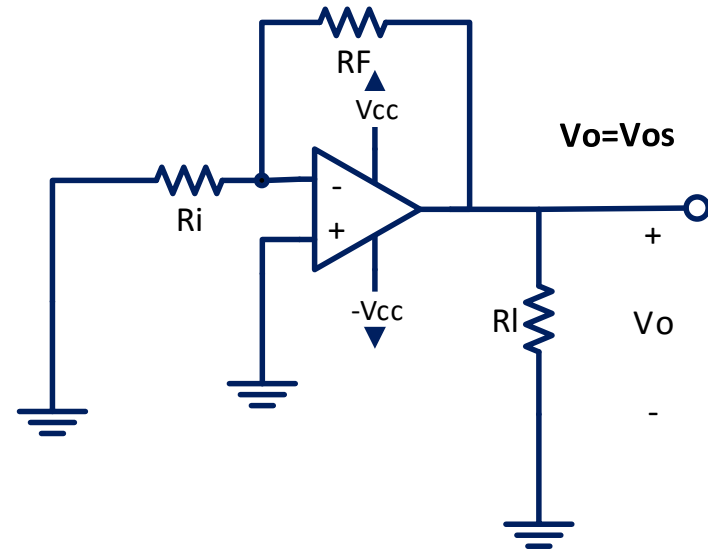

Current source in parallel with short




short


Current source in parallel with a resistor



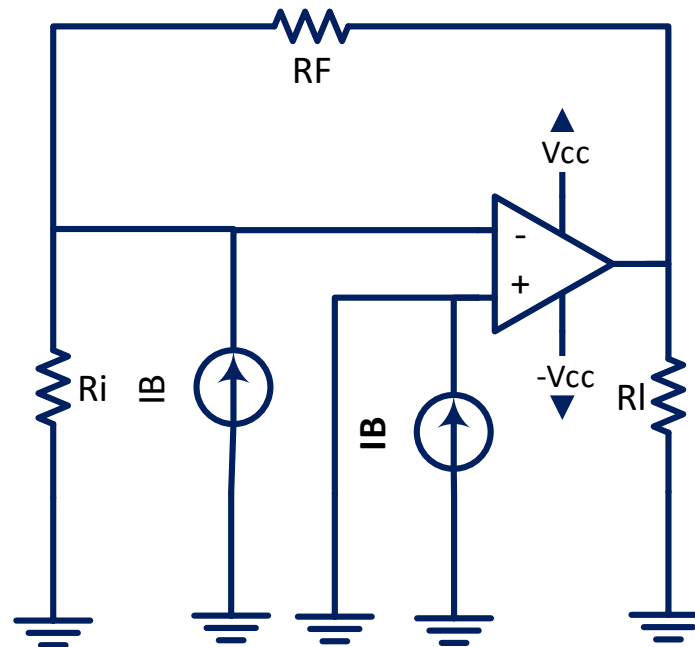Voltage source in series with the same resistor




Output offset Voltage

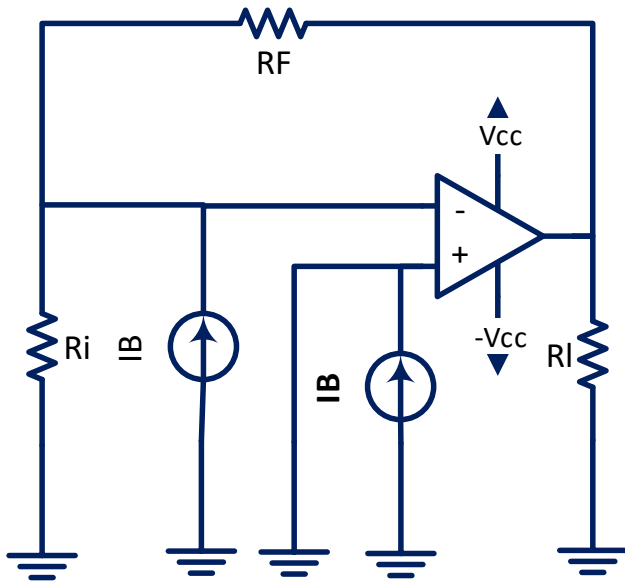


$$V_O = V_{OS} = - \frac{R_f}{R_I} R_i I_B$$

$$V_{OS} = - R_f I_B$$


Using source transformation

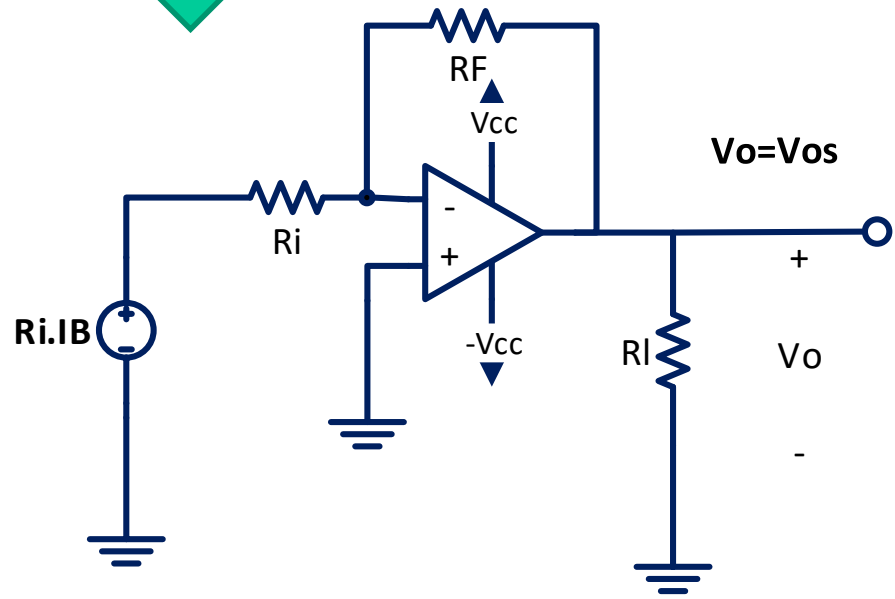


Output offset Voltage

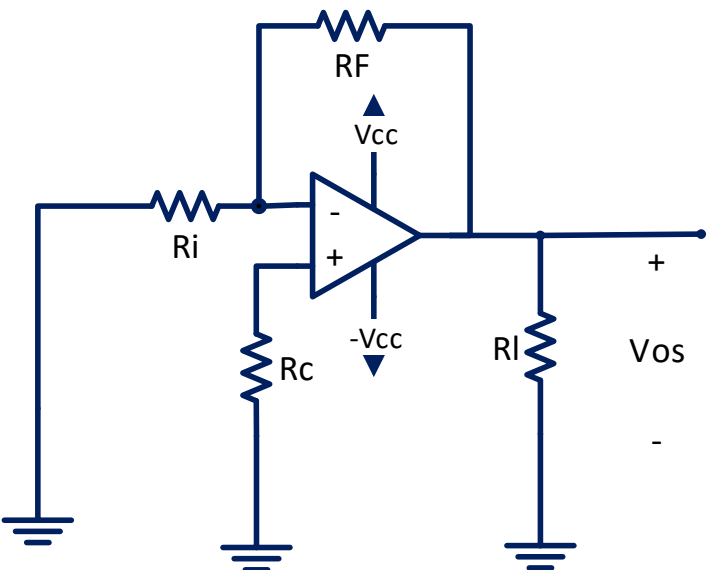

R_c is a compensation resistor

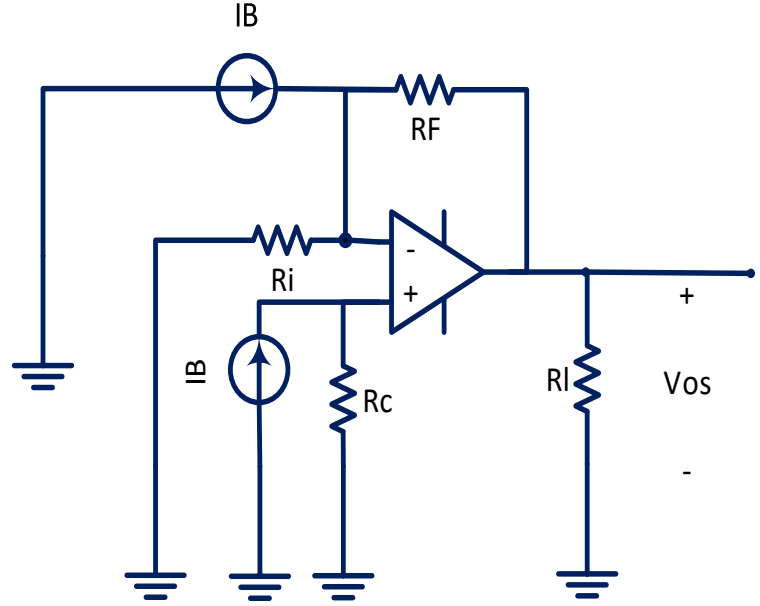

Using source transformation

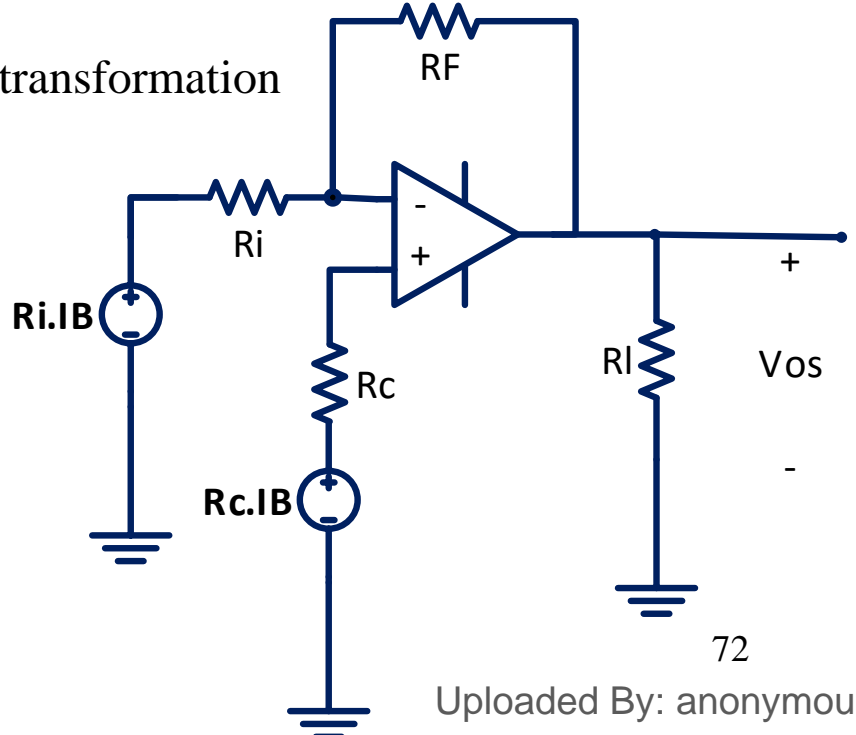

Output offset Voltage



Using Superposition

$$V_{OS} = \left(1 + \frac{R_f}{R_I}\right) R_C I_B - \frac{R_f}{R_I} R_i I_B = 0$$


For V_O to be zero:

$$\left(1 + \frac{R_f}{R_I}\right) R_C - R_f = 0$$

$$\therefore R_C = R_i \parallel R_f$$

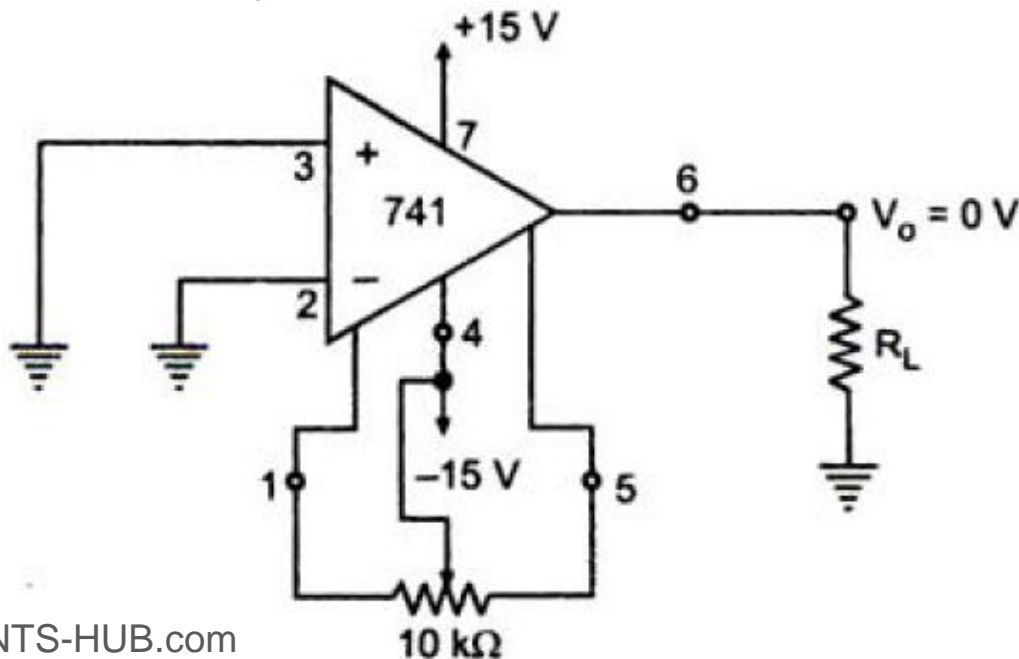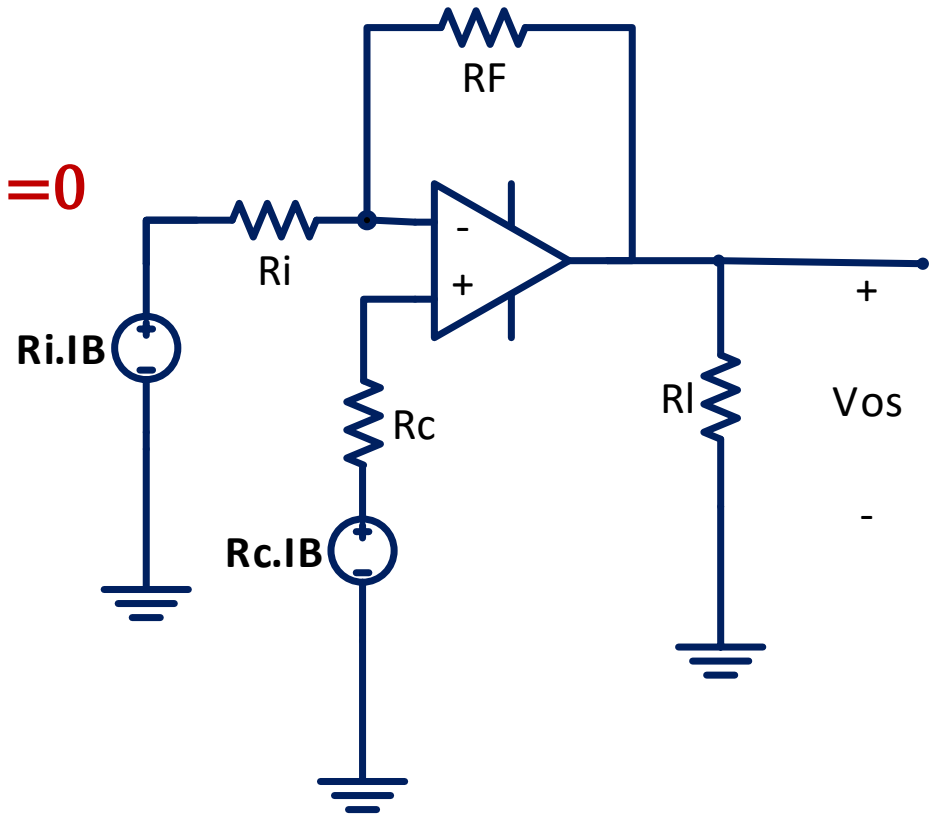

Inverting Amplifier

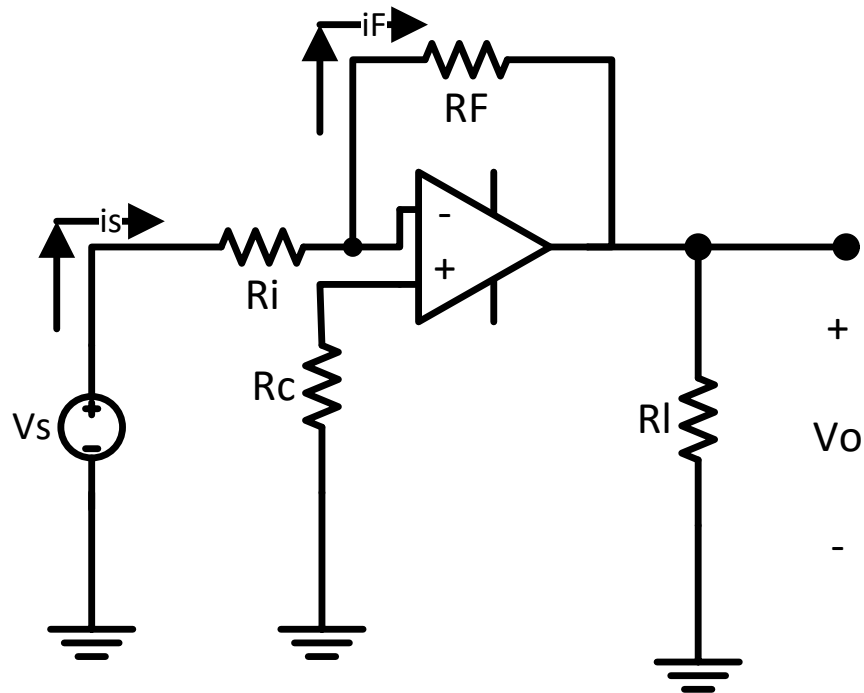

$$V_o = -\frac{R_f}{R_i} V_s$$