


Started on	Monday, 29 January 2024, 6:03 PM
State	Finished
Completed on	Monday, 29 January 2024, 6:31 PM
Time taken	28 mins 11 secs
Grade	12.00 out of 12.00 (100%)

Question 1

Correct

Mark 1.00 out of 1.00

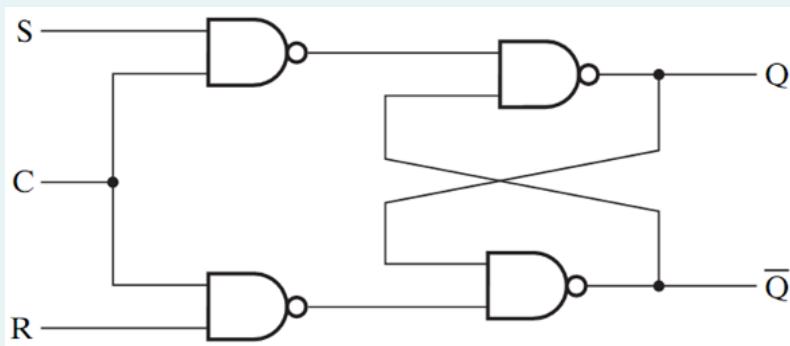In the following circuit, the present state is 0, and $S=R=0$. When the clock is its positive level, then \bar{Q} (Q') has the value of:



- a. 0
- b. Cannot determine from the given information
- c. X
- d. Z
- e. 1 ✓




Question 2

Correct


Mark 1.00 out of 1.00

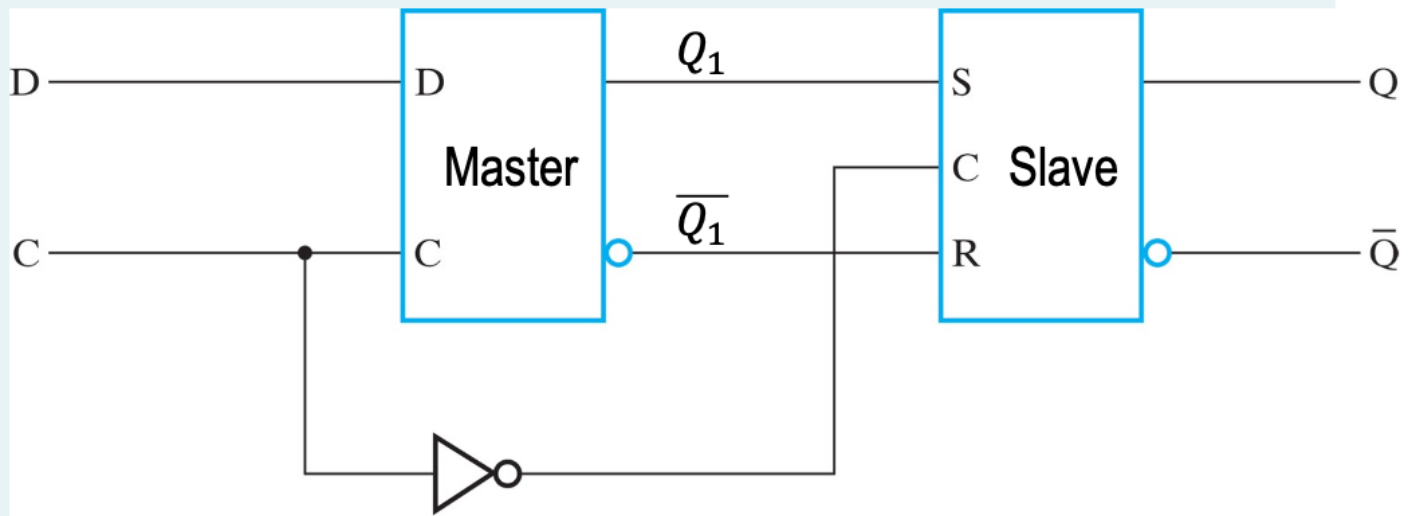What is the correct output waveform of the below circuit:




a. None


b.

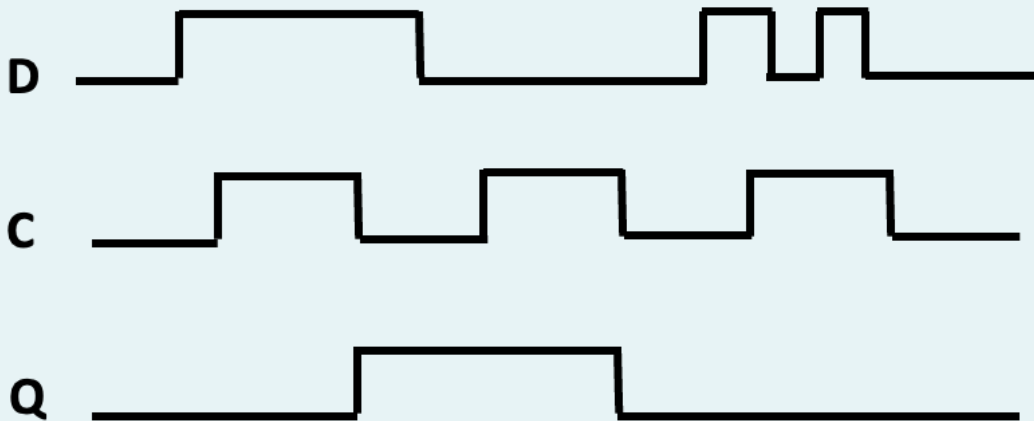


c.

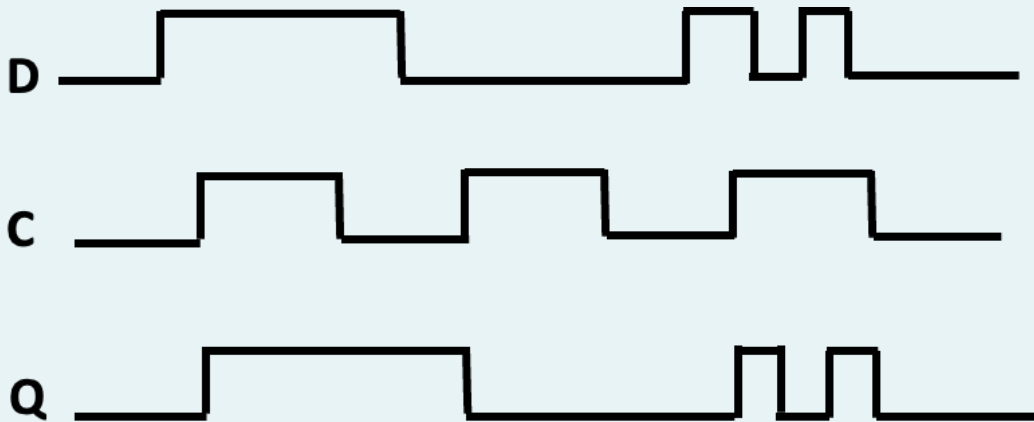

d.

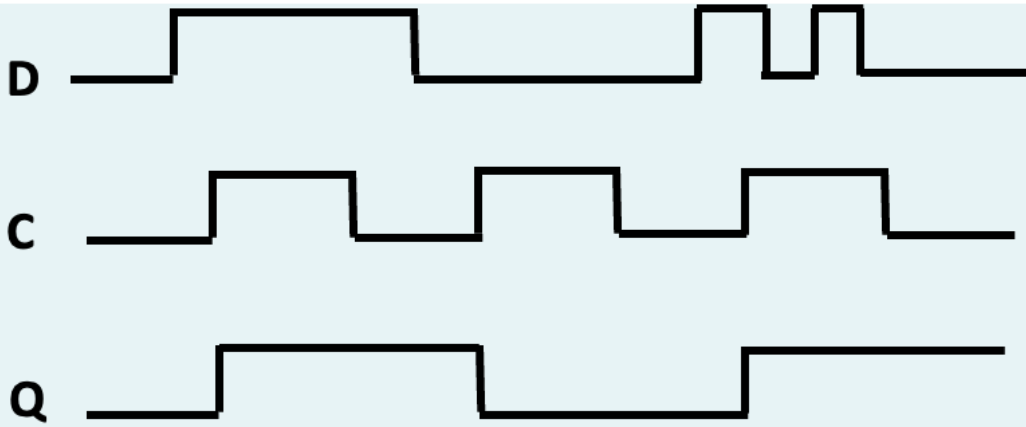

e.

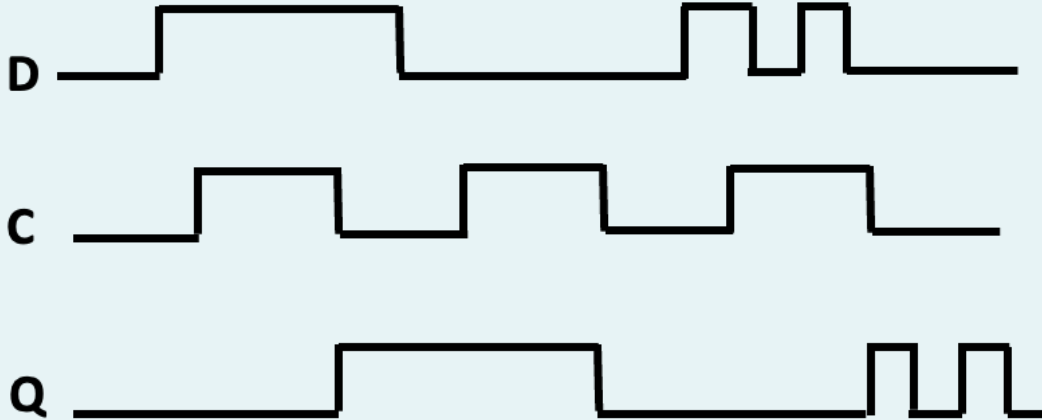

Question 3

Correct

Mark 1.00 out of 1.00

A positive edge-triggered D flip-flop will store a 0 when _____

- a. The D input is HIGH and the clock transitions from HIGH to LOW
- b. The D input is HIGH and the clock is LOW
- c. The D input is LOW and the clock is HIGH
- d. The D input is LOW and the clock transitions from LOW to HIGH ✓
- e. The D input is LOW and the clock transitions from HIGH to LOW




Question 4

Correct

Mark 1.00 out of 1.00

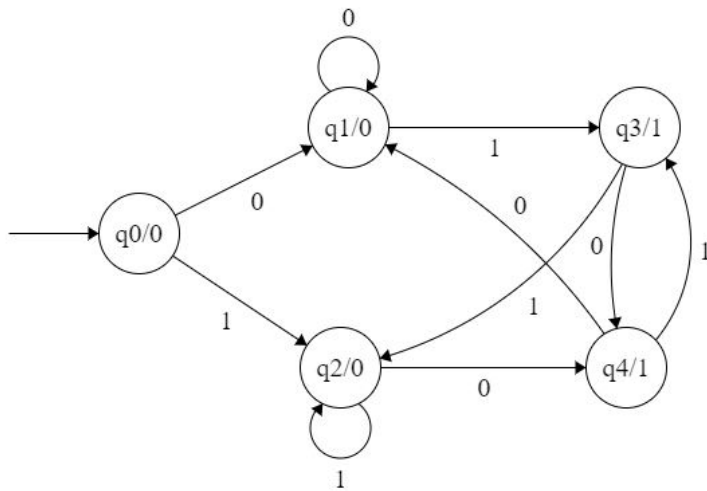The minimum number of Flip Flops required to implement the below machine is _____



- a. 3 ✓
- b. 4
- c. 5
- d. 2
- e. 2^5




Question 5

Correct

Mark 1.00 out of 1.00

What is true about the below schematic?

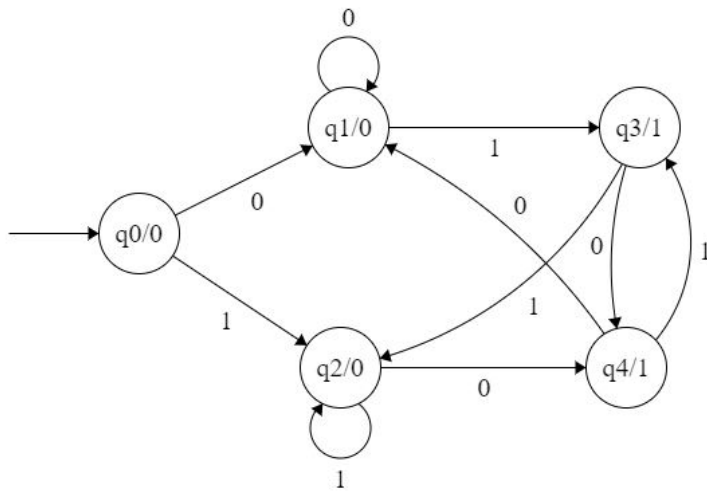

- a. The machine can be implemented using a combinational logic circuit
- b. The machine has no outputs
- c. q1 is unreachable state
- d. q2 and q3 are equivalent states
- e. The machine has 1 input and 1 output ✓




Question 6

Correct

Mark 1.00 out of 1.00

The below schematic represents

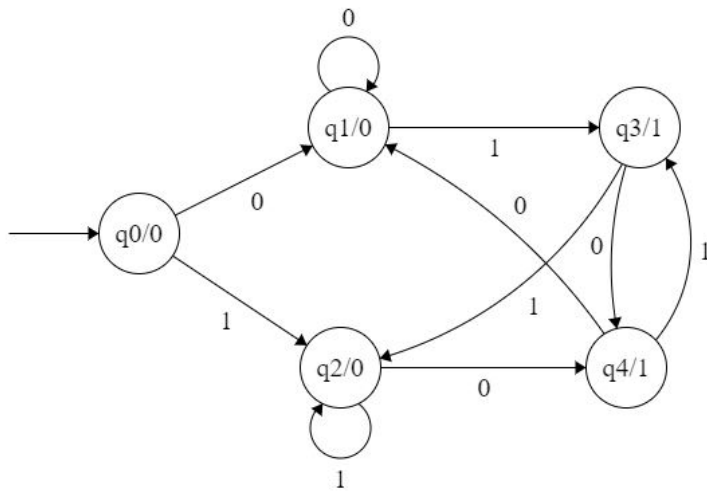

- a. Q Flip Flop state machine
- b. State table
- c. Mealy state machine
- d. None
- e. Moore state machine ✓

Question 7

Correct

Mark 1.00 out of 1.00

In synchronous sequential circuit, changes in the memory elements can happen at any instance of time.

- a. True
- b. False ✓




Question 8

Correct

Mark 1.00 out of 1.00

The below schematic represents:

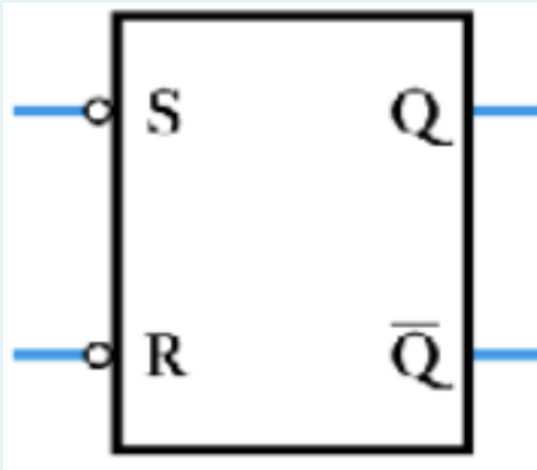

- a. Active low SR Flip Flop
- b. Active high Flip Flop
- c. Active low SR latch ✓
- d. Master-Slave latch configuration
- e. Active high SR latch



Question 9

Correct

Mark 1.00 out of 1.00

Given the following state table, the following states are equivalent

Present State	Next State		Output	
	Input = 0	Input = 1	Input = 0	Input = 1
A	B	B	1	1
B	A	A	1	0
C	A	B	0	1
D	B	B	1	1
E	A	A	0	1

- a. A and D ✓
- b. A and D, B and E
- c. A, D, and E
- d. B and E
- e. None

Question 10

Correct

Mark 1.00 out of 1.00

If a sequential circuit is designed using three T flip flops. Assume the current state is $abc = 001$. To transition to the next state 110, then the values of $T_a T_b T_c$ is:

- a. 001
- b. 110
- c. 000
- d. 111 ✓
- e. 110



Question **11**

Correct

Mark 1.00 out of 1.00

Choose the most correct answer. To design a synchronous sequential circuit that counts even numbers from 0 to 10. When it reaches the value of 10, it restarts counting from zero, then it has

- a. None
- b. 10 states
- c. 6 states
- d. 6 used states, 10 unused states ✓
- e. 16 states

Question **12**

Correct

Mark 1.00 out of 1.00

How is a J-K flip-flop made to toggle?

- a. Connect J input to XOR gate such that $J = K' \oplus Q$
- b. Connect J and K inputs to 1 ✓
- c. Connect J input to XOR gate such that $J = K \oplus Q'$
- d. Connect K input to XOR gate such that $K = J \oplus Q$
- e. Connect J and K inputs to 0

