

Exp 4: DC Circuits

The aim:


is to test a material and determine if its an ohmic material or non-ohmic.

Theory:-

* The resistance R of a metallic conductor defined by


$$R = \frac{V}{I} = \frac{\text{Voltage}}{\text{Current}}$$

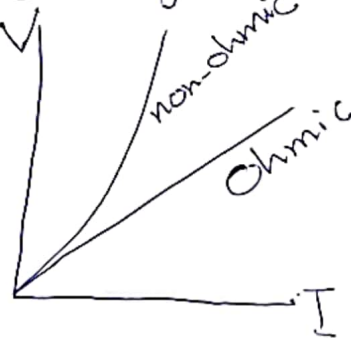- if V depend linearly on I then the material is ohmic



* Resistors:-

A. in parallel

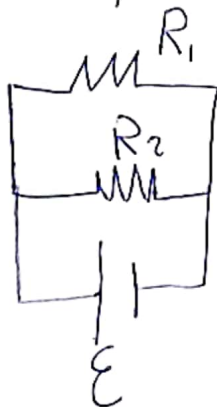


$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

or

$$R_p = \frac{R_1 R_2}{R_1 + R_2}$$


B. resistors in ~~parallel~~ series :-

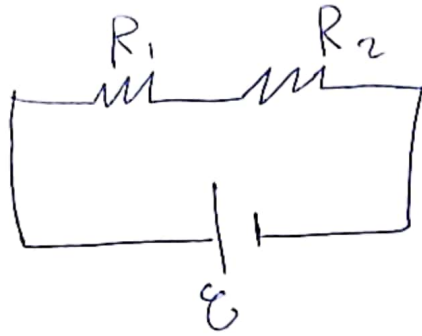

$$R_s = R_1 + R_2$$

* Procedure :-


part A :- one-resistor, DC-circuit

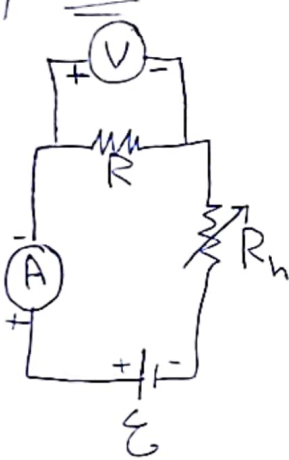

No	1	2	3	4	5	6	Avg
I (mA)							
V (Volts)							

$\Delta I =$ التغيير
 $\Delta V =$ تقدير الجهد


part B :- two-resistors in series

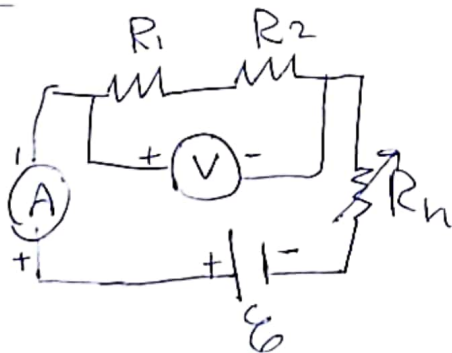

- write down the readings of the I_s and V_s only once

same ΔI
 ΔV

part C: Two resistors in parallel.

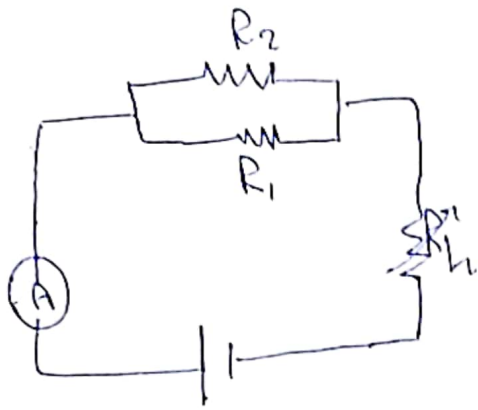

- write down the readings of the I_p and V_p

only once

Same ΔI
 ΔV

Calculations:

(A) 1. Find R from the graph V vs $I \Rightarrow R = \text{slope}$

$$2. \frac{\Delta R}{R} = \frac{\Delta V}{V} + \frac{\Delta I}{I}$$

The true value

$R, \Delta R \Rightarrow$ color code

$$(B) (R_s)_{\text{cap}} = \frac{V_s}{I_s}$$

true value $\Rightarrow R_s = R_1 + R_2$ color code


Conclusions :-

Range test :-

Example :- A student has the following measurement

$$R = 36 \pm 7 \Omega$$

and the true value $R = 35 \pm 2 \Omega$

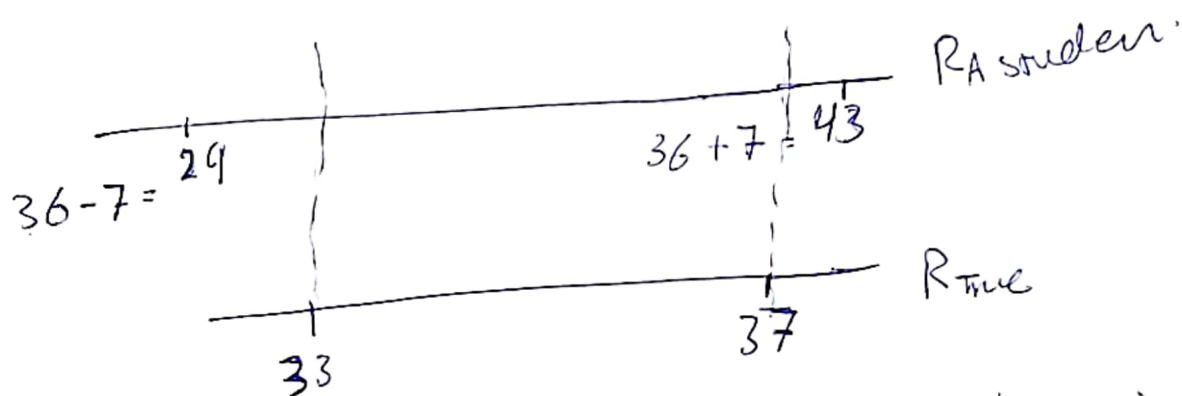

→ The value accepted since there is common area.