

Student name: Izzedin... Yaraub Student number: ...12...3...12...5.....

Question 1 : Consider RC circuit powered using a square wave from the signal generator. The figure below represents the voltage on the resistor displayed on the CRO screen. If the capacitance  $C = 0.022\mu F$ , the value of the resistance is:

